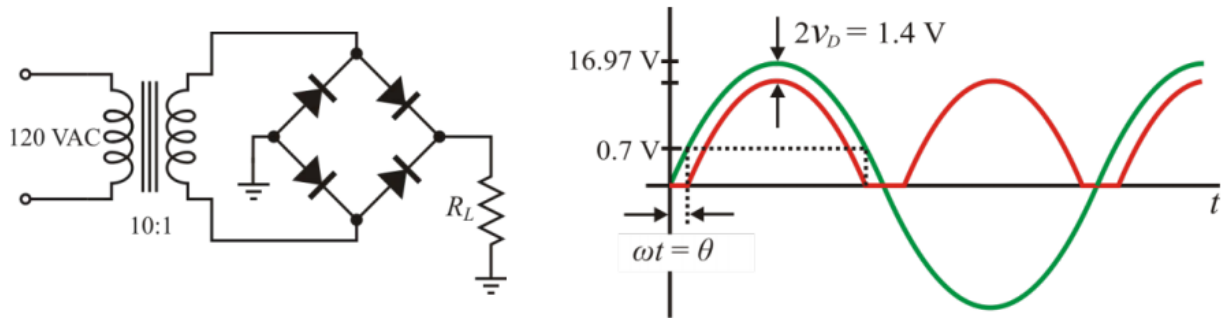


CE 432 Robotics II Homework Package - Solutions

Chapter 1 Power Supply for Robots

1. 1. A full-wave, 4-diode bridge rectifier circuit with a 1 kΩ load operates from a 120-V (rms) 60-Hz household supply through a 10-to-1 step-down transformer. It uses silicon diodes that one can model to have a 0.7-V drop for any current. (a) What is the peak voltage of the rectified output?




(a) The peak voltage after the 10-to-1 step down is $V_P = (12)(\sqrt{2}) = 16.97 \text{ V}$ so the peak voltage of the rectified output is this, minus two diode drops, or $V_P(\text{load}) = 16.97 - 1.4 = 15.57 \text{ V}$

(b) 81.13%

(c) $\text{PIV} = 16.97 - 0.7 = 16.27 \text{ V}$

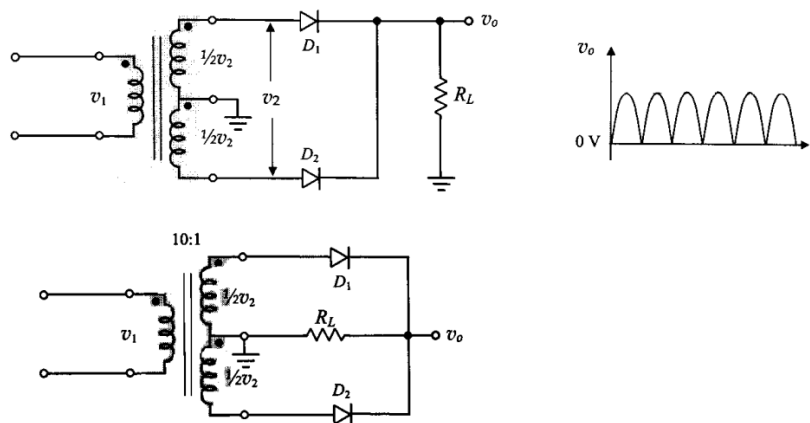2. For the following Full Wave Center-Tapped Rectifier, find the rectified DC voltage output. V_{in} (RMS) == 110V (60Hz), Turns Ratio 10:1.



Given: $v_{in}(\text{RMS}) = 110 \text{ V}$ (60 Hz) Turns Ratio 10:1 Find: $V_{out}(\text{DC Effective})$

$$v_{in}(\text{Peak Center}) = 1.414 * V(\text{RMS})$$

$$v_{in}(\text{RMS}) = 1.414 \times 110 = 155.5 \text{ V}$$

$$v_{out}(\text{Peak}) = (1/2) (1/10)$$


$$v_{in}(\text{RMS}) = 1/20 \times 155.5 = 7.8 \text{ V}$$

$$v_{\text{Diode}} = 7.8 - 0.7 = 7.1 \text{ V}$$

$$V_{out} (\text{DC Effective}) = 0.636 \text{ (which comes from } 2 \cdot v_m / 3.14)$$

$$v_{\text{Diode}} = 0.636 \times 7.1 \approx 4.5 \text{ VDC}$$

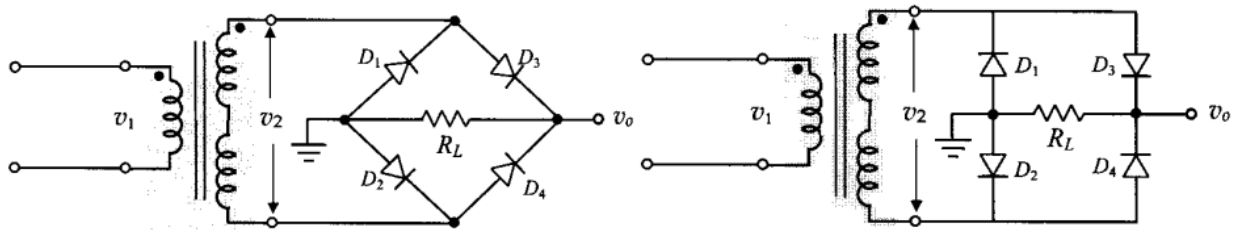3. For the following Full Wave Bridge Rectifier, find the rectified DC voltage output. V_{in} (RMS) = 110V ($f_{in} = 60\text{Hz}$), Turns Ratio 10:1.



Given: $v_{in}(\text{RMS}) = 110 \text{ V}$ (60 HZ)

Turns Ratio 10:1

(a) Find: $V_{out}(\text{DC Effective})$

$$v_{in}(\text{Peak}) = 1.414$$

$$v_{in}(\text{RMS}) = 1.414 \times 110 = 155.5 \text{ V}$$

$$v_{out}(\text{Peak}) = 1/10$$

$$v_{in}(\text{RMS}) = 1/10 \times 155.5 = 15.6 \text{ V}$$

$$v_o (\text{RMS}) = 15.6 - 2(0.7) = 14.2 \text{ V}$$

$$v_{out}(\text{DC Effective}) = 0.636 \times v_o = 0.636 \times 14.2 \approx 9 \text{ VDC}$$

(b) Smoothing filter:

$$V_{\text{ripple}} = I_{out}(\text{DC}) / fC$$

$$I_{out}(\text{DC}) = v_{out}(\text{DC}) / R_{Load} = 9/100 = 90\text{mA}$$

$$C = I_{out}(\text{DC}) / V_{\text{ripple}f} = 90\text{mA} / (1\text{V} \cdot 120\text{Hz}) = 0.75 \text{ mF} \text{ (note: } f \text{ is } 2 \cdot f_{in} = 120\text{Hz)}$$