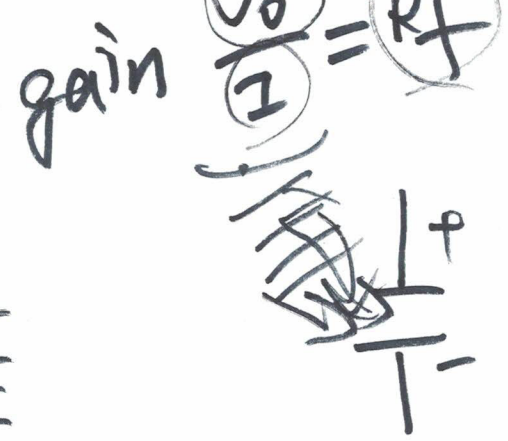




Forward Biased $R_f = 1k$

$$\frac{V_o - 0}{R_f} = I \Rightarrow \text{gain} = \frac{V_o}{I} = R_f$$



Reverse Biased


photodiode
photo-current

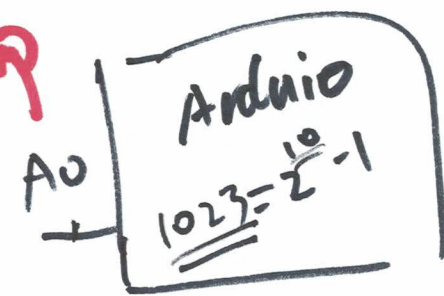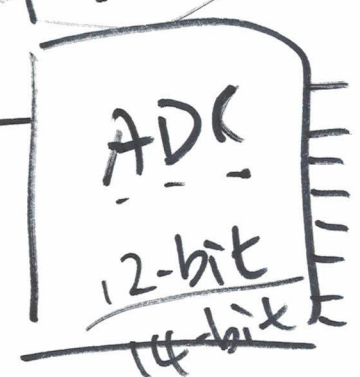

Inverting configuration of an op amp

TIA Transimpedance Amplifier

① Quarter Bridge.

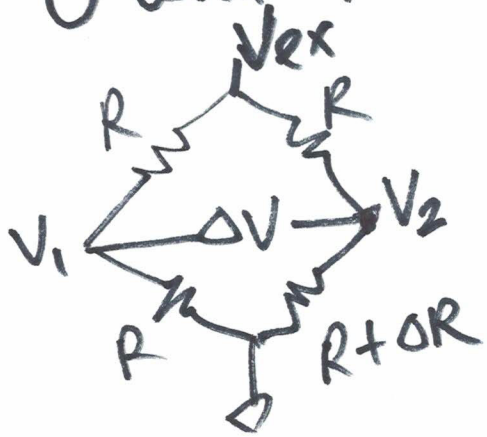

$$\Delta V = V_2 - V_1 = V_{ex} \frac{R + \Delta R}{R + R + \Delta R} - V_{ex} \frac{1}{2}$$

$$= V_{ex} \left(\frac{R + \Delta R}{2R + \Delta R} - \frac{1}{2} \right)$$

$$= V_{ex} \left(\frac{2R + 2\Delta R - 2R - \Delta R}{2(2R + \Delta R)} \right)$$

$$= V_{ex} \frac{\Delta R}{4R + 2\Delta R}$$

$$= V_{ex} \frac{\Delta R}{4R}$$



$$\frac{V_0}{R_2} = \frac{V_i}{R_1 + R_2}$$

$$V_0 = V_i \cdot \frac{R_2}{R_1 + R_2}$$

$$\frac{V_0}{V_i} = \frac{R_2}{R_1 + R_2}$$

Voltage divider theory

②