
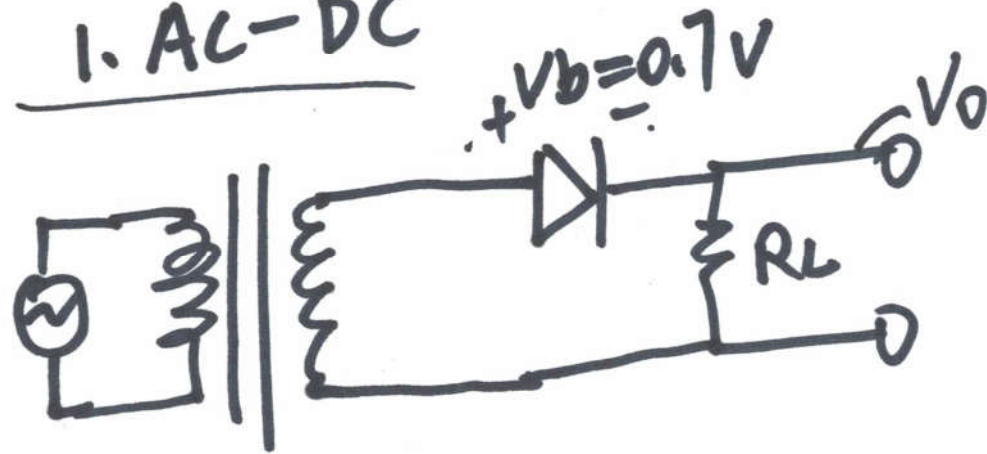


1. AC-DC

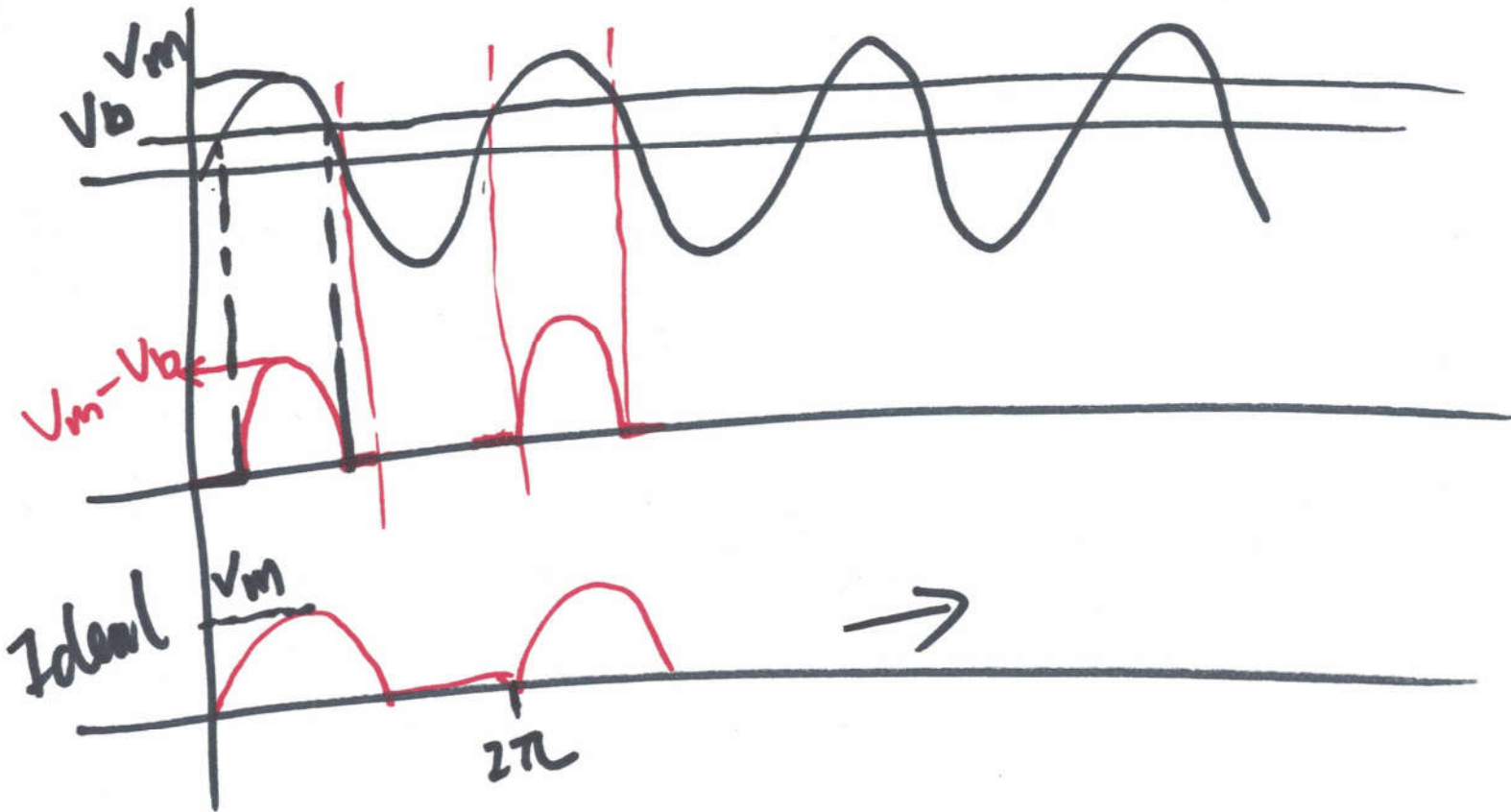

Half-wave rectifier



①

rectified output:

$$V_{av} = \frac{1}{2\pi} \int_0^{2\pi} V_m \sin \omega t \, d\omega t$$


Average voltage  
output  
OR the  
rectified  
DC output  
voltage

$$= \frac{1}{2\pi} \left( \int_0^{\pi} V_m \sin \omega t \, d\omega t + \int_{\pi}^{2\pi} \cancel{V_m \sin \omega t} \, d\omega t \right)$$

$$= \frac{V_m}{2\pi} \int_0^{\pi} \sin \omega t \, d\omega t$$

$$= \frac{V_m}{2\pi} (-\cos \omega t) \Big|_0^{\pi}$$

$$= \frac{V_m}{2\pi} (-(-1) - (-1))$$

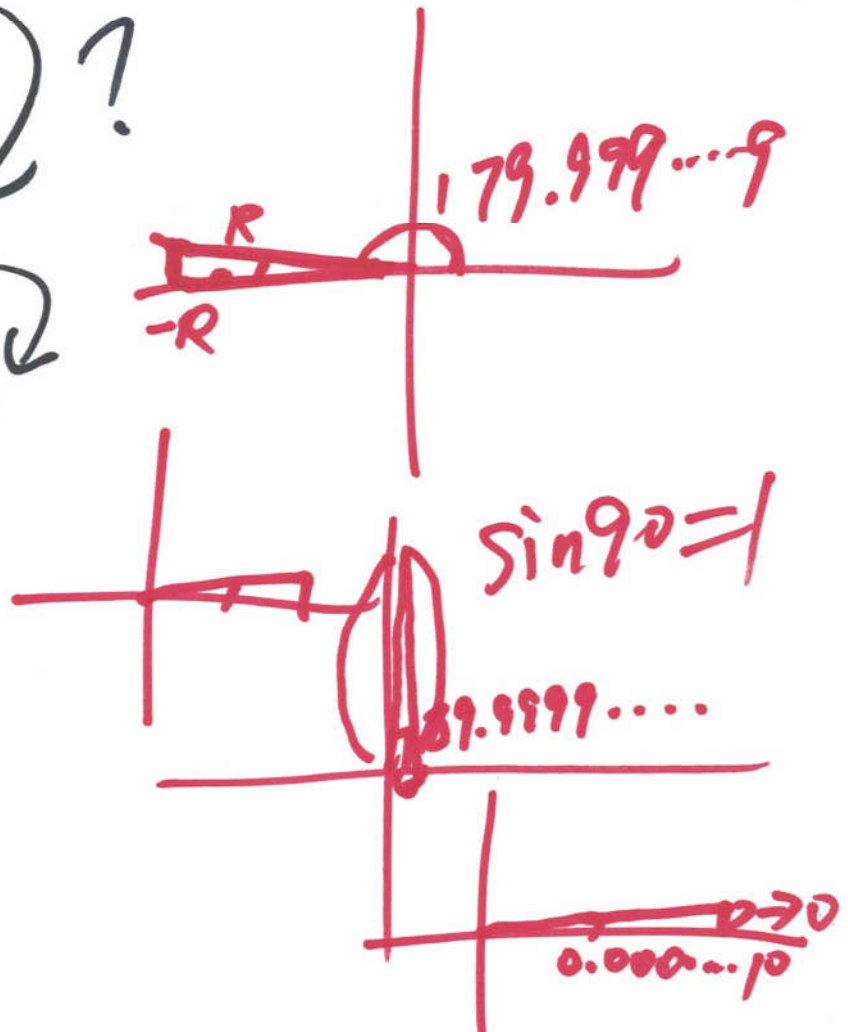

(2)

$$= -\frac{V_m}{2\pi} (\cos \omega t) \Big|_0^\pi$$

$$= -\frac{V_m}{2\pi} (\cos \pi - \cos 0)$$

$$= -\frac{V_m}{2\pi} (-1 - 1)$$

$$= -\frac{V_m}{2\pi} \cdot (-2) = \boxed{\frac{V_m}{\pi} = V_{av}}$$

$$\boxed{I_{av}} = \frac{V_{av}}{R_L} = \frac{V_m}{\pi} / R_L = \frac{V_m}{R_L} / \pi = \boxed{\frac{I_m}{\pi}}$$

(3)

RMS current at the output

$$I_{\text{rms}} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} I_m^2 \sin^2 \omega t \, d\omega t}$$

$$= \sqrt{\frac{1}{2\pi} \left( \int_0^{\pi} I_m^2 \sin^2 \omega t \, d\omega t + 0 \right)}$$

$$= \sqrt{\frac{I_m^2}{2\pi} \int_0^{\pi} \sin^2 \omega t \, d\omega t}$$

$$= \sqrt{\frac{I_m^2}{2\pi} \int_0^{\pi} \frac{1}{2} (1 - \cos 2\omega t) \, d\omega t}$$

$$= \sqrt{\frac{I_m^2}{4\pi} \int_0^{\pi} (1 - \cos 2\omega t) \, d\omega t}$$

$$\begin{cases} \cos 2\theta = \cos^2 \theta - \sin^2 \theta \\ 1 = \cos^2 \theta + \sin^2 \theta \end{cases}$$

$$1 - \cos 2\theta = 2 \sin^2 \theta$$

$$\sin^2 \theta = \frac{1}{2} (1 - \cos 2\theta)$$

(4)



$$= \sqrt{\frac{I_m^2}{4\pi} \left( \pi - \int_0^\pi \cos 2\omega t \, d\omega t \right)}$$

$$= \sqrt{\frac{I_m^2}{4\pi} \left( \pi - \left( \frac{1}{2} \sin 2\omega t \Big|_0^\pi \right) \right)}$$

$$= \sqrt{\frac{I_m^2}{4}} = \frac{I_m}{2} = I_{rms}$$

$$V_{rms} = \underline{I_{rms}} \cdot R_L = \frac{I_m}{2} \cdot R_L = \frac{V_m}{2}$$

5