
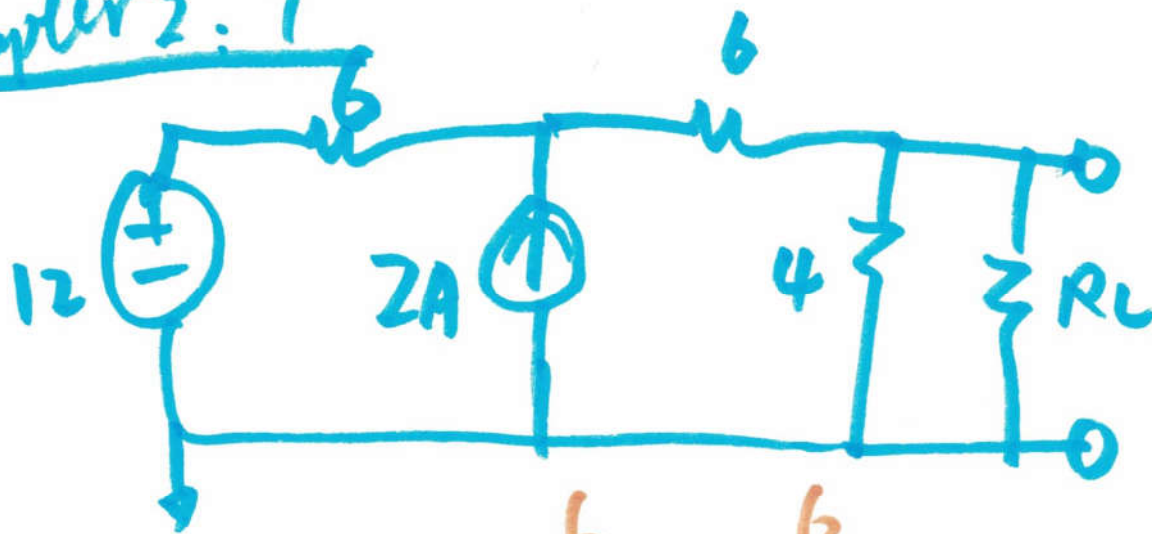



chapter 2: 7

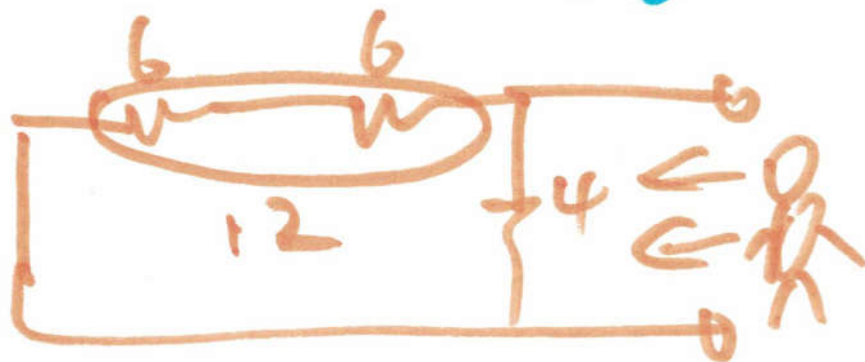

$R_{TH} =$



$R_{TH} = 4 // 12$

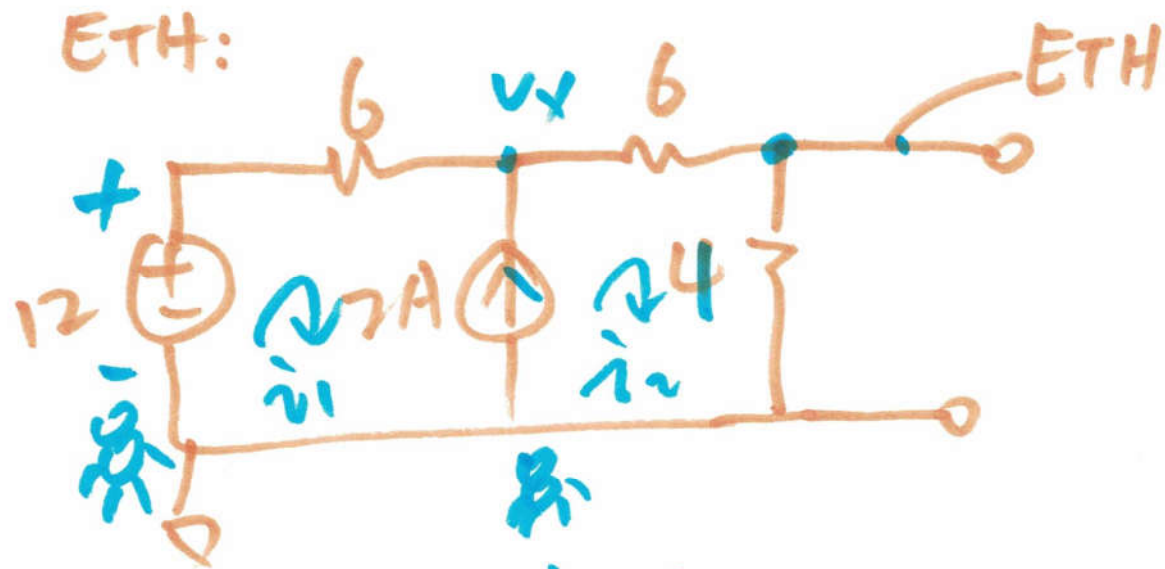


$$\begin{cases} -12 + 6 \cdot i_1 + v_x = 0 \\ -v_x + 6 \cdot i_2 + 4 \cdot i_2 = 0 \\ i_2 - i_1 = 2 \end{cases}$$


$$\begin{cases} -12 + 6i_1 + 6i_2 + 4i_2 = 0 \\ i_2 - i_1 = 2 \Rightarrow i_2 = i_1 + 2 \end{cases}$$

②

8.

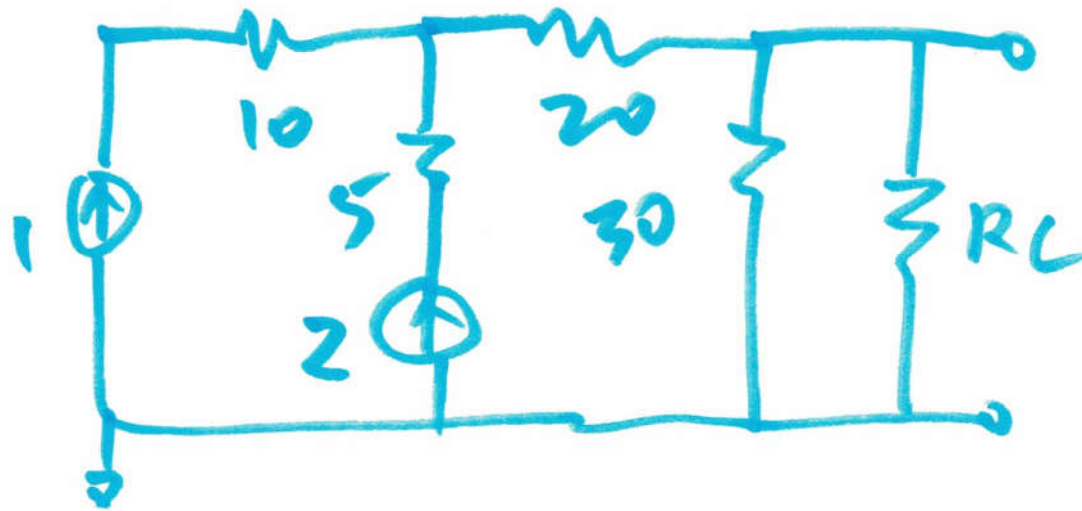


R_{TH} :

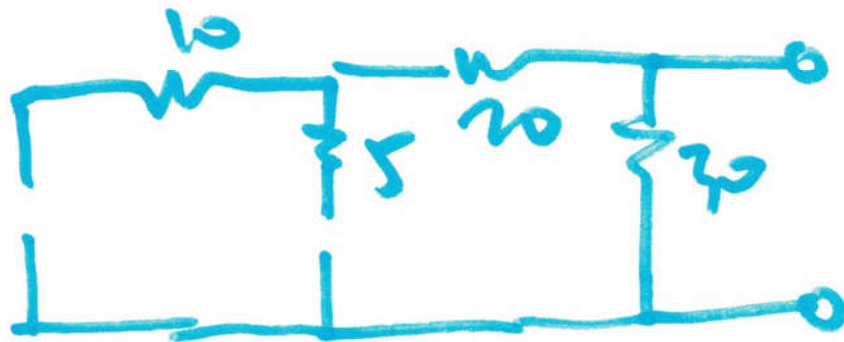


$$R_{TH} = 30 \Omega$$


3

E_{TH} :

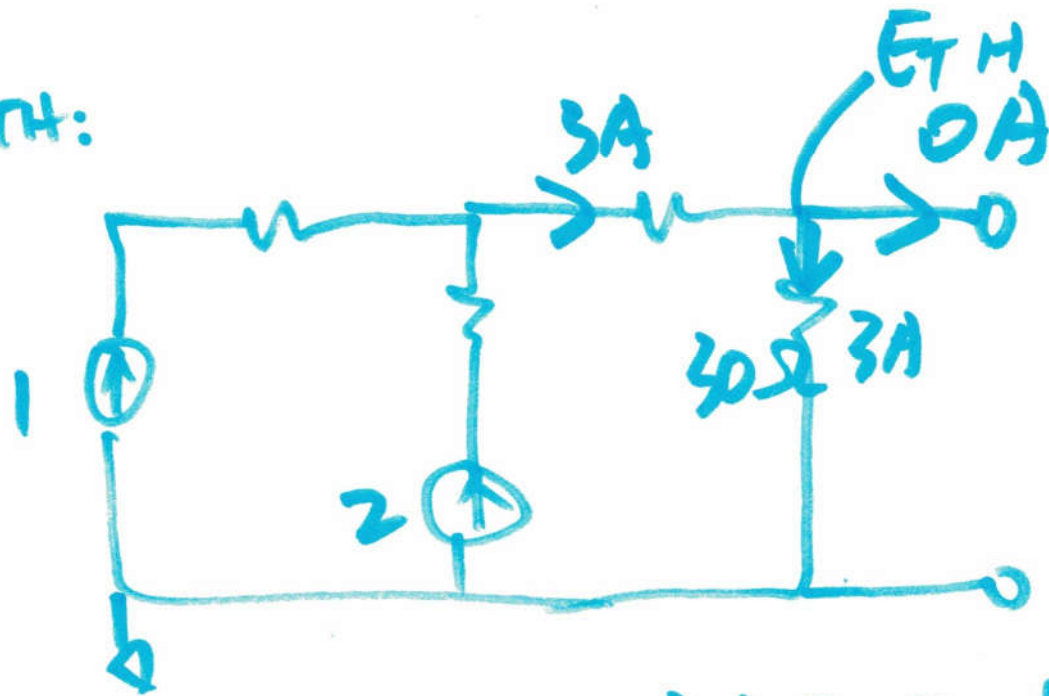


$$E_{TH} = 3A \cdot 30\Omega = 90V.$$

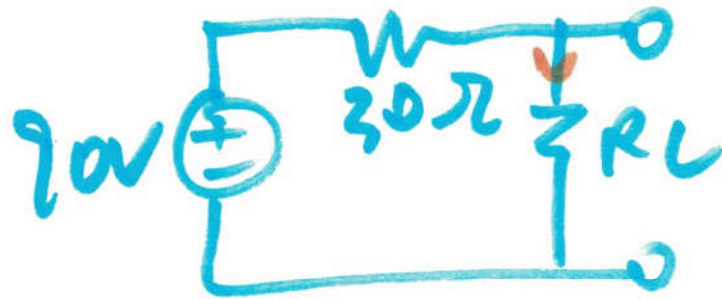


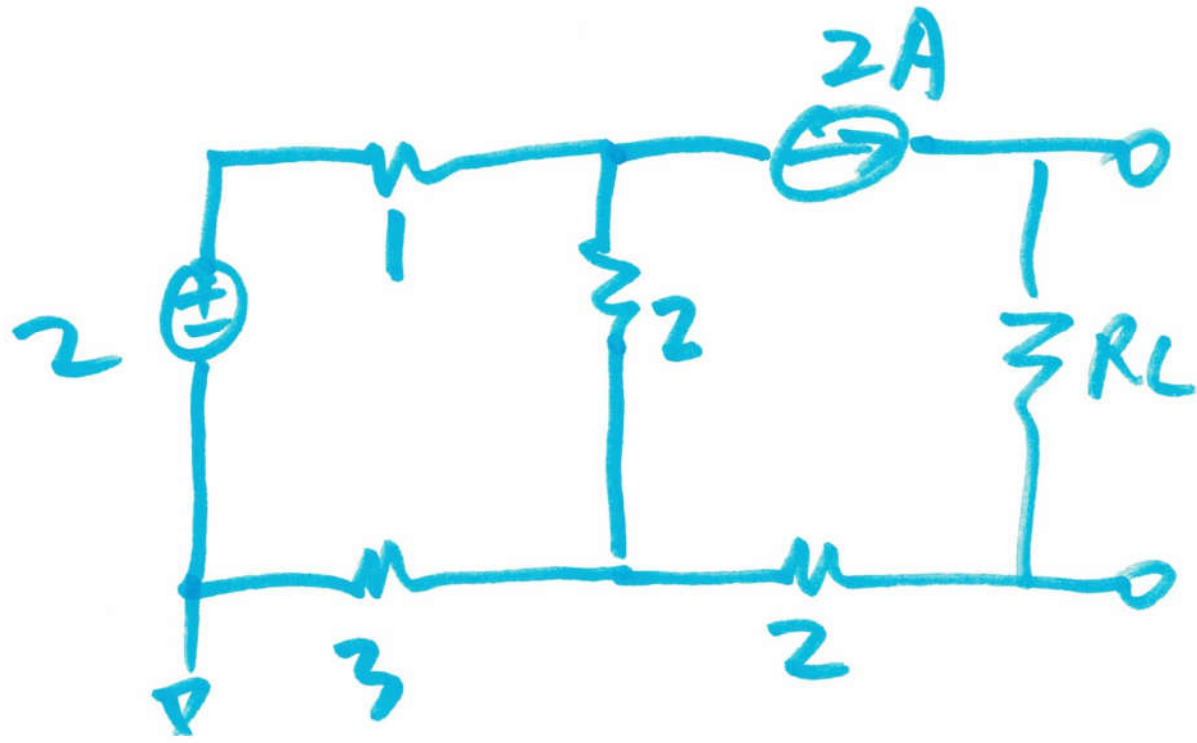


R_N :

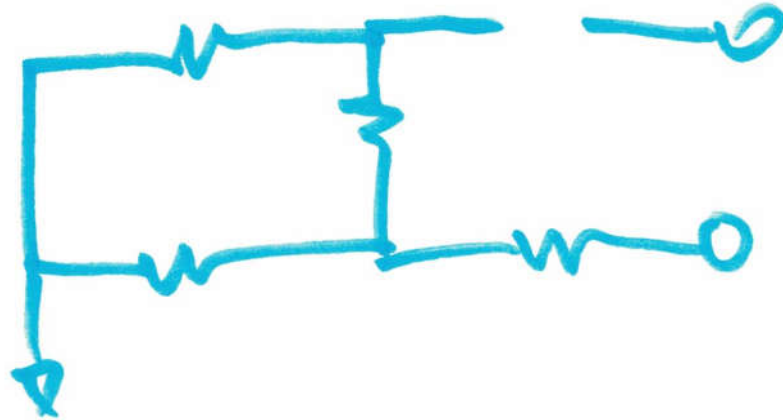

$R_N = \infty$

5

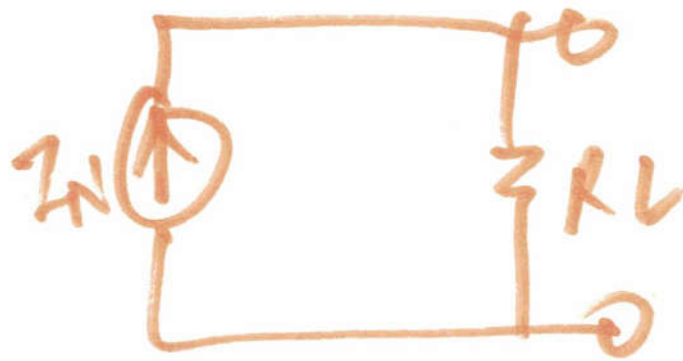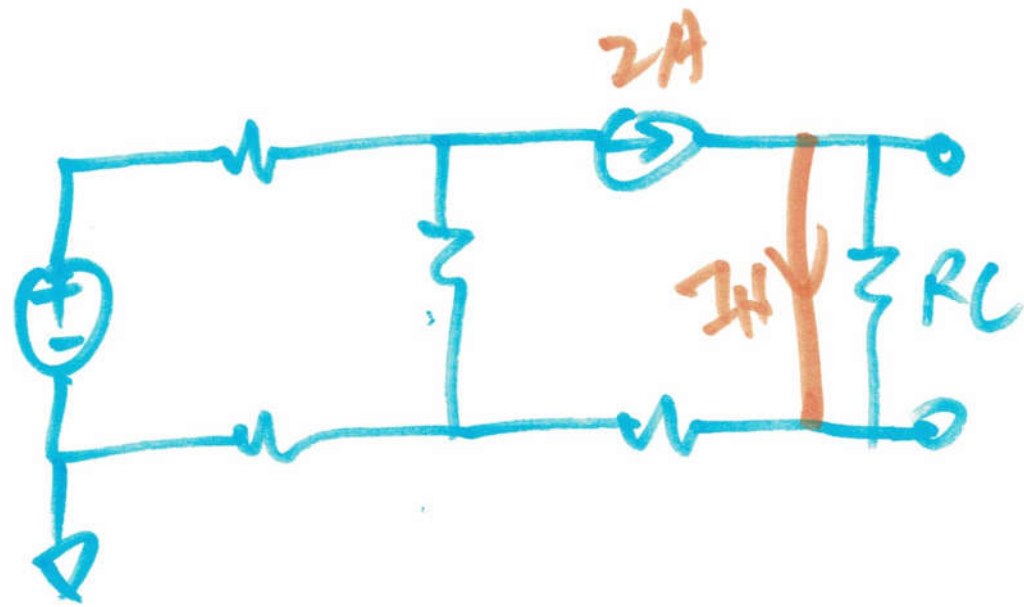

6


$$\begin{cases} i_1 = 2A \\ -8 + (i_2 - i_1) \cdot 8 + i_2 \cdot 2 = 0 \end{cases}$$

$$-8 + (i_2 - 2) \cdot 8 + i_2 \cdot 2 = 0$$

$$-8 + 8i_2 - 16 + i_2 \cdot 2 = 0$$


$$10i_2 = 24$$

$$i_2 = 2.4 A$$

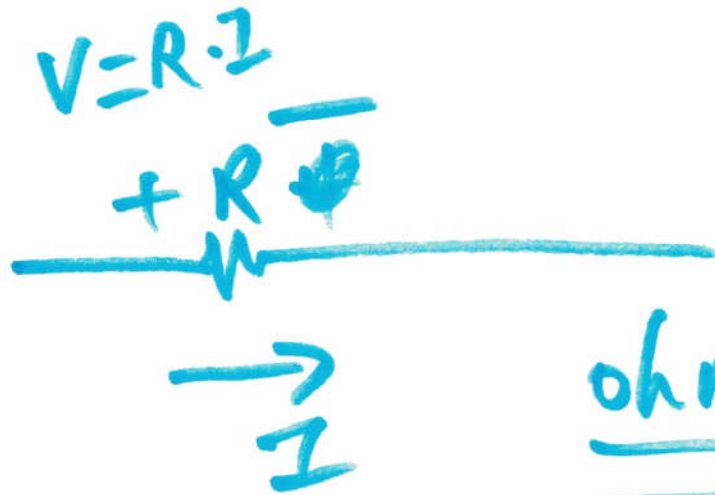

ohm's Law

8

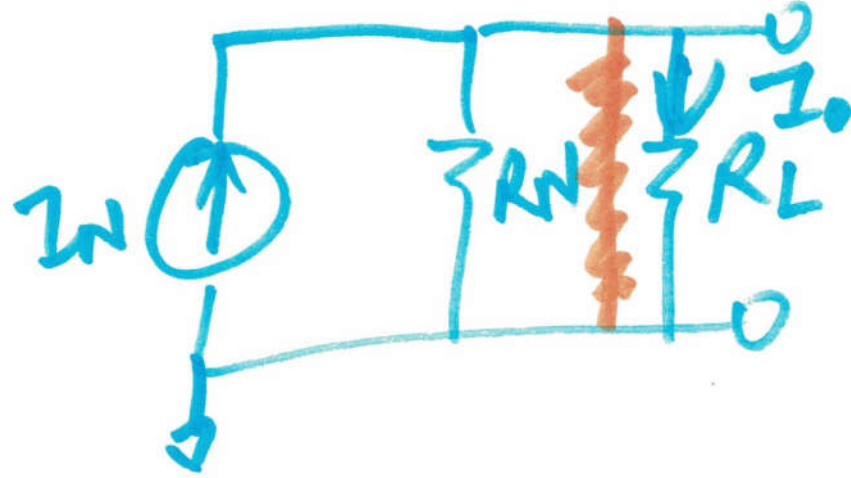

$$I_0 = \frac{\cancel{R_N}}{\cancel{R_N} + R_L} \cdot I_N$$

9