
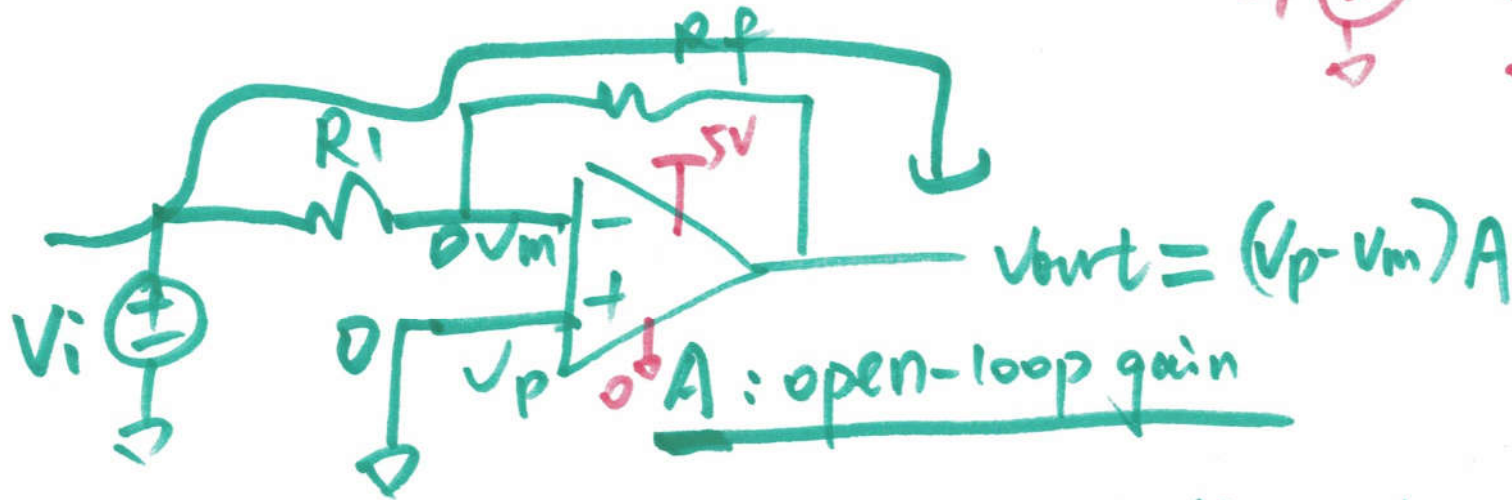


Lec 22

Op Amp IV

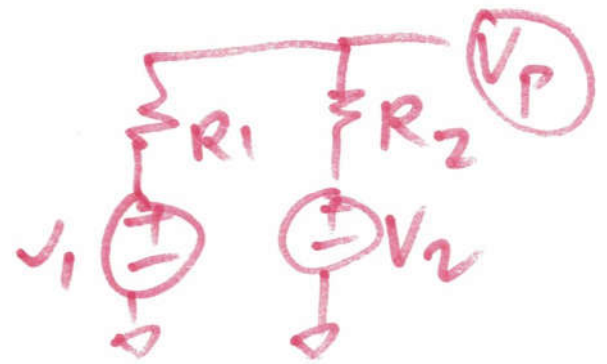

① Infinite open-loop gain A , then $V_p = V_m$.

② Finite open-loop gain A .

$$\propto A: \frac{V_i - 0}{R_i} = \frac{0 - V_o}{R_f} \Rightarrow \boxed{\frac{V_o}{V_i} = -\frac{R_f}{R_i}}$$

$$\boxed{V_p = V_m = 0}$$

$$\left\{ \begin{array}{l} \frac{V_i - V_m}{R_i} = \frac{V_m - V_o}{R_f} \\ V_o = (V_p - V_m) \cdot A \\ V_p = 0 \end{array} \right\} \Rightarrow V_o = -V_m \cdot A$$

$$\Rightarrow V_m = -\frac{V_o}{A}$$

V_o, V_i

~~$$\frac{V_i + \frac{V_o}{A}}{R_i} = \frac{-\frac{V_o}{A} - V_o}{R_f}$$~~

$\frac{R_f}{R_i} \approx 0$

$$V_i R_f + \frac{V_o}{A} R_f = -\frac{V_o}{A} R_i - V_o R_i$$

$A = \infty$
 $R_f = 100 R_i$


$$V_i \cdot R_f = -\frac{V_o}{A} R_f - \frac{V_o}{A} R_i - V_o R_i$$

$$= -\left(\frac{R_f}{A} + \frac{R_i}{A} + R_i\right) V_o$$

$$\frac{V_o}{V_i} = -\frac{R_f}{\frac{R_f}{A} + \frac{R_i}{A} + R_i} \approx -\frac{R_f}{R_i} (A \rightarrow \infty)$$

②

Non-inverting Topology

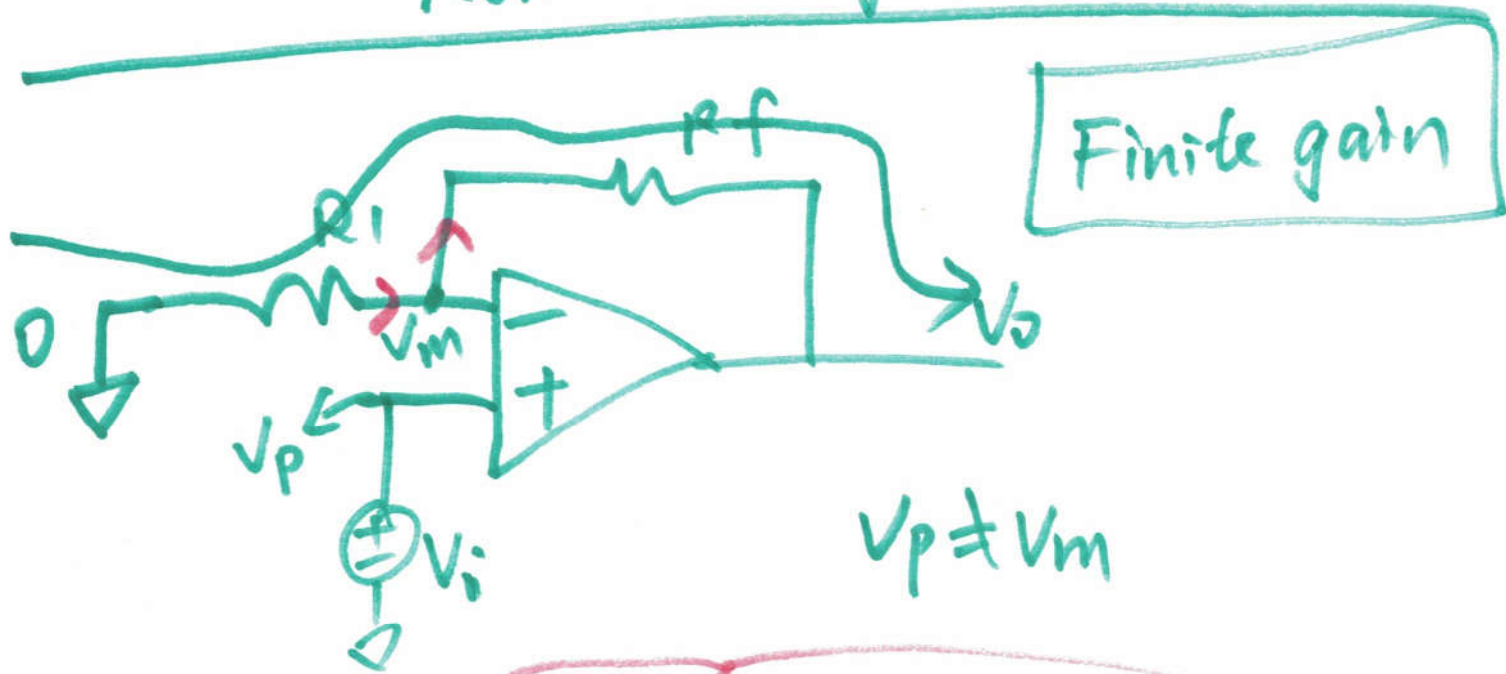

$$\frac{0 - V_m}{R_i} = \frac{V_m - V_o}{R_f}$$

$$\left((V_p - V_m) \cdot A = V_o \right) \Rightarrow (V_i - V_m) \cdot A = V_o$$

$$V_p = V_i \Rightarrow V_m = \frac{V_o}{A} V_i - \frac{V_o}{A}$$

$$\frac{0 - V_i + \frac{V_o}{A}}{R_i} \quad \cancel{=} \quad \frac{V_i - \frac{V_o}{A} - V_o}{R_f}$$

$$-V_i \cdot R_f + \frac{V_o}{A} \cdot R_f = V_i R_i - \frac{V_o}{A} \cdot R_i - V_o R_i$$

$$+ V_i (R_f + \alpha_i \cdot R_i) = \left(\frac{R_f}{A} + \frac{R_i}{A} + R_i \right) \cdot V_o$$

$$\frac{V_o}{V_i} = \frac{R_f + R_i}{\frac{R_f}{A} + \frac{R_i}{A} + R_i}$$


if $A = \infty$

$$\frac{V_o}{V_i} = \frac{R_f + R_i}{R_i} = \boxed{1 + \frac{R_f}{R_i}}$$

(4)


Difference Amplifier

Infinite Gain

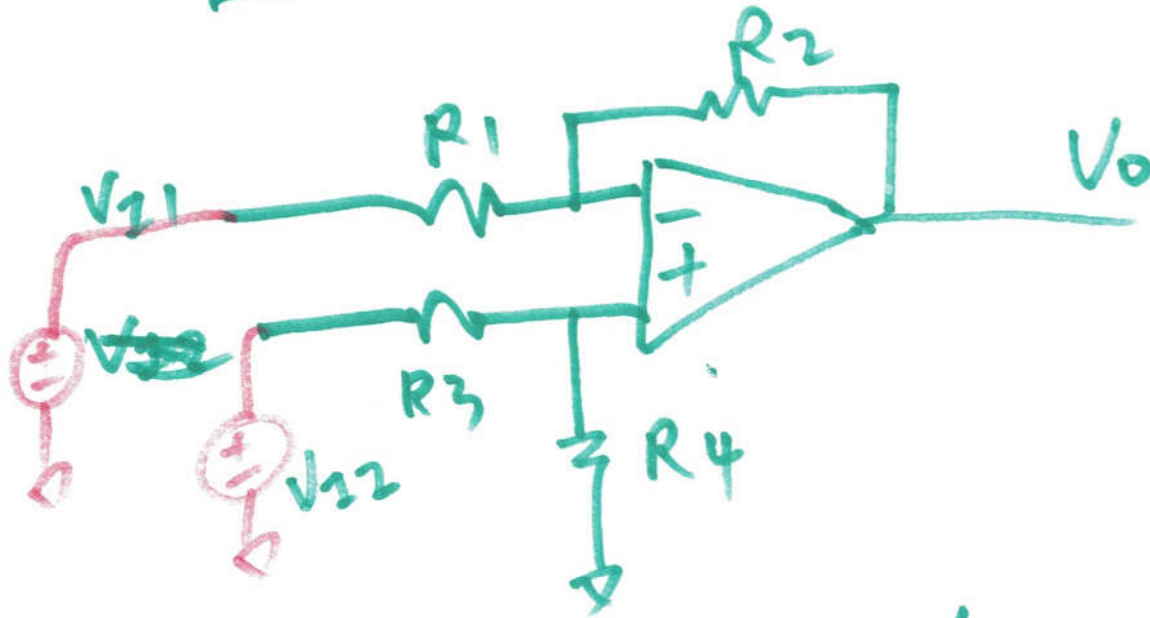

① Differential Gain A_d

Short V_2 :

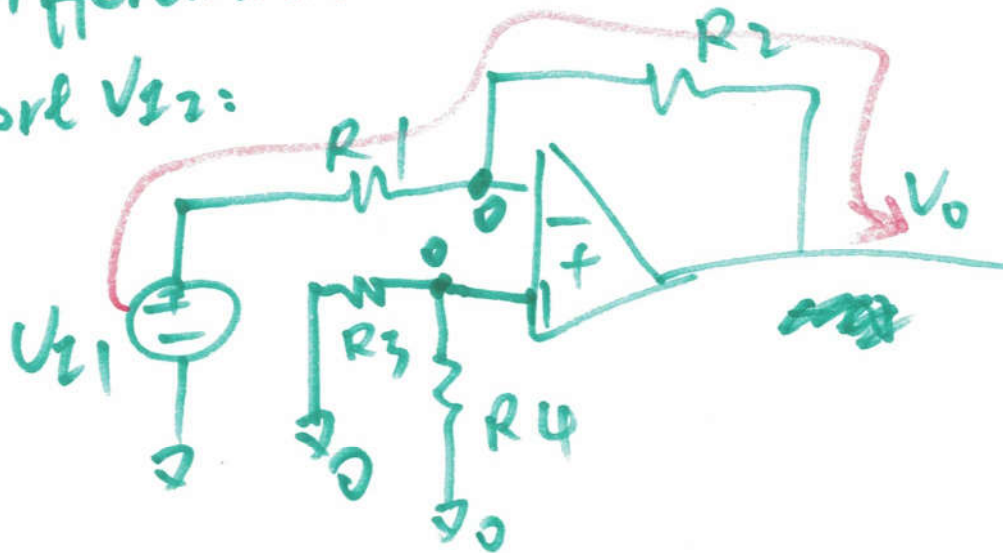


$$\frac{-R_f}{R_i}$$

⑤

$$\frac{V_{I1} - 0}{R_1} = \frac{0 - V_0}{R_2}$$

$$\frac{R_2}{R_1} = -\frac{V_0}{V_{I1}}$$
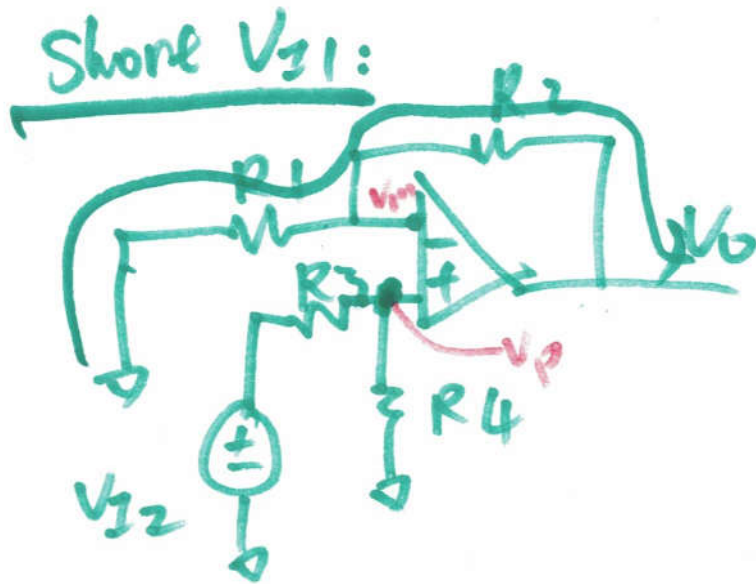
$$\frac{V_0}{V_{I1}} = -\frac{R_2}{R_1}$$



$$V_p = V_{I2} \cdot \frac{R_4}{R_3 + R_4}$$

$$\frac{0 - V_m}{R_1} = \frac{V_m - V_0}{R_2}$$

$$V_m = V_p$$

⑥

$$0 - V_{I2} \cdot \frac{R_4}{R_4 + R_3} = \frac{V_{I2} \cdot \frac{R_4}{R_3 + R_4} - V_0}{R_2}$$

$$\frac{R_2}{R_1} = \frac{V_0 - V_{I2} \cdot \frac{R_4}{R_3 + R_4}}{V_{I2} \cdot \frac{R_4}{R_3 + R_4}}$$

$$= \frac{V_0}{V_{I2} \cdot \frac{R_4}{R_3 + R_4}} - 1$$

$$\frac{V_0}{V_{I2}} = \left(1 + \frac{R_2}{R_1}\right) \cdot \frac{R_4}{R_3 + R_4}$$

Given/choose $\boxed{\begin{matrix} R_1 = R_3 \\ R_2 = R_4 \end{matrix}}$ $\frac{V_0}{V_{I2}} = \frac{\cancel{R_1 + R_2}}{R_1} \cdot \frac{R_2}{\cancel{R_1 + R_2}}$

①

$$\frac{V_0}{V_{I_2}} = \frac{R_2}{R_1}$$

Finally (super-position),

$$V_0 = V_{I_2} \cdot \frac{R_2}{R_1} + (-V_{I_1} \cdot \frac{R_2}{R_1})$$

$$= (V_{I_2} - V_{I_1}) \cdot \frac{R_2}{R_1}$$

$$\therefore V_d = \frac{V_0}{V_{I_2} - V_{I_1}} = \frac{R_2}{R_1} = \frac{R_4}{R_3}$$