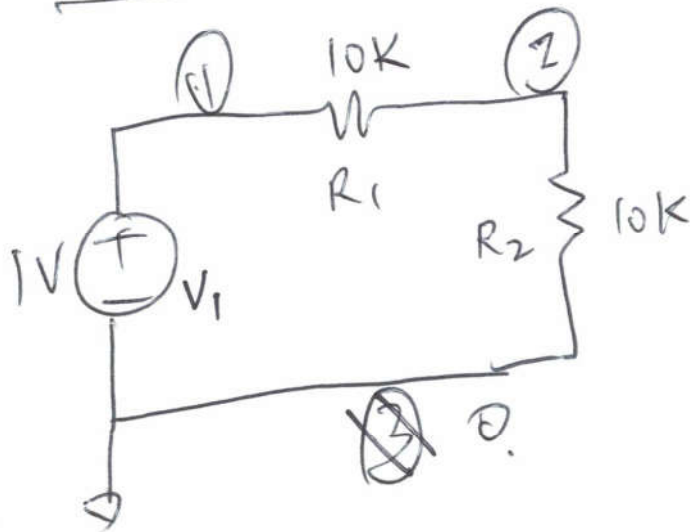


lec 3

LT 741

Spice Code

AD



voltage nodes

Method I:

Open a text editor, type the following spice code, and open the text file in LT Spice.

Example 1:

V1 1 0 dc 1

R1 1 2 10K

R2 2 0 10K

.tran 0 1 0.01

transient analysis

starting point
ending point
→ intervals

Method II:

Use .op to type the Spice code

Method IV:

Draw the schematic

