

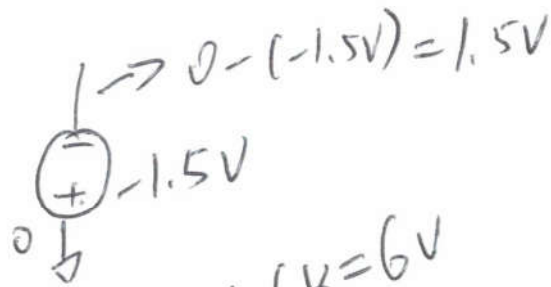
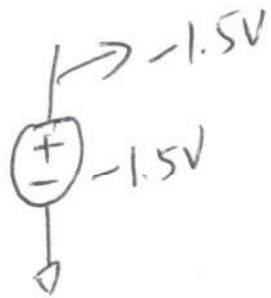
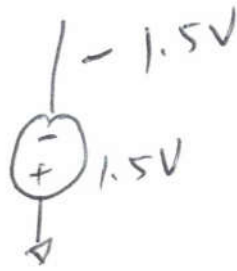
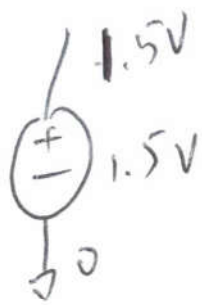



HW1 / Quiz / Review

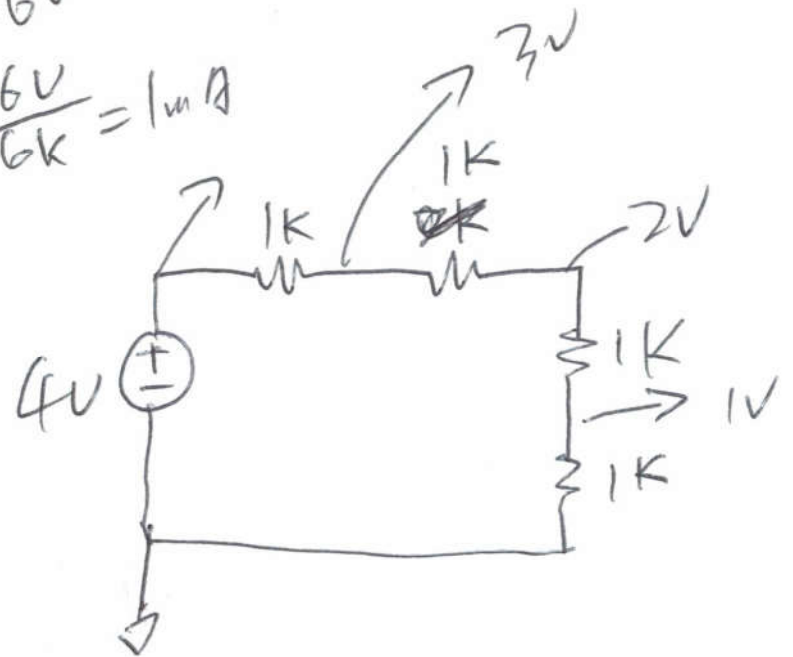

$$1.6k = 1mA \cdot 6k = 6V$$

$$I = \frac{6V}{6k} = 1mA$$

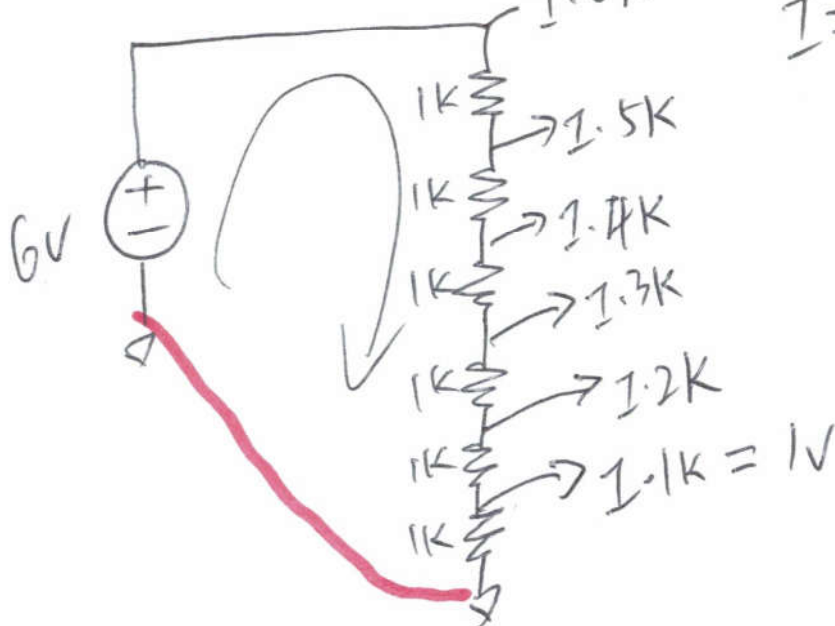

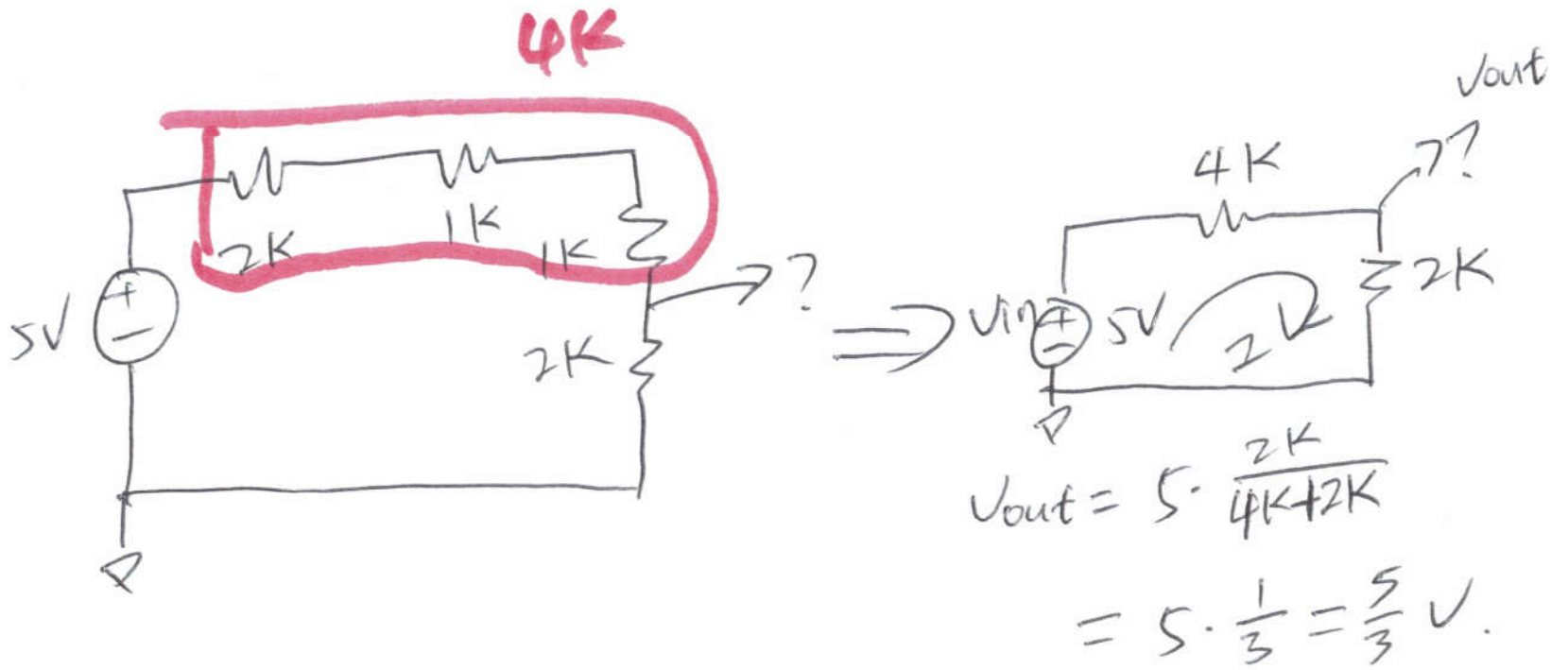


$$V_{out} = 5 \cdot \frac{2K}{4K + 2K}$$

$$= 5 \cdot \frac{1}{3} = \frac{5}{3} V$$

$$\frac{V_{out}}{V_{in}} = \frac{I \cdot 2K}{I \cdot 6K} = \frac{1}{3}$$

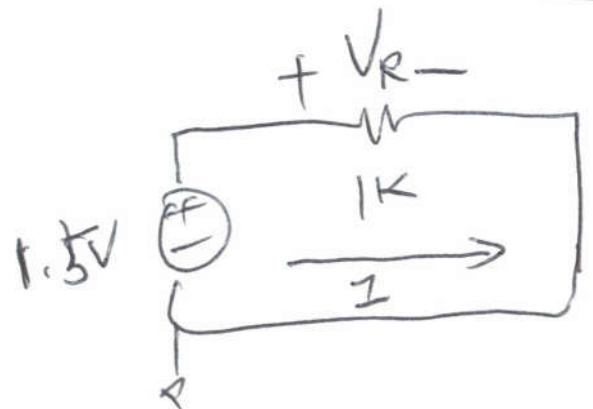
$$V_{out} = \frac{1}{3} \cdot V_{in} = \frac{5}{3} V$$



$$V_R = 1.5V$$

$$I = \frac{1.5V}{1K} = 1.5mA$$

(2)

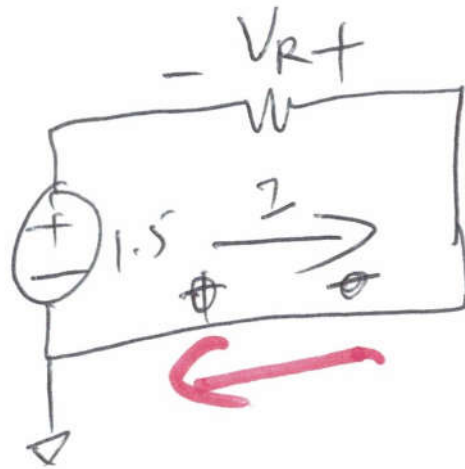

$$V_R = -1.5V$$
$$I = \frac{1.5V}{1k} = 1.5mA$$

(3)

Lab 2

2.

Calculation		Simulation		Measurement	
I	Vout	I	Vout	I	Vout

• tran. 0 | 0.01

3.

• dc V₁ 0 5 0.01

↑
the source
to be
swept

↓
starting
point

→
ending
voltage

→ increment

Kirchoff's voltage Law (KVL)

Kirchoff's Current Law (KCL)

KVL: The sum of all voltages in an electrical circuit

Loop is 0. $\sum_k V_k = 0$



$$-V + V_{R1} + V_{R2} = 0$$


$$V_{R1} + V_{R2} = V$$

$$V = 1.5V$$

$$V_{R1} = \frac{1.5}{2k} \cdot 1k = 0.75V$$

$$V_{R2} = 0.75V$$

$$-1.5 + 0.75 + 0.75 = 0$$

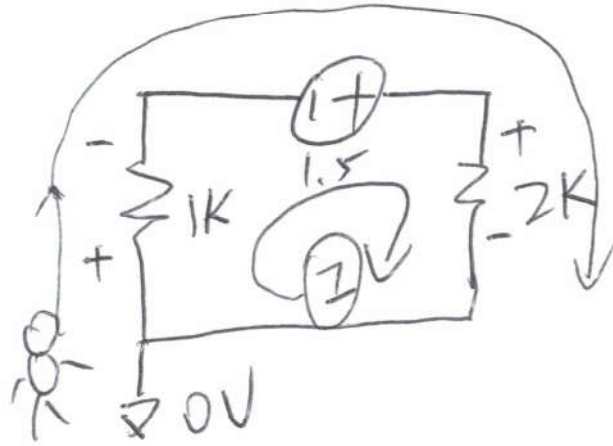

$$+1K \cdot I - 1.5 + 2K \cdot I = 0$$

$$3K \cdot I = 1.5$$

$$I = \frac{1.5}{3K} = 0.5 \text{ mA}$$



KCL: The sum of all currents enter an electrical junction

$$\text{TS D. } \sum_k I_k = 0.$$



$$-I_1 + I_2 + I_3 = 0$$


$$\underline{I_2 + I_3 = -I_1}$$

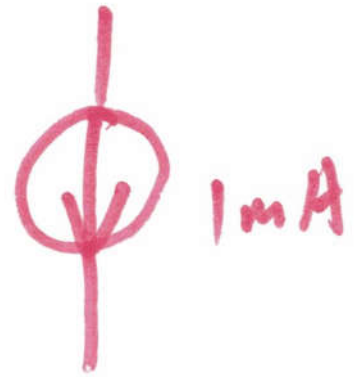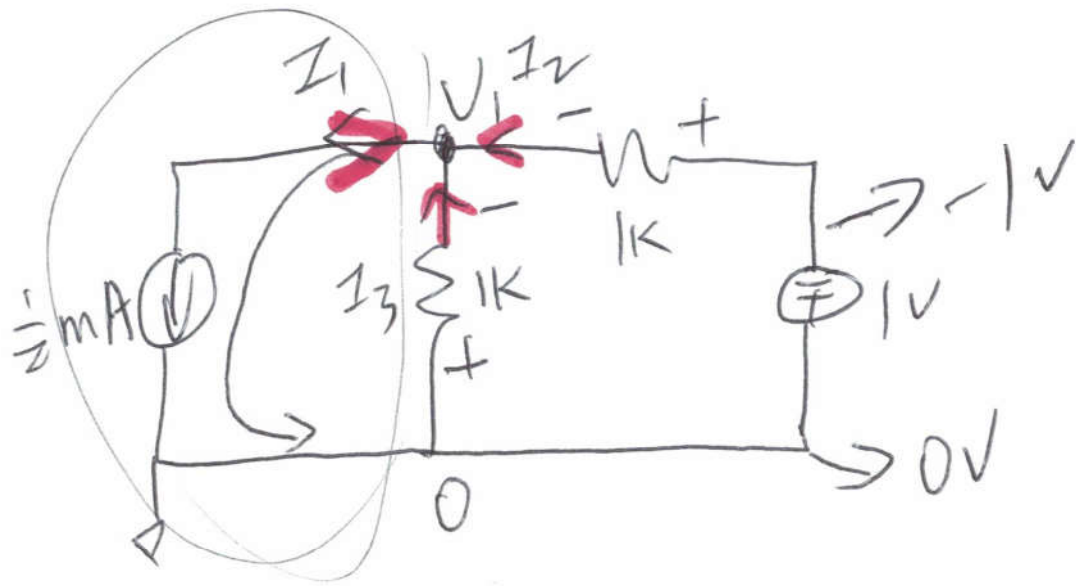

50 Ω

100k Ω
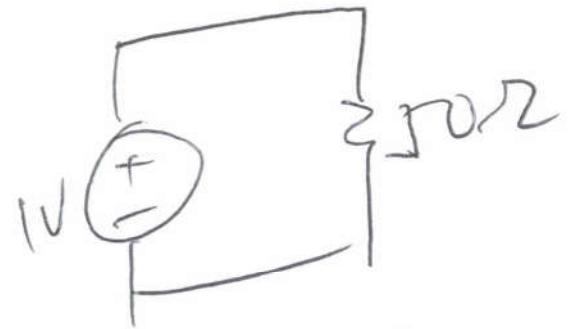
$$\begin{cases} I_1 + I_2 + I_3 = 0 & \textcircled{1} \\ I_1 = -0.5 \text{ mA} & \textcircled{2} \\ I_2 = \frac{-1 - V_1}{1\text{k}} & \textcircled{3} \\ I_3 = \frac{0 - V_1}{1\text{k}} & \textcircled{4} \end{cases}$$



plug $\textcircled{2}$ $\textcircled{3}$ $\textcircled{4}$ into $\textcircled{1}$

$$-0.5 \text{ mA} + \frac{-1 - V_1}{1\text{k}} + \frac{0 - V_1}{1\text{k}} = 0$$

$$\frac{1\text{V}}{50\Omega}$$

$$-0.5 + (-1 - V_1) + 0 - V_1 = 0$$

⑦


$$-0.5 - 1 - V_1 - V_1 = 0$$

$$2V_1 = -1.5$$

$$V_1 = -0.75V$$

$$I_2 = \frac{-1 + 0.75}{1K} = -0.25 \text{ mA}$$
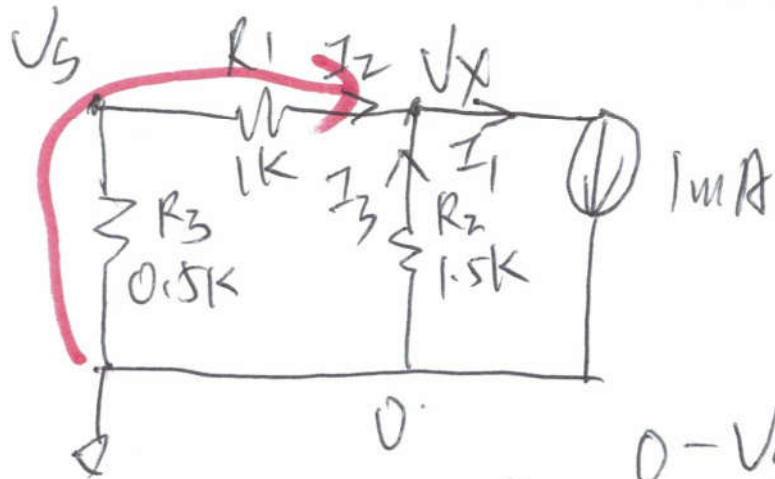
$$I_3 = \frac{0 + 0.75}{1K} = 0.75 \text{ mA}$$



$$I_2 = \frac{0 - V_S}{R_3}$$

$$I_1 = I_2 + I_3$$

$$I_1 = 1 \text{ mA}$$

$$\frac{0 - V_X}{R_2} = I_3$$

$$\frac{V_S - V_X}{1K} = I_2$$

8