
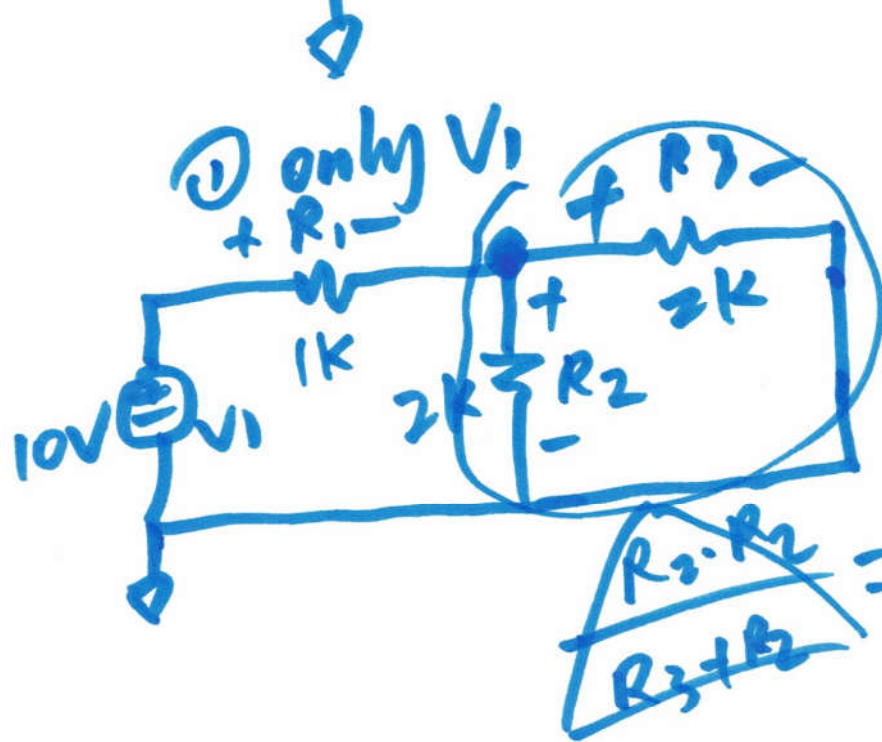


Superposition

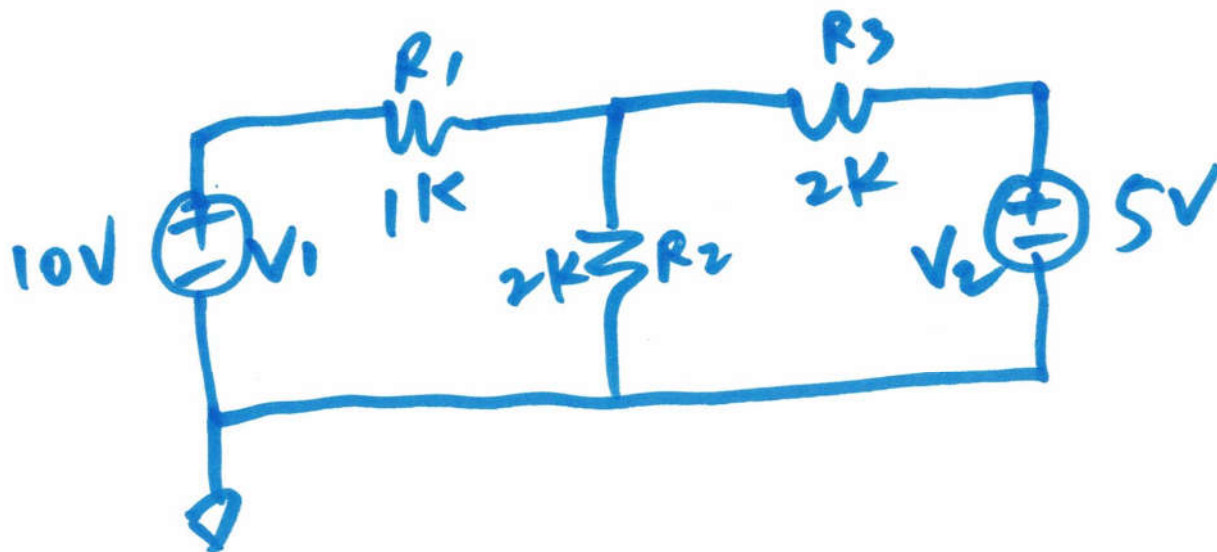


$$V_{R1} = 5V, \quad V_{R2} = \overset{5V}{\cancel{0V}} = V_{R3}$$

$$I_{R1} = \frac{V_{R1}}{1k} = 5mA$$

$$I_{R2} = \frac{V_{R2}}{2k} = 2.5mA$$

$$I_{R3} = 2.5mA$$

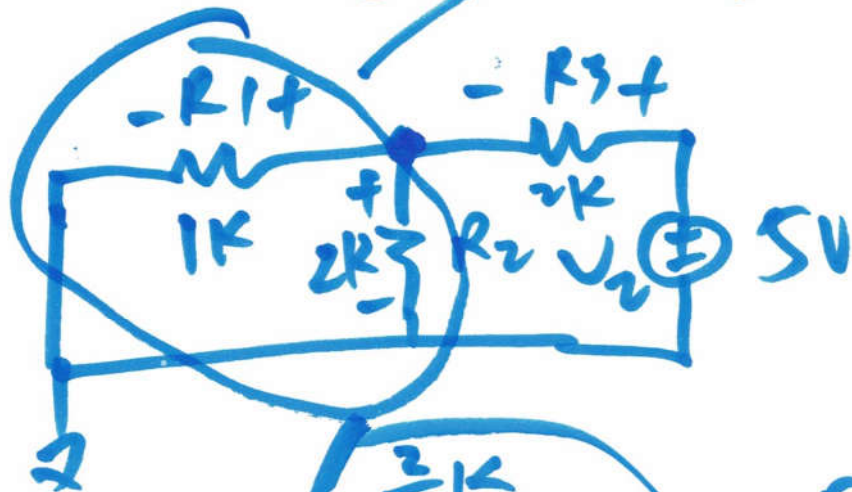② V_2 only $\rightarrow R_{eq} = \frac{1k \cdot 2k}{1k + 2k} = \frac{2}{3}k$




$$V_{R1} = 5 \cdot \frac{\frac{2}{3}k}{2k + \frac{2}{3}k} = 5 \cdot \frac{0.67k}{2.67k} = 1.25V$$

$$V_{R2} = V_{R1} = 1.25V, \quad V_{R3} = 5 \cdot \frac{2k}{2.67k} = 3.75V$$

$$I_{R1} = \frac{V_{R1}}{1k} = 1.25mA, \quad I_{R2} = \frac{1.25V}{2k} = 0.625mA$$

$$I_{R3} = \frac{V_{R3}}{2k} = \frac{3.75V}{2k} = 1.875mA$$

②

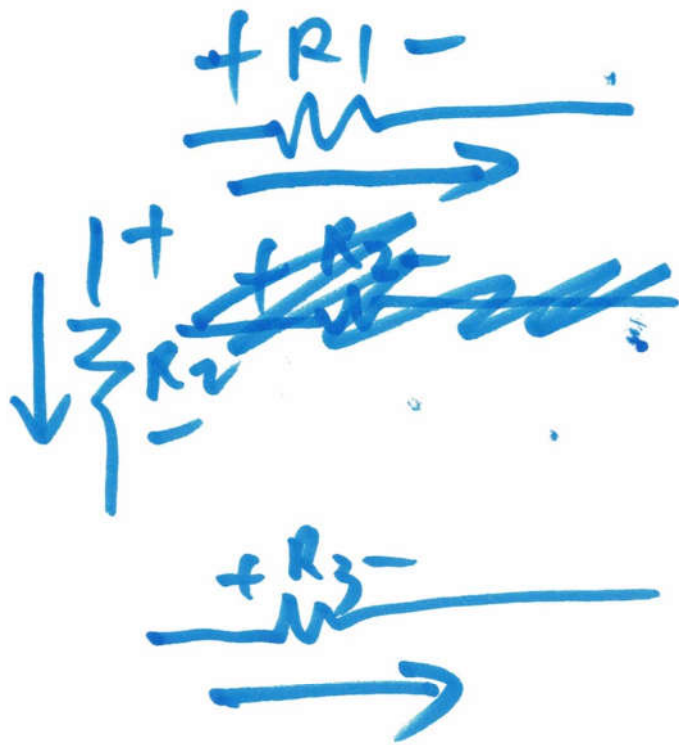

$$V_{R1} = 5V - 1.25V = 3.75V$$

$$V_{R2} = 5V + 1.25V = \cancel{6.25V} \\ 6.25V$$

$$V_{R3} = 5V - 3.75V = 1.25V$$

$$I_{R1} = 5mA - 1.25mA = 3.75mA$$


$$I_{R2} = 2.5mA + 0.625mA = 3.125mA$$

$$I_{R3} = 2.5mA - 1.875mA$$


$$= 0.625mA$$

③

2-2 (a)

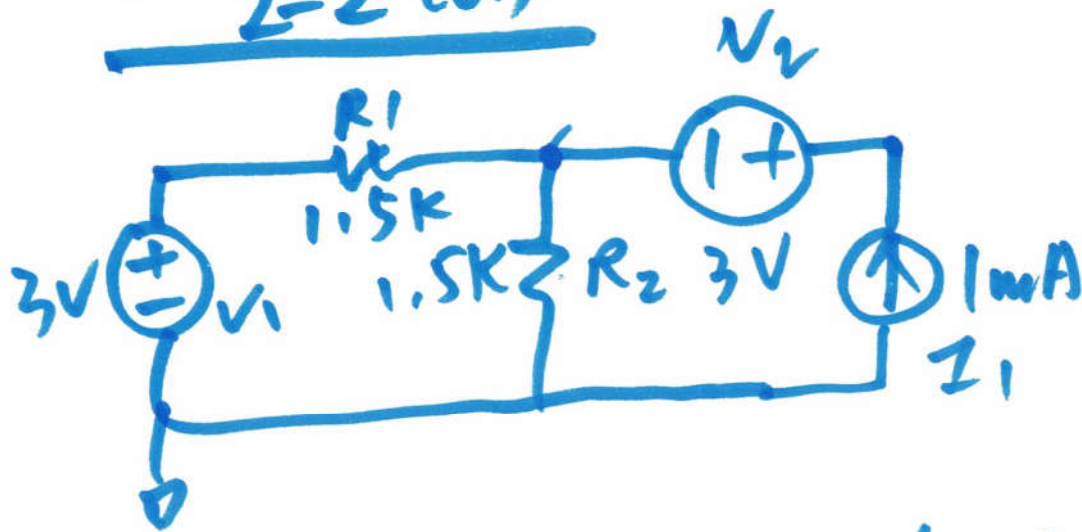


① V_1 only:

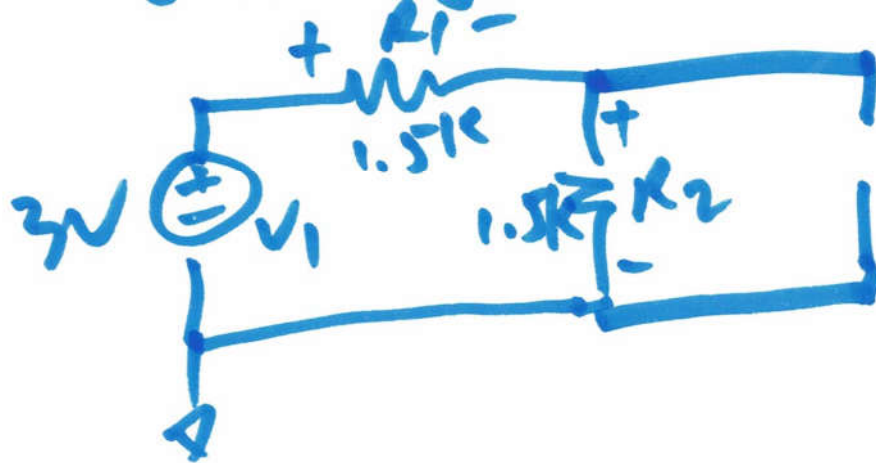

$$V_{R1} = 1.5V, V_{R2} = 1.5V$$

$$I_{R1} = 1mA, I_{R2} = 1mA$$

② ~~V_1~~ V_2 only

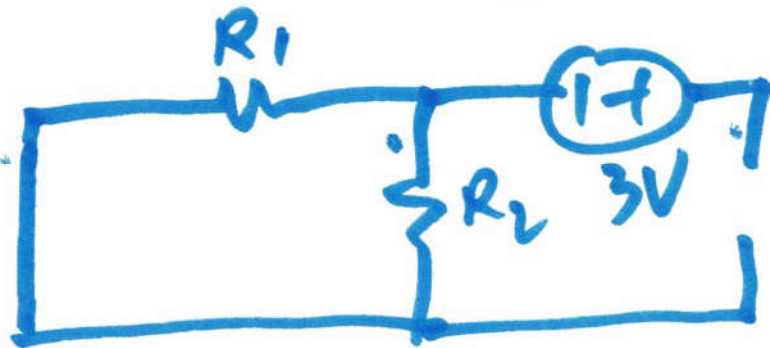

$$V_{R1} = 0V = V_{R2}$$

$$I_{R1} = 0 = I_{R2}$$


③ I_1 only



$$V_{R1} = 0.5mA \cdot 1.5K = 0.75V$$

$$V_{R2} = V_{R1} = 0.75V$$

$$I_{R1} = 0.5mA = I_{R2}$$

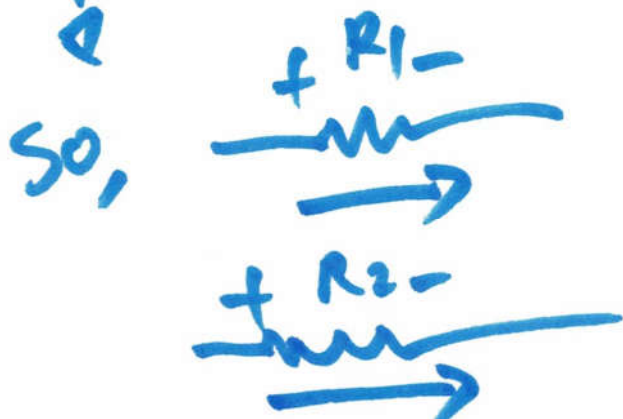

$$V_{R1} = 1.5V - 0.75V = 0.75V$$

$$V_{R2} = 1.5V + 0.75V = 2.25V$$

$$I_{R1} = 1mA - 0.5mA = 0.5mA$$

$$I_{R2} = 1mA + 0.5mA = 1.5mA$$