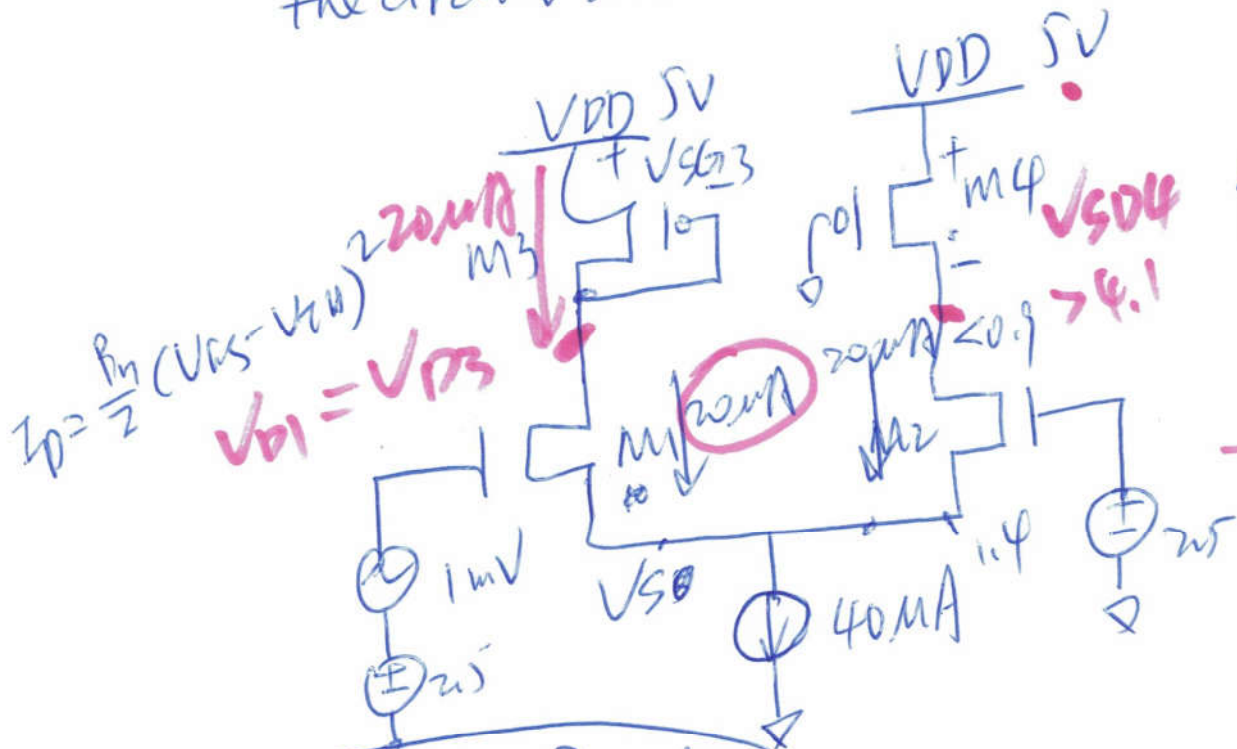


The Differential Pair

Calculate the DC and AC voltages and currents for the circuit seen below:



$\left\{ \begin{array}{l} \text{NMOS: } 10/2 \\ \text{PMOS: } 30/2 \end{array} \right.$



$I_{D1} = I_{D2}$
 scale: 300nm
 $2 \times 300\text{nm}$
 $= 600\text{nm}$

DC Operating Point

- ① M_1, M_2 have the same V_{GS} .
- ② $V_{GS1} = \sqrt{\frac{2I_D}{\beta_n}} + V_{THN} = \sqrt{\frac{2 \cdot 20\mu\text{A}}{170\mu\text{A} \cdot \frac{10}{2}}} + 0.8 = 1.058\text{V}$

500nm \leftarrow
CS on's Semiconductor.

$$V_S = V_{D1} - V_{GS1} = 2.5 - 1.058 = 1.442 \text{ V}$$

③ M_3 is Gate-Drain connected, operating in saturation

$$\underline{V_{SG3}} = \sqrt{\frac{2I_D}{\beta_p}} + V_{THP} = \sqrt{\frac{2 \times 70 \mu\text{A}}{40 \mu\text{A} - \frac{30}{2}}} + 0.9 = 1.158 \text{ V}$$

④ ~~V_{D3}~~ $V_{D3} = V_{D1} = 5 - V_{SG3} = 5 - 1.158 = 3.842 \text{ V}$.

⑤ $V_{G4} = 0$. $V_{SG4} = 5 \text{ V}$.

$$\underline{V_{SD4}} > \underline{V_{SG4}} - V_{THP}$$


$$= 5 - 0.9 = 4.1 \text{ V}$$

$\Rightarrow V_{D4} = V_{D2} < 0.9$ to make M_4 operates in saturation region.

⑥ M_4 is not in saturation)
 M_4 is not off

M_4 is operating in
the linear region.

AC Analysis

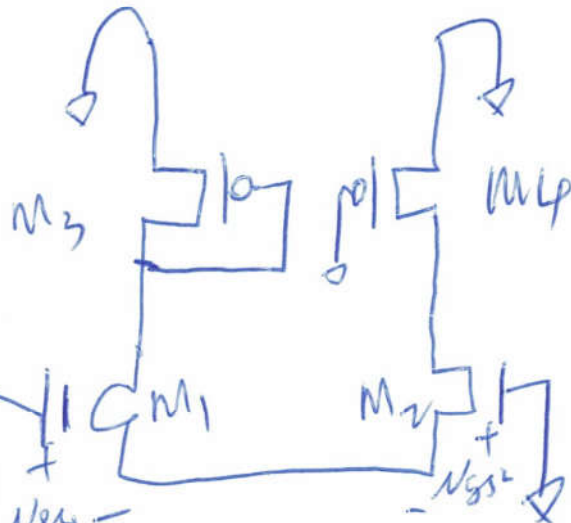

DC source is the AC ground

$$V_{GS} = \sqrt{\frac{2I_D}{\beta_n}} + V_{TN}$$

$$\textcircled{1} g_{m1} = g_{m2} = \sqrt{2\beta_n I_D}$$

$$= \sqrt{2 \cdot 200 \mu \frac{10}{2} \cdot 20 \mu} = 150 \mu A/V$$

$$\textcircled{2} g_{m3} = \sqrt{2\beta_p I_D} = \sqrt{2 \cdot 400 \mu \frac{30}{2} \cdot 20 \mu A} = 150 \mu A/V$$



$$\textcircled{3} M4: I_D = \beta_n \left[(V_{GS} - V_{TNP}) V_{SD} - \frac{V_{SD}^2}{2} \right]$$

$$\frac{1}{R_{eff}} = \frac{\partial I_D}{\partial V_{SD}} = \beta_n (V_{GS} - V_{TNP} - V_{SD}) \approx \beta_n (V_{GS} - V_{TNP})$$

$$z_p = \frac{\beta_n}{2} (V_{GS} - V_{TNP})^2$$

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \beta_n (V_{GS} - V_{TNP})$$
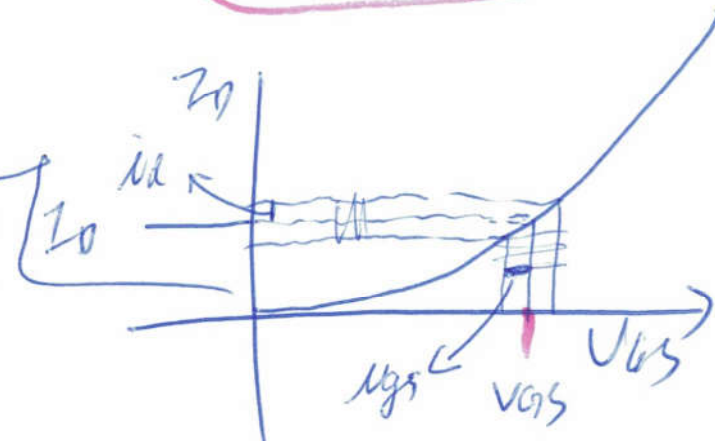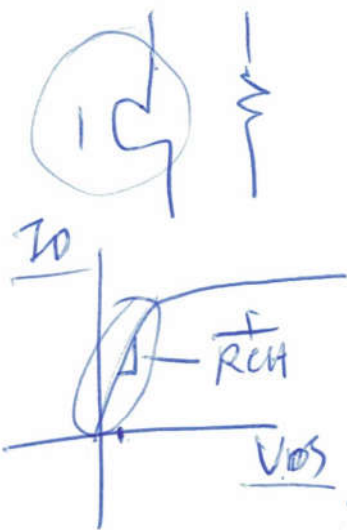
$$\frac{\partial z_p}{\partial V_{GS}} = g_m$$



$$\frac{1}{R_{CH}} = 40\mu - \frac{30}{2} (1.159 - 0.9)$$

$$R_{CH} = 407 \Omega$$

④ M_3 . $\frac{g_{m3} \cdot \cancel{V_{gs3}}}{N_{sg3}} = \frac{g_{m3} \cdot V_{sd3}}{\cancel{V_{sd3}}}$

$$g_m = \beta_p (V_{gs3} - V_{thp})$$

$$= i_d$$

$$g_{m3} = \frac{i_d}{V_{sd3}}$$

