
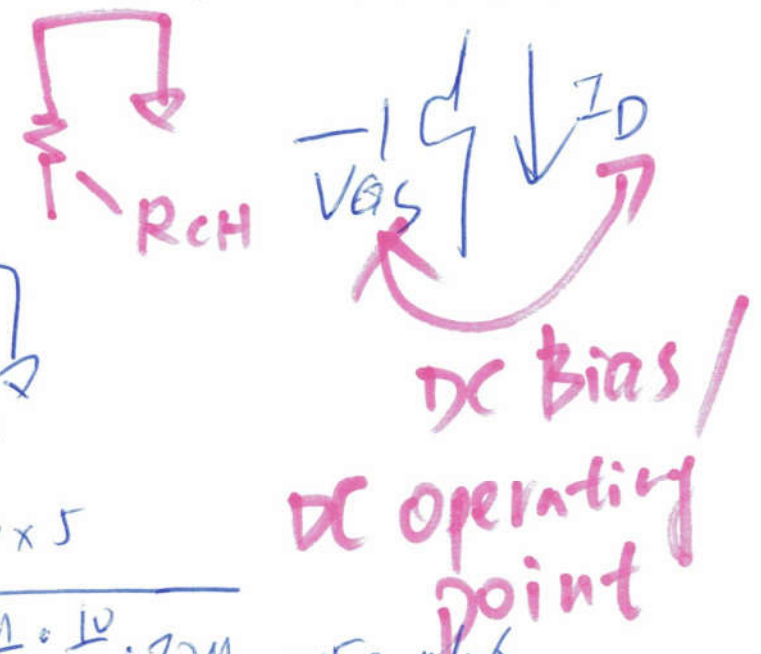


AC Analysis

CMOS Book: Chapter 9.

NMOS 10/2
PMOS 30/2

60nm
50nm

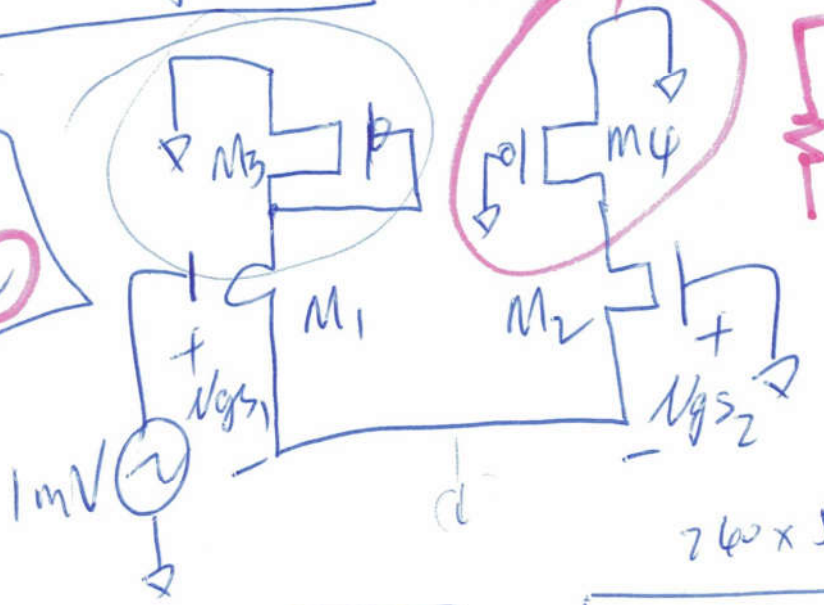


$$① g_{m1} = g_{m2} = \sqrt{2 \beta_n I_D} = \sqrt{2 \times \frac{120\mu\text{M}}{2} \cdot \frac{10}{2} \cdot 20\mu\text{M}} = 150 \mu\text{A/V}$$

$$② g_{m3} = \sqrt{2 \beta_p I_D} = \sqrt{2 \times \frac{40\mu\text{M}}{2} \cdot \frac{30}{2} \cdot 20\mu\text{A}} = 150 \mu\text{A/V}$$

$$③ M4: I_D = \beta_p \left[(V_{SG4} - V_{THP}) V_{SD4} - \frac{V_{SD4}^2}{2} \right]$$
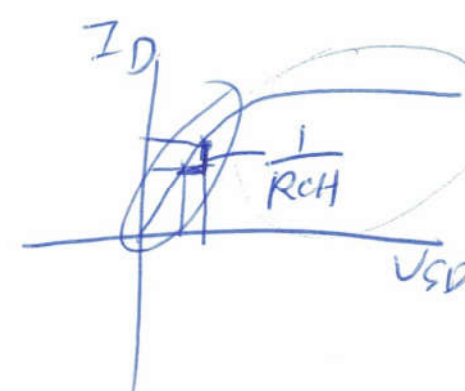
$$\frac{1}{R_{CH}} = \frac{\delta I_D}{\delta V_{SD}} = \beta_p \left[(V_{SG4} - V_{THP}) - V_{SD4} \right]$$




In the linear region, if $V_{SD} \ll V_{SG}$,
 $\frac{1}{R_{CH}} = \beta_p (V_{SG4} - V_{THP})$

(4)



$$g_{m3} v_{gsq} = i_d$$

$$v_{gsq} = v_{gsd}$$

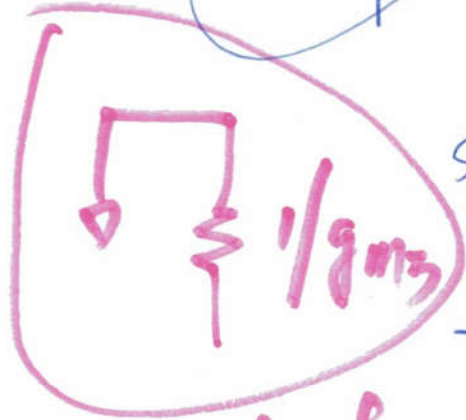


important

so, $i_d = g_{m3} v_{gsd}$

$$\frac{i_d}{v_{gsd}} = g_{m3}$$

$$\frac{v_{gsd}}{i_d} = \frac{1}{g_{m3}}$$

(5)

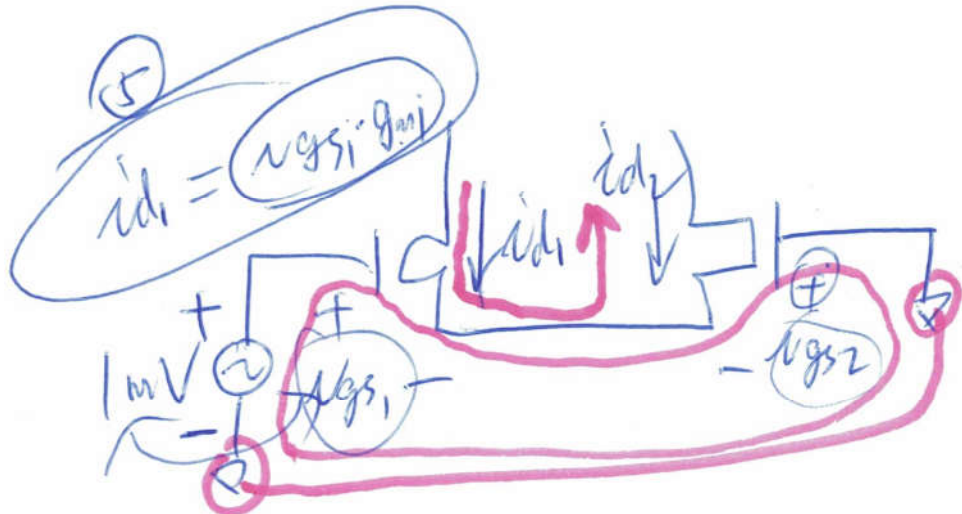

$$i_{d1} = v_{gs1} \cdot g_{m1}$$

$$\frac{-i_d}{v_{gs}} = g_{m1}$$

KVL:

$$-1mV + v_{gs1} - v_{gs2} = 0$$

$$v_{gs1} - v_{gs2} = 1mV$$

$$i_{d1} = -i_{d2}$$

$$\frac{i_{d1}}{g_{m1}} = -\frac{i_{d2}}{g_{m2}}$$

$$v_{gs1} = -v_{gs2}$$

(2)

$$V_{gs1} - (-V_{gs1}) = 1 \text{ mV}$$


$$V_{gs1} = 0.5 \text{ mV}$$

$$i_{d1} = -i_{d2} = g_m V_{gs} = 150 \mu \cdot 0.5 \text{ mV} = 75 \text{ nA}$$

The overall AC+DC drain current of M_1/M_2


$$i_{D3} = (i_{D1}) = \overbrace{20 \mu \text{A}}^{\text{DC}} + \overbrace{75 \text{ nA}}^{\text{AC}}$$
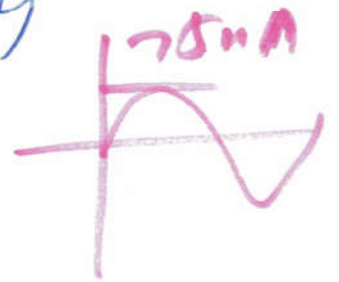
$$= \overbrace{20 \mu \text{A}}^{\text{DC}} + \overbrace{0.075 \sin 2\pi f t}^{\text{AC}}$$




AC+DC drain current of M_2/M_4
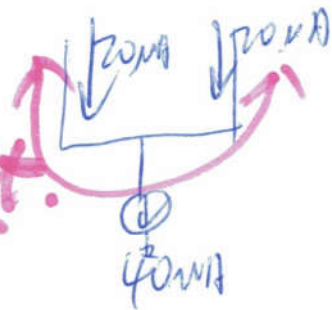
$$i_{D2} = i_{D4} = \overbrace{20 \mu \text{A}}^{\text{DC}} - \overbrace{0.075 \sin 2\pi f t}^{\text{AC}}$$



Current Mirrors Chapter 20.

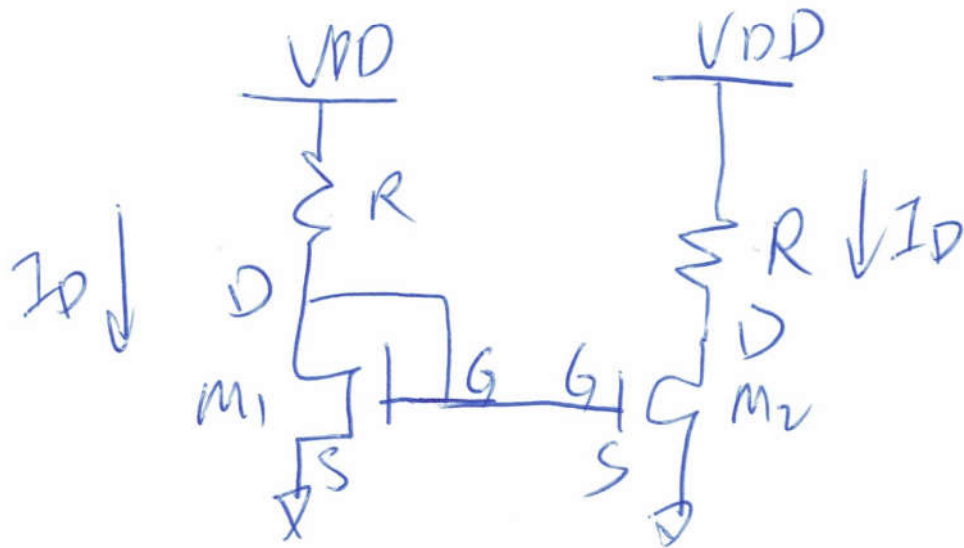


A Basic Current Mirror



① $V_{GS1} = V_{GS2} = V_{DS1}$

② same structure, same V_{GS} , **same I_D** , \Rightarrow
 same R .

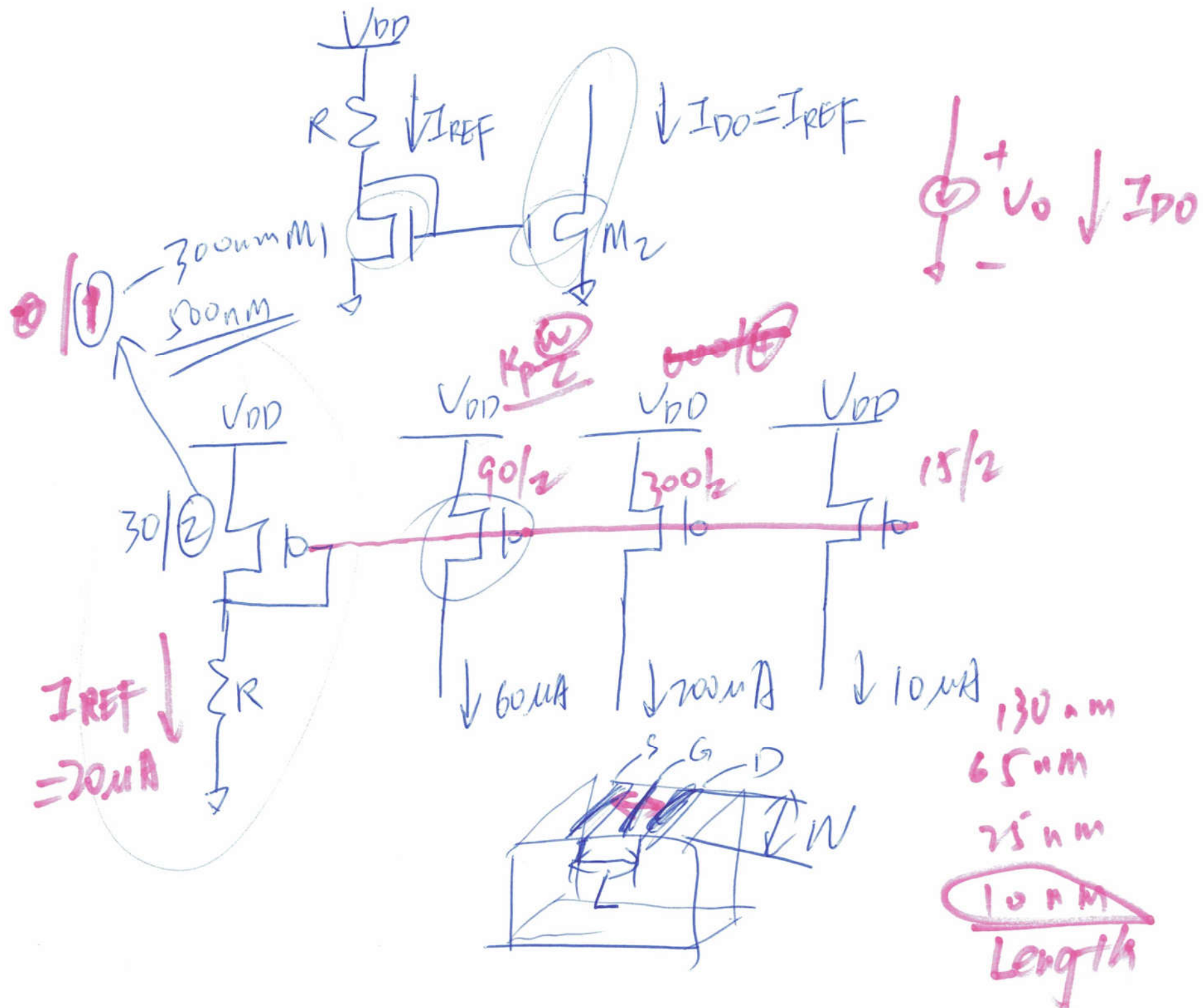same $V_{DS} \Rightarrow$ $V_{GS1} = V_{GS2} = V_{DS1} = V_{DS2}$



(5)

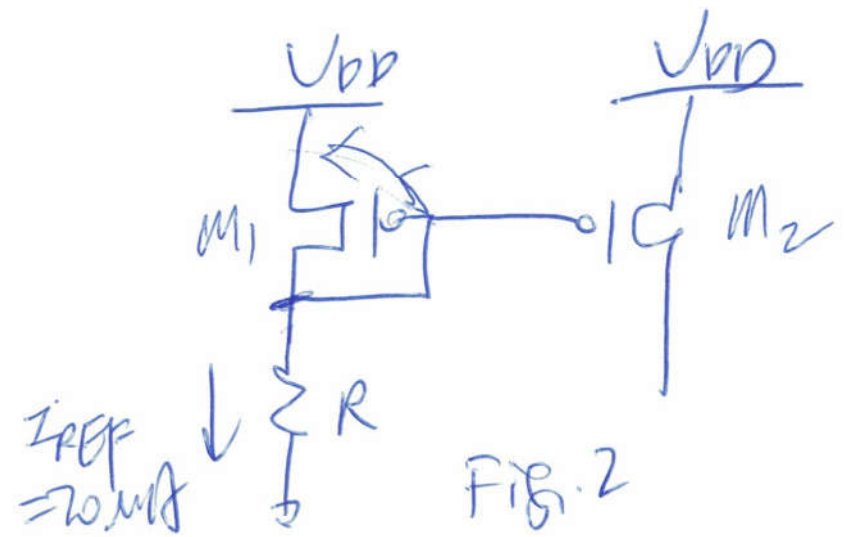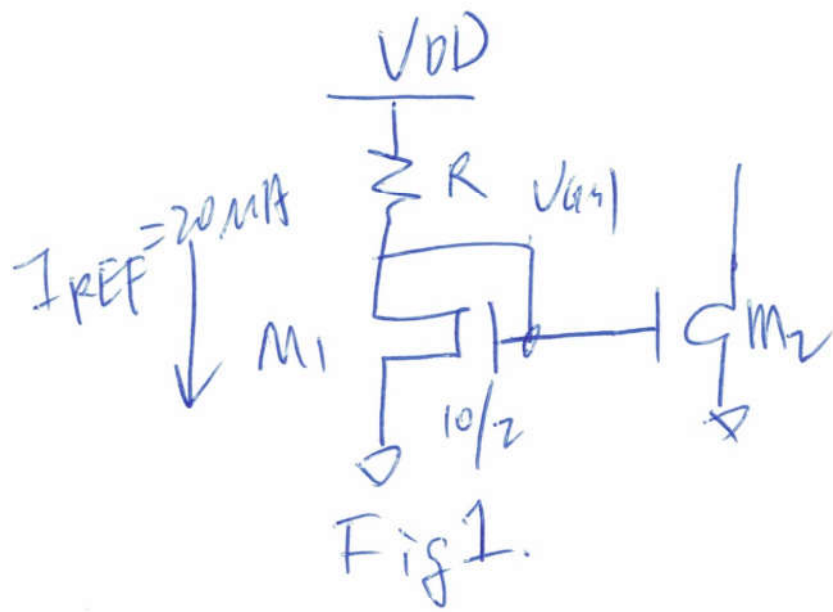

△ Determine the value of the resistor needed in Fig. 1 and Fig. 2, so the reference drain currents are 20µA.

$$I_{REF} = \frac{V_{DD} - V_{GS1}}{R} = \left(\frac{K_P}{2} \cdot \frac{10}{2} \right)^{P_n} (V_{GS1} - V_{THNM})^2 \quad \frac{40}{600}$$

$$I_D = I_{REF} \quad (V_{GS1}) = \sqrt{\frac{2 I_D}{\frac{K_P}{2} \cdot \frac{10}{2}}} + V_{THNM} = \sqrt{\frac{2 \cdot 20\mu A}{120\mu A \cdot \frac{10}{2}}} + 0.8$$

$$\frac{V_{DD} - V_{GS1}}{R} = 20\mu A \quad = 0.25 + 0.8$$

$$= 1.05 V$$

$$\frac{5 - 1.05}{R} = 20\mu A, \quad R = \frac{3.95}{20\mu A} = \frac{3.95}{20 \times 10^{-6}} = 197.5 K$$

(b)

$$\frac{V_{DD} - V_{SG1}}{R} = I_D = 20 \mu A$$

$$V_{SG1} = \sqrt{\frac{2I_D}{\beta_P}} + V_{THP}$$

$$= \sqrt{\frac{2 \times 20 \mu A}{40 \mu \cdot \frac{30}{2}}} + 0.9$$

$$= 0.259 + 0.9 = 1.159$$

$$\frac{5 - 1.159}{R} = 20 \mu A$$

$$R = 200 k \Omega$$