
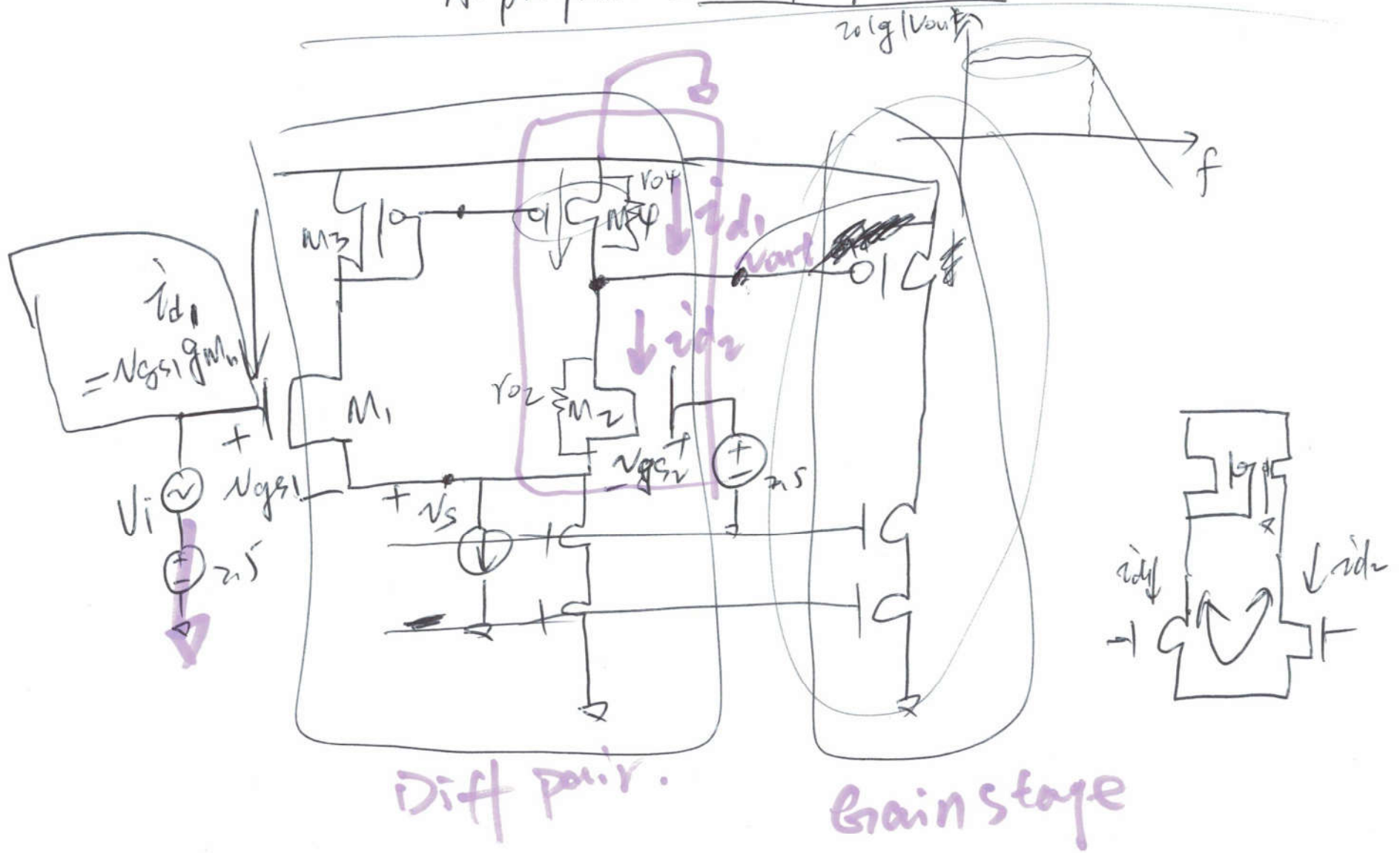


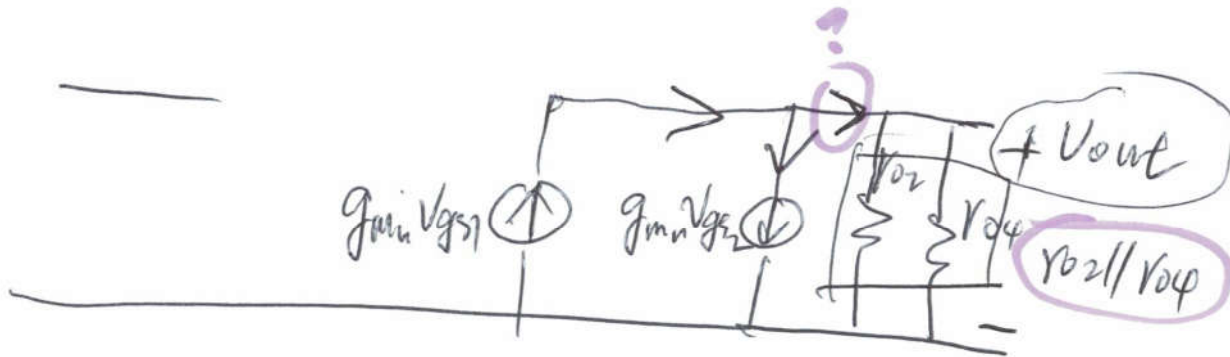Amplifiers (low-frequency open-loop gain)



small-signal model.



$$v_{out} = (g_{m1} v_{gs1} - g_{m2} v_{gs2}) (r_{o2} \parallel r_{o4})$$

$$\underline{v_{di}} = (v_{gs1} + v_s) - (v_{gs2} + v_s) = \underline{v_{gs1} - v_{gs2}}$$

$$v_{out} = g_{m1} \underline{(v_{gs1} - v_{gs2})} (r_{o2} \parallel r_{o4})$$




$$= g_{m1} \cdot v_{di} (r_{o2} \parallel r_{o4})$$

$$\boxed{\frac{v_{out}}{v_{di}} = g_{m1} (r_{o2} \parallel r_{o4})}$$

$$g_{m1} = \beta (v_{GS} - v_{TH})$$

$$r_o = \frac{1}{\lambda I_D}$$

Common Source Amplifier.

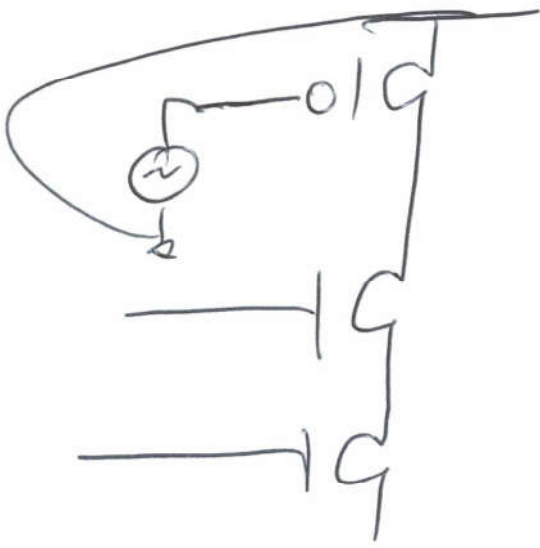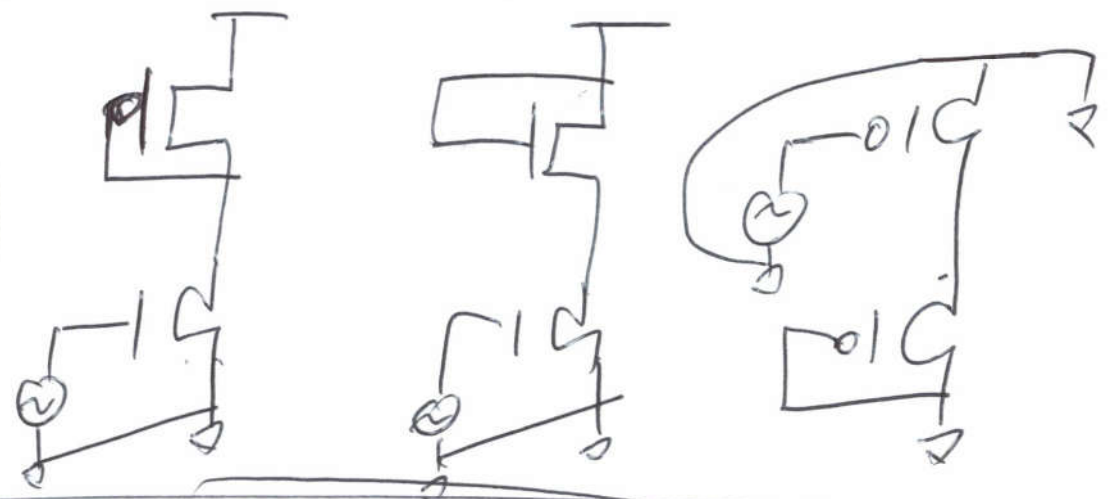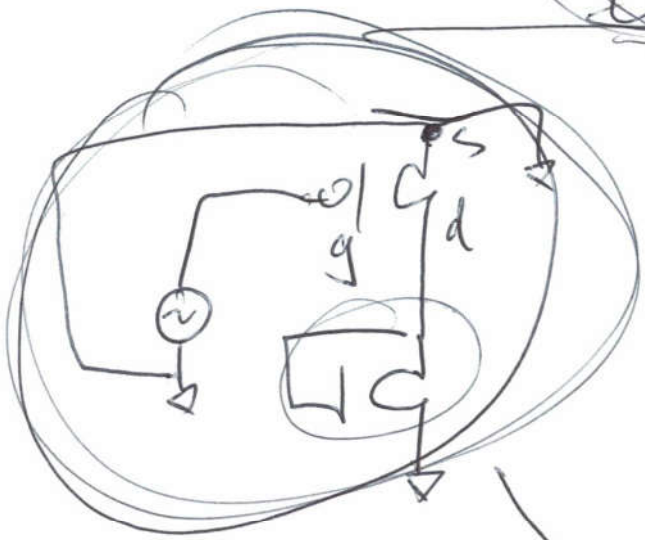

$$\frac{v_{gs} + i_s}{g_m} \Rightarrow \frac{1}{g_{mp}}$$



remember

$$i_d = g_{mp} v_{gs} = g_{mp} v_{sd}$$

$$\frac{v_{sd}}{i_d} = \frac{1}{g_{mp}}$$

$$\frac{1}{g_{mn}} \Rightarrow \frac{1}{g_{mn}}$$

remember

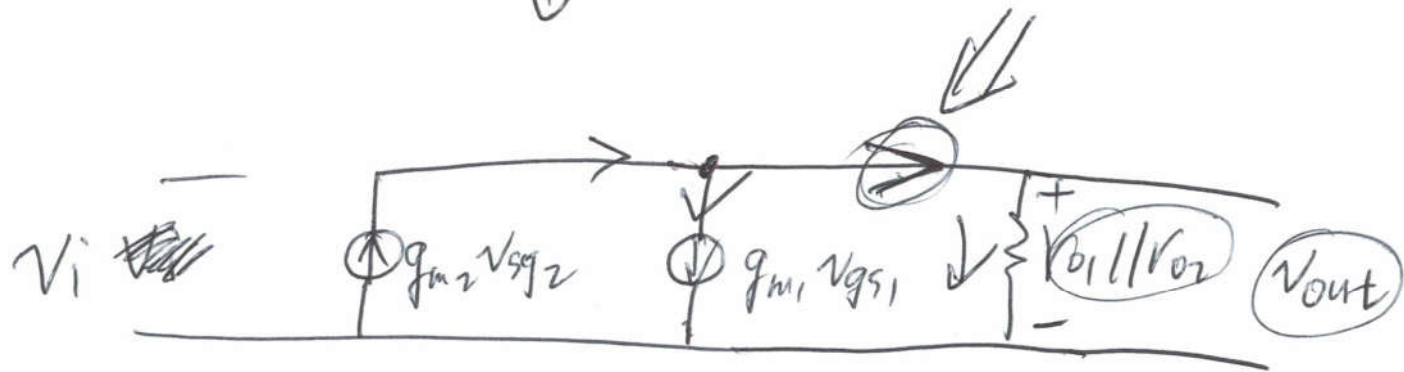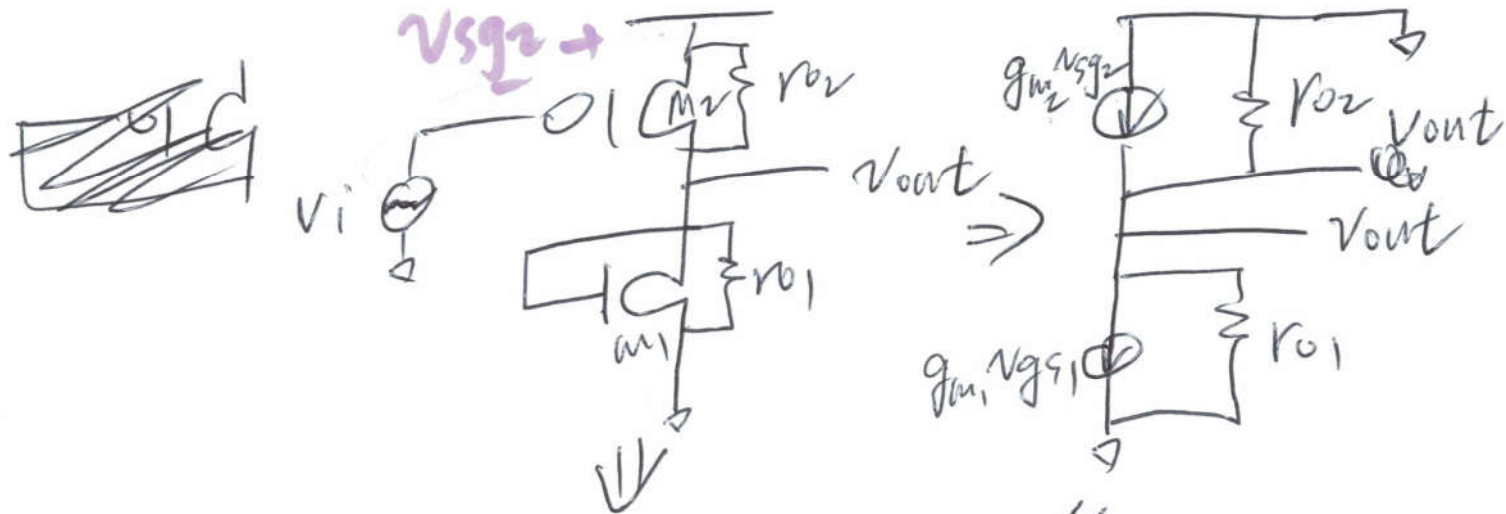




$$\frac{v_{out}}{v_i}$$

$$v_{out} = \left(\underbrace{g_{m2} v_{sg2}}_{-v_i} - \underbrace{g_{m1} v_{gs1}}_{v_{out}} \right) (r_{o1} || r_{o2})$$

$$v_{out} = (-g_{m2} v_i - g_{m1} v_{out}) (r_{o1} || r_{o2})$$



$$v_{out} (1 + g_{m1} (r_{o1} || r_{o2})) = -g_{m2} v_i (r_{o1} || r_{o2})$$

$$\frac{v_{out}}{v_i} = \frac{-g_{m2} (r_{o1} || r_{o2})}{1 + g_{m1} (r_{o1} || r_{o2})} = -\frac{g_{m2}}{g_{m1}}$$

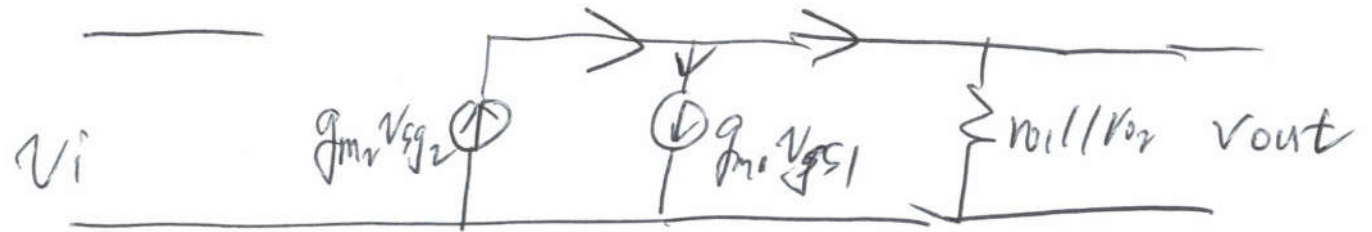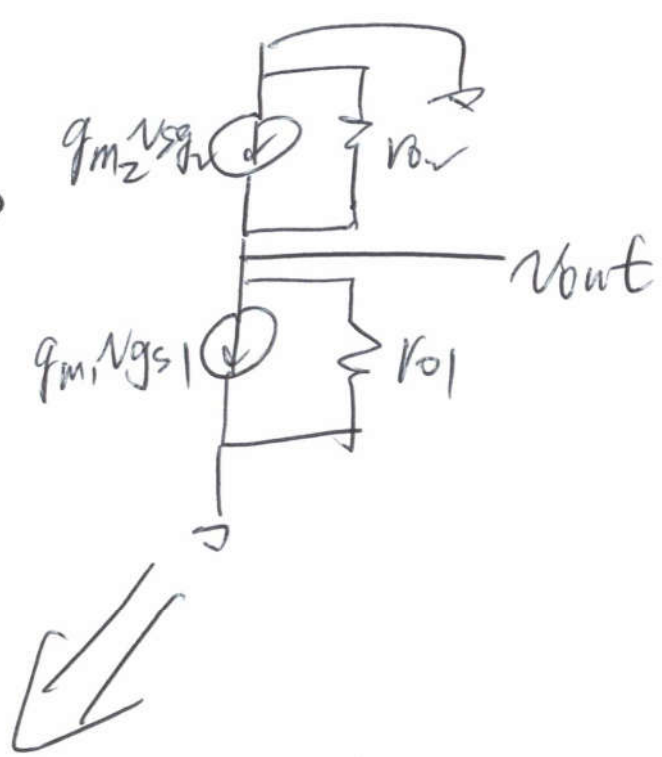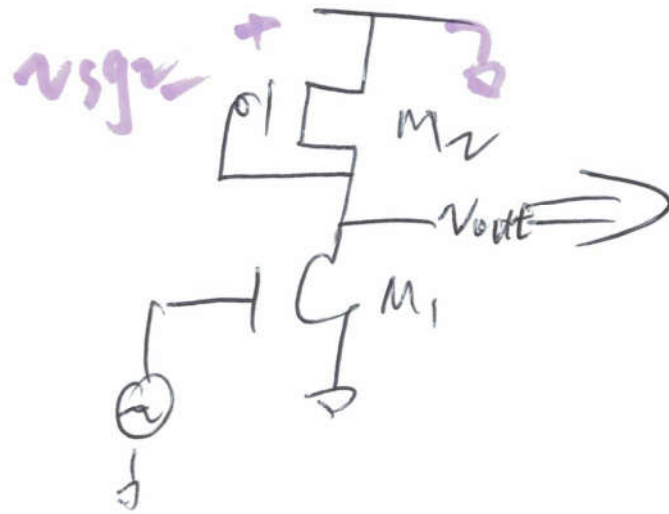

$$\begin{aligned}
 v_{out} &= (g_{m2} v_{sg2} - g_{m1} v_{gs1}) (r_{o1} \parallel r_{o2}) \\
 &\quad - v_{out} \quad v_i \\
 &= (-g_{m2} v_{out} - g_{m1} v_i) (r_{o1} \parallel r_{o2}) \\
 v_{out} (1 + g_{m2} (r_{o1} \parallel r_{o2})) &= -g_{m1} v_i (r_{o1} \parallel r_{o2}) \\
 \frac{v_{out}}{v_i} &= \frac{-g_{m1} (r_{o1} \parallel r_{o2})}{1 + g_{m2} (r_{o1} \parallel r_{o2})} = -\frac{g_{m1}}{g_{m2}}
 \end{aligned}$$

(5)

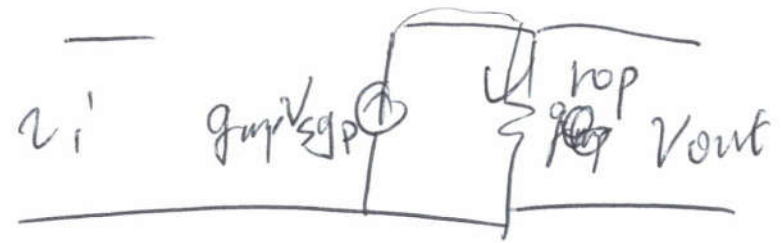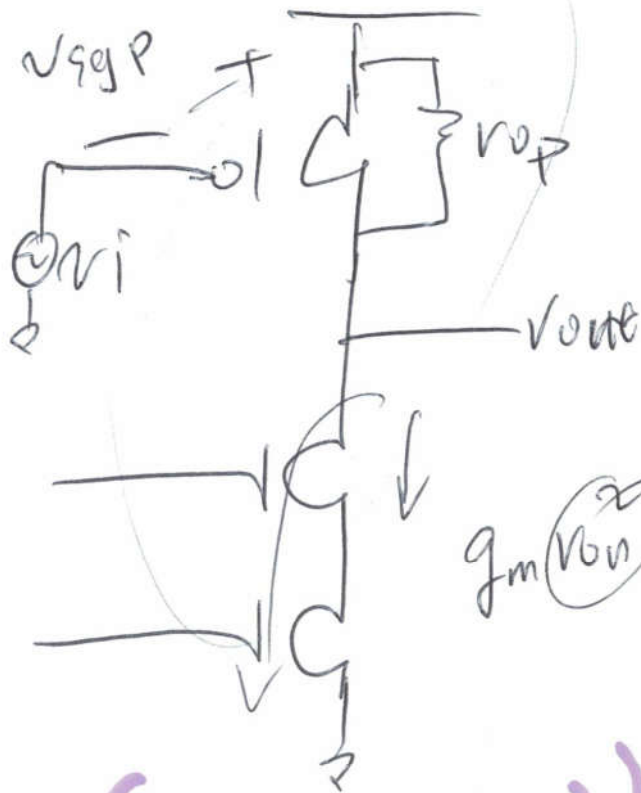

$$\begin{cases} v_{out} = (g_m V_{sgp}) r_{Op} \\ V_{sgp} = -v_i \end{cases}$$

$$\frac{v_{out}}{v_i} = -g_m r_{Op}$$

$-(g_m (r_{ov} || r_{Op})) (g_m r_{Op})$

