

$$i = \frac{V_{in} - V_{out}}{1/j\omega C_f} = j\omega C_f (V_{in} - V_{out})$$



$$V_{out} = V_{in} \cdot A_v$$

$$i = j\omega C_f (1 + |A_v|) V_{in}$$

$$= j\omega C_f (1 + \frac{1}{|A_v|}) V_{out}$$


$(1/g_{m2} || R_{o1} || R_{o2})$
 $\sim 1/g_{m2}$

$$A_v = - \frac{g_{m1}}{g_{m2}}$$

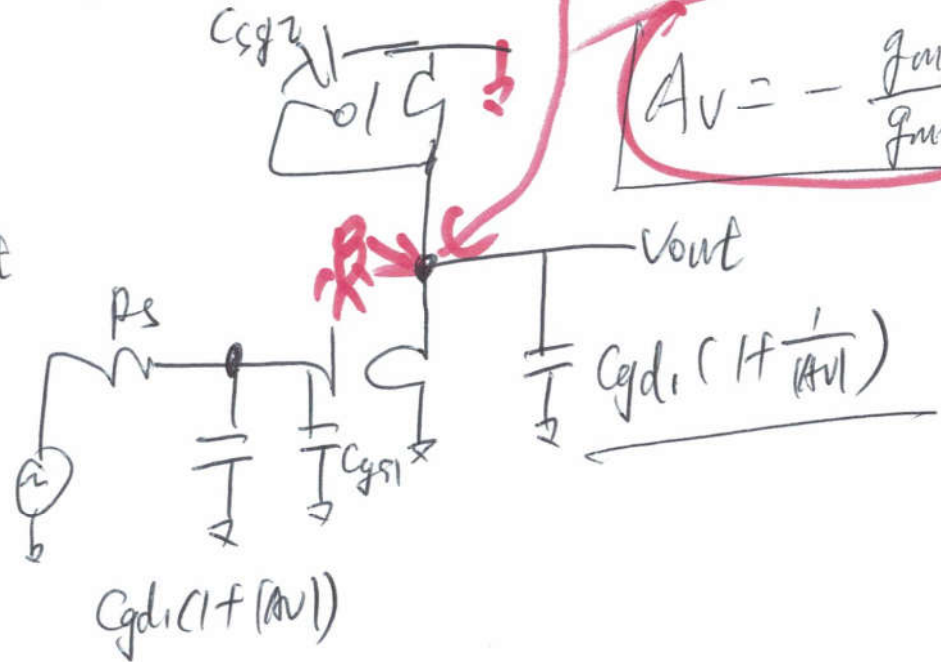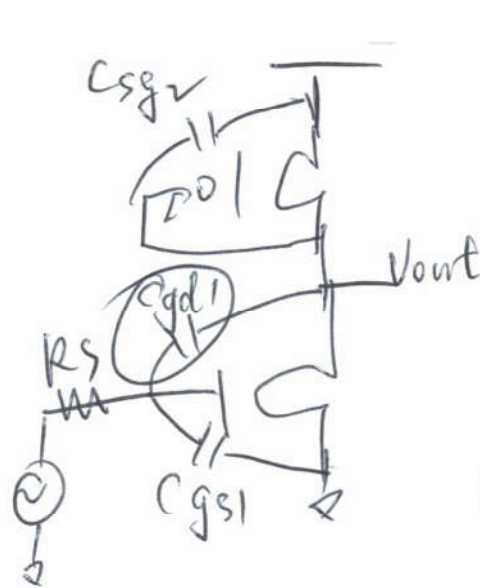

$$\begin{cases} C_{m1} = C_{gd1} \left(1 + \frac{g_{m1}}{g_{m2}} \right) \\ C_{m0} = C_{gd1} \left(1 + \frac{g_{m2}}{g_{m1}} \right) \end{cases}$$

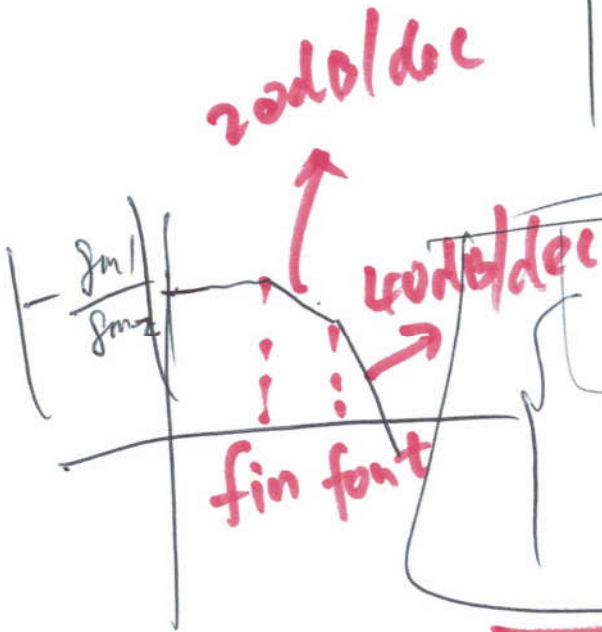
$$\begin{cases} \tau_{in} = R_1 C_1 = R_S (C_{m1} + C_{gs1}) \\ \tau_{out} = R_2 C_2 = \frac{1}{g_{m2}} (C_{m0} + C_{gs2}) \end{cases}$$




$$f_{in} = \frac{1}{2\pi R_1 C_1} = \frac{1}{2\pi R_S (C_{m1} + C_{gs1})}$$

$$f_{out} = \frac{1}{2\pi R_2 C_2} = \frac{1}{(2\pi/g_{m2}) (C_{m0} + C_{gs2})}$$





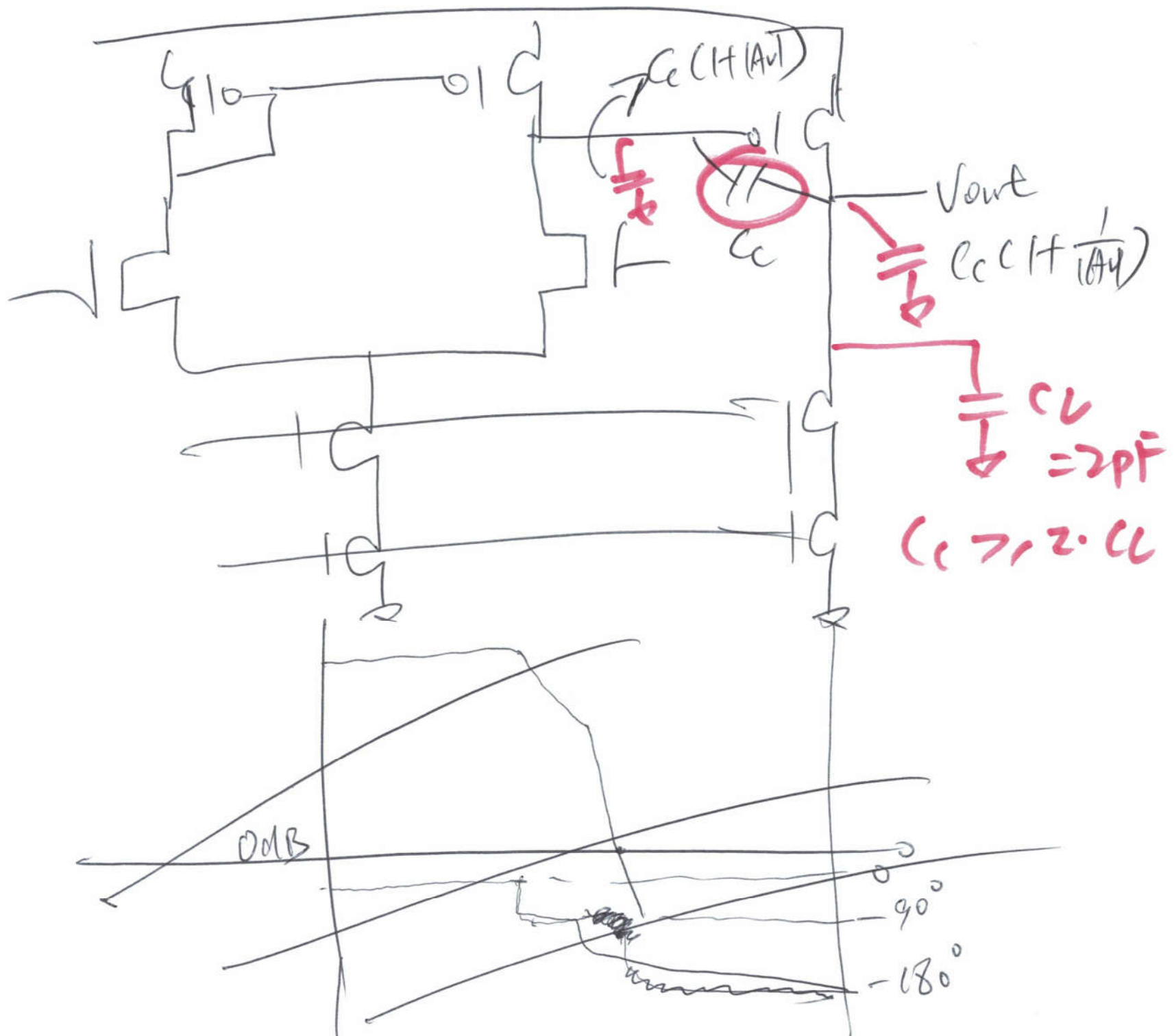
$$A_v(f) = \frac{-g_{m1}}{g_{m2}} \frac{1}{\left(1 + j \frac{f}{f_{in}} \right) \left(1 + j \frac{f}{f_{out}} \right)}$$




(3)

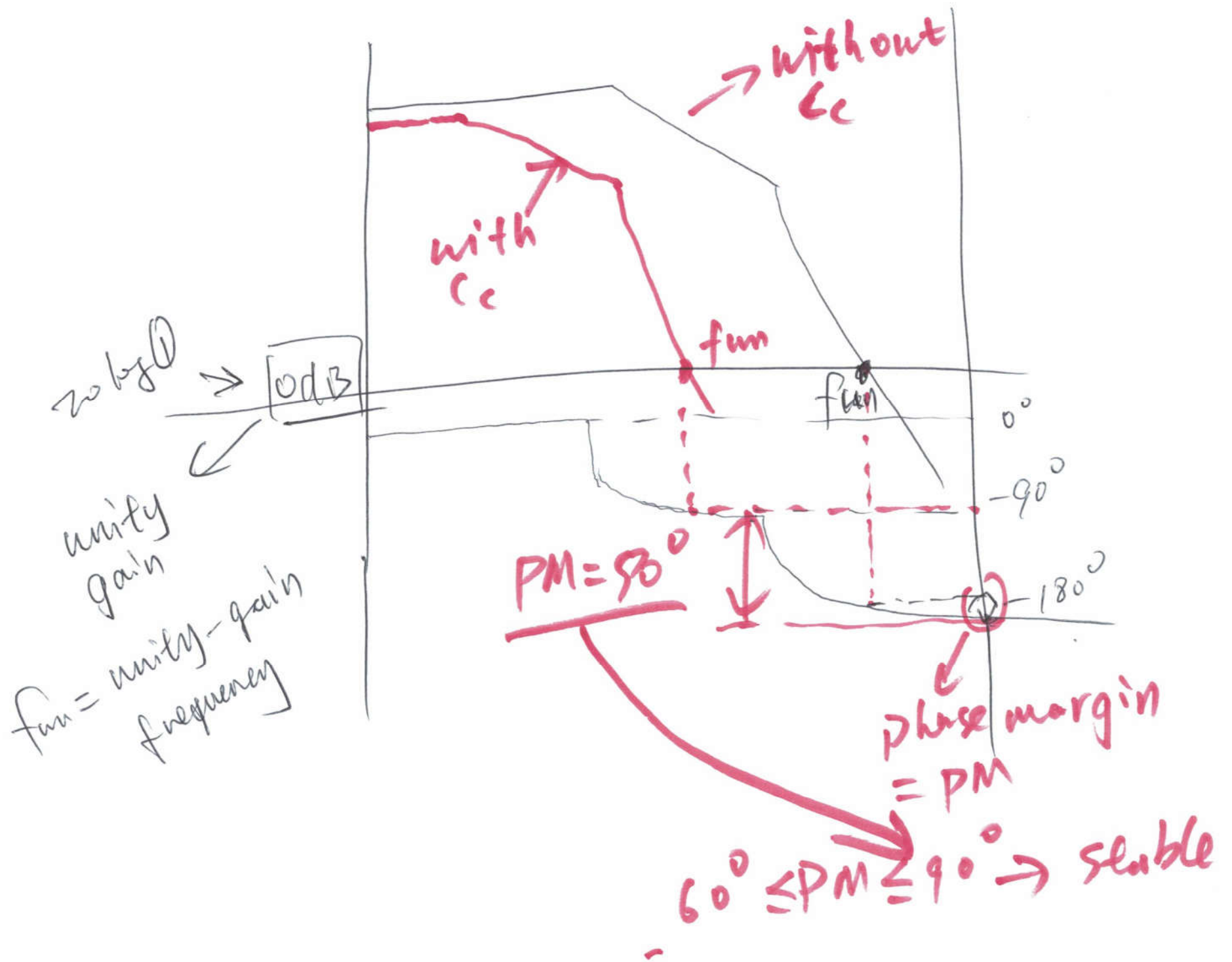

BJT - Transistors

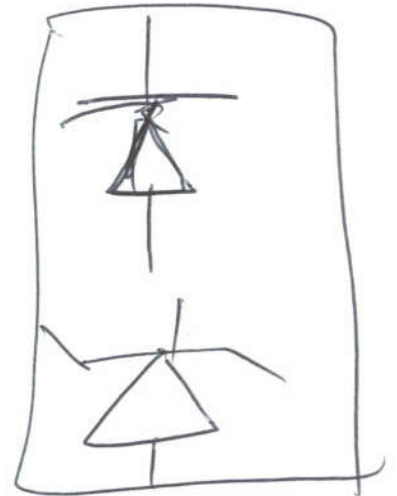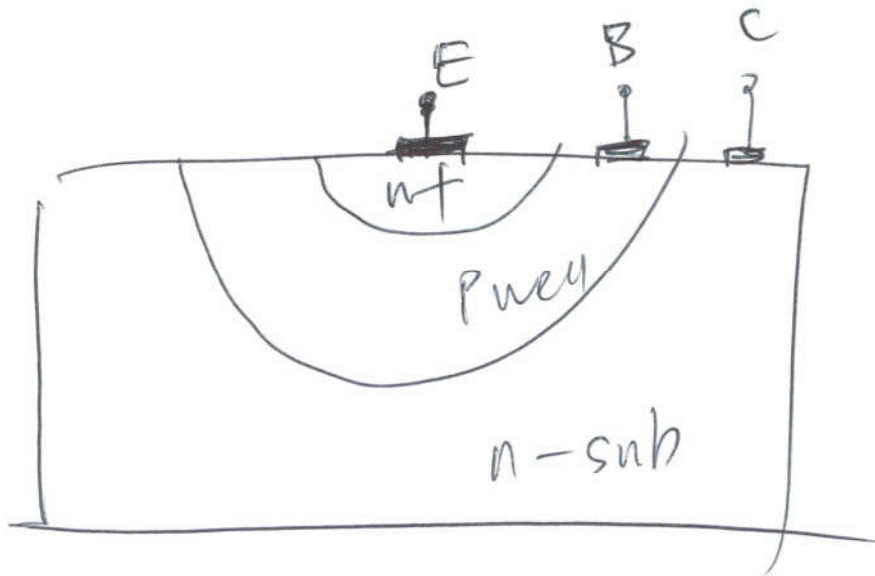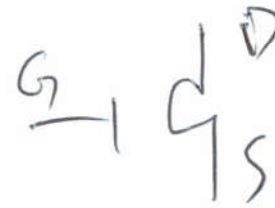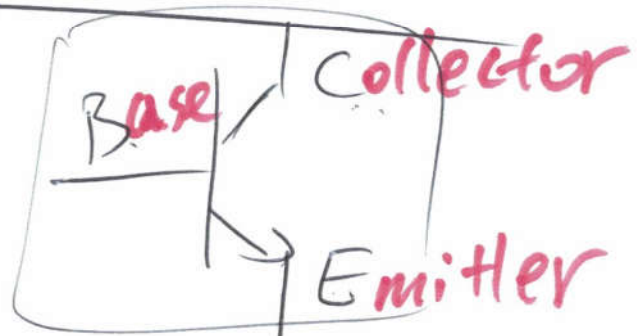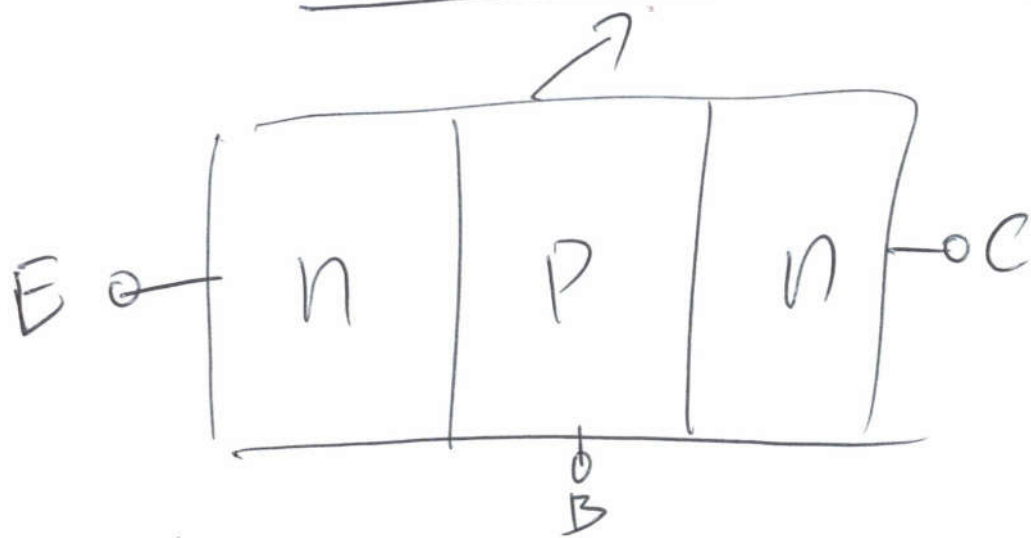


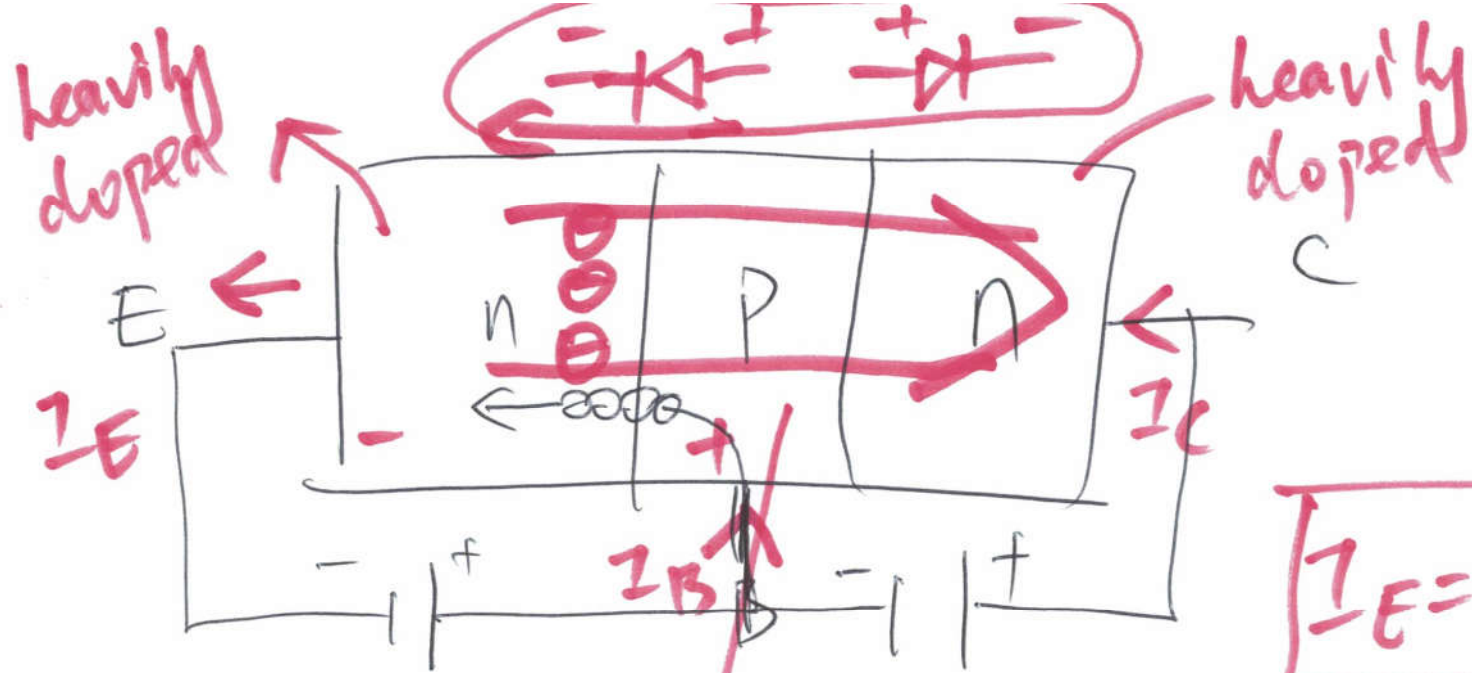



Forward Bias

Reverse Bias

very thin

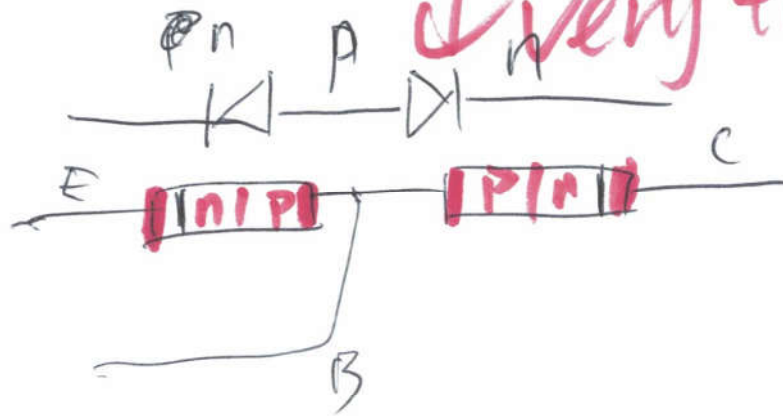

X won't work because of the metal plate.

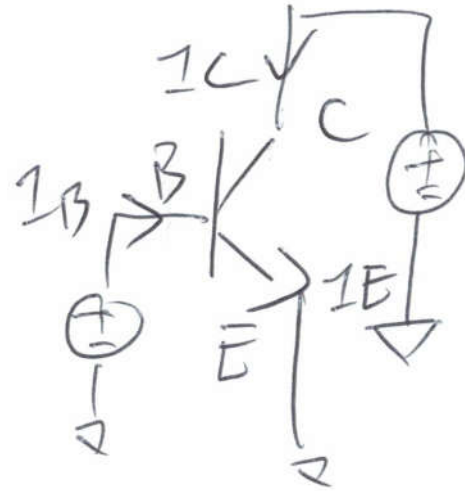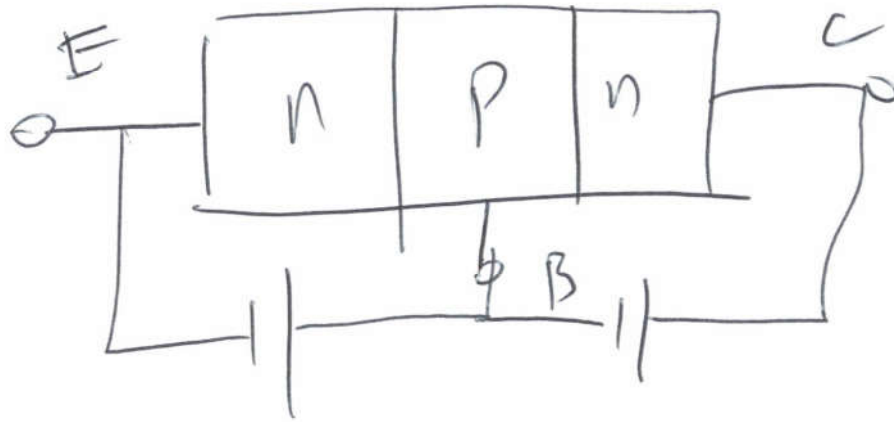

$$I_E = I_B + I_C$$

$$I_B = \frac{I_C}{\beta}$$

$$= \frac{I_E}{\beta + 1}$$

$$\beta = 100$$

$$I_C = \beta I_B$$

$$= \alpha I_E$$

$$\alpha = \frac{\beta}{\beta + 1}$$

$$I_E = \frac{I_C}{\alpha}$$

$$= (\beta + 1) I_B$$

①

$$I_C = I_S e^{V_{BE}/V_T}$$

$V_T = 0.25V$ in $25^\circ C$

$I_S = \text{Given}$

Depends on ~~Temp~~
Temperature

$$\left(1 + \frac{1}{n}\right)^n = e$$

↓

~~$$V_{BE} = V_T \ln \frac{I_C}{I_S}$$~~

$$\frac{d e^x}{dx} = e^x$$

$$V_{BE} = V_T \ln \frac{V_C}{I_S}$$