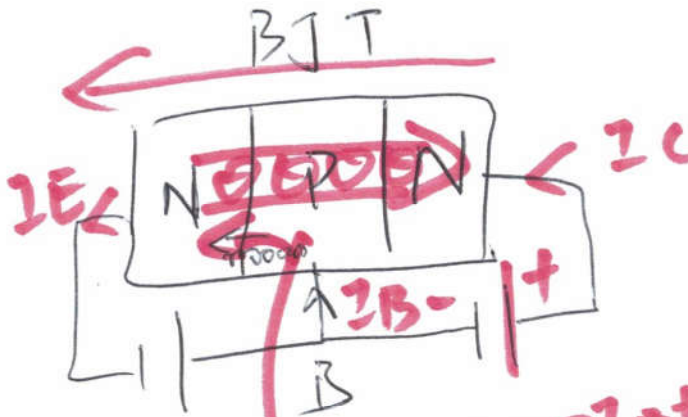


The DC Bias Point of BJT.



$$I_E = I_B + I_C$$


thin

$$\beta = 100$$

$$\begin{cases} I_B \cdot \beta = I_C \\ I_E = I_B + I_C \end{cases}$$

current controlled current source

CCCS

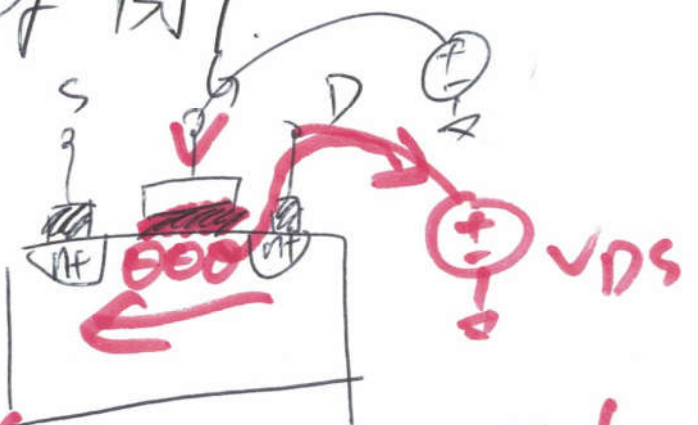

voltage controlled current source (VCCS)


$$I_{cm} = \beta (V_{GS} - V_{TH})$$

$$= \sqrt{2 I_D \beta}$$

$$I_D = \frac{\beta}{2} (V_{GS} - V_{TH})^2$$

BJT	CMOS
High power consumption	smaller.
Higher speed (RF)	

BJT DC operating point

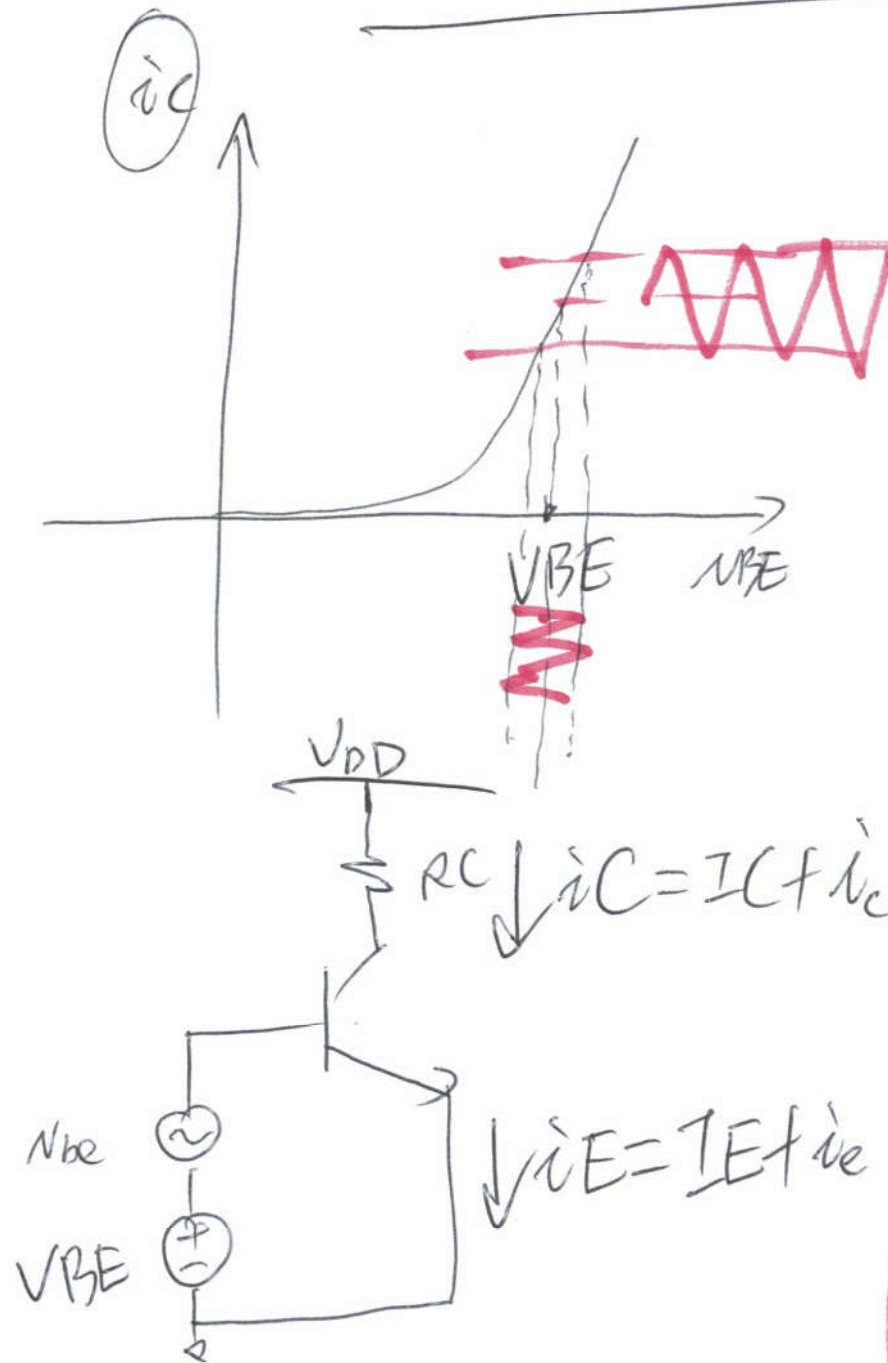

V_{BE} : DC Bias Voltage
 N_{be} : AC small signal
 $v_{BE} = V_{BE} + N_{be}$

$$v_{BE} = V_{BE} + N_{be}$$

$$i_c = I_S e^{v_{BE}/V_T}$$

$V_T = 25 \text{ mV}$
 (at room temp.)

$$\frac{\delta i_c}{\delta v_{BE}} = g_m$$

$$= \frac{\delta (I_S \cdot e^{v_{BE}/V_T})}{\delta v_{BE}}$$

$$= I_S \cdot e^{v_{BE}/V_T} \cdot \frac{1}{V_T} \approx \frac{I_C}{V_T}$$

$$i_c = g_m \cdot N_{be}$$

$$r_b = \frac{i_c}{\beta} = \frac{g_m v_{be}}{\beta} = \frac{I_C v_{be}}{V_T \beta} = \frac{I_B}{V_T} \cdot v_{be}$$

$$v_{be} = \frac{v_{be}}{i_b} = \frac{V_T}{\beta}$$

Example: $I_C = 0.5 \text{ mA}$, β changes from $50 \rightarrow 200$,
 what are the possible ranges of g_m , I_B , and v_{be} ?

$$g_m = \frac{I_C}{V_T} = \frac{0.5 \text{ mA}}{0.025 \text{ V}} = 20 \text{ mA/V}, \text{ doesn't change.}$$

$$I_B = \frac{I_C}{\beta} \quad I_{B1} = \frac{0.5 \text{ mA}}{50} \quad I_{B2} = \frac{0.5 \text{ mA}}{200}$$

$$I_B \sim (0.01 \text{ mA} - 0.0025 \text{ mA}) = (2.5 \mu\text{A} \rightarrow 10 \mu\text{A})$$

$$v_{be} \sim \left(\frac{0.025 \text{ V}}{20 \text{ mA}}, \frac{0.025 \text{ V}}{10 \mu\text{A}} \right) = (\text{~~10K~~ } 2.5 \text{ K}, 10 \text{ K})$$

$$I_C + I_B = I_E$$

$$I_C + \frac{I_C}{\beta} = I_E$$

$$\frac{\beta I_C + I_C}{\beta} = I_E$$


$$\frac{(\beta + 1) I_C}{\beta} = I_E$$

$$I_C = \frac{\beta}{\beta + 1} I_E$$


$$I_C = \alpha I_E$$

$$i_e = \frac{i_c}{\alpha} = \frac{g_m V_{be}}{\alpha} = \frac{I_C}{V_T} \cdot \frac{V_{be}}{\alpha} = \frac{I_E V_{be}}{V_T} \Rightarrow$$

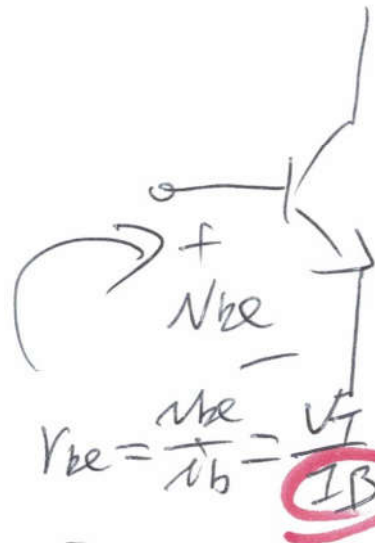
$$\Rightarrow \frac{V_{be}}{i_e} = \frac{V_T}{I_E} = r_e$$



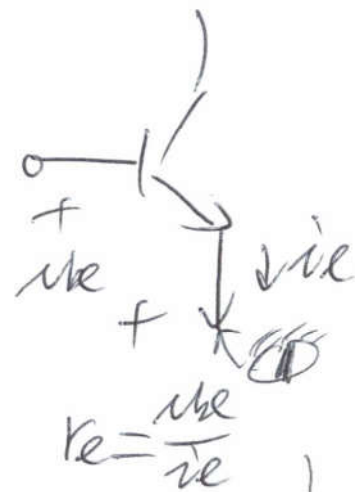
$$r_{be} = \frac{V_{be}}{i_b} = \frac{V_T}{I_B}$$



$$r_e = \frac{V_{be}}{i_e}$$

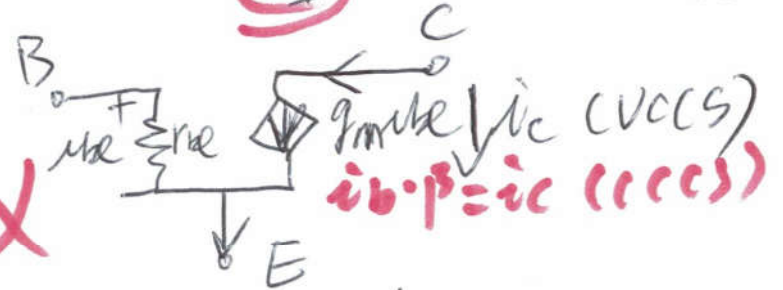
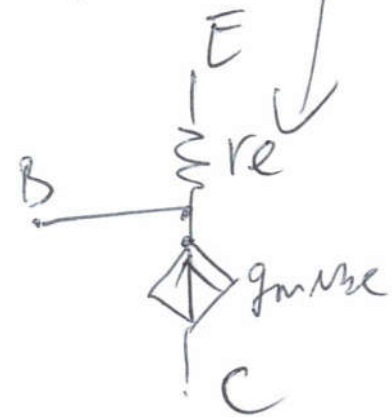
$$\beta = 100, \alpha = \frac{100}{1+100} \approx 1$$



The Voltage Gain


$$\text{Gain} = \frac{\text{Output}}{\text{Input}}$$

$$A_V = \frac{V_{ce}}{V_{be}} = \frac{-i_c \cdot R_C}{V_{be}}$$

$$= \frac{-g_m V_{be} \cdot R_C}{V_{be}}$$

$$= -g_m R_C$$

$$= -\frac{I_C}{V_T} R_C$$

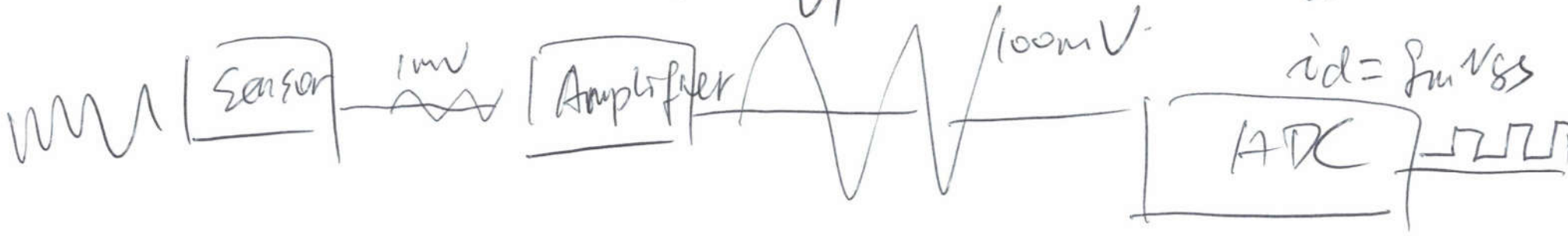

$$I_D = g_m V_{gs}$$


Example:

$I_C = 1 \text{ mA}$, $V_{CC} = 15 \text{ V}$ (power supply), $V_{BE} = 0.005 \sin \omega t$, $R_C = 10 \text{ k}\Omega$, $\beta = 100$, if find $v_C(t)$ and $i_B(t)$? V_{out}

$$\textcircled{1} A_V = -g_m R_C = -\frac{I_C}{V_T} \cdot R_C$$

$$= -\frac{1 \text{ mA}}{0.025} \cdot 10 \text{ k}\Omega$$
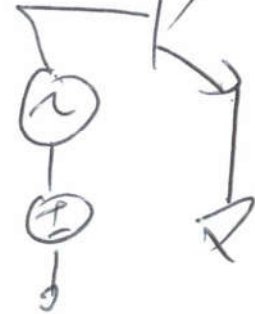
$$= -0.04 \cdot 10 \text{ k} = -0.4 \text{ k}$$



$$\textcircled{2} v_C(t) = V_C(t) + \underline{v_C(t)} = 5 \text{ V} + (-i_C \cdot R_C)$$

$$= 5 \text{ V} + (-g_m v_{BE}(t) \cdot R_C)$$

5V

$$= 5 \text{ V} - \left(\frac{I_C}{V_T} \cdot R_C \cdot 0.005 \sin \omega t \right)$$

$$= 5 \text{ V} - 0.4 \text{ k} \cdot 0.005 \sin \omega t$$

$$= 5 \text{ V} - 2 \cdot \sin \omega t$$

$$\textcircled{3} v_B(t) = \underline{V_B} + v_b(t) = \frac{I_C}{\beta} + \frac{v_{BE}(t)}{\beta} = \frac{I_C}{\beta} + \frac{v_{BE}(t)}{V_T / I_B} = \dots$$

⑥