


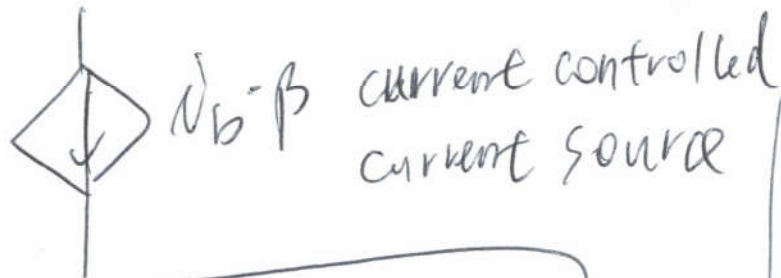
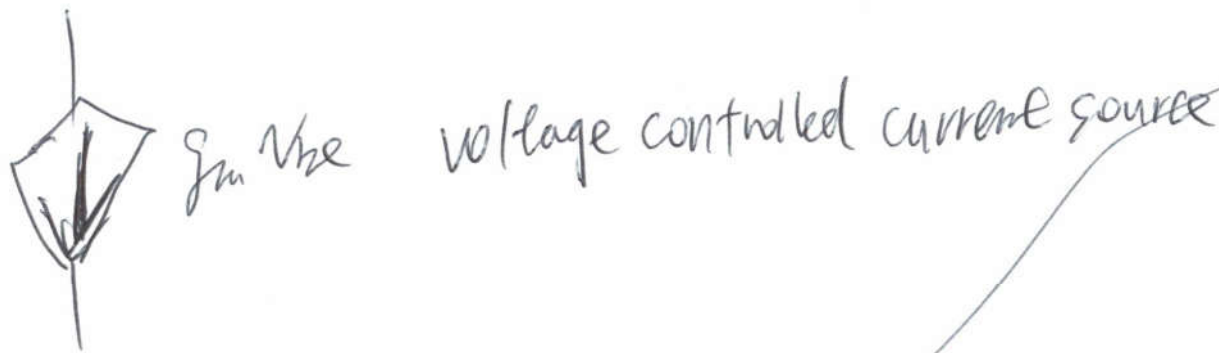


Small signal model

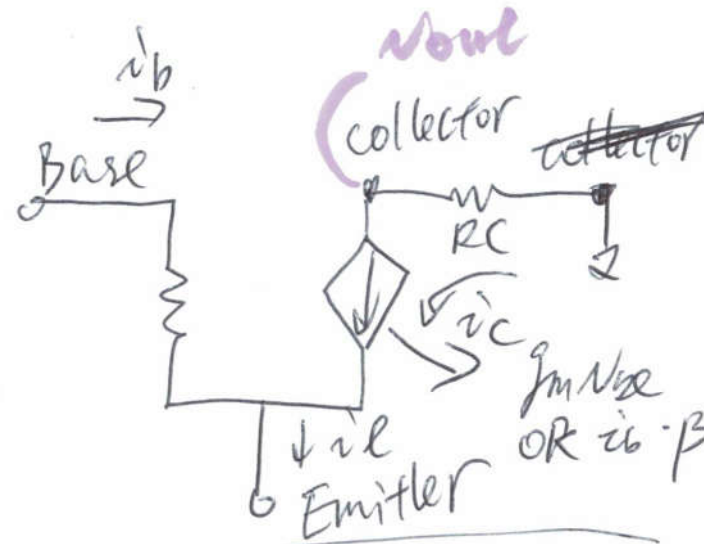


dependent source

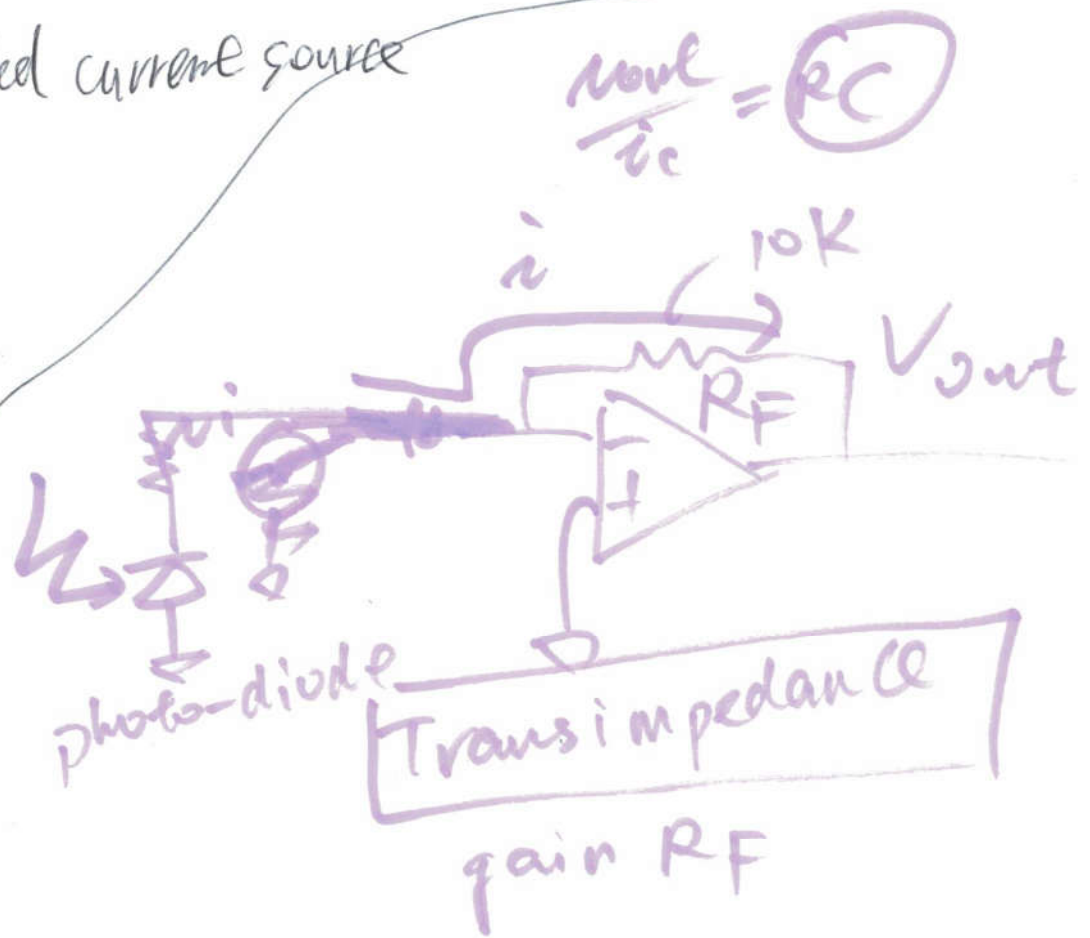

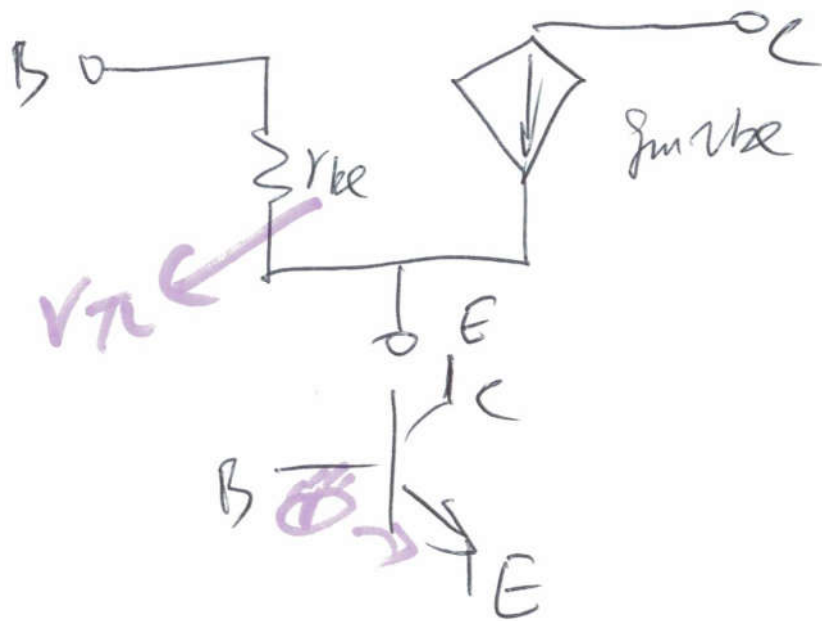



Hybrid- $\pi$  model

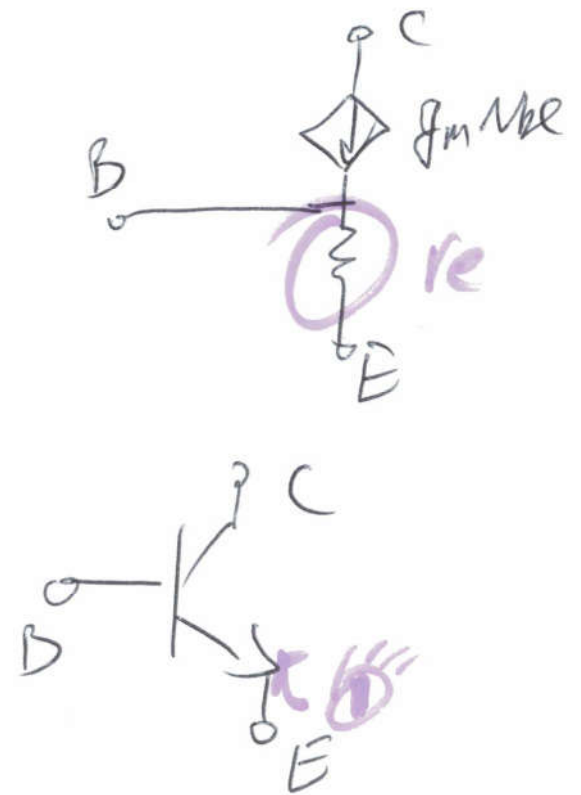

The T-model.

# P410 7.5. Examples.

DC operating points:

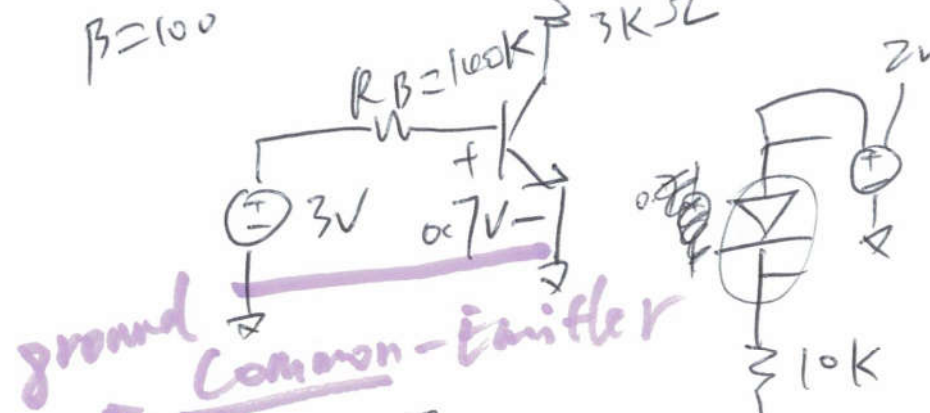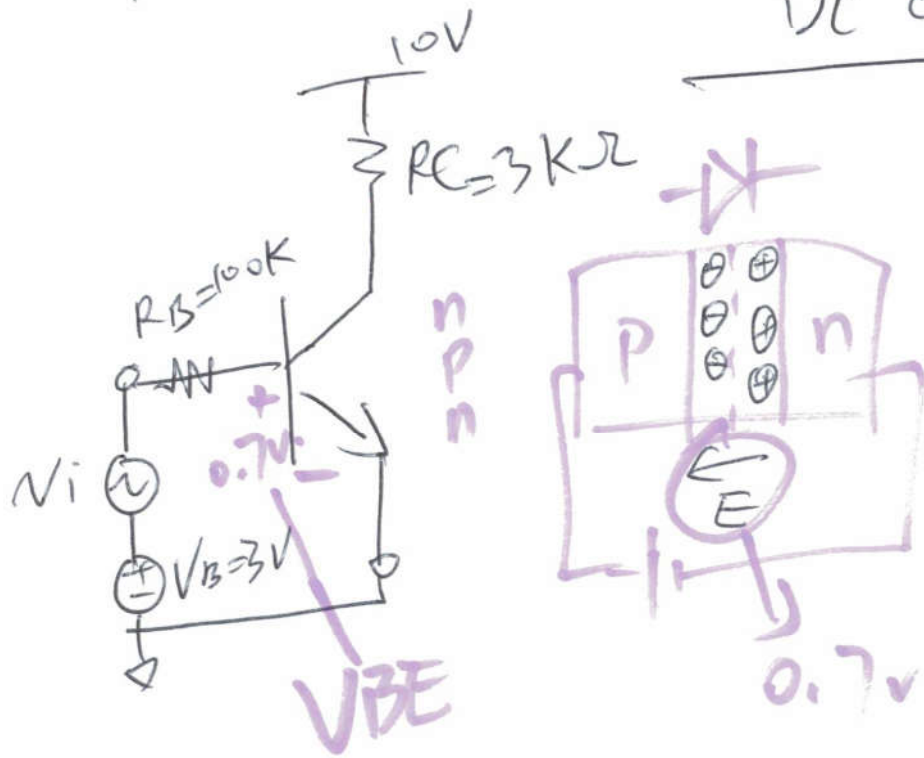

$$I_B = \frac{3 - 0.7}{100k} = 23 \mu A$$


$$I_C = I_B \cdot \beta = 2.3 \mu A$$

$$I_E = I_B + I_C$$

$$\alpha = \frac{\beta}{\beta + 1}$$

$$I_E = I_B + I_C = 23 \mu A + 2.3 \mu A = 25.3 \mu A$$
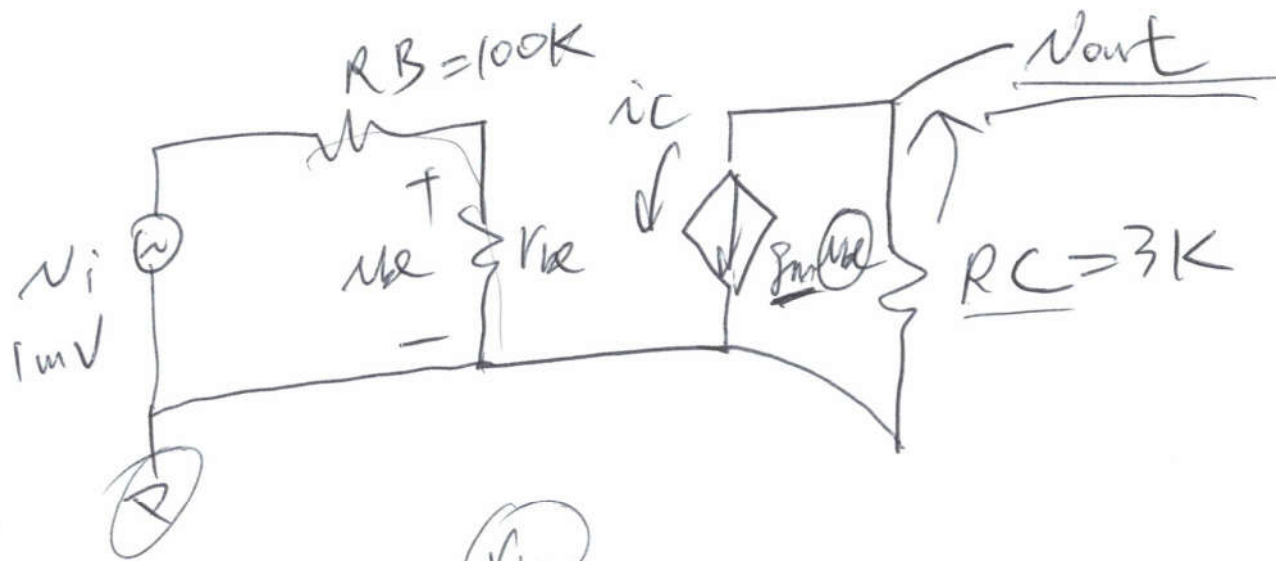
$$J_m = \frac{I_C}{V_T} = \frac{2.3 \mu A}{25 mV} = 0.09 A/V$$



$$v_{be} = v_i \cdot \frac{r_{be}}{r_{be} + R_B}$$

$$r_{be} = \frac{V_T}{I_B} = \frac{25\text{mV}}{23\mu\text{A}} = 1.1\text{K}\Omega$$



$$v_{be} = v_i \cdot \frac{1.1\text{K}}{101.1\text{K}} \approx 0.01 \cdot v_i = \cancel{0.01\text{mV}}$$

$$i_c = \beta_m v_{be} = 0.09\text{mA} \cdot \cancel{0.01\text{mV}} = 0.01 v_i$$

$$v_{out} = -i_c \cdot R_C = -0.09 \times 0.01 v_i \cdot R_C, \quad R_C = 3\text{K}\Omega$$

$$\frac{v_{out}}{v_i} = -2.7\text{V/V}$$

# Example 7.7 P415

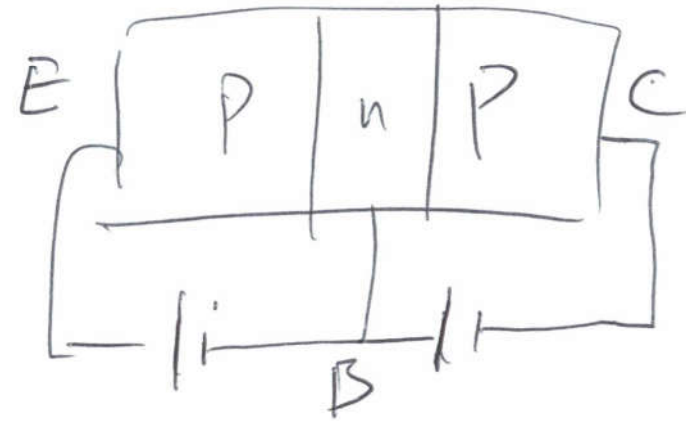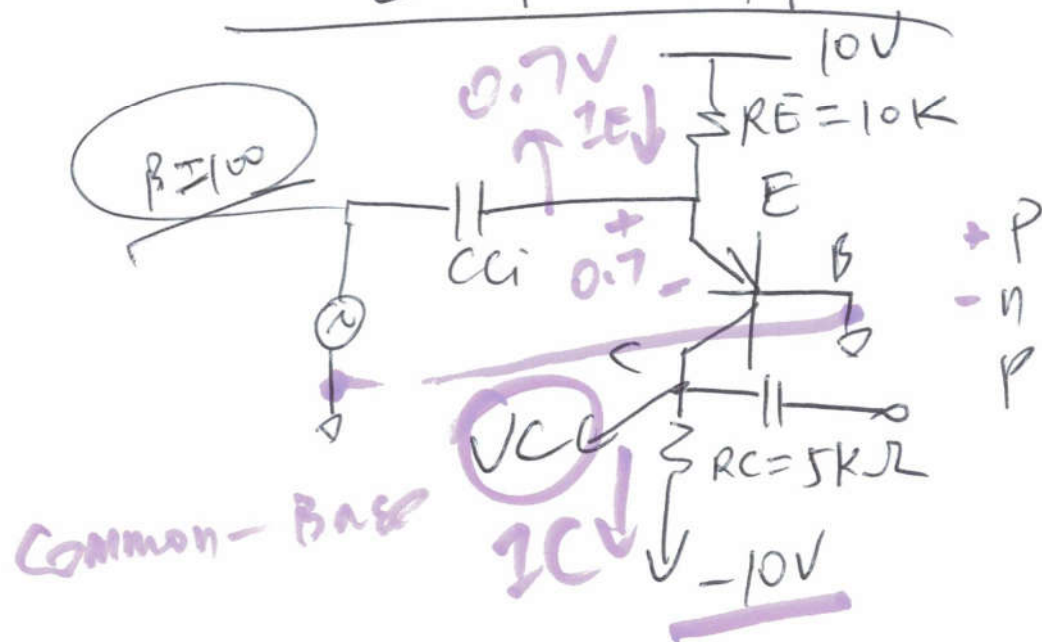

DC operating point:

$$I_E = \frac{10 - 0.7}{10K} = \frac{9.3}{10K} = 0.93 \text{ mA}$$



$$I_C = \alpha I_E = \frac{\beta}{\beta + 1} \cdot I_E = \frac{100}{101} \cdot 0.93 \text{ mA}$$

$$I_B = \frac{I_C}{100} = \frac{0.92 \text{ mA}}{100} = 9.2 \mu\text{A}$$

$$V_C = -10 + I_C \cdot R_C = -10 + 0.92 \text{ mA} \cdot 5K = -5.4 \text{ V}$$

$$g_m = \frac{I_C}{V_T} = \frac{0.92 \text{ mA}}{25 \text{ mV}} = 36.8 \text{ mA/V}$$

# AC analysis

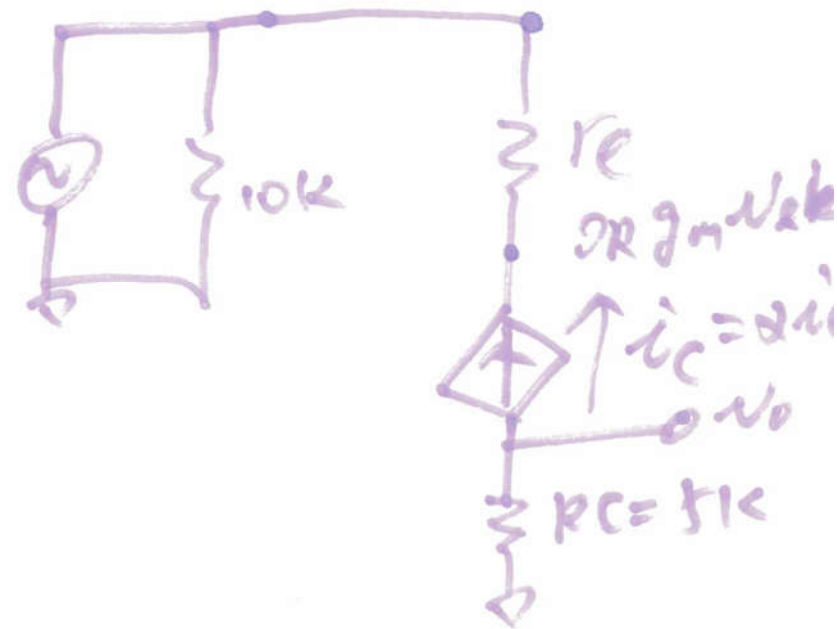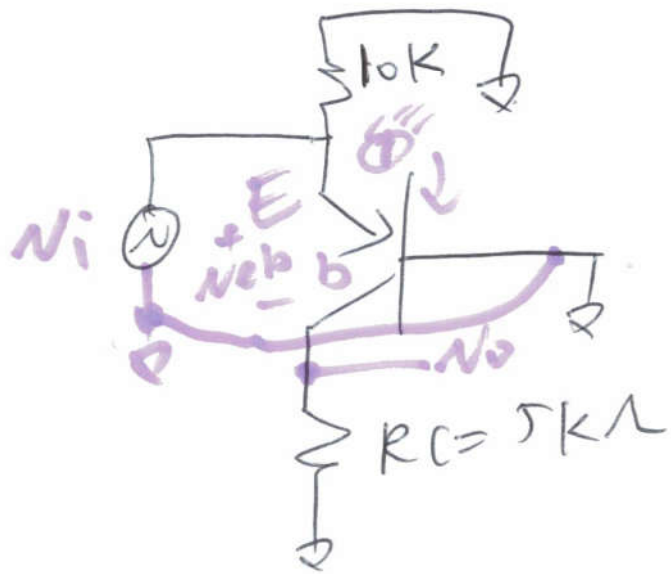


$$v_i = v_{be}$$

$$i_c = g_m \cdot v_{be} = g_m \cdot v_i$$

$$v_o = -i_c \cdot R_C = -g_m v_i \cdot R_C$$

$$\frac{v_o}{v_i} = -g_m R_C.$$


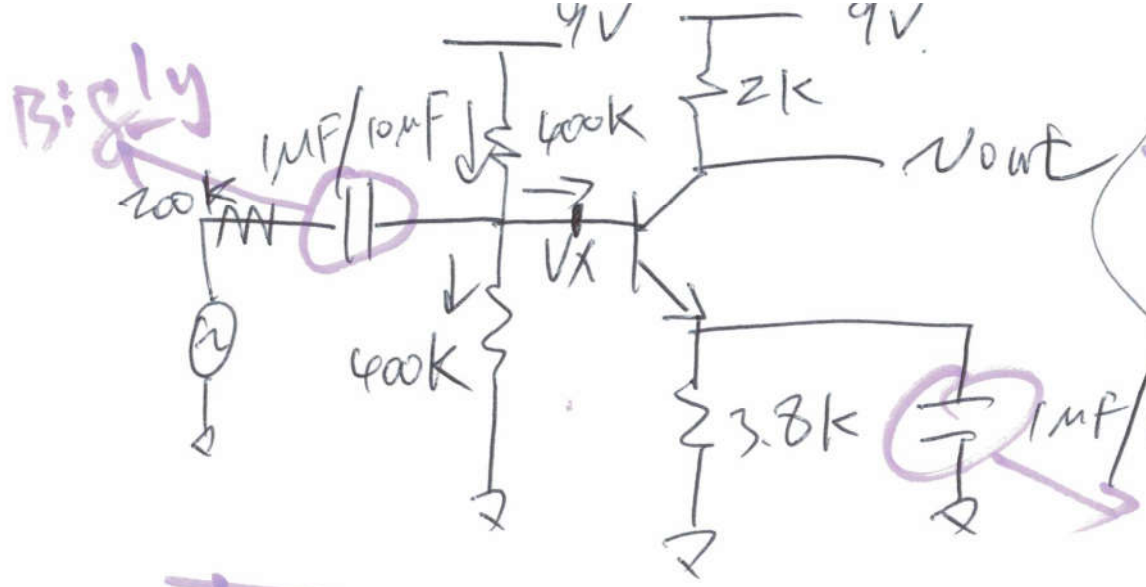


$$\frac{9 - V_X}{400k} = \frac{V_X}{400k}$$

$$= \frac{1E \cdot \beta}{\beta} = 1E$$

$$= \frac{1E}{1 + \beta}$$

$$1E = \frac{V_X - 0.7}{3.8k}$$

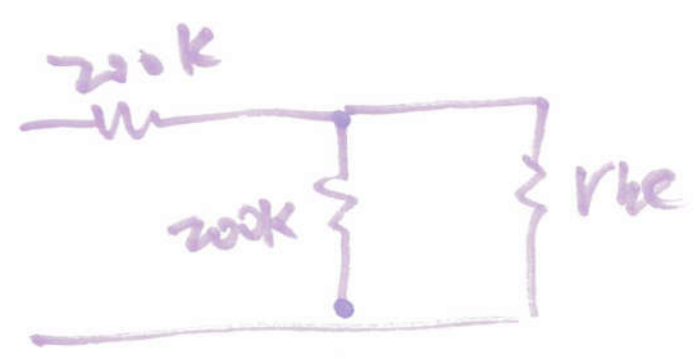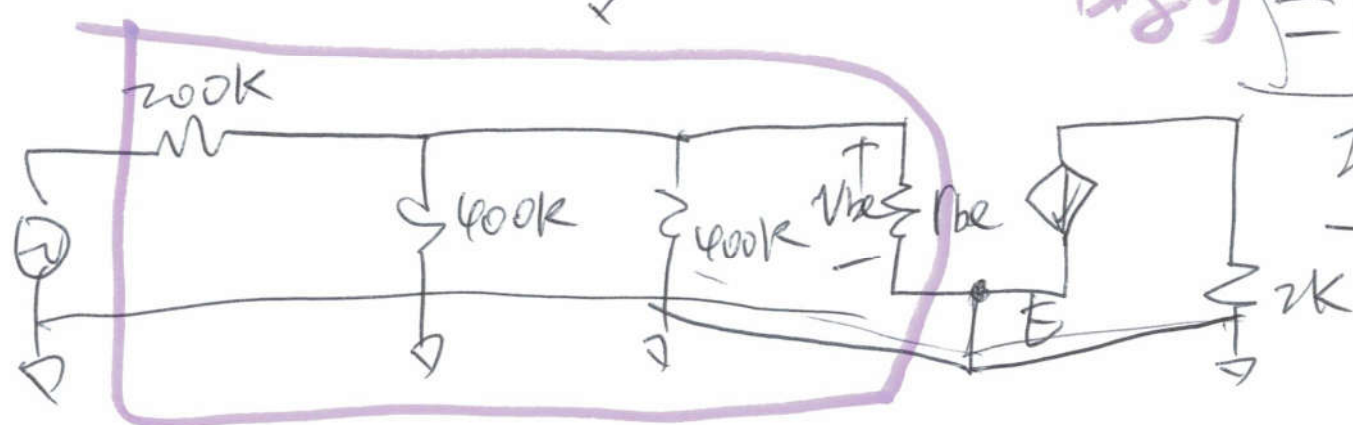

①