

$$\begin{aligned}
 v_{out} &= -i_c R_C \\
 &= -g_m v_{be} R_C \\
 \frac{v_{out}}{v_{be}} &= -g_m R_C
 \end{aligned}$$

(2)



$$\frac{I_C}{I_E} = \alpha = \frac{I_C}{I_C + I_B} = \frac{\beta I_B}{\beta I_B + I_B} = \frac{\beta I_B}{(\beta + 1) I_B}$$


$$\alpha = \frac{\beta}{1 + \beta}$$


$$I_B \cdot \beta = I_C$$

$$\alpha + \alpha \beta = \beta$$

$$\alpha = (1 - \alpha) \beta$$

$$\beta = \frac{\alpha}{1 - \alpha}$$

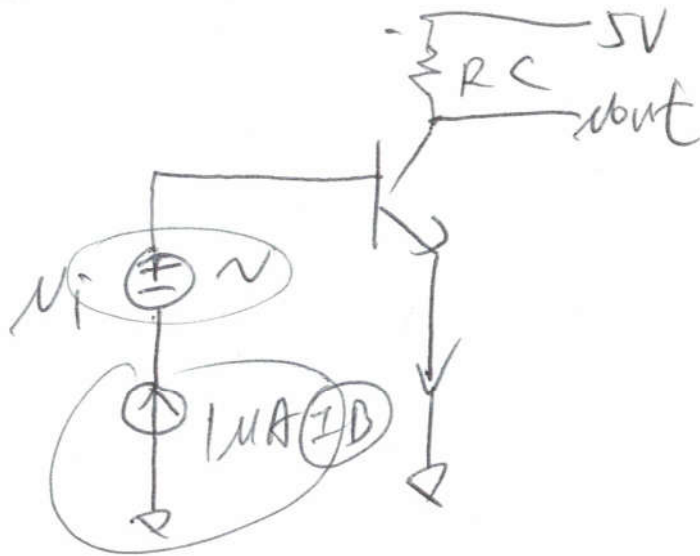

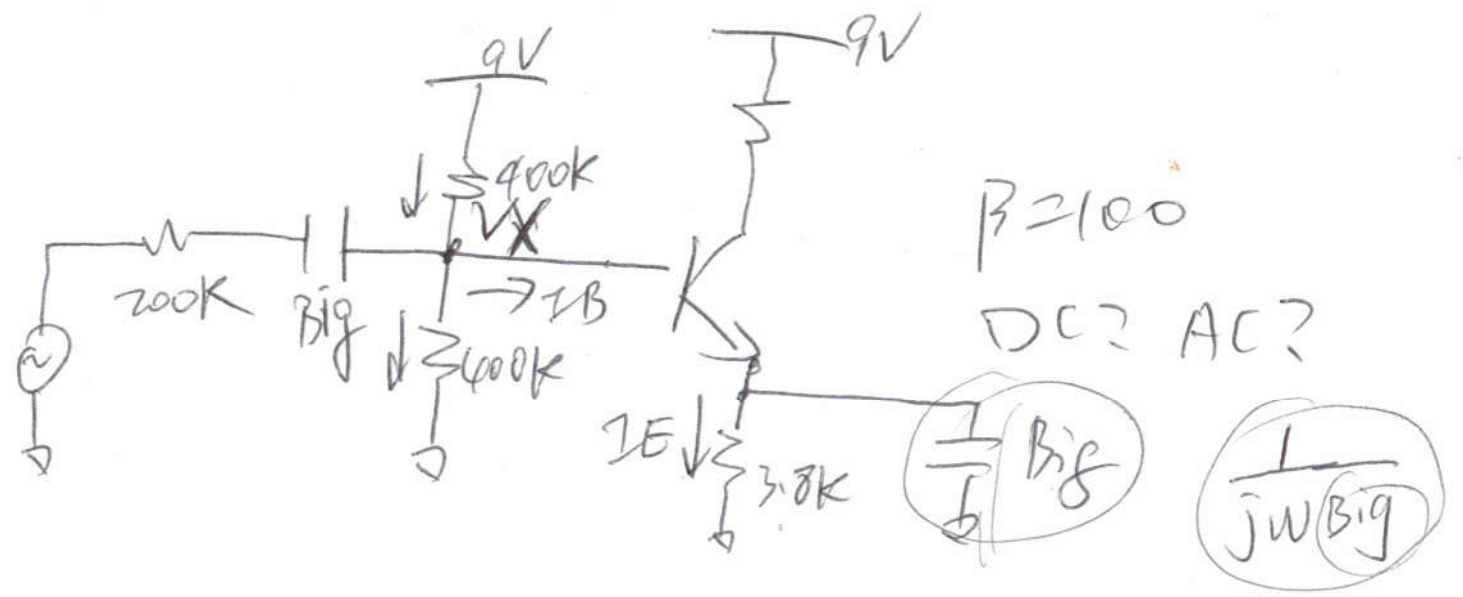

$$\left\{ \frac{9 - V_X}{400k} - \frac{V_X}{400k} = I_B \right.$$

$$I_B = \left(\frac{V_X - 0.7}{3.8k} \right) / (\beta + 1)$$

$$\frac{9 - V_X}{400k} - \frac{V_X}{400k} = \frac{V_X - 0.7}{(3.8k) \cdot 101}$$

$$9 - V_X - V_X = V_X - 0.7$$

$$9.7 = 3V_X$$

$$V_X = 3.23V$$


$$I_B = \frac{V_X - 0.7}{3.8k \cdot 101} = 6.5 \mu A$$

(4)

$$I_E = (\beta + 1) \cdot I_B = 657 \mu A$$

$$I_C = \beta \cdot I_B = 650 \mu A$$

AC:

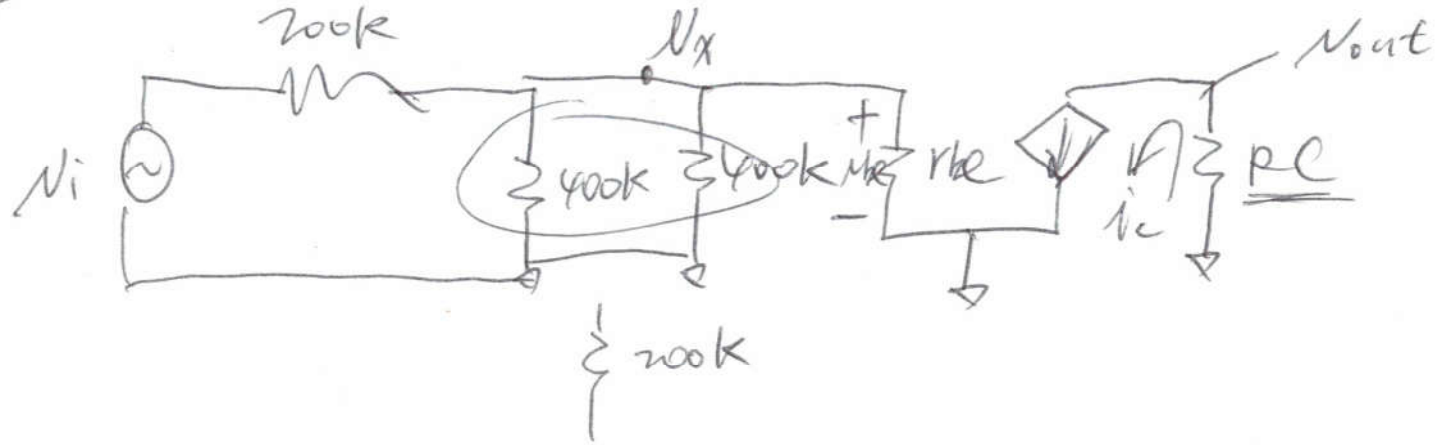


$$i_c = g_m v_{be} = \frac{I_C}{V_T} \cdot v_x$$

$$v_x = \frac{r_{be} \parallel 200k}{(r_{be} \parallel 200k) + 200k} \cdot \underline{v_i}$$

$$r_{be} = \frac{V_T}{I_B}$$

$$v_{out} = -i_c \cdot R_C$$

Ps04 7.137



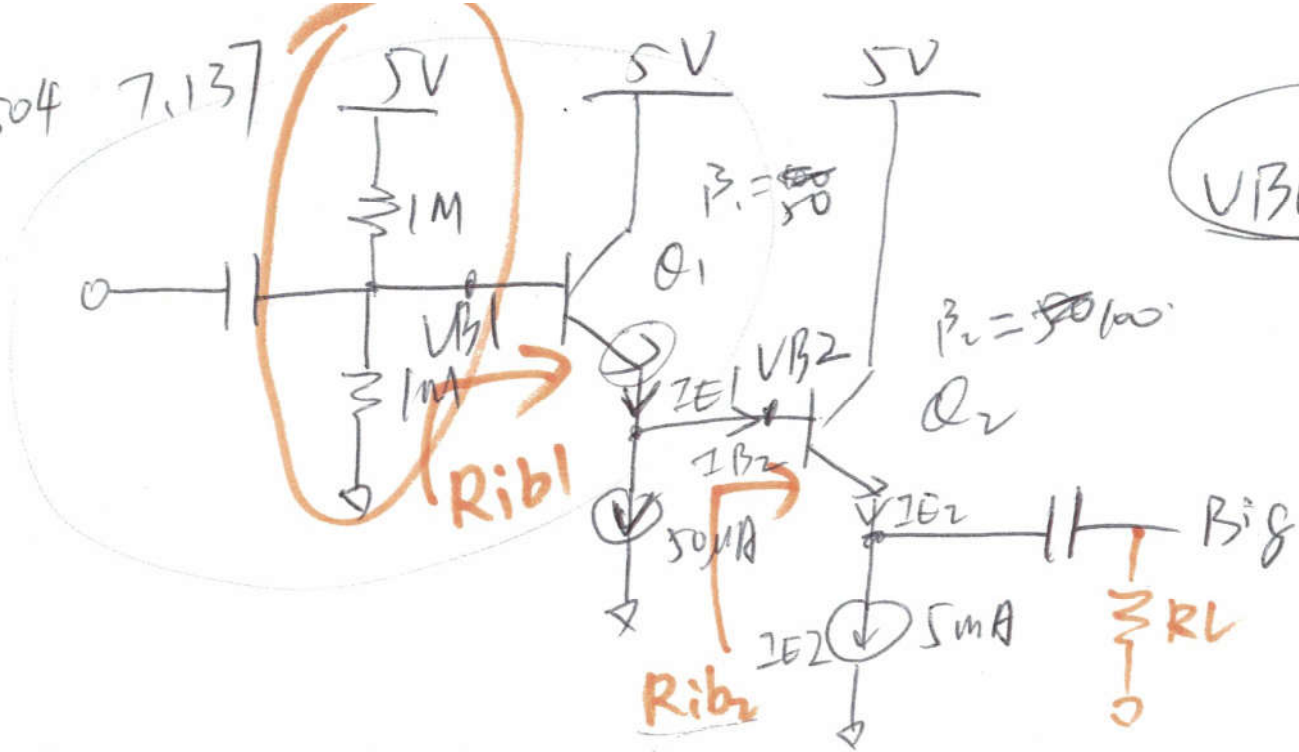


$V_{BE} = 0.7V$

① Find I_{E1} , I_{E2} , V_{B1} , V_{B2}

$$I_{E2} = 5mA, I_{B2} = \frac{I_{E2}}{\beta_2} = \frac{5mA}{101} = 50\mu A$$

$$I_{E1} = 50\mu A + 50\mu A = 0.1mA$$

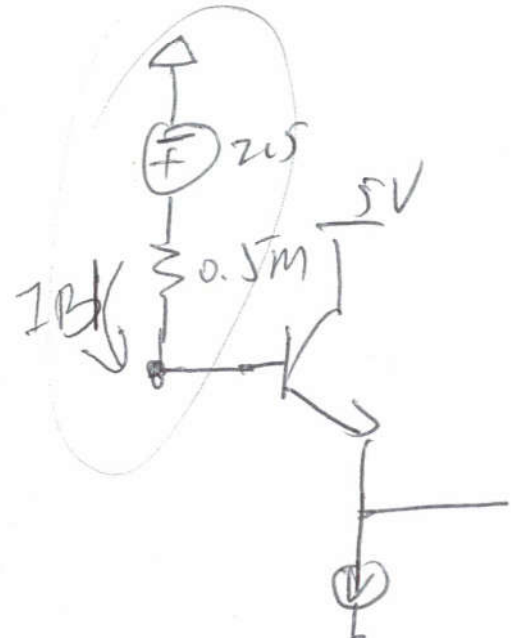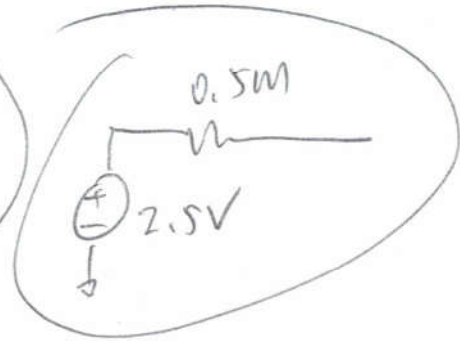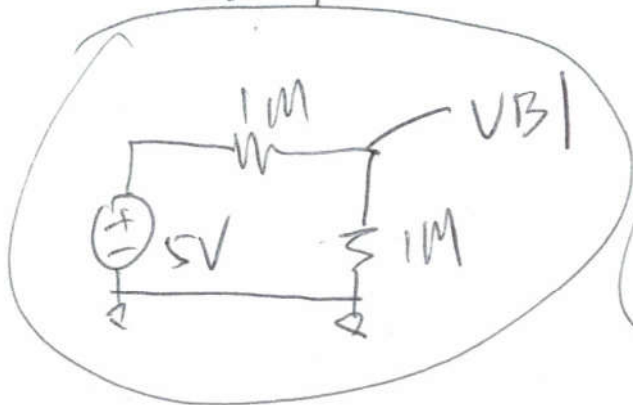


$$V_{B1} = 2.5 - 0.5M \cdot I_{B1} =$$

$$I_{B1} = \frac{2.5}{R_{T1}} =$$



$$V_{B2} = V_{B1} - 0.7V = -$$

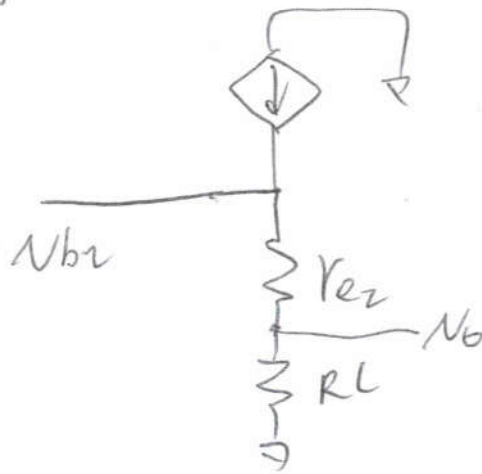
(2) if we have a R_L , ~~the~~ $\frac{V_{B2}}{V_{B1}}$? R_{ib2} ?


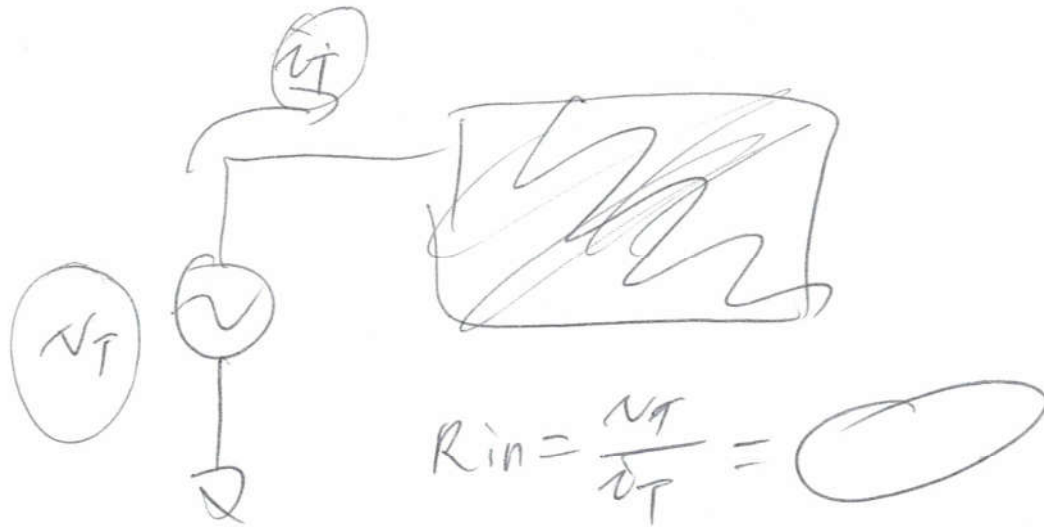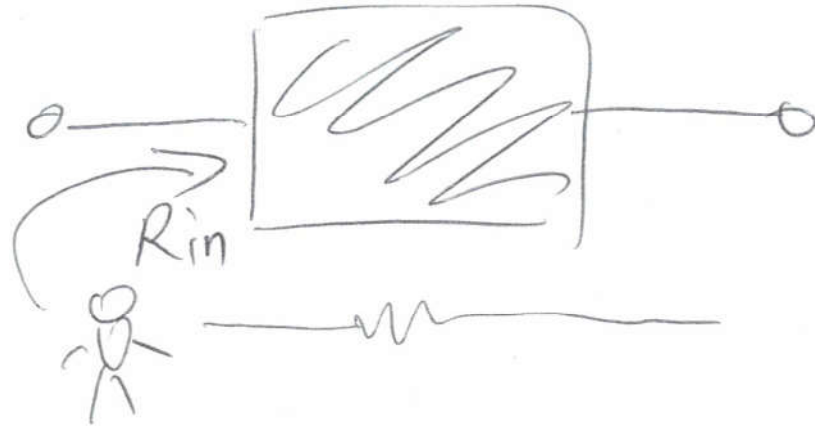
$$\left. \begin{aligned} \frac{V_{B2}}{V_{B1}} &= \frac{R_L}{R_{B2} + R_L} \\ \text{① } V_{B2} &= \frac{V_T}{I_{B2}} \end{aligned} \right\}$$





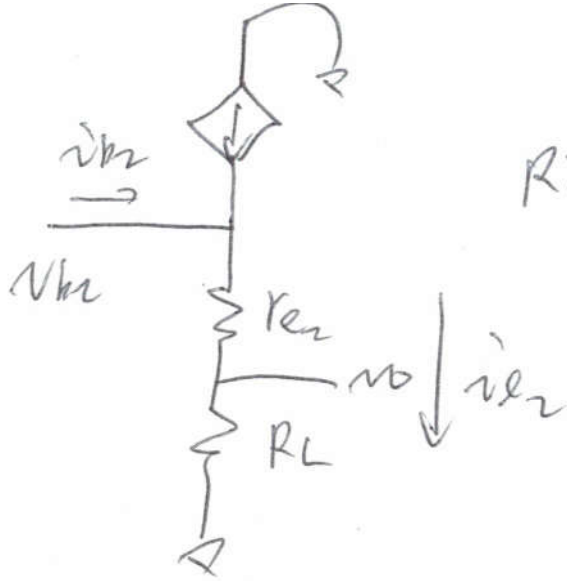


$$R_{ib2} = \frac{v_{b2}}{i_{b2}} = \frac{v_{b2}}{\frac{v_{b2}}{1+\beta_2}} = \frac{v_{b2}}{v_{e2}} (1+\beta_2)$$


$$v_{e2} + R_L$$

$$v_{e2} = \frac{v_{b2}}{2\beta_2}$$

3

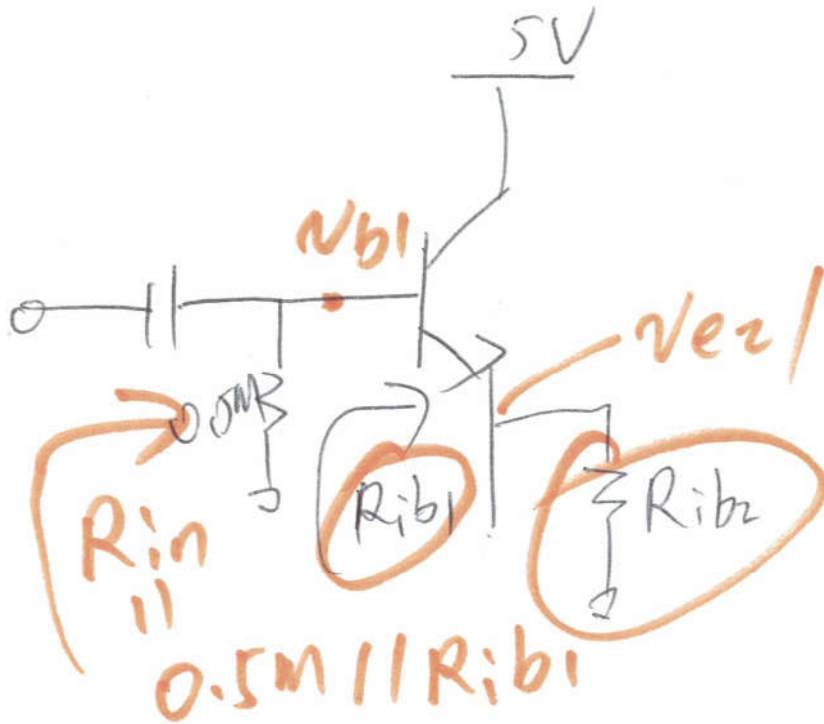

$$v_{e2} / N_{b1} =$$

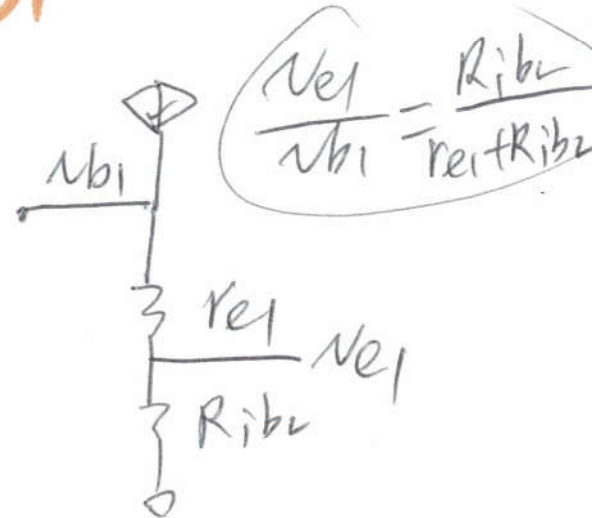

$$\frac{N_{e1}}{N_{b1}} = \frac{R_{ib2}}{r_{e1} + R_{ib2}}$$

④ The overall gain

$$\frac{v_o}{v_i} = \frac{N_{e2}}{\cancel{v_o}} \cdot \frac{\cancel{v_o}}{v_i} = \frac{v_{e2}}{v_i} = \frac{v_o}{v_i}$$