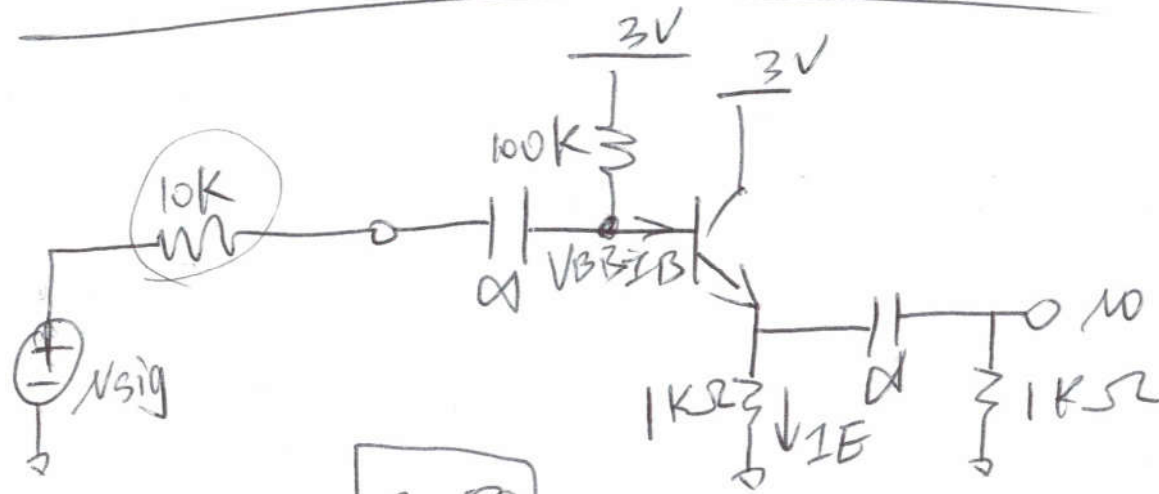


More BJT Examples



DC? AC?

$$\beta = 50$$

$$\left\{ \begin{aligned} \frac{3 - V_{BE}}{100k} &= I_B \\ \frac{V_{BE} - 0.7}{1k} &= (\beta + 1) I_B = 51 \cdot I_B \end{aligned} \right.$$

$$\frac{V_{BE} - 0.7}{1k \cdot 51} = \frac{3 - V_{BE}}{100k}$$

$$2V_{BE} - 1.4 = 3 - V_{BE}$$

$$3V_{BE} = 4.4$$

$$\underline{V_{BE} = 1.47V}$$


$$I_B = \frac{3 - 1.47}{100k} = 15.3 \mu A$$

$$I_E = (\beta + 1) \cdot I_B = 51 \cdot 15.3 \mu A = 780.3 \mu A$$

$$I_C = \alpha \cdot I_E = \frac{\beta}{\beta + 1} \cdot I_E \approx 780.3 \mu A$$

$$V_E = V_{BE} - 0.7 = 1.47 - 0.7 = 0.77V$$

T-mode

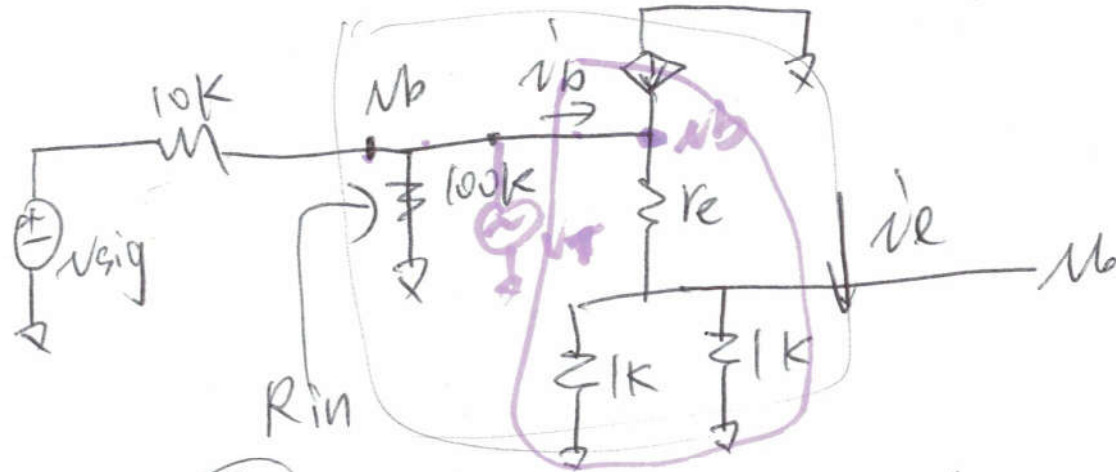

$$g_m = \frac{I_C}{V_T} = \frac{100.3 \mu A}{25 mV} = 3.2 \text{ mA/V}$$

$$\frac{v_b}{v_{sig}} = \frac{R_{in}}{10k + R_{in}}$$

$$R_{in} = 100k \parallel (r_e \parallel (1k \parallel 1k))$$

$$R_{in} = 100k \parallel \frac{v_b}{v_b}$$

$$\frac{v_b}{v_b} = \frac{v_b}{\left(\frac{r_e}{\beta}\right)} = \frac{v_b}{r_e} (\beta) = (r_e \parallel (1k \parallel 1k)) (\beta)$$


$$R_{in} = 100k \parallel (r_e \parallel (1k \parallel 1k)) (\beta)$$

$$\frac{v_b}{v_{sig}} = \frac{R_{in}}{10k + R_{in}}$$

$$\frac{v_o}{v_b} = \frac{1k \parallel 1k}{r_e \parallel (1k \parallel 1k)}$$

$$\frac{v_o}{v_{sig}} \cdot \frac{v_o}{v_o} = \frac{v_o}{v_{sig}} = \frac{R_{in}}{10k + R_{in}} \cdot \frac{1k \parallel 1k}{r_e + (1k \parallel 1k)}$$

$$r_e = \frac{V_T}{I_E}$$

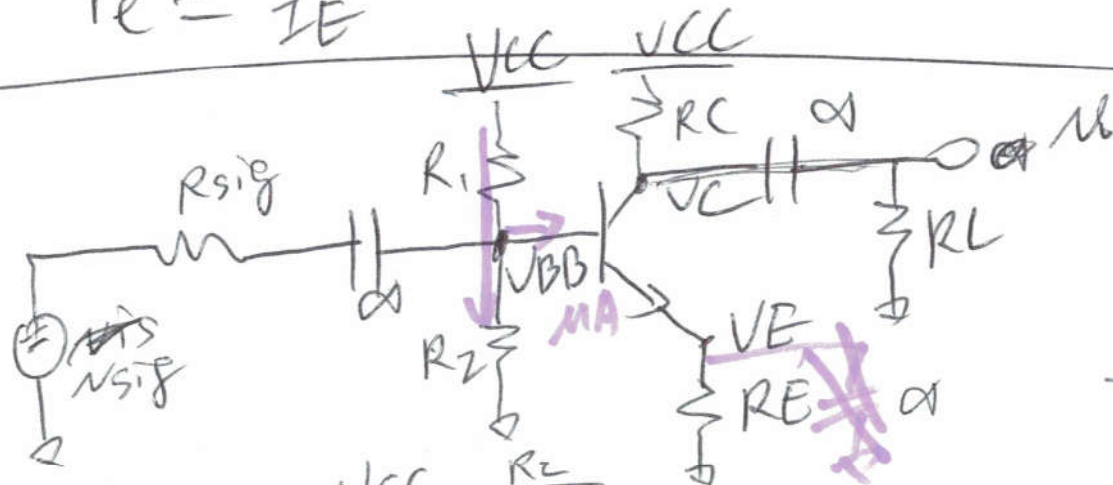

$$\beta = 100$$

$$V_{BB} = V_{CC} \cdot \frac{R_2}{R_1 + R_2}$$

$$V_E = V_{BB} - 0.7 = \frac{V_{CC} \cdot R_2}{R_1 + R_2} - 0.7$$


$$I_E = \frac{V_E}{R_E} = \frac{V_{CC} \cdot R_2}{R_1 + R_2} - 0.7$$

$$I_C = \alpha \cdot I_E = \frac{\beta}{1 + \beta} \cdot \frac{V_{CC} \cdot R_2}{R_1 + R_2} - 0.7$$

$$V_C = V_{CC} - R_C \cdot I_C$$

$$g_m = \frac{I_C}{V_T} = \frac{I_C}{V_T}$$

Hybrid- π model

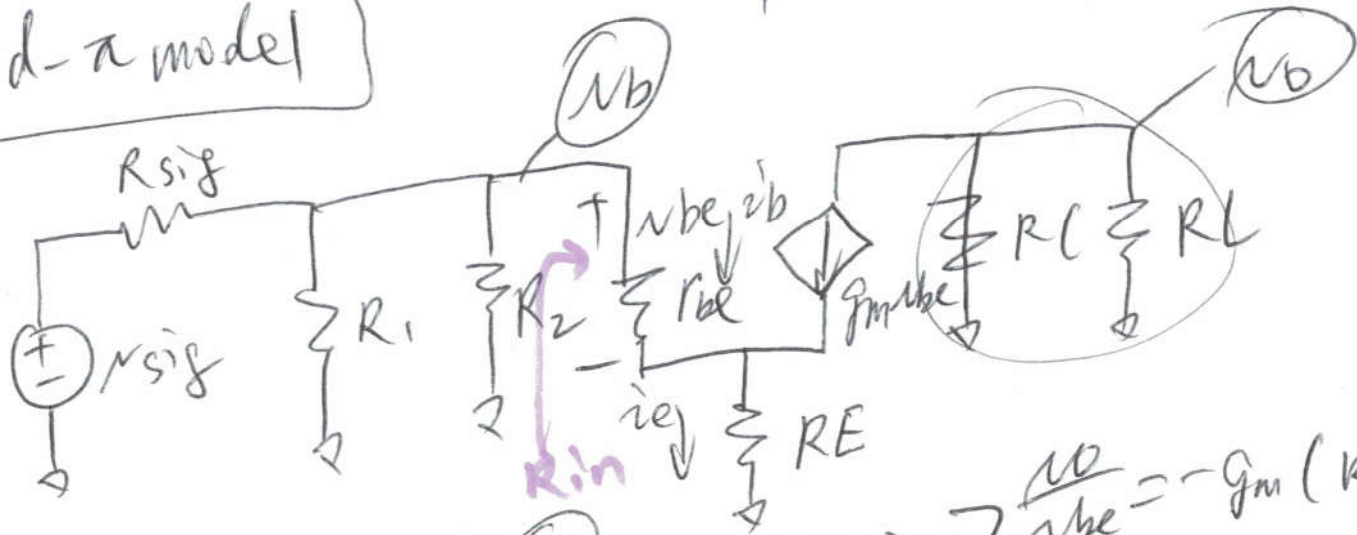

$$v_o = -g_m v_{be} \cdot (R_C \parallel R_L) \Rightarrow \frac{v_o}{v_{be}} = -g_m (R_C \parallel R_L)$$

$$v_b = v_{be} \cdot i_b + R_E \cdot i_e = v_{be} \cdot i_b + R_E \cdot (H_B) i_b$$

$$\frac{v_b}{i_b} = v_{be} + R_E (H_B) = R_{in}$$

$$\frac{v_b}{v_{sig}} = \frac{R_1 \parallel R_2 \parallel R_{in}}{R_{sig} + R_1 \parallel R_2 \parallel R_{in}}$$

$$\frac{v_{be}}{v_b} = \frac{v_b \cdot v_{be}}{v_b + (H_B) i_b \cdot R_E} = \frac{v_{be}}{v_{be} + (H_B) R_E}$$

$$\frac{16}{\cancel{16}} \cdot \frac{\cancel{16}}{\sqrt{576}} \cdot \frac{\cancel{16}}{\cancel{16}} = \frac{16}{\sqrt{576}} = \text{---}$$

(5)