

$$4.6 \text{ (1)} \quad 10\mu = \frac{120\mu \cdot 50}{2} (V_{GS} - V_{THN})^2 = \frac{\beta_n}{2} (V_{GS} - V_{THN})^2$$


$$V_{GS} = \sqrt{\frac{2I_D}{\beta_n}} + V_{THN}$$

$$= \sqrt{\frac{2 \cdot 10\mu}{3000\mu}} + 0.8$$

$$= \sqrt{\frac{20\mu}{3000\mu}} + 0.8$$

$$= \cancel{0.8} + 0.08 + 0.8$$

$$= \cancel{0.8} + 0.88V$$

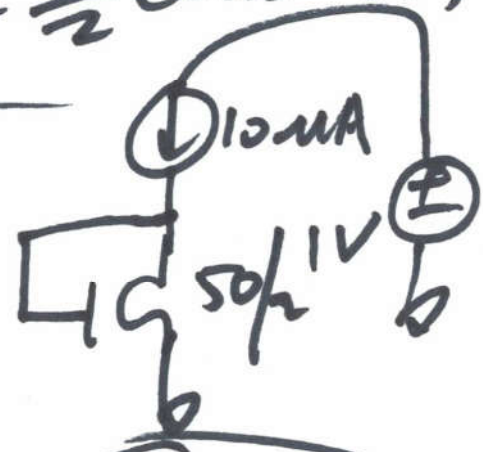

$$\beta_n = \frac{K'_N \cdot W}{L}$$

①

$$V_{TH} = 0.9$$

$$V_S = 1$$


$$V_G = 0.025V$$

$$V_{SG} = V_S - V_G = 1 - 0.025 = 0.975V$$


$$V_{SG} = \sqrt{\frac{2 \cdot I_{DQ}}{\beta_P}} + V_{THP}$$

$$\beta_P = \frac{K_{PP} \cdot \frac{100}{2}}{2} = 40M \cdot 50 = 2000 \mu$$
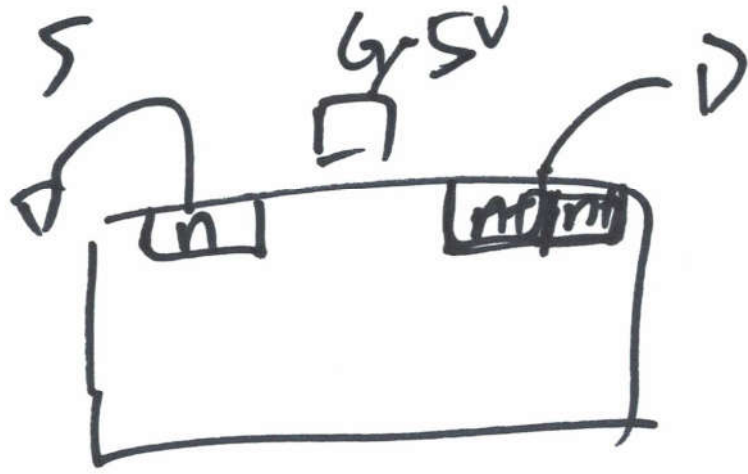
$$V_{SG} = \sqrt{\frac{20 \mu}{2000 \mu}} + V_{THP} = 0.1 + 0.9 = 1V$$



$$C_S = \underline{\underline{20V}}$$

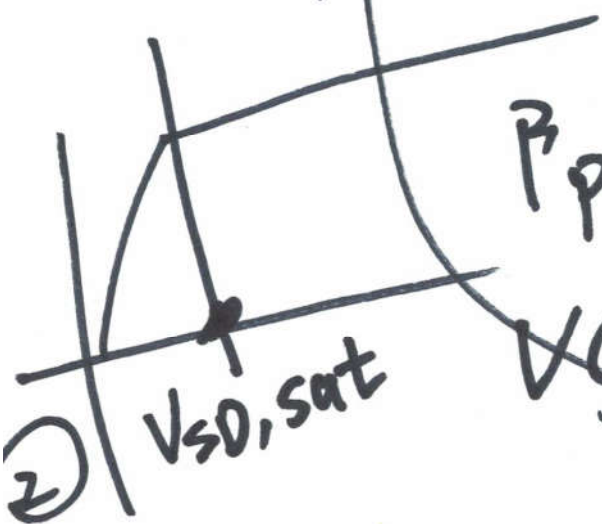

2)