
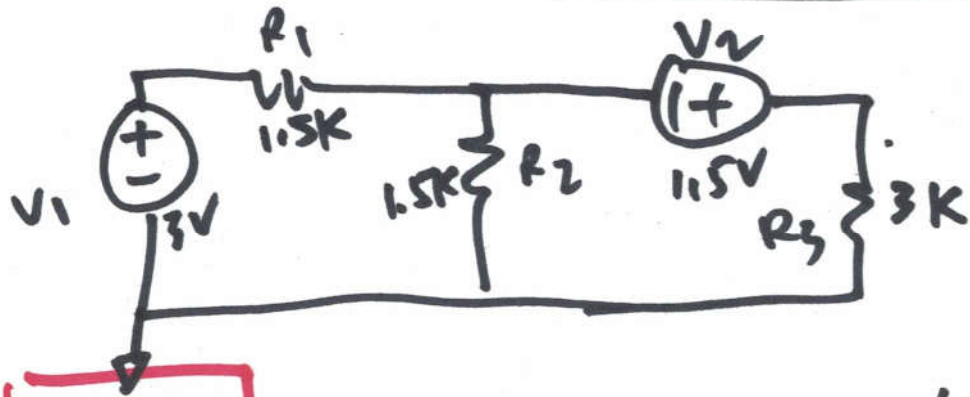



Monday, 10 PM

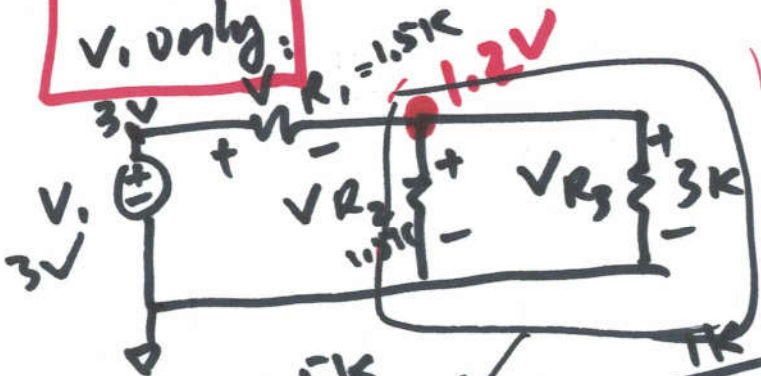


V₁ only:



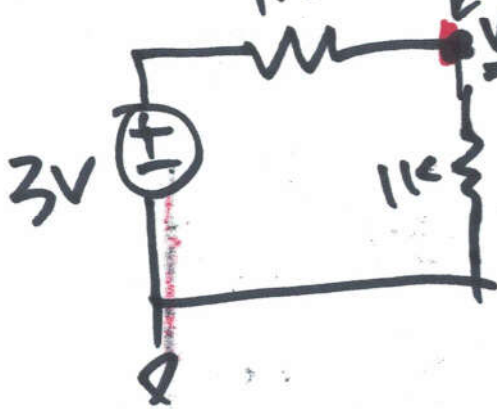$V_0 = 3V \cdot \frac{1K}{1.5K + 1K} = 1.2V$



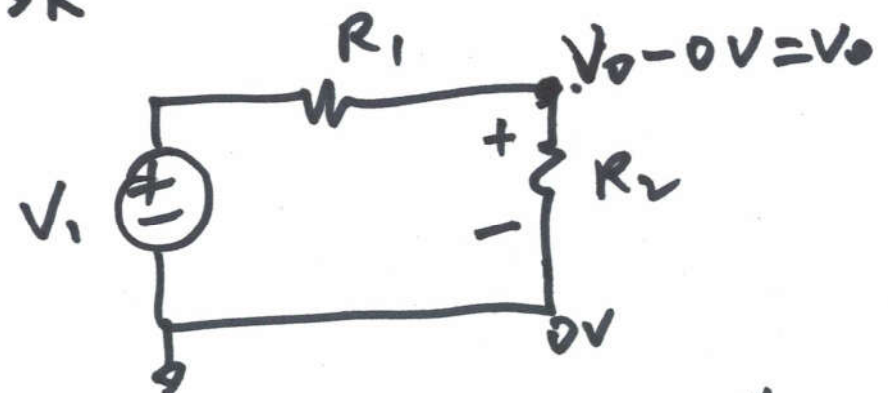$\frac{1}{\frac{1}{R_2} + \frac{1}{R_3}} = \frac{R_2 \cdot R_3}{R_2 + R_3} = \frac{4.5K^2}{4.5K} = 1K$



~~$\frac{R_2}{R_1 + R_2} = \frac{V_{R_2}}{V_{(R_1 + R_2)}} = \frac{V_0}{V_1}$~~

$V_0 = \frac{R_2}{R_1 + R_2} \cdot V_1$

1

$$V_{R_1} = 3V - 1.2V = 1.8V \quad I_{R_1} = \frac{V_{R_1}}{R_1} =$$


$$V_{R_2} = 1.2V$$

$$I_{R_2} = \frac{V_{R_2}}{R_2} =$$

$$V_{R_3} = 1.2V$$

$$I_{R_3} = \frac{V_{R_3}}{R_3} =$$

V_2 only:

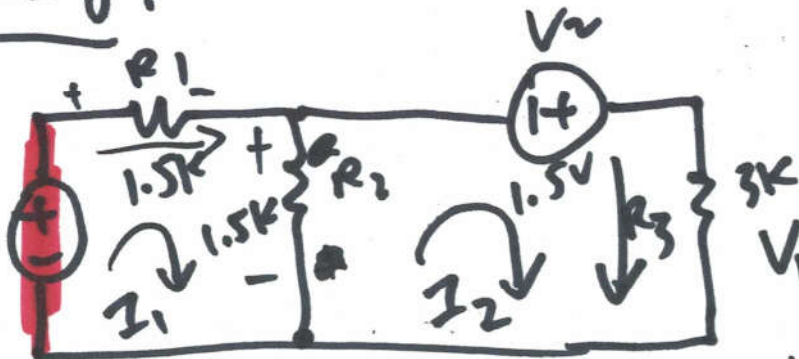

$$V_{R_3} = I_2 \cdot 3k = 0.4mA \cdot 3k = 1.2V$$

$$V_{R_1} = 1.5k \cdot 0.2mA = 0.3V$$

$$V_{R_2} = (6.2mA - 0.4mA) \cdot 1.5k = -0.3V$$

$$\left\{ \begin{aligned} I_1 \cdot R_1 + (I_1 - I_2) R_2 &= 0 \quad (\text{KVL}) \end{aligned} \right.$$

$$\left\{ \begin{aligned} (I_2 - I_1) \cdot R_2 - 1.5 + I_2 \cdot R_3 &= 0 \end{aligned} \right.$$

$$\left\{ \begin{aligned} I_1 \cdot 3k - I_2 \cdot 1.5k &= 0 \Rightarrow I_1 = 0.2mA \end{aligned} \right.$$

$$\left\{ \begin{aligned} I_2 \cdot 4.5k - I_1 \cdot 1.5k &= 1.5 \Rightarrow 9k \cdot I_2 - 3k I_1 = 3 \end{aligned} \right.$$

$$7.5k \cdot I_2 = 3V$$

$$I_2 = \frac{3V}{7.5k} = 0.4mA$$

(2)

$$V_{R1} = 1.8V + 0.3V = 2.1V$$

$$V_{R2} = 1.2V - 0.3V = 0.9V$$



$$V_{R3} = 1.2V + 1.2V = 2.4V$$

$$I_{R1} = \frac{V_{R1}}{R_1} = \dots$$

$$I_{R2} = \frac{V_{R2}}{R_2} = \dots$$



$$I_{R3} = \frac{V_{R3}}{R_3} = \dots$$

(3)

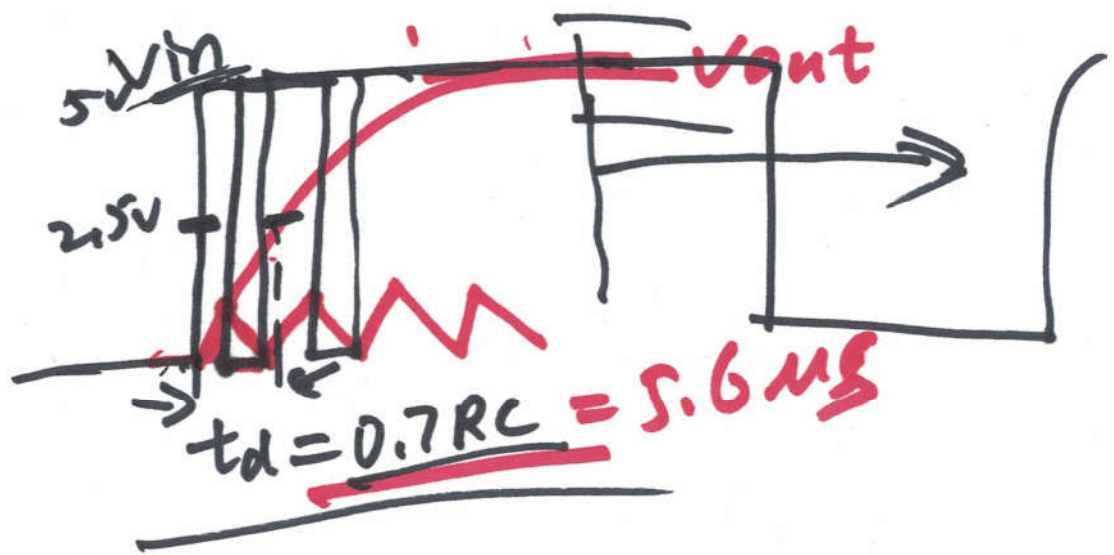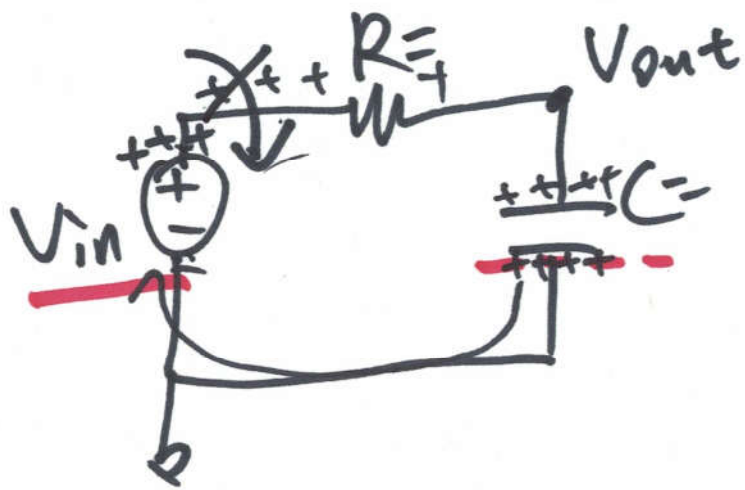


$$V_R = \frac{1}{R} \cdot R = 0$$

V_{TH} R_{TH}

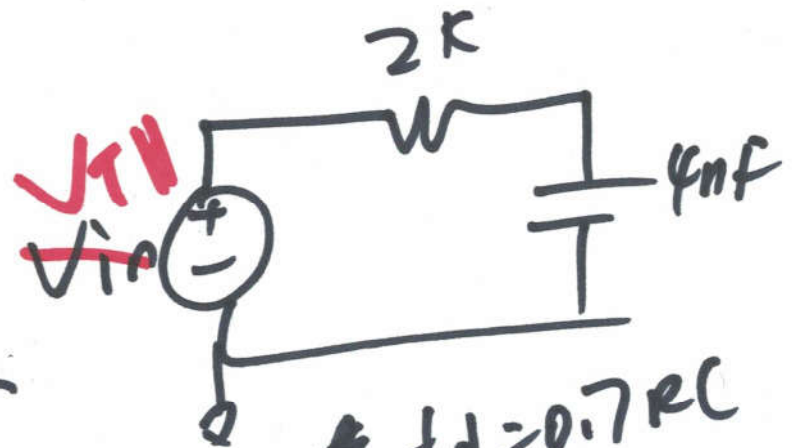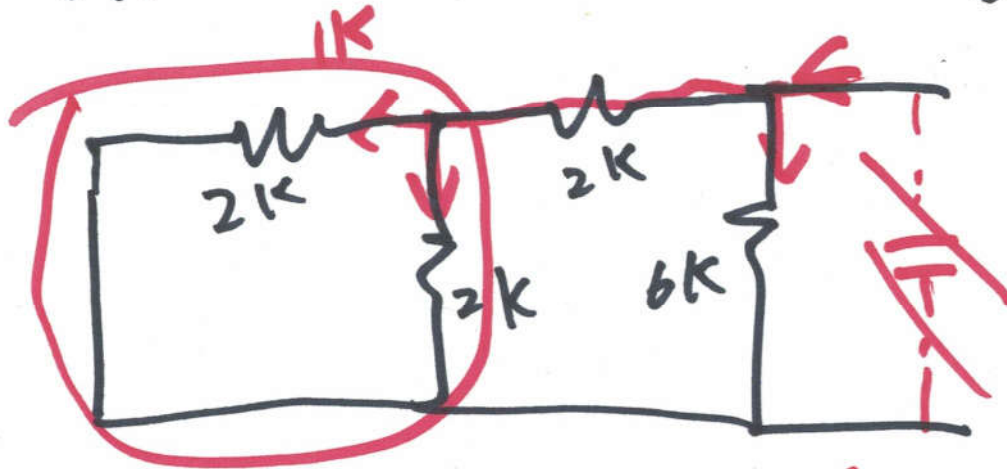
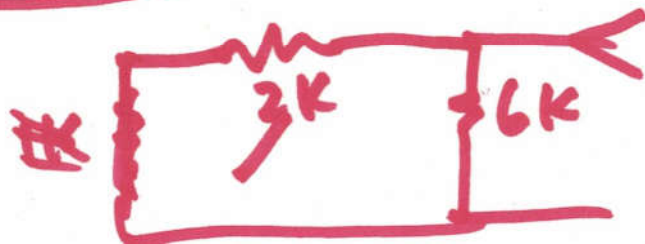
$$\begin{aligned}
 \tau &= t_d = 0.7RC \\
 &= 0.7 \cdot 2k \cdot 4n \\
 &= 5.6 \mu s
 \end{aligned}$$



$$R_{TH} = 2k$$