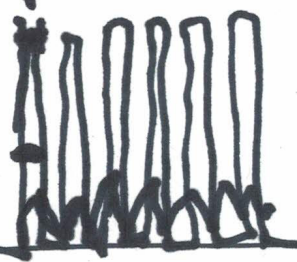


$t_d = 0.7RC$

$\tau = RC$ (time constant)



For the original circuit

PULSE(0 5 0 1P 1P 10n 2n)

vin 1 0 PULSE(

⋮

