

HW1 (100 points)

1.1. Determine the number of quantization levels needed if one wanted to make a digital thermometer that was capable of measuring temperatures to within $0.1\text{ }^{\circ}\text{C}$ accuracy over a range from $-50\text{ }^{\circ}\text{C}$ to $150\text{ }^{\circ}\text{C}$. What resolution of ADC would be required? (25 points)

1.2. A digitally programmable signal generator uses a 14-bit DAC with a 10-volt reference to generate a DC output voltage. What is the smallest incremental change at the output that can occur? What is the DAC's full-scale value? (25 points)

1.3. (a) Use Superposition and Thevenin's equivalent circuit theory to verify the LSB of the following R-2R DAC is $V_{DD}/2^N$. (b) If the digital input is 10101, find the analog output use Superposition and Thevenin's equivalent circuit theory. (50 points)

