

## Chapter 2 Semiconductor Basics (pn junction and BJTs)

2.1. Explain what are  $n_i$ ,  $n_n$ ,  $n_p$ ,  $p_n$ ,  $p_p$ ,  $N_A$ , and  $N_D$ .

2.2. Consider an n-type silicon for which the dopant concentration  $N_D=10^{17}/\text{cm}^3$ . Find the electron and the hole concentration at  $T=300\text{K}$  (room temperature). Show the calculation process for the credit.

2.3. Find the resistivity of (a) intrinsic silicon and (b) n-type silicon with  $N_D=10^{15}/\text{cm}^3$ . Use  $n_i=1.5 \times 10^{10}/\text{cm}^3$ , and assume that for intrinsic silicon  $\mu_n=1350 \text{ cm}^2/\text{V s}$  and  $\mu_p=480 \text{ cm}^2/\text{V s}$ , and for the doped silicon  $\mu_n=1000 \text{ cm}^2/\text{V s}$  and  $\mu_p=400 \text{ cm}^2/\text{V s}$ . ( $q=1.6 \times 10^{-19} \text{ C}$ )

2.4. Draw the pn junction and explain:

1) Without an external voltage, the formation of a depletion region, and the formation of the diffusion current and the drift current.

2) With an external voltage, explain the changes of the width of the depletion region under 'forward bias' and 'reverse bias' operations.


3) Explain how the depletion region will be changed, and how the diode capacitance will be changed with an increasing voltage under both 'forward bias' and 'reverse bias' operations?

4) If a pn junction is reverse biased, is  $I_D$  larger or  $I_s$  larger? What if it is forward biased?


5) Hand-draw the I-V curve of a real diode (with a 0.7 built-in voltage and no reverse breakdown) and the IV curve of an ideal diode.

6) Hand-draw the IV curve of a real Zener diode (with a 0.7 built-in voltage and a  $-V_z$ ) and the IV curve of an ideal Zener diode.

 2.5 Ideal diodes (no built-in voltages and no reverse breakdown) find the values of the voltages and currents indicated in the following figure.




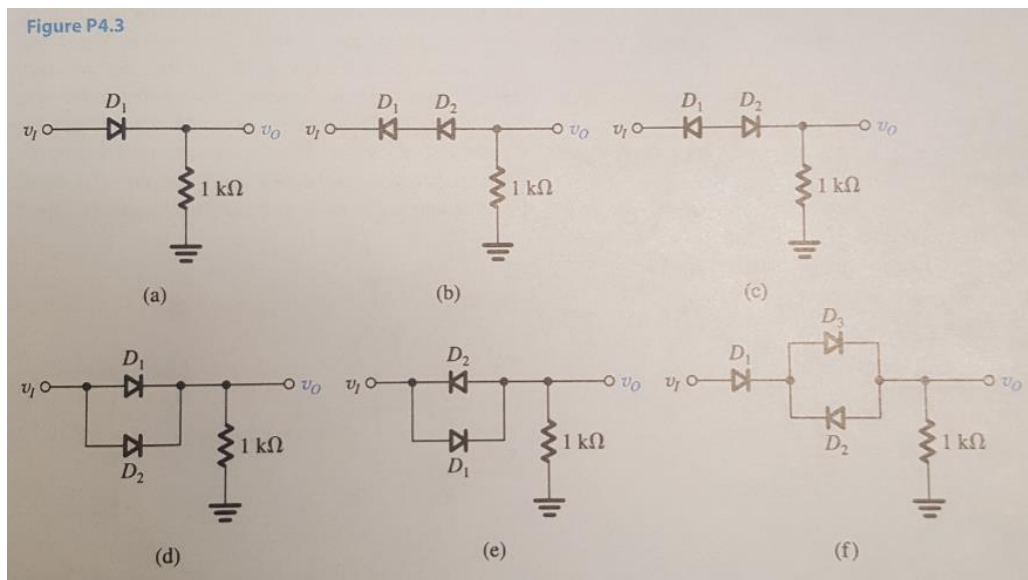2.6. In the following figure,  $V_i$  is a 1kHz 5-V peak-peak sine wave (centered at 0V), sketch the waveform of  $V_o$  and label the peak values. (ideal diodes, no built-in voltages and no reverse breakdown)



 2.7. The following circuit is being used for ESD (Electrostatic discharge) protection in ICs. The SPICE code is to simulate the accidental high voltage discharge from the input ( $V_{in}$ ). Depends on

$V_{in}$ , draw the  $V_{out}$  of this circuit. (assume 10V is the safe voltage for the digital circuit. You don't need to run this in LTSpice, just hand draw it). (the diodes are real diodes with a 0.7 built-in voltage and no reverse breakdown).




2.8. Consider an npn transistor with  $V_{BE} = 0.7V$  at  $I_C = 1mA$ . Find  $V_{BE}$  at  $I_C = 10mA$  ( $V_T = 25$  mV).

2.9. Transistors of a certain type are specified to have  $\beta$  values in the range of 50 to 150. Find the range of their  $\alpha$  values.

2.10. Calculate  $\beta$  for two transistors for which  $\alpha = 0.99$  and  $0.98$ . For collector currents of 10 mA, find the base current of each transistor.

 2.11 (a) Assume  $V_{CC} = 8$  V,  $R_B = 300$  k and  $R_C = 1$  k,  $\beta = 100$ . Determine whether the transistor is biased in cutoff, saturation or linear region. (b) Determine the Q-point values of  $I_C$  and  $V_{CE}$  for the following circuit. (c) Find  $I_{Cmax}$  and  $V_{CE(cutoff)}$  ( $V_{CE}$  when  $I_C = 0A$ ) and hand draw the DC load line and label the Q-point (just simply label the  $I_C$  and  $V_{CE}$  of the Q point on the load line). (d) Find the maximum peak value of base current for linear operation.



2.12 Select appropriate  $R_1$ ,  $R_2$ , and  $R_E$  to bias the following common emitter amplifier in linear region. Given that  $R_L=2k$ ,  $V_{CC}=15V$ ,  $V_{RE}=1V$ ,  $\beta =100$ . (Assume the current flows through  $R_2$  is 10 times higher than the Base current).

