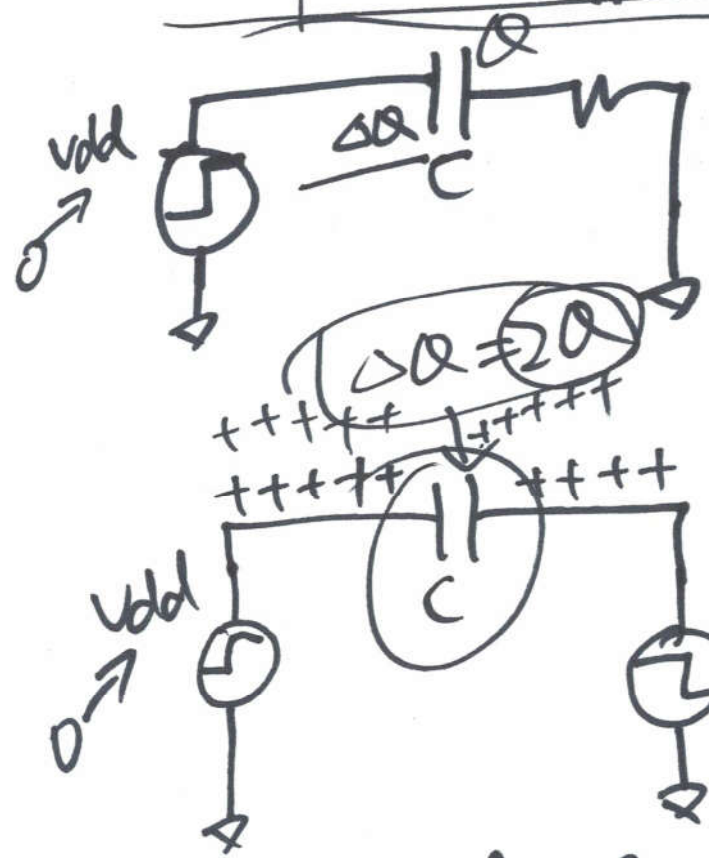


Models for Digital Design


① The Miller Effect



$$\Delta Q = C \cdot V$$



$$C = \frac{\Delta Q}{V}$$


$$V = \frac{\Delta Q}{C}$$

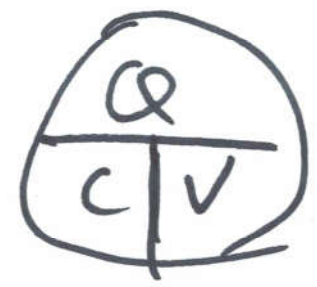


$$2Q = C_{eff} \cdot V_{dd}$$

$$C_{eff} = \frac{2Q}{V_{dd}} = 2C$$

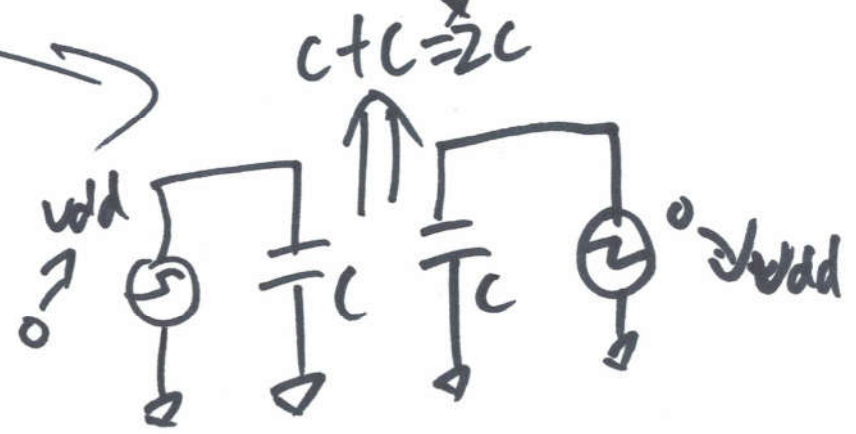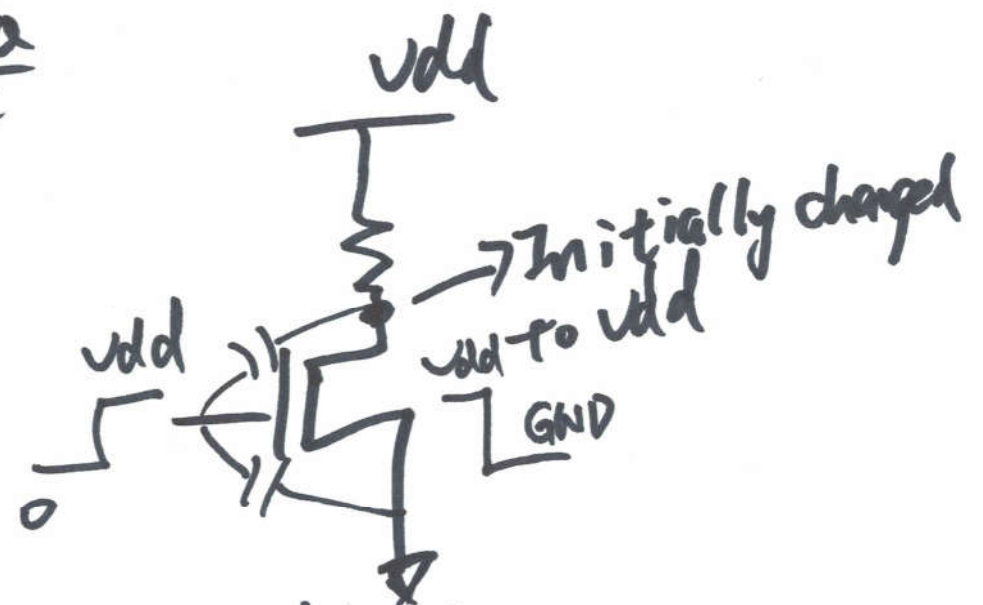


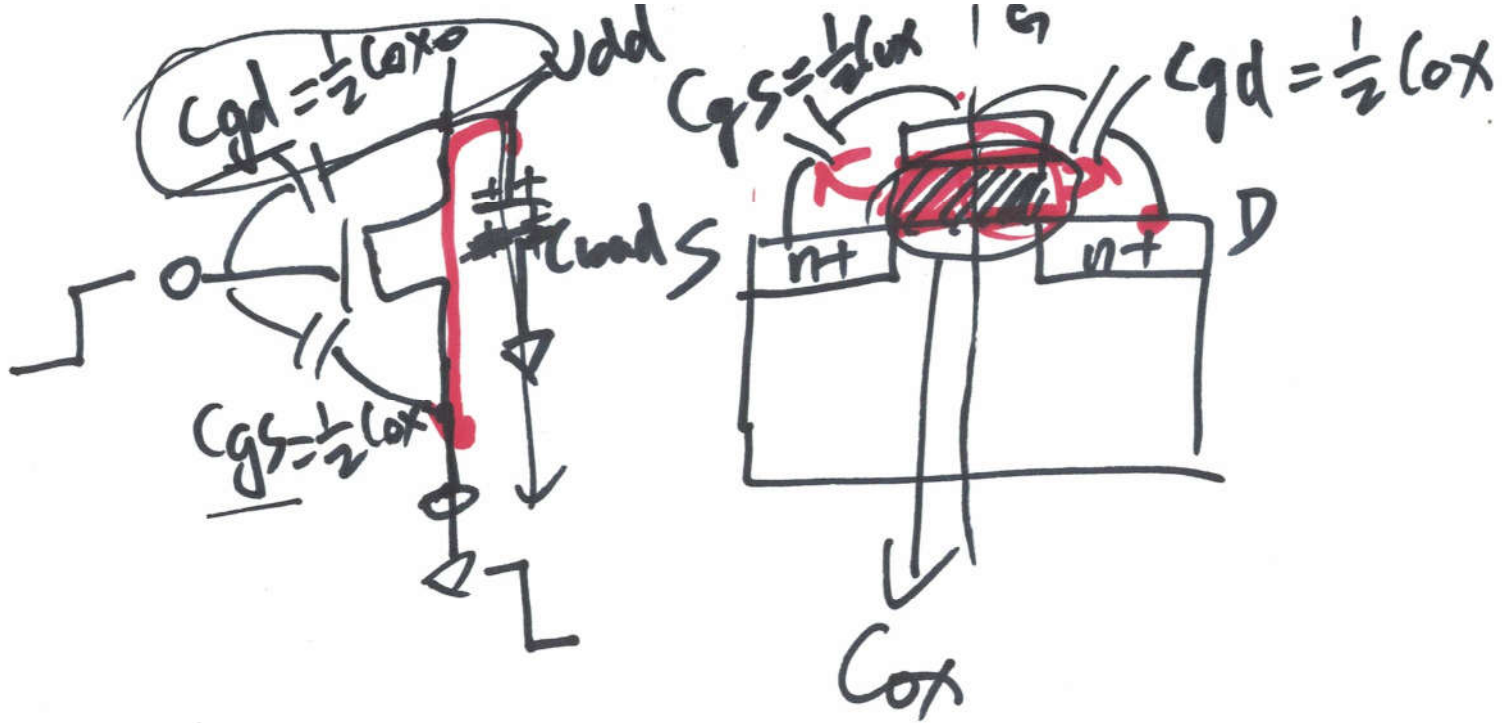


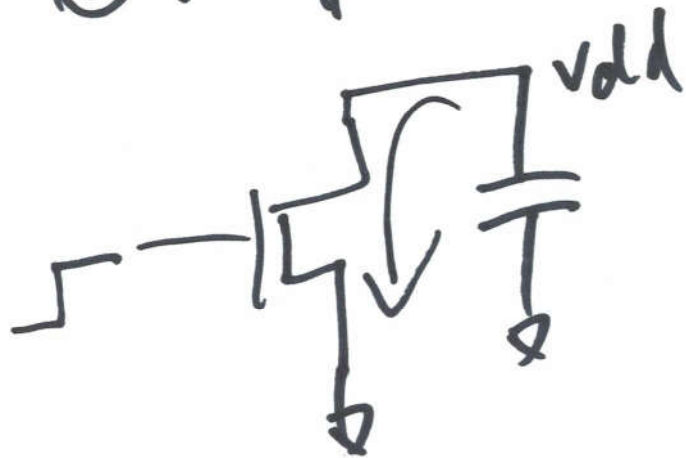② The Effective switching resistance of CMOS R_n, R_p



②

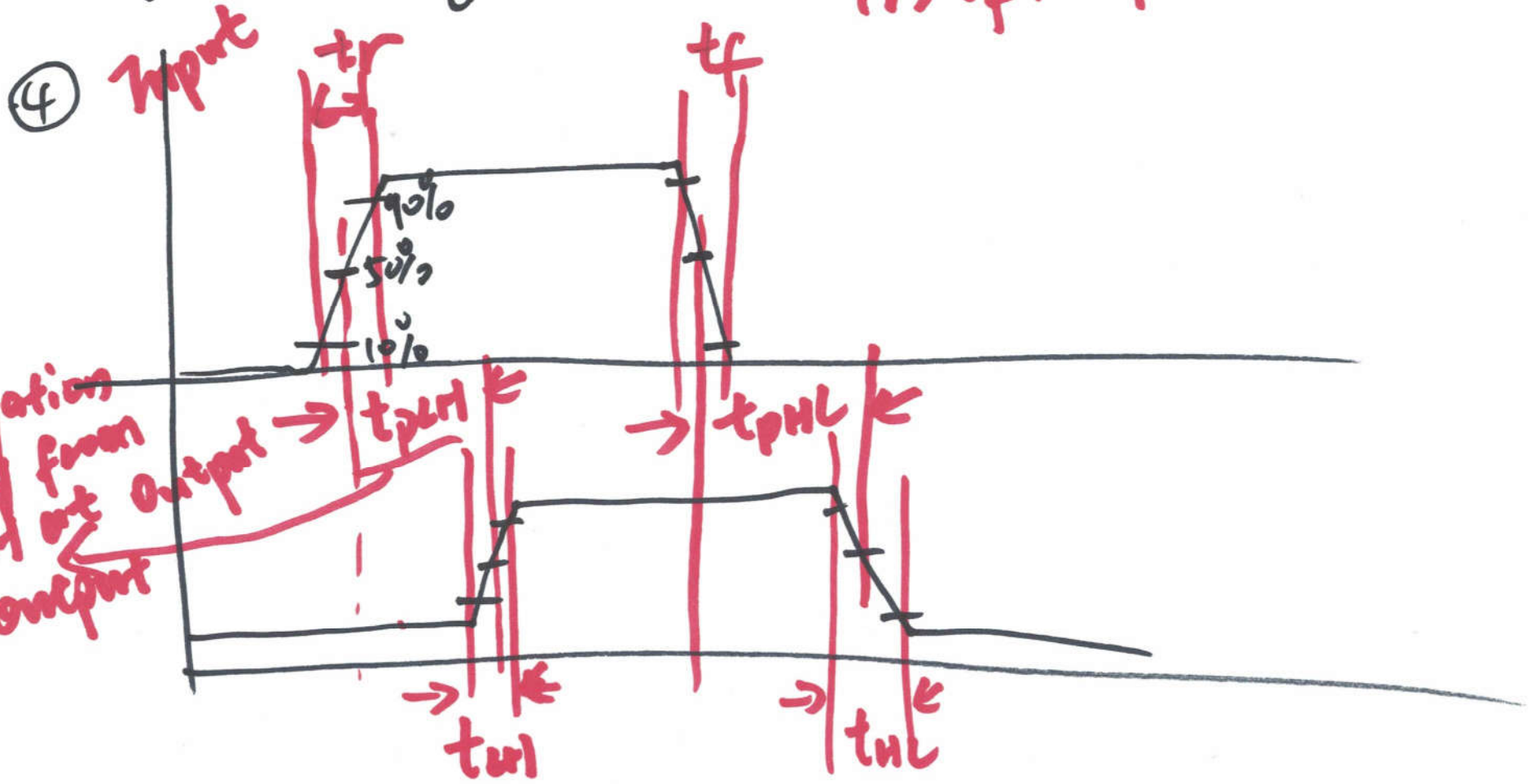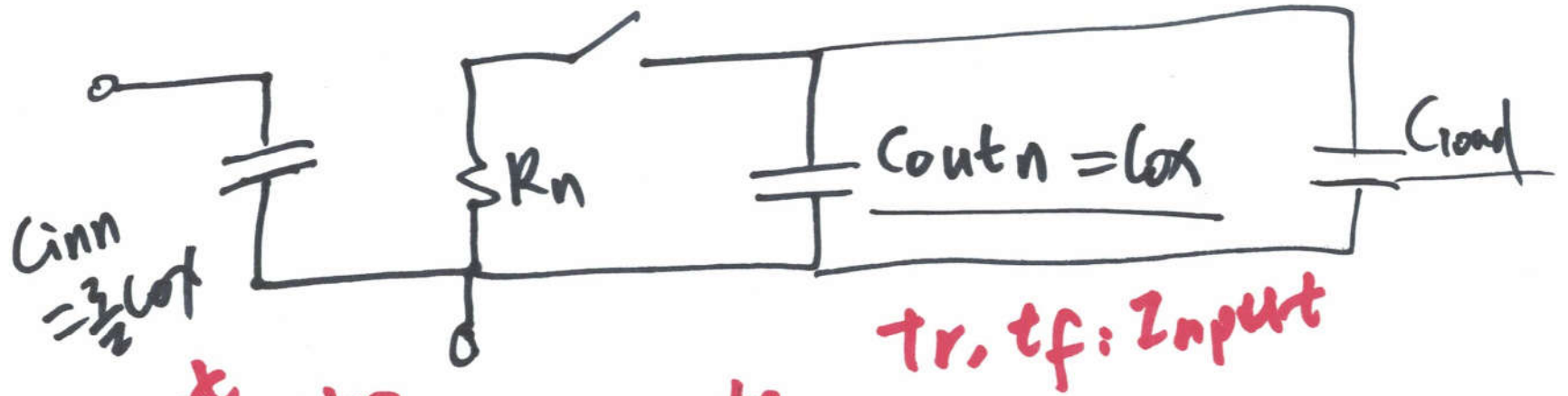② The complete resistive/capacitive switching MOSFET model:




③


$t_{PHL} \text{ or } t_{PLH} = 0.7RC$
 $t_{HL} \text{ or } t_{LH} = 2.2RC$

(PSO of the CMOS Book)

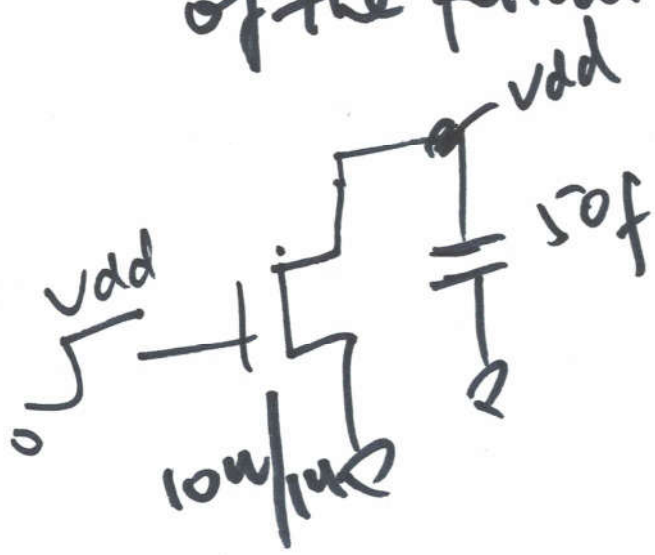Example: Estimate the fall and delay times (output) of the following circuit: (P320)




	Size	$R_{n,p}$	$C_{oxn,p}$
NMOS	1 μm	1.5K	17.5f
PMOS	30 μm	1.5K	52.5f

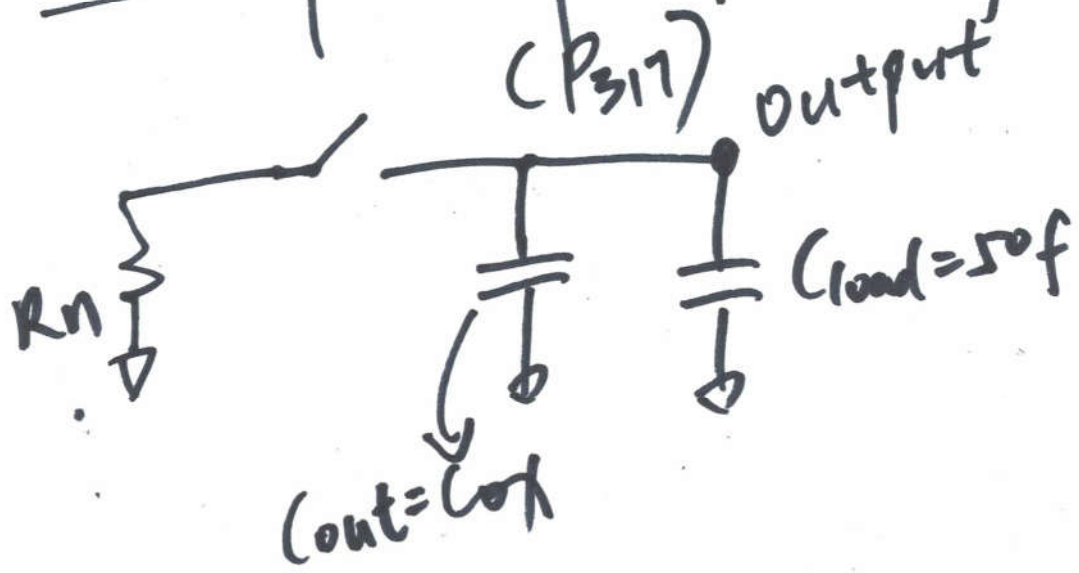

$$t_{HL} = 2.2RC = 2.2 \times 1.5K \cdot (17.5f + 50f) = 220ps$$

$$t_{pHL} = 0.7RC = 0.7 \times 1.5K \times (17.5f + 50f) = 70ps$$

what if it is a pmos?

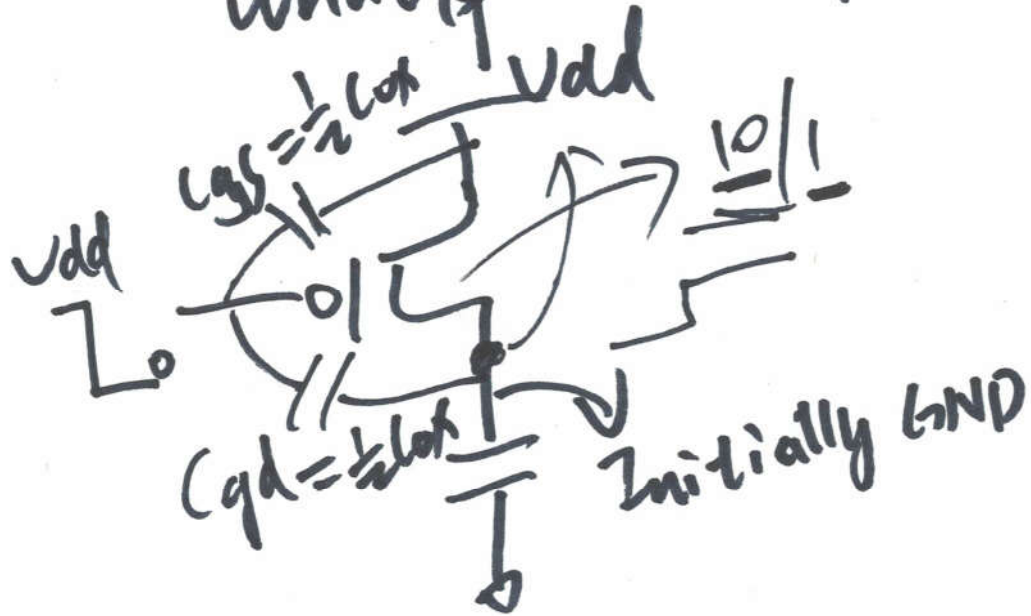

$$R_p = 1.5K \times 3 = 4.5K$$

$$C_{exp} = \frac{52.5f}{3} = 17.5f$$

$$t_{LH} = \cancel{2.2RC} 2.2RC$$

$$= 2.2 \times 4.5K \times (17.5f + 50f)$$



$$= 660ps$$

$$t_{pLH} = 0.7RC = 0.7 \times 4.5K \times (17.5f + 50f)$$

$$= 210ps$$

5

⑤ PG and TG

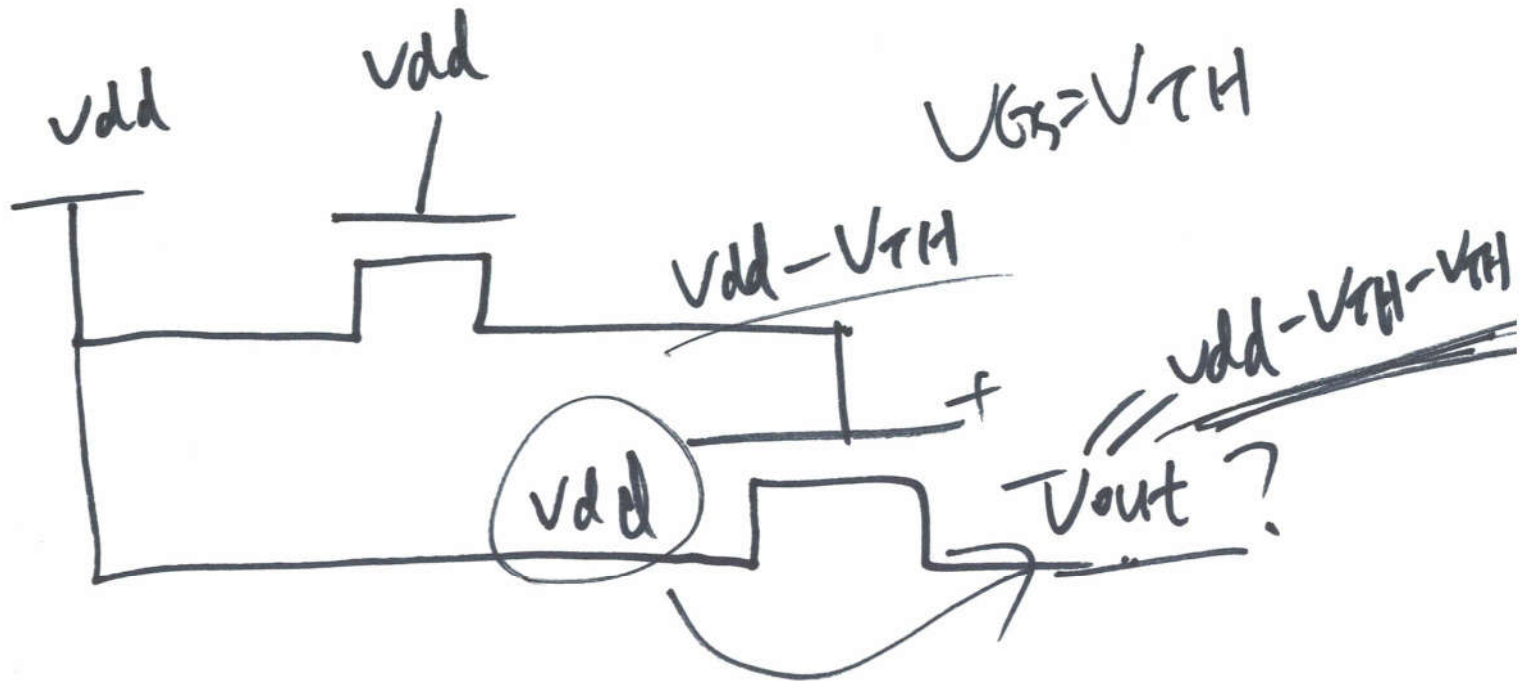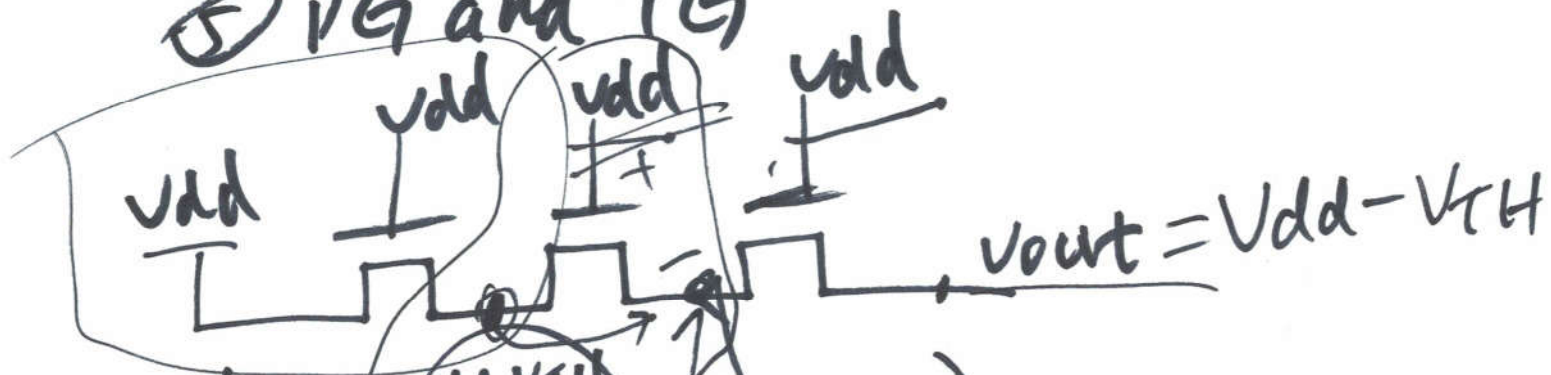

⑥