

HW 2 Solutions

2.2 $N_D = n_n = 10^{17} / \text{cm}^3$

$p_n \cdot n_n = n_i^2$

$p_n = \frac{n_i^2}{n_n} = \frac{(1.5 \times 10^{10} / \text{cm}^3)^2}{10^{17} / \text{cm}^3}$

$= 2.25 \times 10^3 / \text{cm}^3$

Electron conc. : $10^{17} / \text{cm}^3$

hole conc. : $2.25 \times 10^3 / \text{cm}^3$

2.3. (a) $\rho = \frac{1}{q \cdot (\mu_n \cdot n + \mu_p \cdot p)}$

$= \frac{1}{1.6 \times 10^{-19} (1350 \times 1.5 \times 10^{10} + 480 \times 1.5 \times 10^3)}$

$= \frac{1}{1.6 \times 10^{-19} \times 2745 \times 10^{10}}$

$= 2.27 \times 10^5 \Omega \cdot \text{cm}$

(b) $N_D = n_n = 10^{15} / \text{cm}^3$


$p_n = \frac{n_i^2}{n_n} = \frac{(1.5 \times 10^{10})^2}{(10^{15})^2}$

$= 2.25 \times 10^5 / \text{cm}^3$

$\rho = \frac{1}{1.6 \times 10^{-19} (1000 \cdot 10^{15} + 400 \cdot 2.25 \times 10^5)}$

$= \frac{1}{1.6 \times 10^{-19} \cdot 1000 \cdot 10^{15}} = 6.25 \Omega \cdot \text{cm}$

2.4 (1)

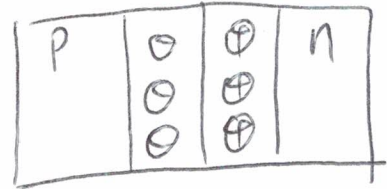


I_D : Diffusion current

I_S : saturation current (Drift current)


I_D : Caused by concentration gradient

I_S : Caused by Electric Field.

(2)

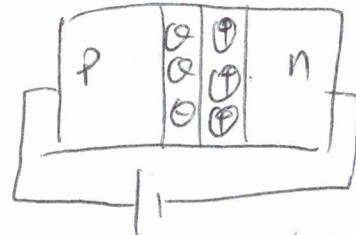

Forward Bias, depletion region thinner.




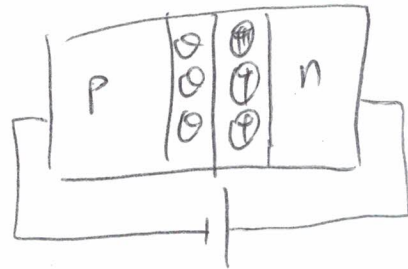


Reverse Bias, depletion region thicker.






(3) Forward Bias: capacitance increases.

Reverse Bias: capacitance decreases.

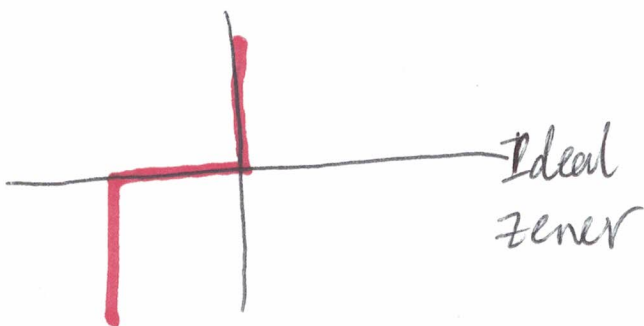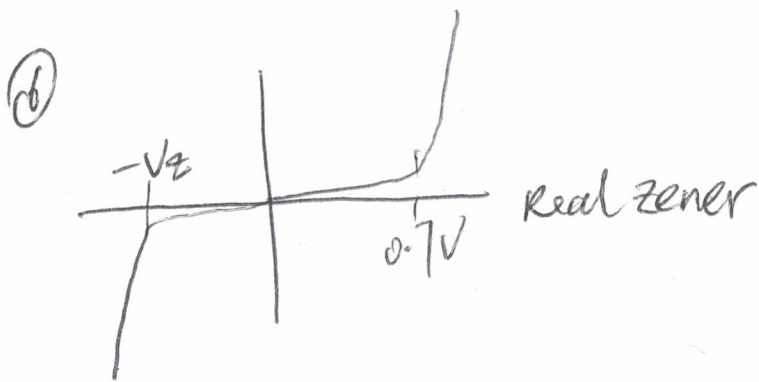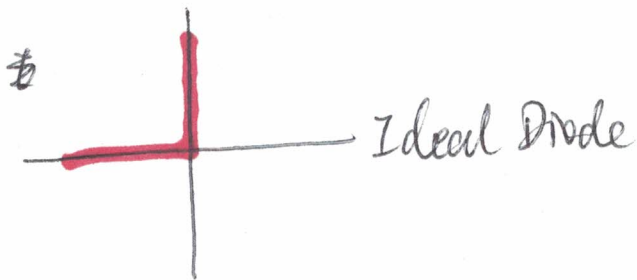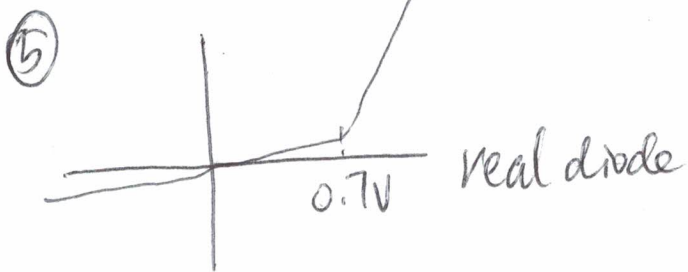(4) I_S is larger than I_D when a diode is reverse biased.





(d) $V = -3V$
 $I = 0A$

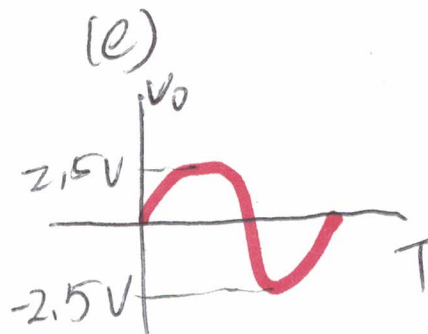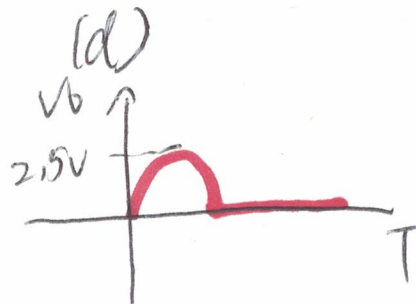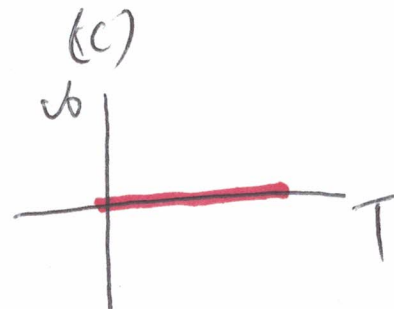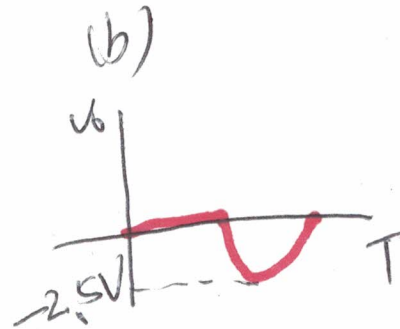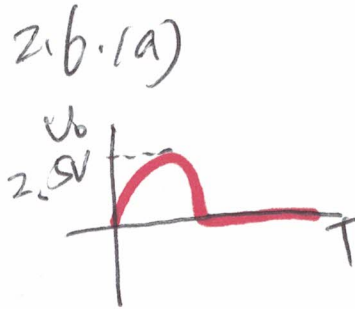

(1) (a) $V = -3V$
 $I = \frac{6V}{10k} = 0.6mA$

(b) $V = 3V$
 $I = 0A$

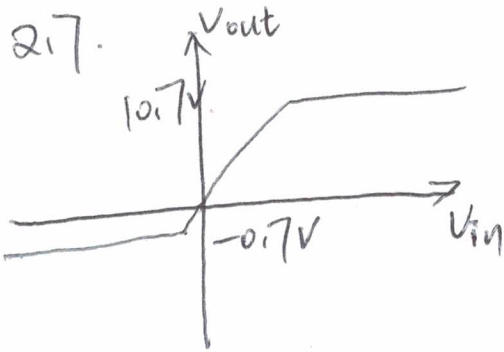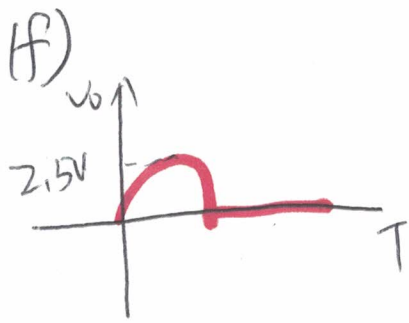(c) $V = 3V$
 $I = \frac{6V}{10k} = 0.6mA$



2.8.

$$I_C = I_S e^{V_{BE}/V_T}$$

$$\left\{ \begin{array}{l} 1 \text{ mA} = I_S e^{0.7/25 \text{ mV}} \\ 10 \text{ mA} = I_S e^{x/25 \text{ mV}} \end{array} \right.$$

$$\frac{1}{10} = e^{(0.7-x)/25 \text{ mV}}$$

$$\ln(0.1) = (0.7-x)/25 \text{ mV}$$

$$x = V_{BE} = \cancel{0.642 \text{ V}} \cdot 0.76 \text{ V}$$

2.9.

$$\alpha = \frac{\beta}{1 + \beta}$$

$$\beta = 50 \sim 150$$

$$\alpha = 0.98 \sim 0.99$$

2.10. $\beta = \frac{\alpha}{1 - \alpha}$

when $\alpha = 0.99$, $\beta = 99$

when $\alpha = 0.98$, $\beta = 49$

$$I_{B1} = \frac{10 \text{ mA}}{99} = 0.101 \text{ mA}$$

$$I_{B2} = \frac{10 \text{ mA}}{49} = 0.204 \text{ mA}$$

2.11. (a) Assume it is biased in the linear region,

$$I_B = \frac{8 \text{ V} - 0.7}{300 \text{ k}} = 24 \mu\text{A}$$

$$I_C = \beta I_B = 100 \cdot 24 \mu\text{A} = 2.4 \text{ mA}$$

$$V_{RC} = I_C \cdot R_C = 2.4 \text{ mA} \cdot 1 \text{ k} = 2.4 \text{ V}$$

$$V_{CE} = V_{CC} - V_{RC} = 8 \text{ V} - 2.4 \text{ V} = 5.6 \text{ V} > V_{BE}$$


so the BJT is biased in the linear region.

(b). $I_{CE} = 2.4 \text{ mA}$

$$V_{CE} = 5.6 \text{ V}$$

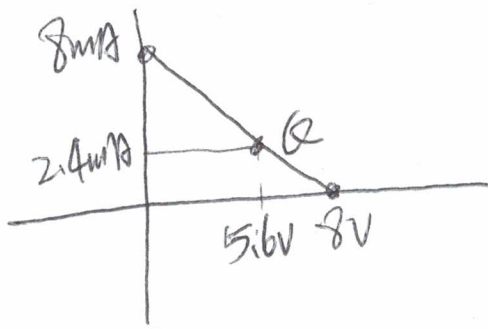(c) $I_{C \text{ max}} = \frac{V_{CC}}{R_C} = \frac{8 \text{ V}}{1 \text{ k}} = 8 \text{ mA}$

$$V_{CE}(\text{cutoff}) = V_{CC} = 8 \text{ V}$$



$$R_E = \frac{V_{RE}}{I_E} = \frac{1V}{(1+\beta)I_B}$$

$$= \frac{1V}{101 \cdot 35\mu A} = 282.9 \Omega$$

(d) $I_{Epeak} = 2.4 \text{ mA}$

$$I_{Bpeak} = \frac{I_{Epeak}}{\beta} = \frac{2.4 \text{ mA}}{100}$$

$$= 24 \mu A$$

2.12. $I_{Cmax} = \frac{V_{CC} - 1V}{R_L}$

$$= \frac{11V}{2k} = 7 \text{ mA}$$

$$I_{CQ} = \frac{I_{Cmax}}{2} = 3.5 \text{ mA}$$

$$I_{BQ} = \frac{I_{CQ}}{\beta} = \frac{3.5 \text{ mA}}{100} = 35 \mu A$$

$$I_{R2} = 10 I_B = 350 \mu A$$

$$I_{R1} = 11 I_B = 385 \mu A$$

$$R_1 = \frac{V_{CC} - V_B}{I_{R1}} = \frac{15 - 1.7}{385 \mu A}$$

$$= 34.5 \text{ k}\Omega$$

$$R_2 = \frac{1.7V}{I_{R2}} = \frac{1.7V}{350 \mu A} = 4.86 \text{ k}\Omega$$