

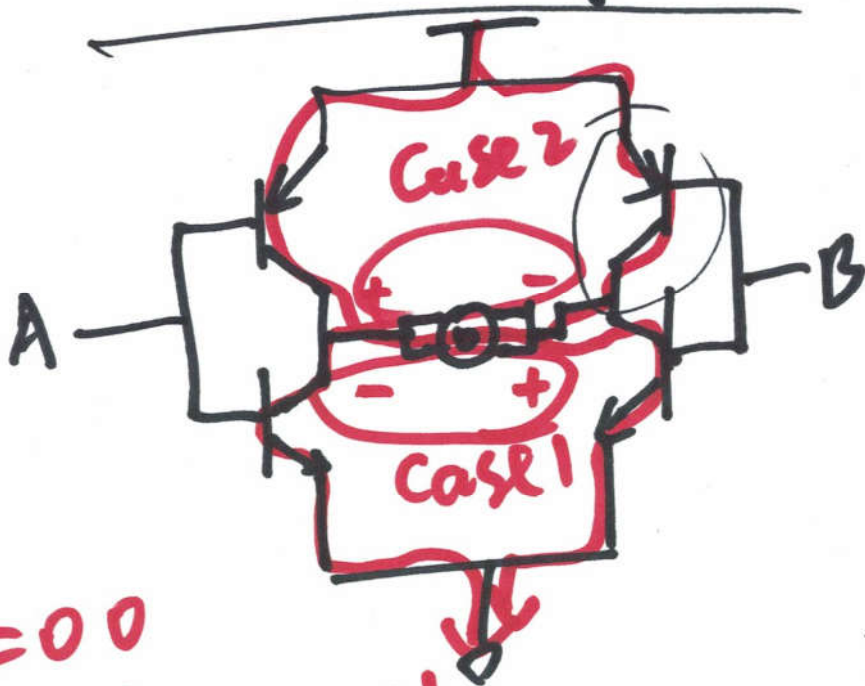
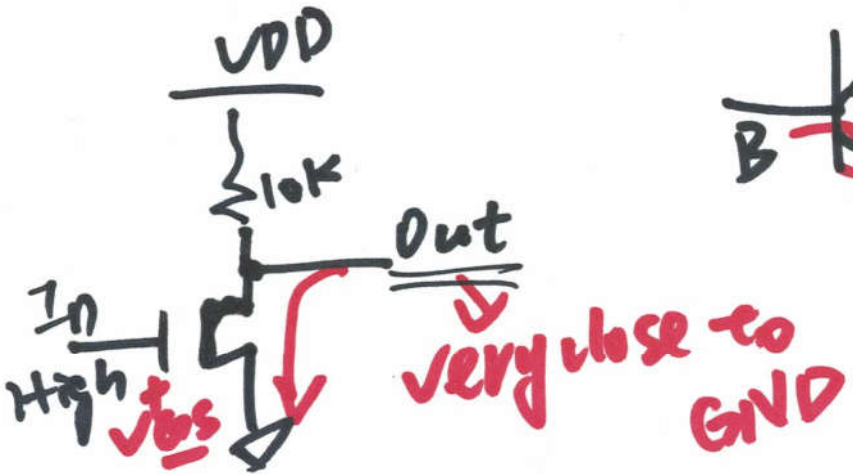


MORE BJTs


① The H-Bridge

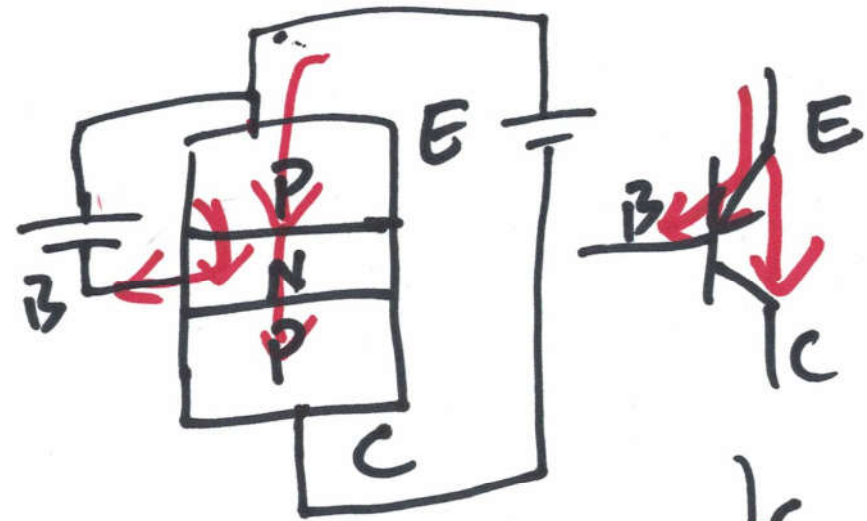


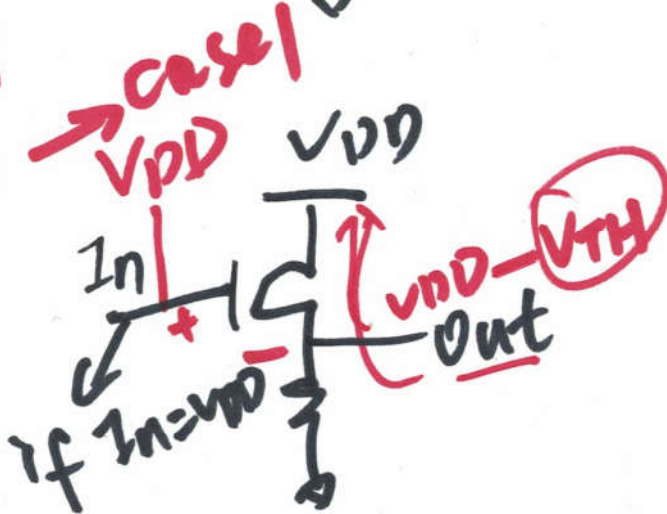
- AB=00
- AB=11
- AB=10
- AB=01
- ↓ case 2




NMOSes are good
at pulling to GND

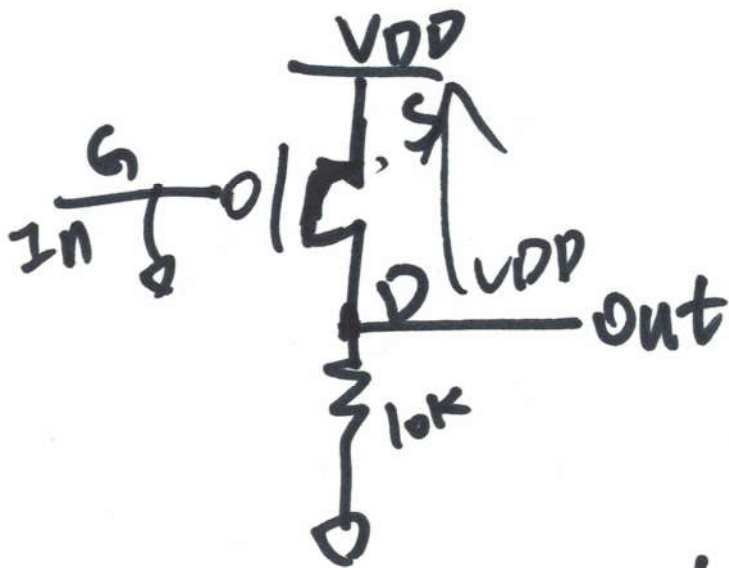

PMOS are good
 out pull out to VDD

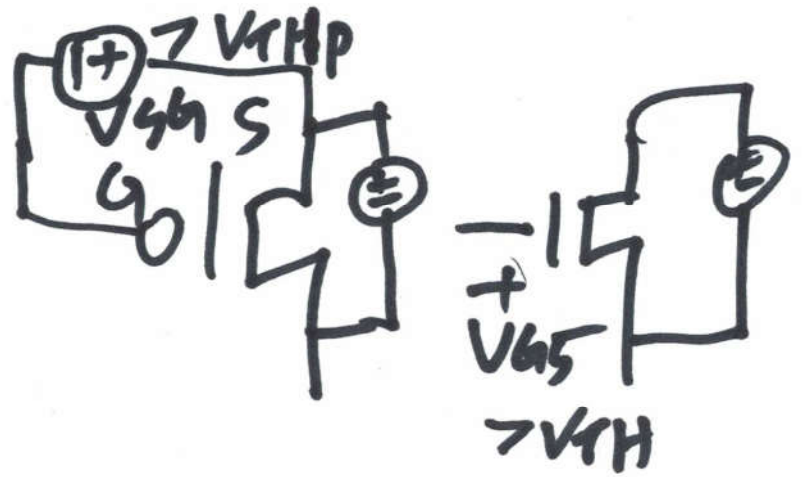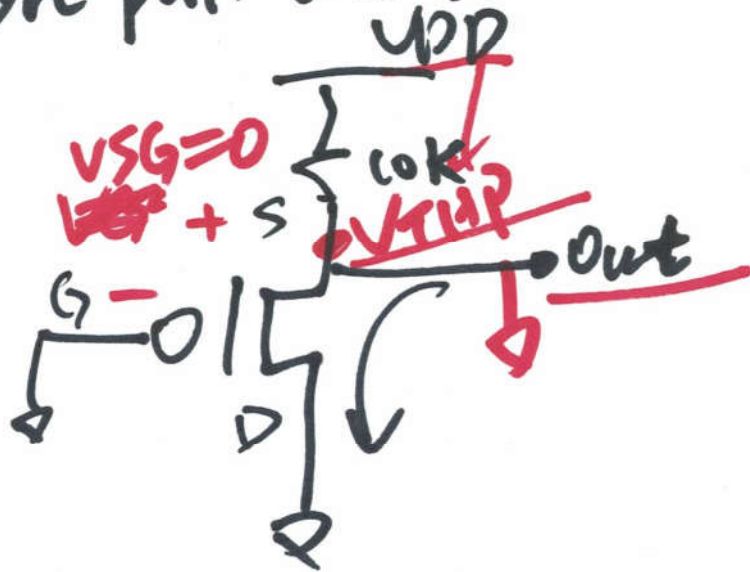

② BJT Amplifier:


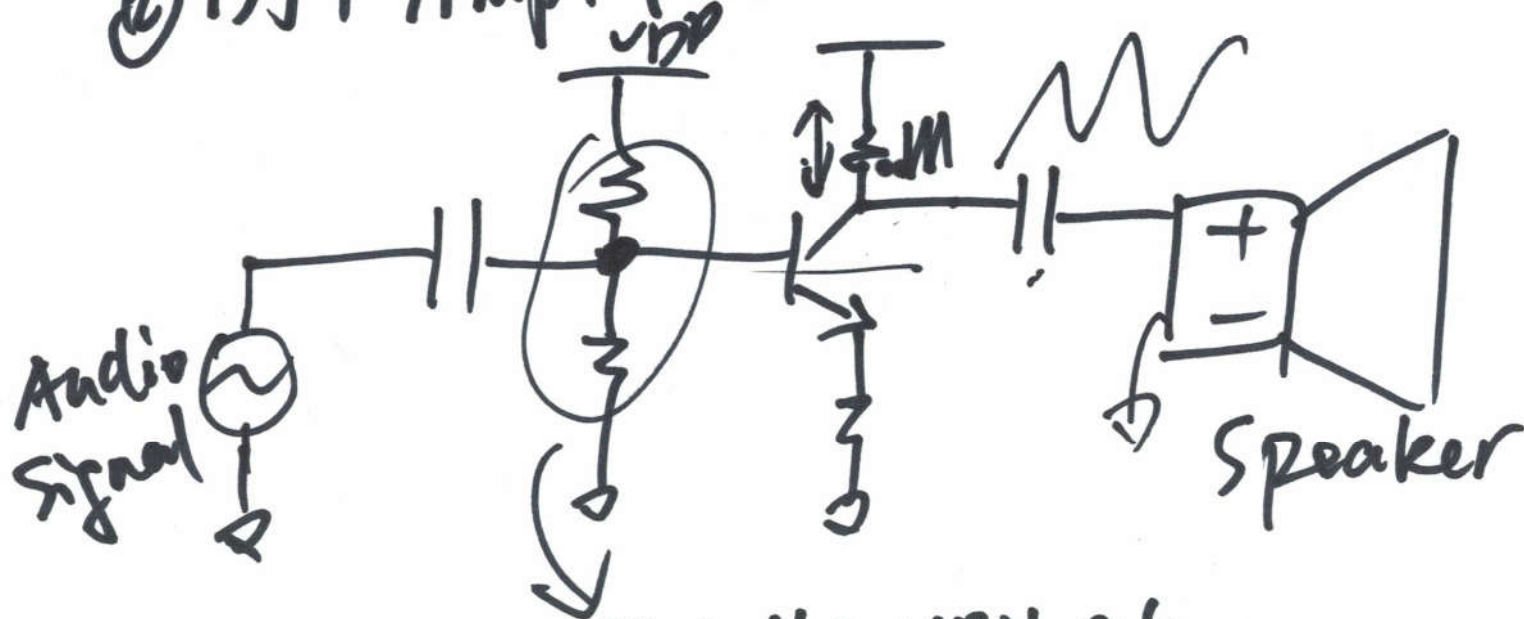


Bias the NPN at
a certain Q point




③ Multi-stage Amplifiers

△ Darlington Amplifier

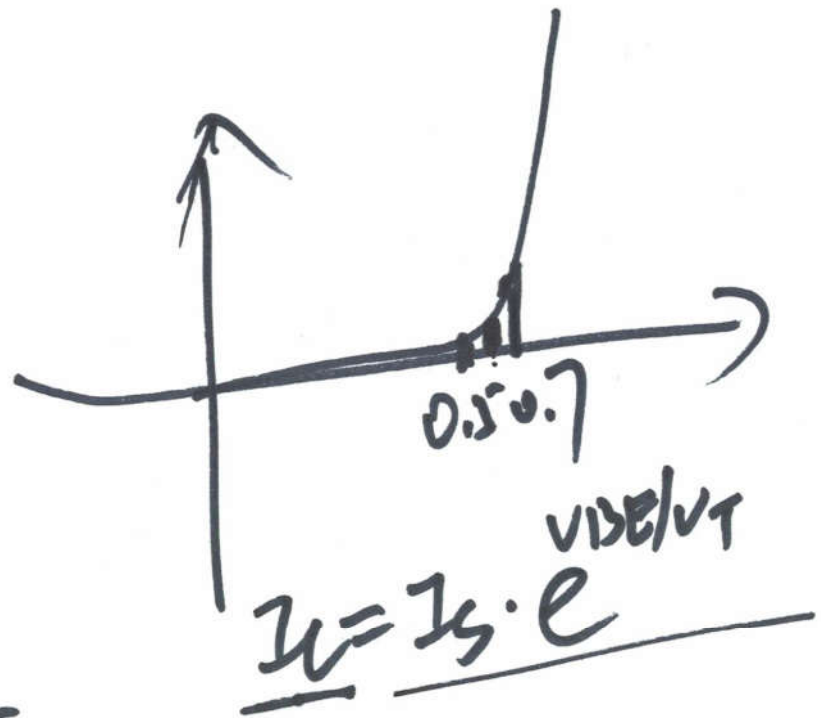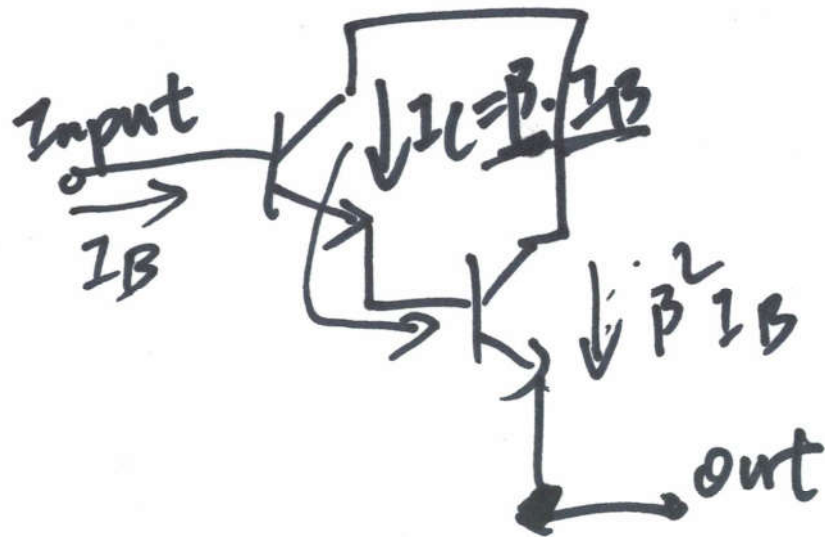

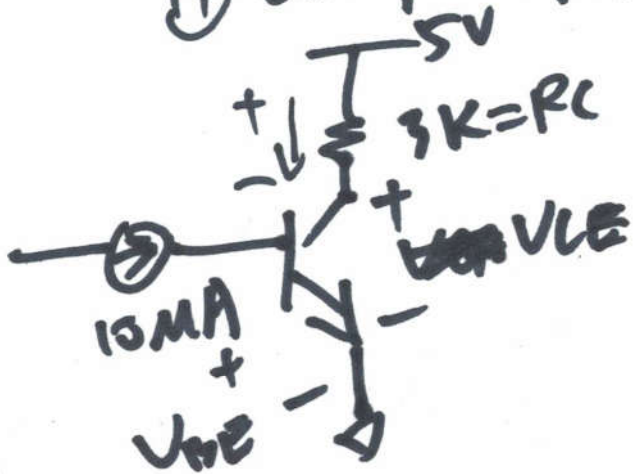④ Example: NPN BJT, $I_S = 10^{-15}$ A, $\beta = 100$, ① what is V_{BE} and V_{CE} ?



$$\textcircled{1} \begin{cases} V_{CE} = 5V - I_C \cdot R_C \\ I_C = \beta \cdot I_B = 100 \cdot 10\mu A \end{cases}$$


$$I_C = I_S \cdot e^{V_{BE}/V_T} \Rightarrow e^{V_{BE}/V_T} = \frac{I_C}{I_S}$$

$$\frac{V_{BE}}{V_T} = \ln \frac{I_C}{I_S} \Rightarrow V_{BE} = V_T \cdot \ln \frac{I_C}{I_S}$$

25mV

④

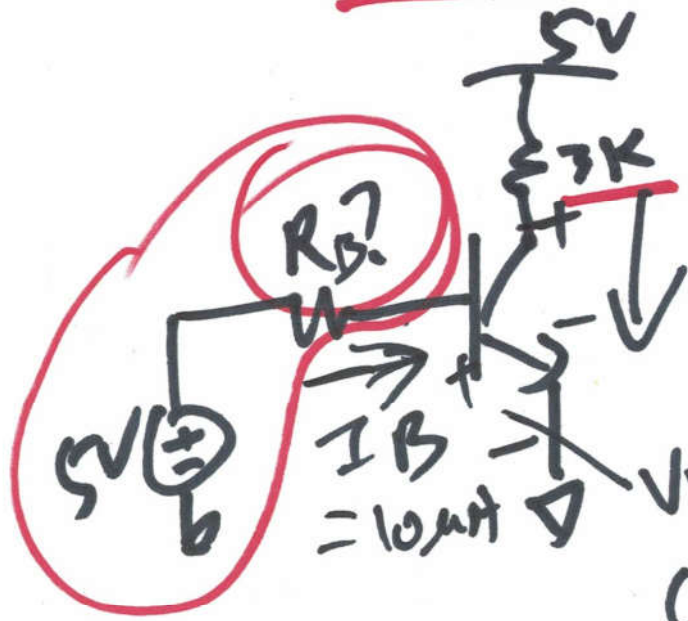② Replace the $10\mu\text{A}$ current source with a resistor and a 5V voltage source. what resistance is required to result in the same operation?



V_{BE} was calculate just now

$$\frac{5\text{V} - V_{BE}}{R_B} = 10\mu\text{A}$$



$\Rightarrow R_B$ can be calculated

\Downarrow
same I_C, I_B
 V_{CE}, V_{BE}

④

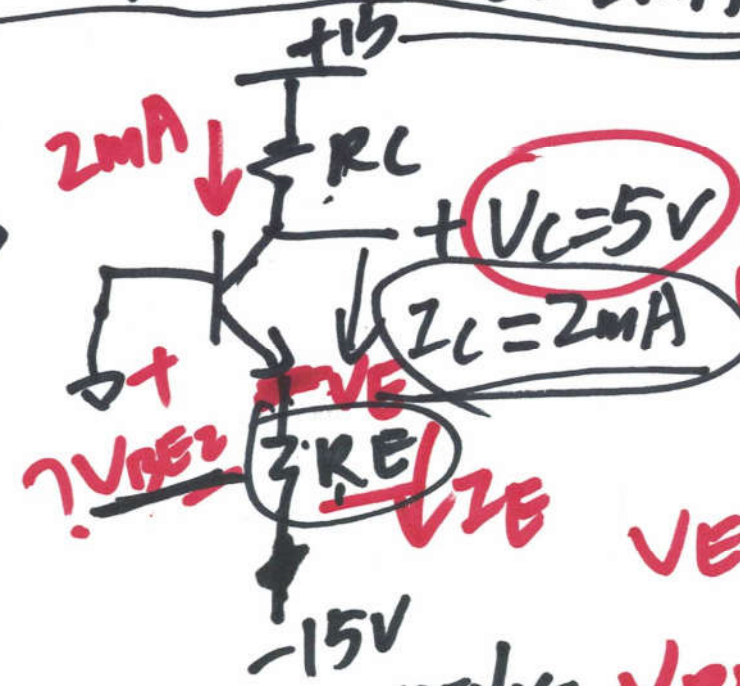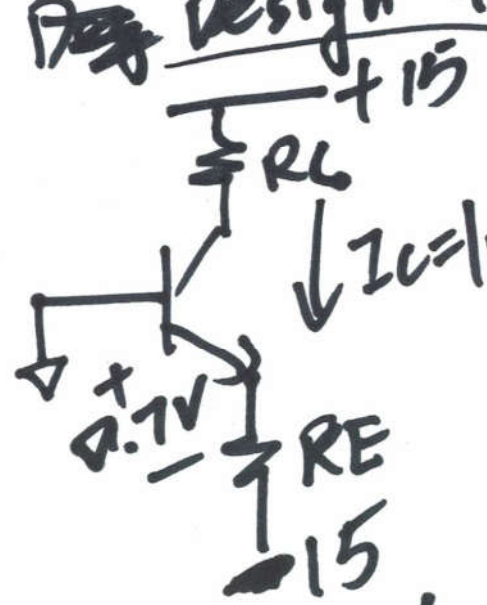Example:
 $\beta = 100$, $V_{BE} = 0.7V$ at $I_C = 1mA$.

Design the circuit so that $I_C = 2mA$, $V_C = 5V$.



$V_{RC} = 15 - 5 = 10V$
 $R_C = \frac{V_{RC}}{I_C} = \frac{10V}{2mA} = 5k\Omega$

$V_E = -V_{BE2} = -0.7V$
 $V_{RE} = \frac{V_E - (-15V)}{I_E}$
 $R_E = \frac{V_{RE}}{I_E}$

$I_C = I_S e^{V_{BE1}/V_T}$
 $1mA = I_S e^{0.7/V_T}$
 $I_{C1} = I_S e^{V_{BE1}/V_T}$
 $I_{C2} = I_S e^{V_{BE2}/V_T}$

$\frac{I_{C1}}{I_{C2}} = \frac{I_S e^{V_{BE1}/V_T}}{I_S e^{V_{BE2}/V_T}}$
 $\frac{1mA}{2mA} = e^{(V_{BE1} - V_{BE2})/V_T}$

$V_{BE2} = \dots$

(6)

$$I_C = \beta I_B$$

$$\alpha I_E = I_C$$

$$\alpha = \frac{\beta}{1 + \beta}$$

$$\beta = \frac{\alpha}{1 - \alpha}$$

$$I_C + I_B = I_E$$

$$\alpha = \frac{\beta}{1 + \beta} = \frac{100}{101}$$

$$I_E = \frac{1}{\alpha} I_C = \frac{1}{\alpha} \cdot 2 \text{mA}$$

(7)