

More BJTs

Example 1:

Consider an npn, $V_{BE} = 0.7V$. at $I_C = 1mA$, Find

V_{BE} at $I_C = 0.1mA$, and $10mA$.

$$I_C = I_S e^{V_{BE}/V_T}$$

$$\left\{ \begin{array}{l} I_C = \beta I_B \\ \alpha I_E = I_C \\ I_E = I_B + I_C \end{array} \right\}$$

$$\Rightarrow \alpha = \frac{\beta}{1+\beta}$$
$$\beta = \frac{\alpha}{1-\alpha}$$

$$\left\{ \begin{array}{l} 1mA = I_S e^{0.7/25mV} \\ 0.1mA = I_S e^{V_{BE}/25mV} \end{array} \right.$$

$$\frac{1mA}{0.1mA} = \frac{I_S e^{0.7/25mV}}{I_S e^{V_{BE}/25mV}}$$

$$10 = e^{(0.7 - V_{BE})/25mV}$$

Example 2:

npn BJT, $I_B = 14.46 \mu\text{A}$, $I_E = 1.46 \text{mA}$, $V_{BE} = 0.7 \text{V}$

calculate α , β , and I_S .

$$\alpha I_E = I_C \quad \alpha = \frac{I_C}{I_E} = \frac{I_E - I_B}{I_E} = \frac{1.46 \text{mA} - 14.46 \mu\text{A}}{1.46 \text{mA}}$$

$$\beta = \frac{\alpha}{1 - \alpha} = \frac{0.99}{0.01} = 99 = 0.99$$

50 ~ 200


$$I_C = I_S e^{V_{BE}/V_T} \Rightarrow I_S = \frac{I_C}{e^{0.7/25\text{mV}}} = \frac{1.46 \text{mA} - 14.46 \mu\text{A}}{e^{0.7/25\text{mV}}}$$

$$= \frac{I_C}{e^{0.7/25\text{mV}}}$$

$$= 10^{-15} \text{A}$$

(2)

Example 3: PNP BJT

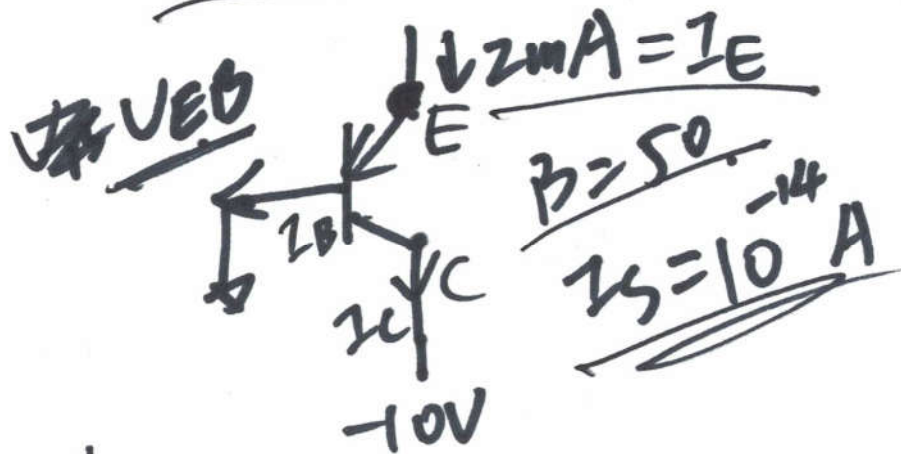

$\beta = 50$
 $I_S = 10^{-14} \text{ A}$

$V_E?$ $I_B?$ $I_C?$

$\alpha I_E = I_C$

$I_C = \frac{\beta}{1+\beta} \cdot 2\text{mA} = \frac{50}{51} \cdot 2\text{mA}$

$= 1.96 \text{ mA}$

$I_B = I_E - I_C = 2\text{mA} - 1.96\text{mA}$

$= 0.04 \text{ mA}$

$V_E = V_{EB}$

$I_C = I_S \cdot e^{V_{EB}/V_T} \Rightarrow \frac{I_C}{I_S} = e^{V_{EB}/V_T}$


$V_{EB} \Rightarrow \ln \frac{I_C}{I_S} = \frac{V_{EB}}{V_T}$

$V_{EB} = V_E = V_T \cdot \ln \frac{I_C}{I_S}$


0.50.7

(3)

Example 4:

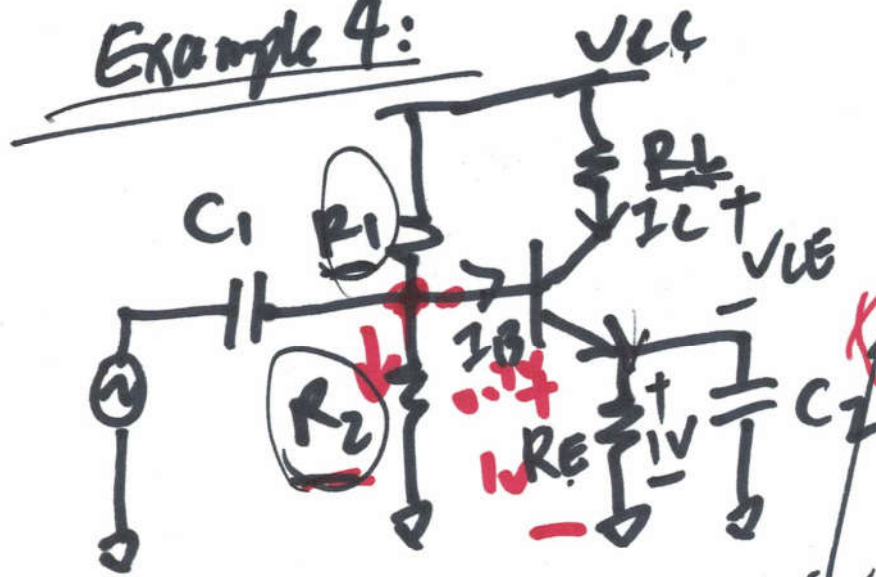

Quiescent Point (Q point)

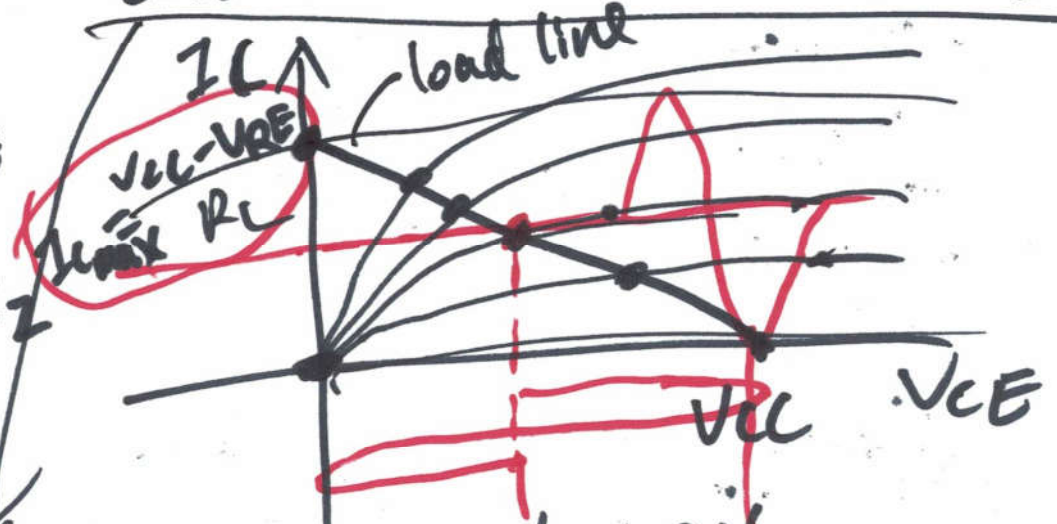

If $R_L = 1.2 \text{ k}\Omega$
 $V_{CC} = 12 \text{ V}$, $V_{RE} = 1 \text{ V}$,
 $\beta = 100$.

$I_{R2} = 10 I_B$


I_C, I_B, V_{BE}
 V_{CE} .

When $V_{CE} = 0 \text{ V}$,

$$I_C = \frac{V_{CC} - V_{RE}}{R_L}$$

$$I_{Cmax} = \frac{V_{CC} - V_{RE}}{R_L} = \frac{12 - 1}{1.2 \text{ k}} = 9.2 \text{ mA}$$
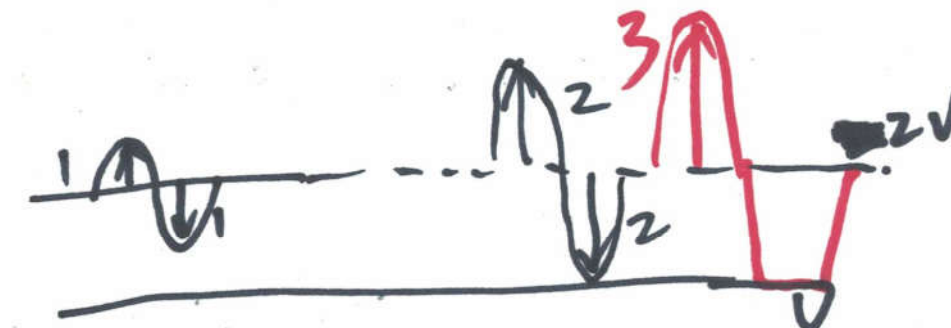
$$I_{CQ} = \frac{I_{Cmax}}{2} = 4.6 \text{ mA}$$



(4)

$$I_{BQ} = \frac{I_{CQ}}{\beta} = 46 \mu A$$

$$I_{R2} = 10 I_B = 10 \cdot 46 \mu A = 460 \mu A$$

$$V_B = V_{R2} = 1.7 V$$

$$R_2 = \frac{V_{R2}}{I_{R2}} = \frac{1.7 V}{460 \mu A} = 3.71 k\Omega$$

$$I_{R1} = 10 I_B + I_B = 11 I_B = 11 \cdot 46 \mu A = 460 \mu A + 46 \mu A$$

$$R_1 = \frac{V_{CC} - V_B}{I_{R1}} = \frac{12 V - 1.7 V}{506 \mu A} = 20.45 k\Omega$$

$$I_E = \frac{1}{2} \cdot I_C = \frac{1 + \beta}{\beta} \cdot I_C = \frac{101}{100} \cdot 4.6 mA = 4.63 mA$$

$$R_E = \frac{1 V}{I_E} = \frac{1 V}{4.63 mA} = 216 \Omega$$

In conclusion, $R_1 = 20 k\Omega$, $R_2 = 3.7 k\Omega$, $R_C = 1.2 k\Omega$
 $R_E = 216 \Omega$

$$I_E = I_C + I_B$$

$$= \beta I_B + I_B$$

$$= I_C + \frac{I_C}{\beta}$$

$$= \left(1 + \frac{1}{\beta}\right) I_C$$

$$= \frac{\beta + 1}{\beta} \cdot I_C$$



$$2 I_E = I_C$$

(5)

Example 5:

Determine the Q-point and find the maximum peak value of the Base current for linear operation.

$$\beta = 200.$$

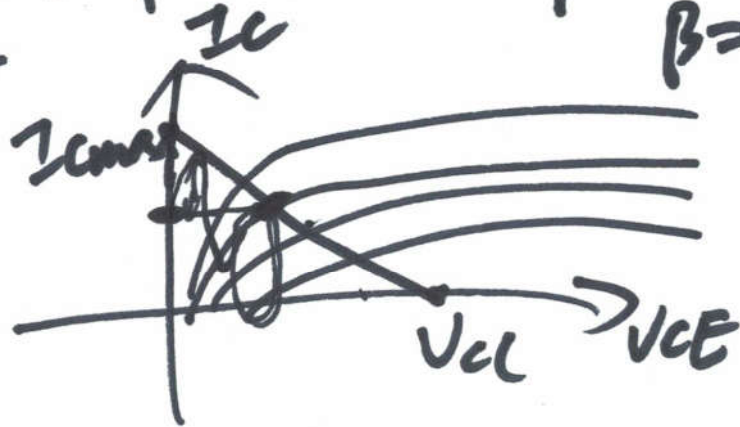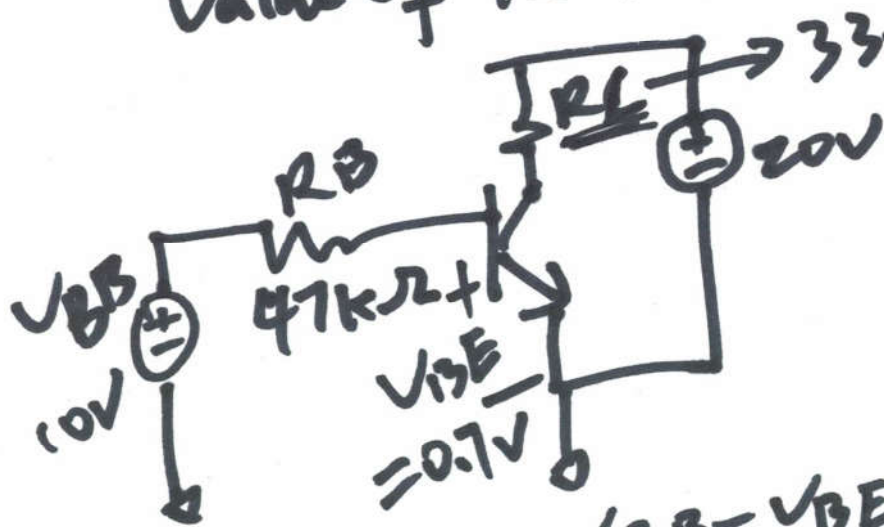

$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{10V - 0.7V}{47k} = 198 \mu A = I_{BQ}$$

$$I_C = \beta \cdot I_B = 200 \cdot 198 \mu A = 39.6 \text{ mA} = I_{CQ}$$

$$I_{Cmax} = \frac{20 - 0}{330\Omega} = \frac{20V}{330\Omega} = 60.6 \text{ mA}$$

39.6 mA is closer to the ~~Q~~ I_{Cmax} ,

$$\text{so the peak } I_{Cp} = 60.6 \text{ mA} - 39.6 \text{ mA} = 21 \text{ mA}$$

(6)

$$I_{Bp} = \frac{I_{Cp}}{\beta} = \frac{21 \text{ mA}}{200} = \dots$$

①