

① Quiz 3 on Wednesday.

- a. Diodes terminal characteristics
- b. BJTs (npn)

② Midterm on Friday (55 min, close-book close-notes)

a. DAC

b. ADC

c. Diode terminal characteristics



d. npns

e. concepts:

CLM, Latch-up, pn depletion region,

Body Effect,  $I_s/I_D$ , N-well resistor sheet

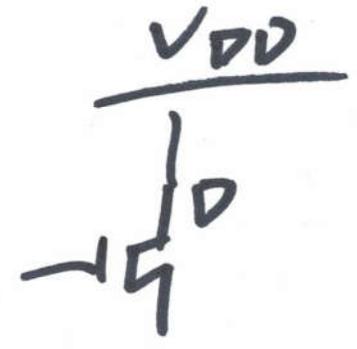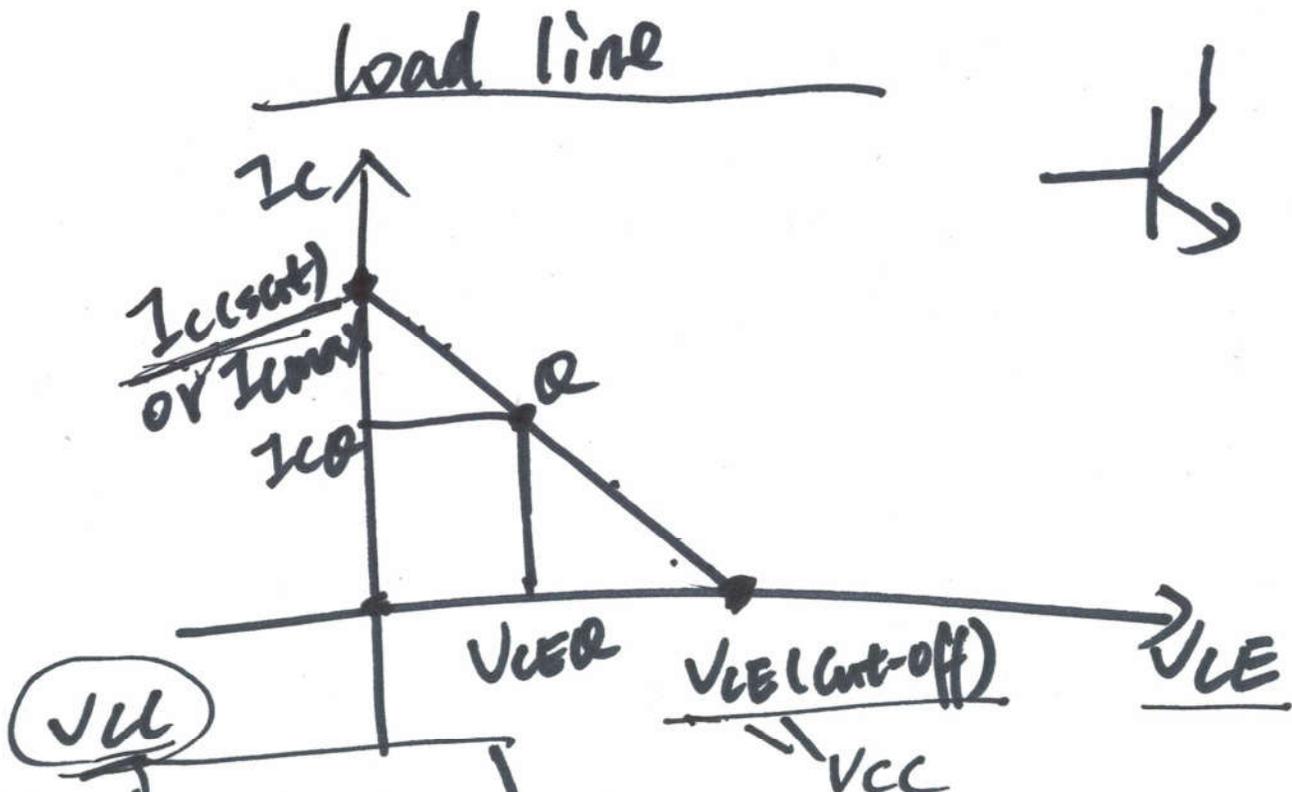resistance,  $n_i/n_n/n_p/p_n/p_a/N_A/A_D$ .



$V_{CC}$




$$I_{C(sat)} = \frac{V_{CC}}{R_L}$$

$$V_{CE(cut-off)} = V_{CC}$$

(2)

Determine the Q-point and find the maximum peak value of the base current for linear operation.

Assume  $\beta = 200$ .

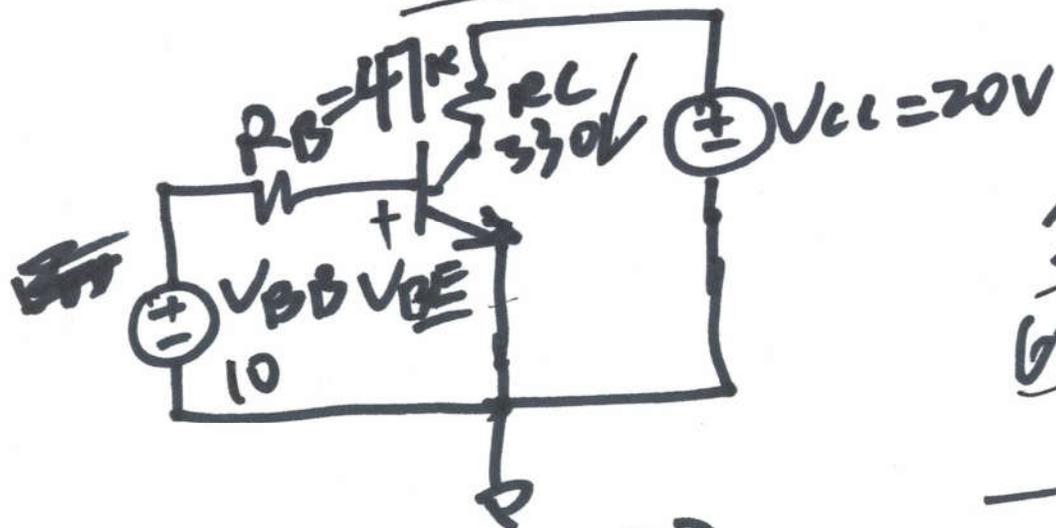


$$I_B = \frac{V_{BB} - 0.7}{R_B}$$

$$I_{CQ} = \beta \cdot I_B = 39.6 \text{ mA}$$

$$I_{C(sat)} = \frac{V_{CC} - 0}{R_C} = \frac{20V}{330} = 60.6 \text{ mA}$$

which is the maximum swing for  $I_C$ .

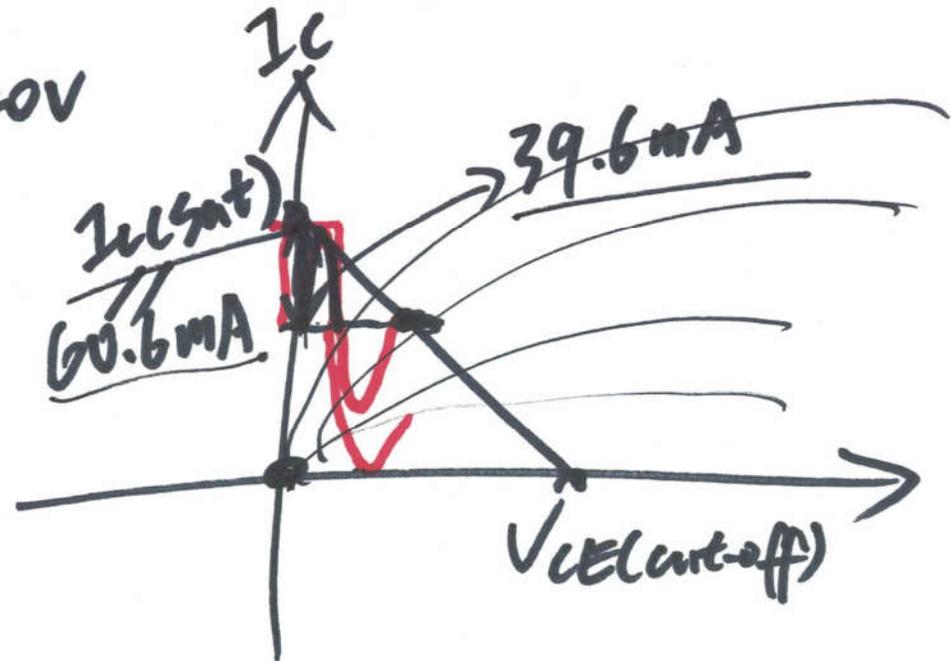


$$I_{C(sat)} - I_{CQ} = 60.6 \text{ mA} - 39.6 \text{ mA} = 21 \text{ mA}$$

Therefore, the peak value of the base current for linear operation is  $\frac{2 \mu\text{A}}{200} = I_B(\text{peak})$   
 $= 105 \mu\text{A}$

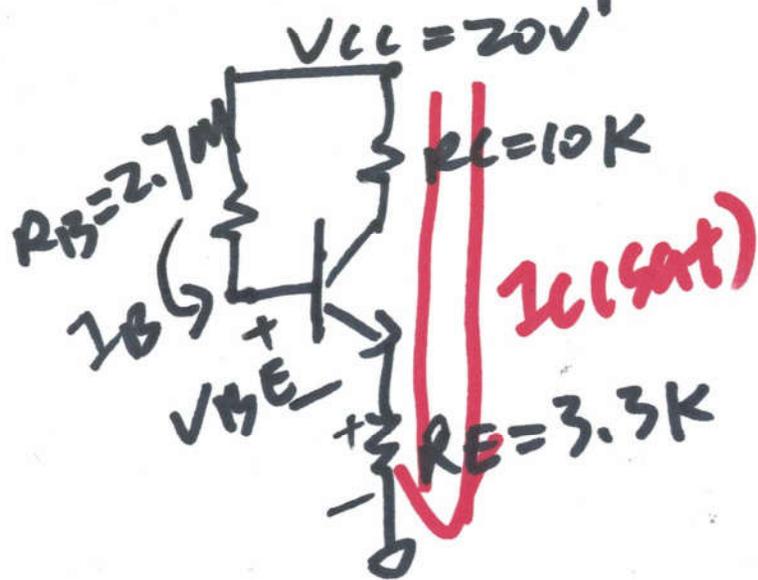Example: Determine the Q point values of  $I_C$ ,  $V_{CE}$ .

Find  $I_C(\text{sat})$ ,  $V_{CE}(\text{cut-off})$ , and construct the DC load line and plot the Q point.  $\beta = 100$ . (Assume  $I_C = I_E$  to find  $I_C(\text{sat})$ )



$$I_B = \frac{V_{CC} - V_{BE} - V_{RE}}{R_B}$$

$$= \frac{20 - 0.7 - V_{RE}}{2.7\text{M}}$$

$$= \frac{20 - 0.7 - (I_E \cdot R_E)}{2.7\text{M}}$$

$$= \frac{20 - 0.7 - ((1 + \beta) I_B \cdot R_E)}{2.7\text{M}}$$

$\Rightarrow I_B = 6.37 \mu\text{A}$

$$I_C = \beta \cdot I_B = 100 \cdot 6.37 \mu\text{A} = \underline{637 \mu\text{A}} = I_{CQ}$$


$$I_E = (\beta + 1) I_B = 101 \cdot 6.37 \mu\text{A} = 643.37 \mu\text{A}$$

$$V_{CE} = V_{CC} - I_C \cdot R_C - I_E \cdot R_E = 11.52 \text{V} = V_{CEQ}$$

when  ~~$V_{CE}$~~   $V_{CE} = 0 \text{V}$ .

$$I_C(\text{sat}) = I_{C\text{max}} = \frac{V_{CC} - 0}{R_C + R_E} = \frac{20 \text{V}}{10 \text{k} + 3.3 \text{k}} = \underline{1.5 \text{mA}}$$

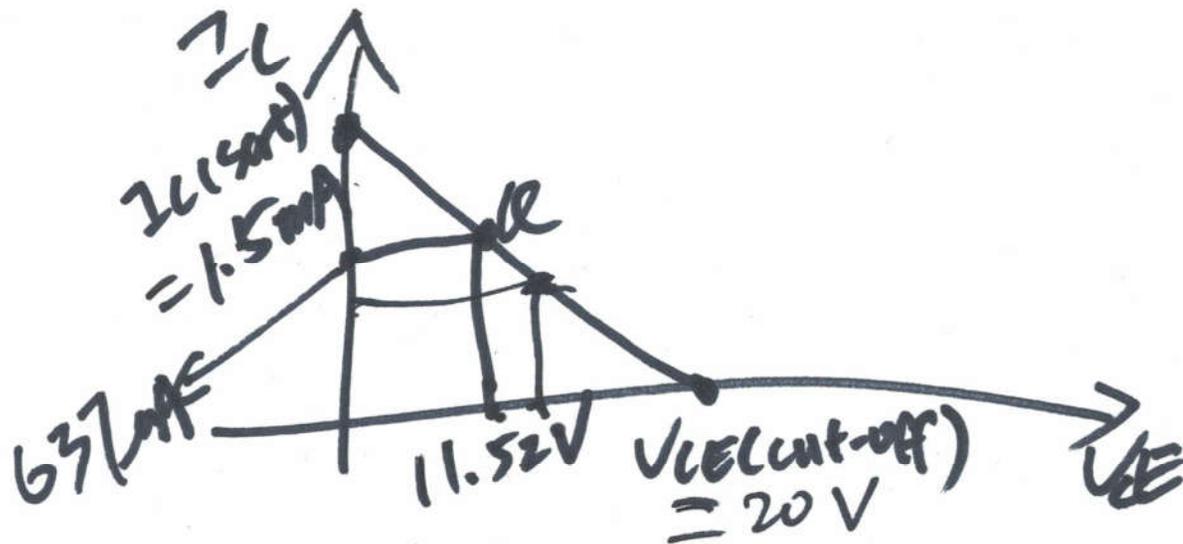
$$V_{CE}(\text{cut-off}) = V_{CC} = 20 \text{V}.$$



⑤

Example: Determine whether the transistor is biased in cut-off, saturation, or linear region.  $\beta = 100$ .

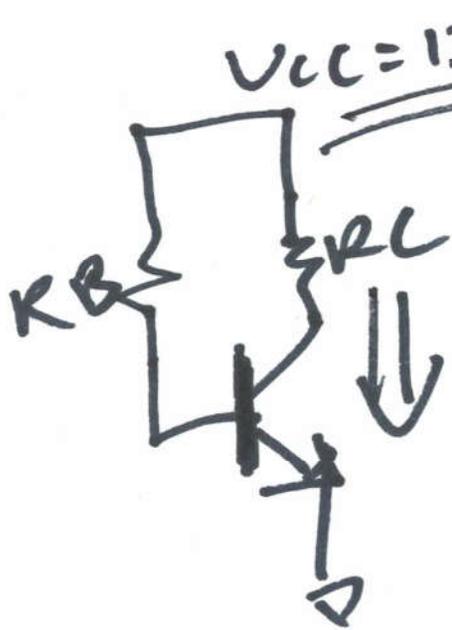(a)  $R_B = 75\text{K}$ ,  $R_C = 1\text{K}$



$$I_{C(sat)} = \frac{V_{CC} - 0}{R_C}$$

$$= \frac{12\text{V}}{1\text{K}}$$

$$= \underline{\underline{12\text{mA}}}$$

$$I_B = \frac{12\text{V} - 0.7\text{V}}{R_B}$$

$$= \frac{11.3\text{V}}{75\text{K}}$$

$$= \underline{\underline{0.15\text{mA}}}$$

$I_C = \beta \cdot I_B = 15\text{mA} > I_{C(sat)}$   
 so, it operates in the saturation region.

(b)


# Static Logic Gates

PMOSes pull out to the power supply

NMOSes - - - - - GND

## NAND

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

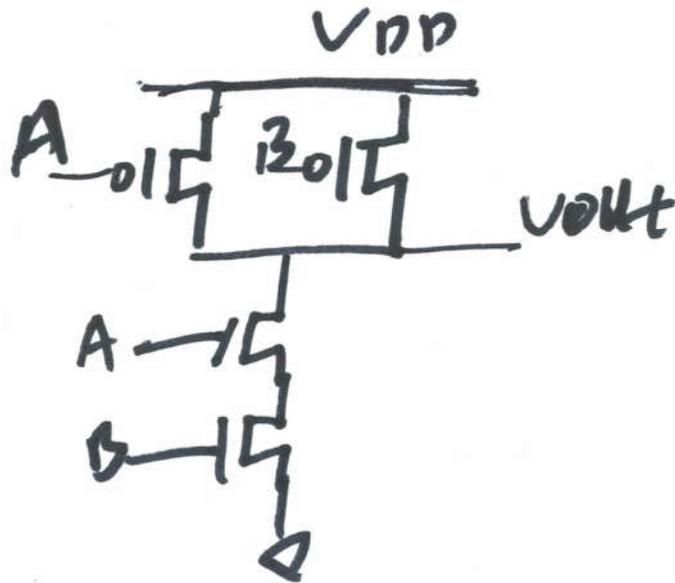

# stick Diagrams

