

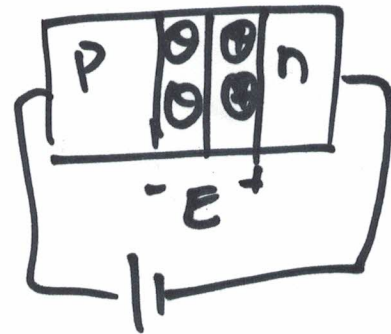
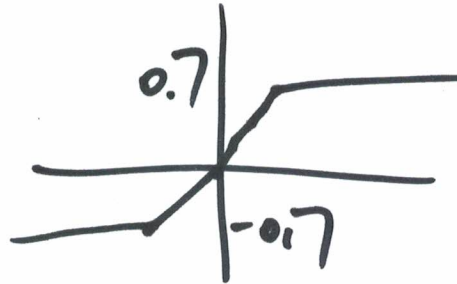
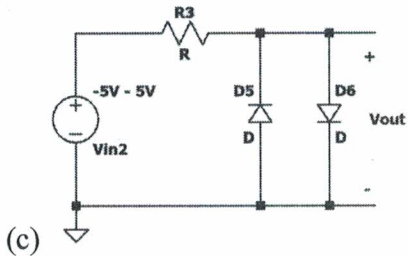
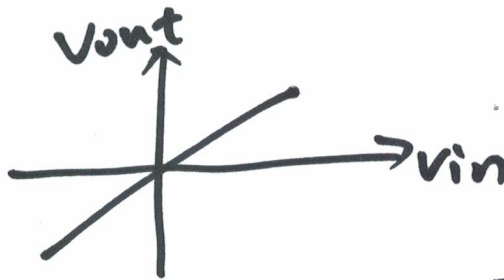
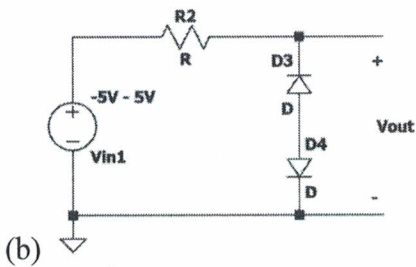


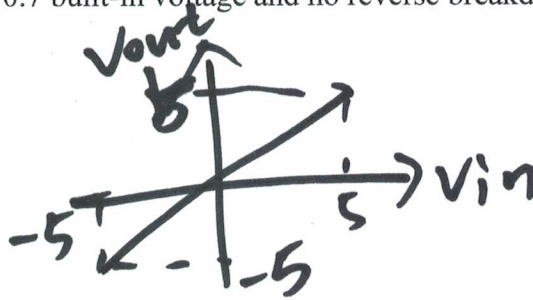


ENGR338 Quiz 3

DC sweep

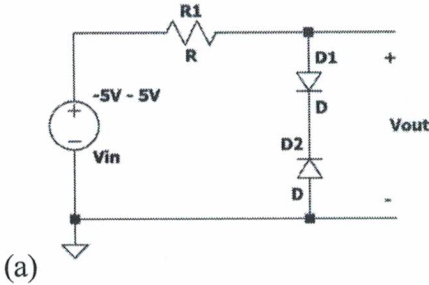1. Draw the V_{in} versus V_{out} curves for the following circuits when V_{in} is swept from $-5V$ to $5V$. (The diodes are real diodes with a $0.7V$ built-in voltage and no reverse breakdown). (60 points)



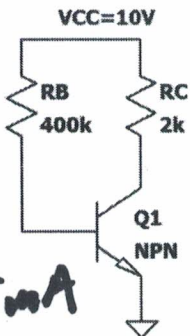2. Determine the Q point values and draw the DC load line of the following circuit. (assume $V_{CC}=10V$, $R_B=400k$, $R_C=2k$, $\beta=100$, $V_{BE}=0.7V$) (20 points)





$$I_B = I_{BQ} = \frac{V_{CC} - 0.7}{R_B} = \frac{10 - 0.7}{400k} = 23.25 \mu A$$

$$I_{CQ} = \beta \cdot I_{BQ} = 100 \cdot 23.25 \mu A = 2.325 mA$$


$$V_{CEQ} = V_{CC} - I_{CQ} \cdot R_C = 10 - 2k \cdot 2.325 mA = 5.35 V$$

$$I_{C_{max}} = \frac{V_{CC}}{R_C} = 5 mA$$

self-biased

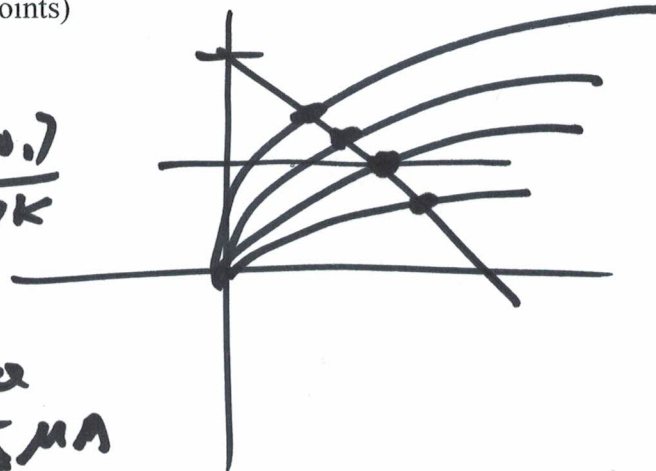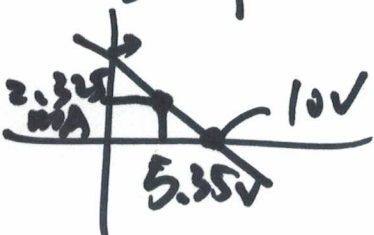

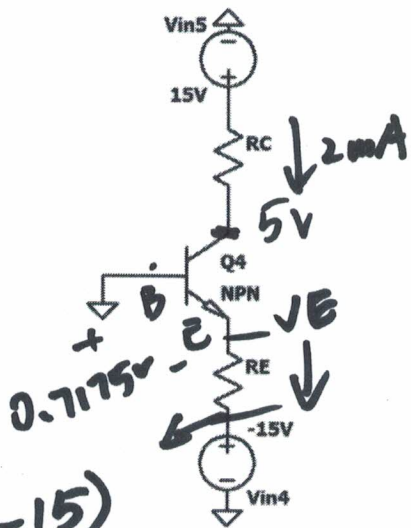3. $\beta=100$, $V_{BE}=0.7V$ at $I_C=1\text{ mA}$. Design the circuit (find appropriate R_C and R_E) so that when $I_C=2\text{ mA}$, $V_C=5V$ ($V_T=25\text{ mV}$ at room temperature). (20 points)



$$R_C = \frac{15 - 5}{2\text{ mA}} = 5\text{ k}\Omega$$

$$I_C = I_S \cdot e^{V_{BE}/V_T}$$

$$\begin{cases} 1\text{ mA} = I_S \cdot e^{0.7/V_T} \\ 2\text{ mA} = I_S \cdot e^{V_{BE}/V_T} \end{cases}$$

$$\begin{cases} I_E = (1 + \beta) I_B \\ I_B = \frac{I_C}{\beta} \end{cases}$$

$$V_E - (-15) = V_{RE}$$

$$\frac{1}{2} = e^{(0.7 - V_{BE})/V_T}$$

$$I_E = \frac{2\text{ mA}}{100} \cdot (1 + \beta)$$

$$\frac{V_{RE}}{I_E} = R_E$$

$$= \frac{-0.7175 - (-15)}{2.02\text{ mA}}$$

$$\ln 0.5 = (0.7 - V_{BE})/V_T$$

$$= \frac{2\text{ mA}}{100} \cdot 101$$

$$-0.7 = (0.7 - V_{BE})/25\text{ mV}$$

$$= 2.02\text{ mA}$$


$$= 7.07\text{ k}\Omega$$

$$-17.5\text{ mV} = 0.7 - V_{BE}$$



$$V_{BE} = 0.7 + 17.5 \times 10^{-3}$$

$$= 0.7 + 0.0175$$

$$= 0.7175\text{ V}$$

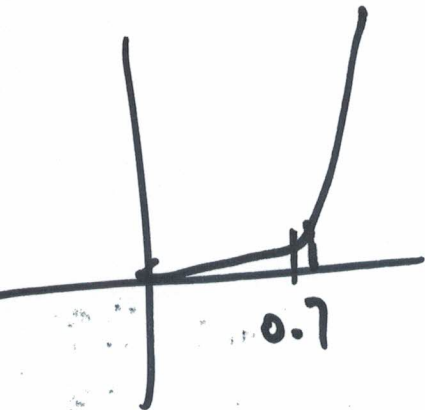

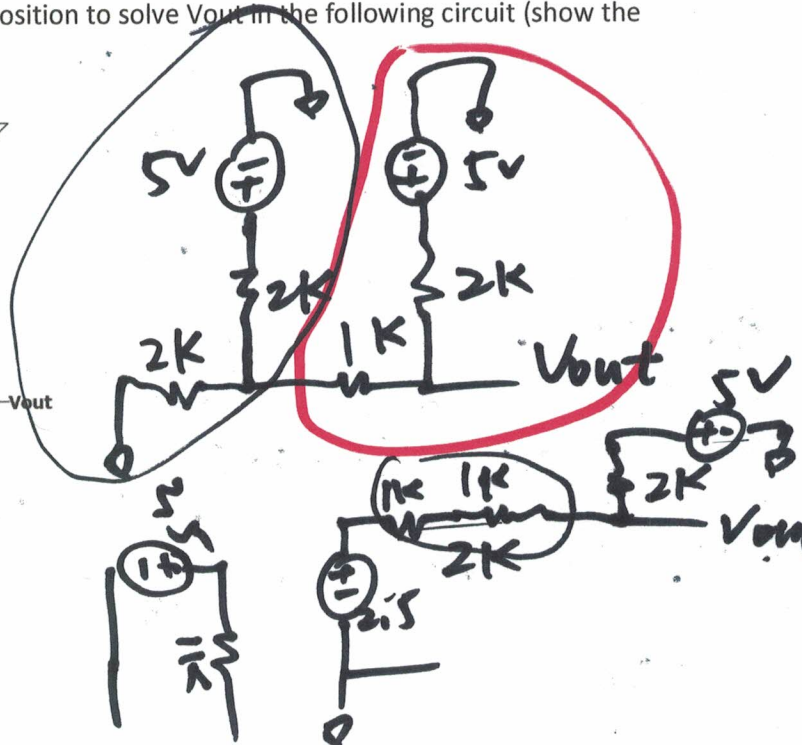
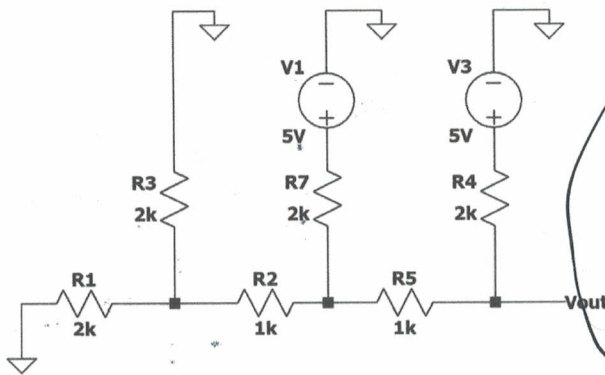
1. Use Thevenin's equivalent theory and superposition to solve V_{out} in the following circuit (show the calculation process for credits). (10 points)







$$V_{out} = 2.5 + 1.25 = 3.75 \text{ V.}$$

2. For a 4-bit SAR ADC, V_{REF} for the DAC is 10 V, V_{in} at a moment is 6.2V. Show all the states of the ADC's output in a state diagram. Show both the analog voltage and the digital voltage for each state. (20 points)


$$\# \text{ States} = N + 1 = 5$$

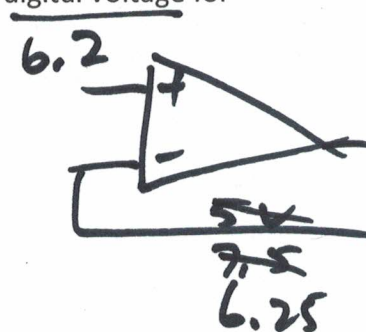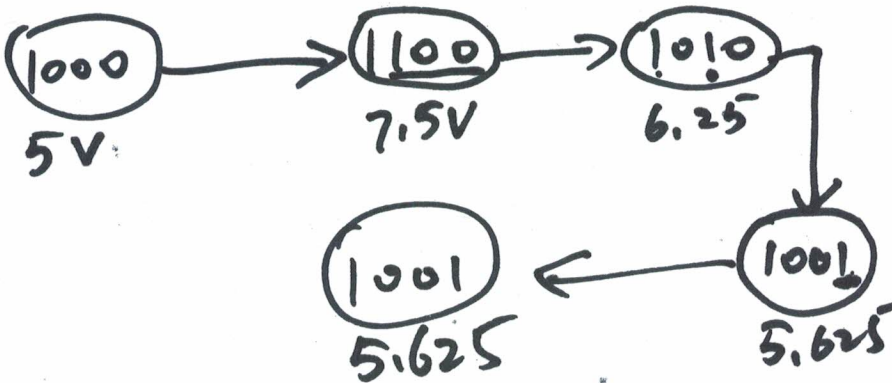

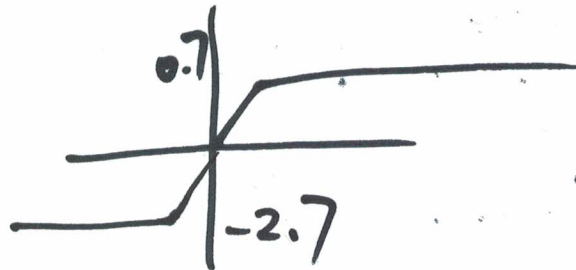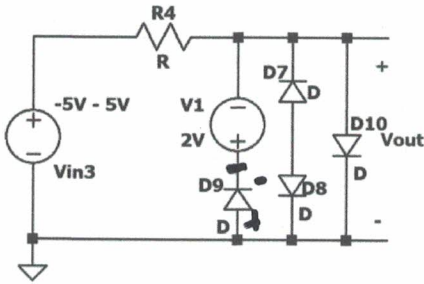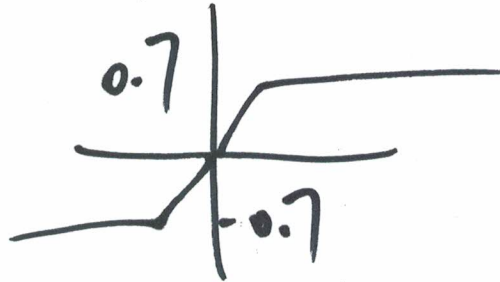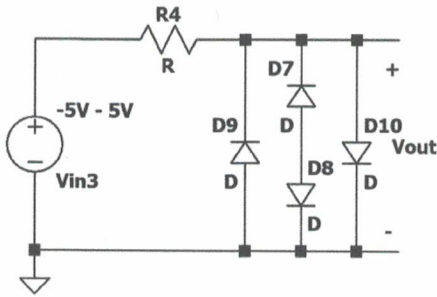3. Draw the $V_{in} - V_{out}$ curves for the following circuits when V_{in} is swept from -5V to 5V. (The diodes are real diodes with a 0.7 built-in voltage and no reverse breakdown). (20 points)



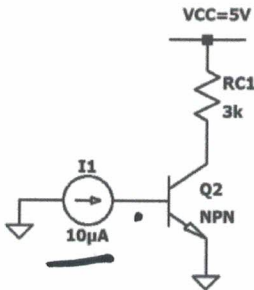4. For the following NPN BJT, $I_s = 10^{-15} \text{A}$, $\beta = 100$. (1) Find V_{BE} and V_{CE} . (2) Replace the $10 \mu\text{A}$ current source with a resistor and a 5V voltage source, what resistance is required to result in the same operation? (20 points)




$$\textcircled{1} I_B = 10 \mu\text{A} \Rightarrow I_C = 100 \cdot I_B = 1 \text{mA}$$

$$V_{CE} = V_{CC} - V_{RC} = 5 \text{V} - 1 \text{mA} \cdot 3 \text{k} = 2 \text{V}$$

$$I_C = I_s e^{V_{BE}/V_T} \Rightarrow V_{BE} = V_T \cdot \ln \frac{I_C}{I_s} =$$

$$\textcircled{2} \begin{matrix} 5 \text{V} \\ \downarrow \\ \text{---} 0.7 \text{V} \\ \downarrow \\ 10 \mu\text{A} \end{matrix} \quad R_B = \frac{5 \text{V} - 0.7 \text{V}}{10 \mu\text{A}} = 430 \text{k}\Omega$$

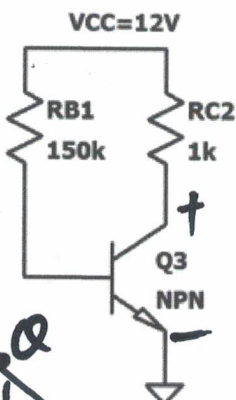5. Is the following NPN BJT operated in linear, saturation, or cutoff region? Determine the Q point and draw the load line. (20 points) ($\beta = 100$)




Assume it is operated in the linear region

$$I_B = \frac{12 - 0.7}{150 \text{k}} = 75.3 \mu\text{A}$$

$$I_C = \beta \cdot I_B = 1.53 \text{mA}$$

$$V_{CE} = V_{CC} - V_{RC} = 12 \text{V} - 7.53 \text{V} = 4.47 \text{V}$$

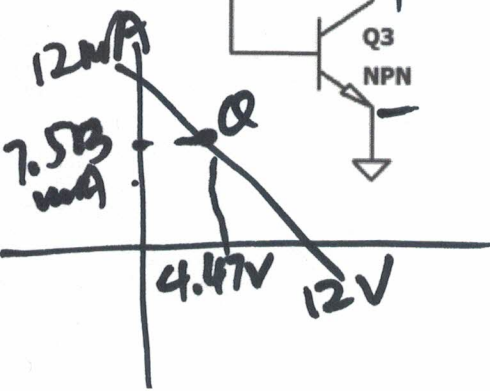So it is in linear region. $\approx V_{BE}$



6. Explain the following concepts. Draw diagrams to help with interpreting the concepts if necessary. (10 points)

a. NMOS Channel Length Modulation (CLM)

b. CMOS Latch-Up

c. NMOS Body Effect

d. Formation of the depletion region of a pn junction

e. I_S and I_D for a forward biased pn junction. Which current is larger? Why?

f. Why the N-Well sheet resistance is a constant?

g. What are n_i , n_n , n_p , p_n , p_p , N_A , and N_D ?