

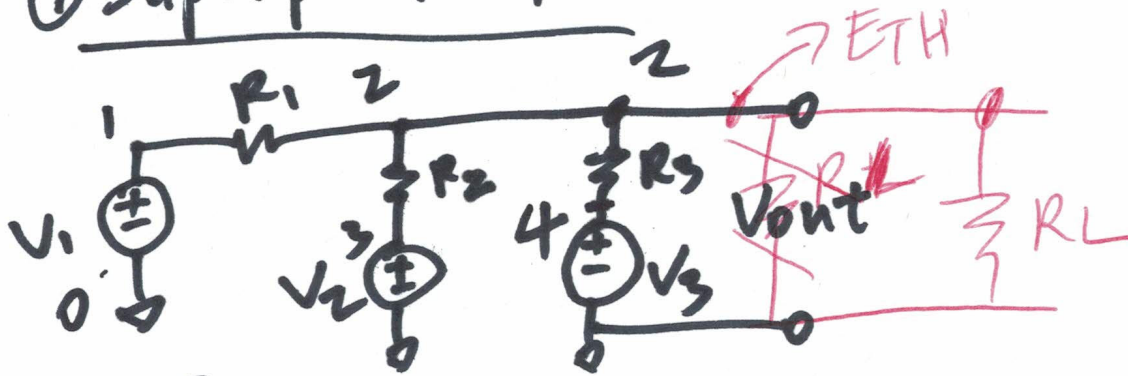


① Superposition

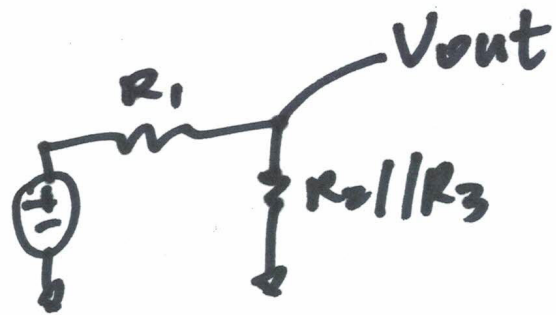


Vout?

V1 only:

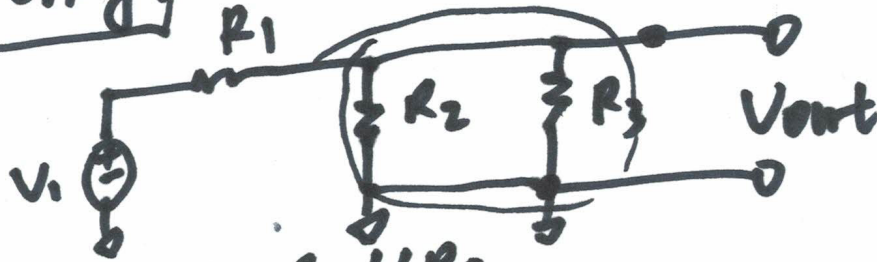


$$V_{out_1} = V_1 \cdot \frac{R_2 // R_3}{R_1 + R_2 // R_3}$$


V2 only:

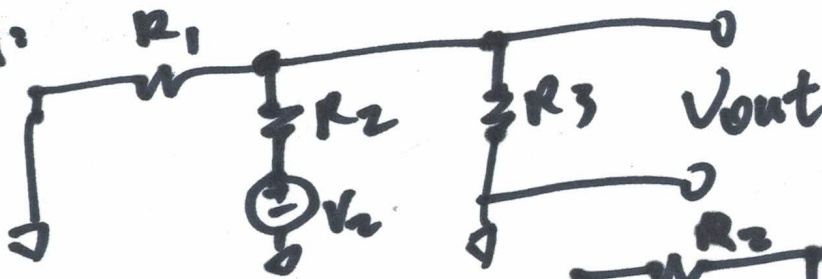
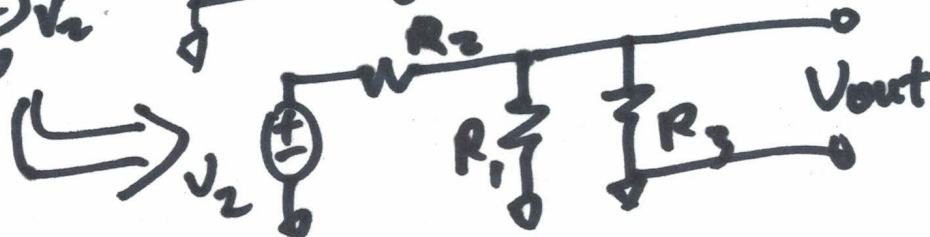
$$V_{out_2} = V_2 \cdot \frac{R_1 // R_3}{R_2 + R_1 // R_3}$$



V_3 only:

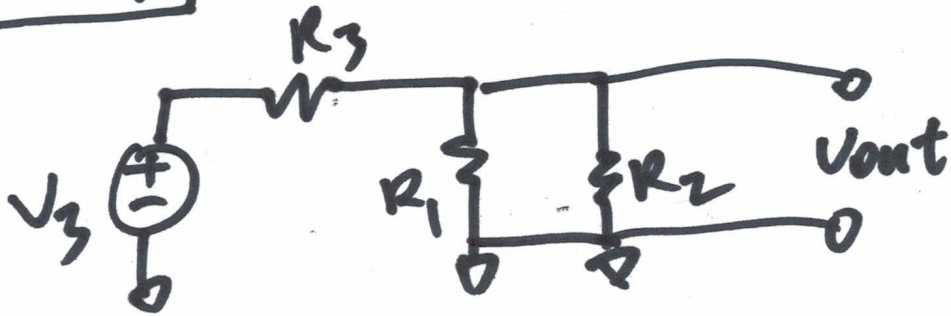

$$\underline{\underline{R_2 || R_3 = \frac{R_2 \cdot R_3}{R_2 + R_3}}}$$

$$V_{out3} = V_3 \cdot \frac{R_1 || R_2}{R_3 + R_1 || R_2}$$

$$V_{out} = V_{out1} + V_{out2} + V_{out3}$$

$$= V_1 \cdot \frac{R_2 || R_3}{R_1 + R_2 || R_3} + V_2 \cdot \frac{R_1 || R_3}{R_2 + R_1 || R_3} + V_3 \cdot \frac{R_1 || R_2}{R_3 + R_1 || R_2}$$

△ Example: $R_1 = 2K$, $R_2 = 4K$, $R_3 = 6K$, $V_1 = 2V$, $V_2 = 4V$, $V_3 = 6V$

$$\textcircled{V_{out}} = 2 \cdot \frac{2.4K \cdot K}{4.4K} + 4 \cdot \frac{1.5K \cdot K}{5.5K} + 6 \cdot \frac{1.3K \cdot K}{7.3K}$$
$$= 1.1 + 1.1 + 1.07 = 3.27V$$

LTSpice Code:

V₁ 1 0 2

R₁ 1 2 2K

R₂ 2 3 4K

V₂ 3 0 4

R₃ 2 4 6K



V₃ 4 0 6

.tran 1


↑
Run it in LTSpice

③

② Thevenin's Equivalent Circuit

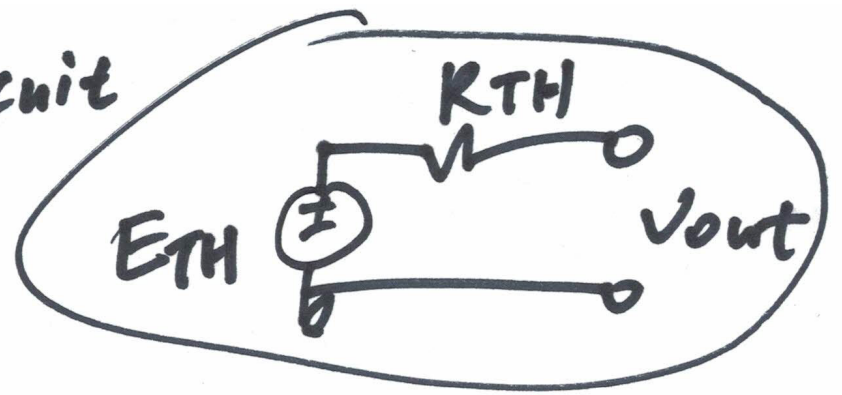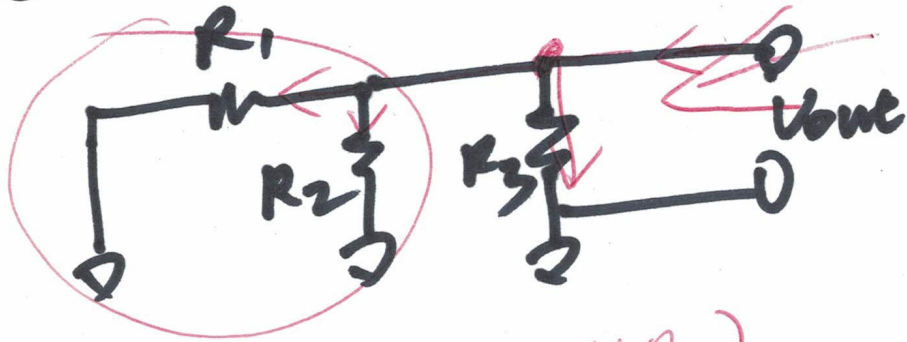
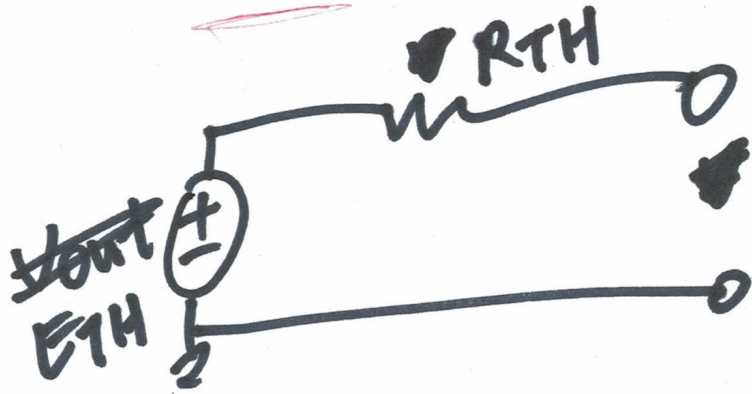
$$R_{TH} = R_3 \parallel (R_1 \parallel R_2)$$



③ PULSE ()

(Low voltage | High voltage delay Rising-time Falling-time On time Period)