
 
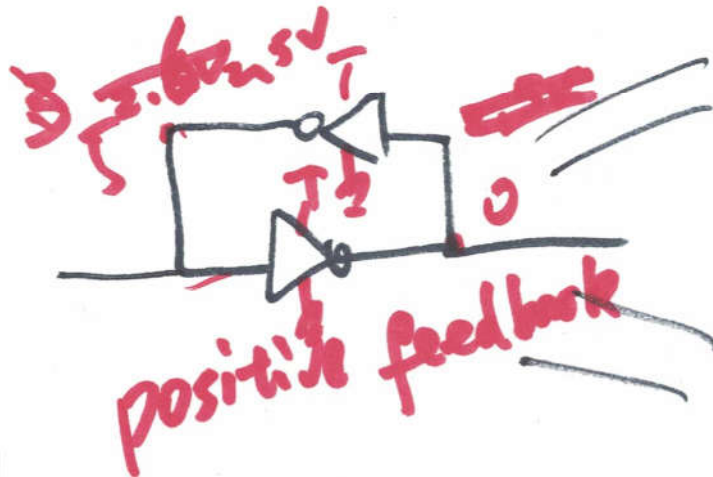
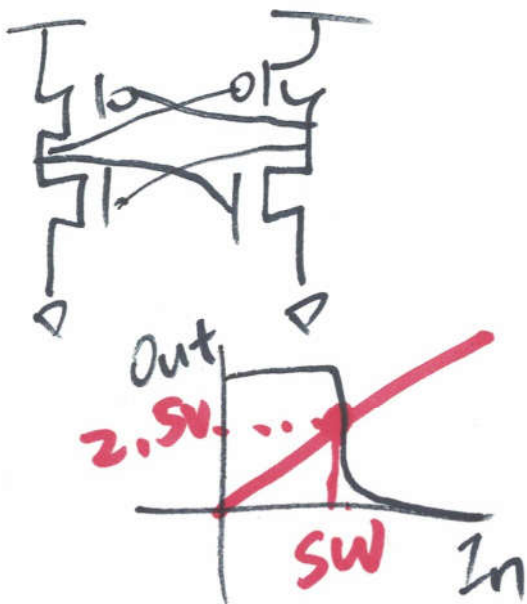




clocked circuit

① A level sensitive latch (level-triggered FF)



Figure 13.21 P386

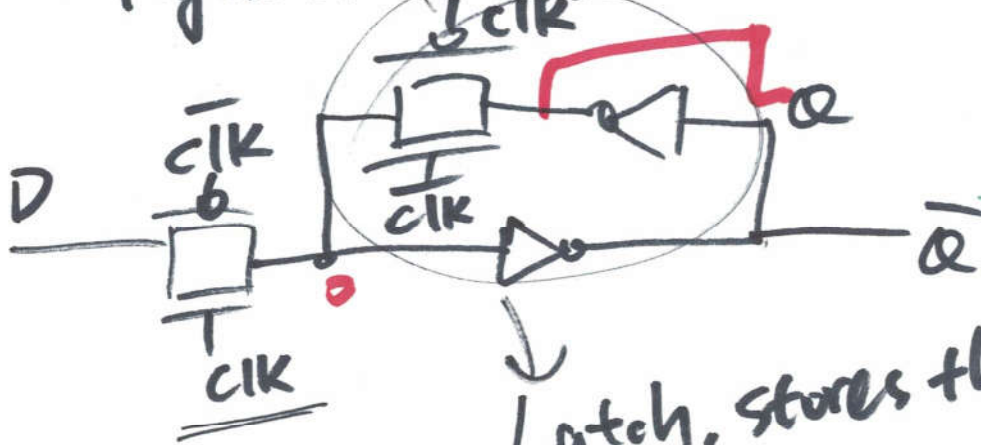

② An edge triggered OFF

 
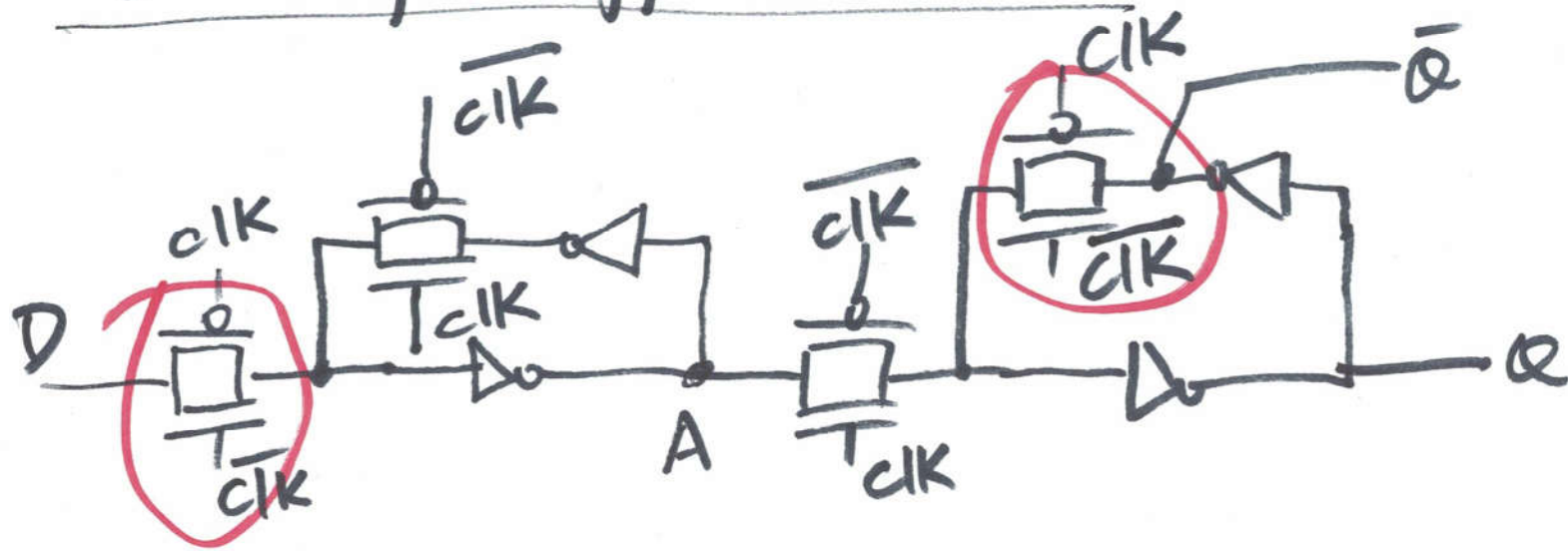


② RC Digital Model for TGs

  

Comp. with

P394.

 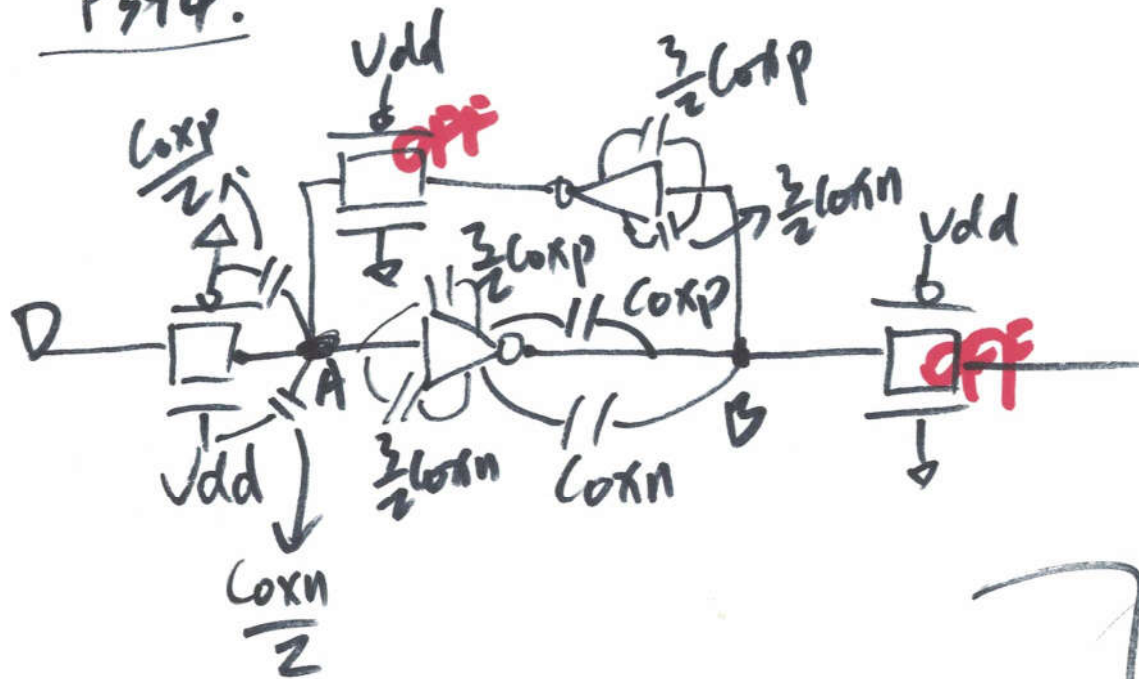

Estimate the Delay from D to A, and B

NMOS: $R_n = 3.4K$, $C_{oxn} = 0.625f$

PMOS: $R_p = 3.4K$, $C_{oxp} = 1.25f$



$$C_A = \frac{C_{oxn}}{2} + \frac{C_{oxp}}{2} + \frac{3}{2} (C_{oxn} + C_{oxp}) = 2 (C_{oxn} + C_{oxp})$$

$$= 2 (1.875f) = 3.75fF$$

$$C_B = C_{oxnt} + C_{oxp} + \frac{3}{2} (C_{oxnt} + C_{oxp})$$

$$= \frac{5}{2} (C_{oxnt} + C_{oxp}) = 4.7 \text{ fF}$$

Delay from D to A: (always look at the output)

$$t_{pHL} = t_{pLH} = 0.7 (R_n || R_p) \cdot C_A$$

$$= 4.5 \text{ ps}$$

P 10^{-12}
f 10^{-15}

Delay from A to B:

$$t_{pLH B} = 0.7 \cdot R_p \cdot C_B = 0.7 \cdot 3.4 \text{ K} \cdot 4.7 \text{ fF}$$

$$= 11.2 \text{ ps}$$

$$t_{pHL B} = 0.7 \cdot R_n \cdot C_B = 0.7 \cdot 3.4 \text{ K} \cdot 4.7 \text{ fF}$$

$$= 11.2 \text{ ps}$$

5

The Propagation delay from D to B is:

$$t_{PHL} = 4.5 \text{ ps} + 11.2 \text{ ps} = 15.7 \text{ ps}$$

$$\underline{t_{PLH}} = 4.5 \text{ ps} + 11.2 \text{ ps} = 15.7 \text{ ps}$$

6

Memory Circuits

	<u>SRAM</u>	DRAM	SDRAM	ROM	Flash
--	-------------	------	-------	-----	-------

volatile

x

x

x

RAM: Random Access Memory

DRAM: Dynamic RAM

SRAM: Static RAM

SDRAM: Synchronous DRAM

SRAM

less power

faster

insensitive
to noise

used inside
the CPU chip
for cache

20-40ns

6-transistor
circuit

DRAM

—

—

—

off-chip
(card)

60-100ns

transistor
capacitor

Double Data Rate SDRAM
↑

DDR → 2000

DDR2 → 2003

DDR3 → 2007

DDR4 → 2014

DDR5 → 2020

16 GB DDR4 SDRAM
\$60.

Main players make
SDRAMs:

Micron, Samsung, Hynix

↑
Boise, ID