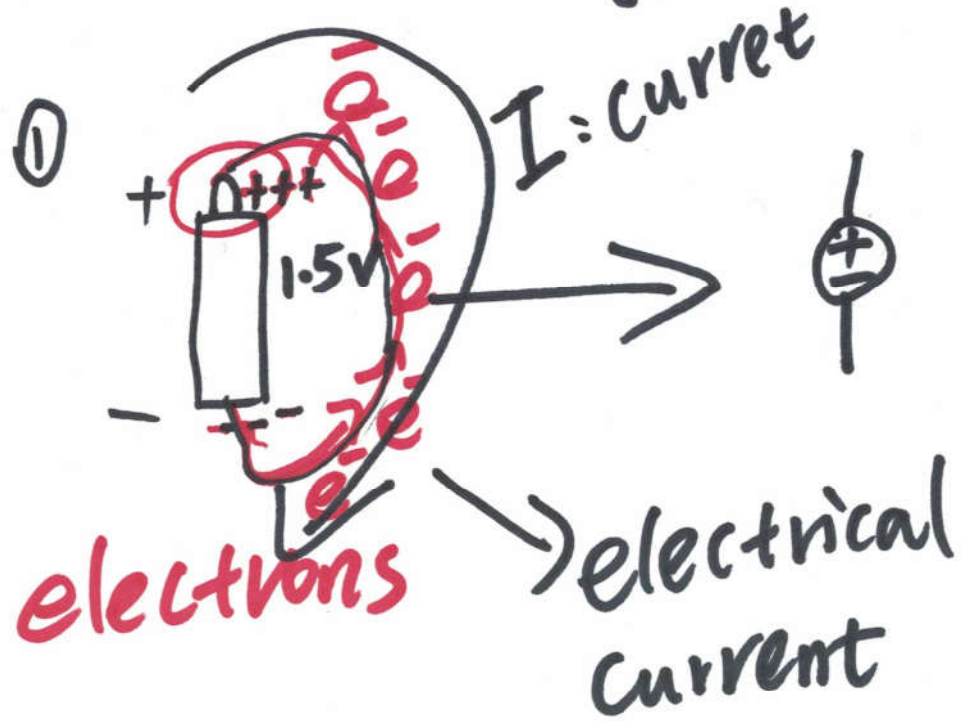


Voltages and Currents




②

H^+

charge voltages Current
voltage

③


② Voltages are relative

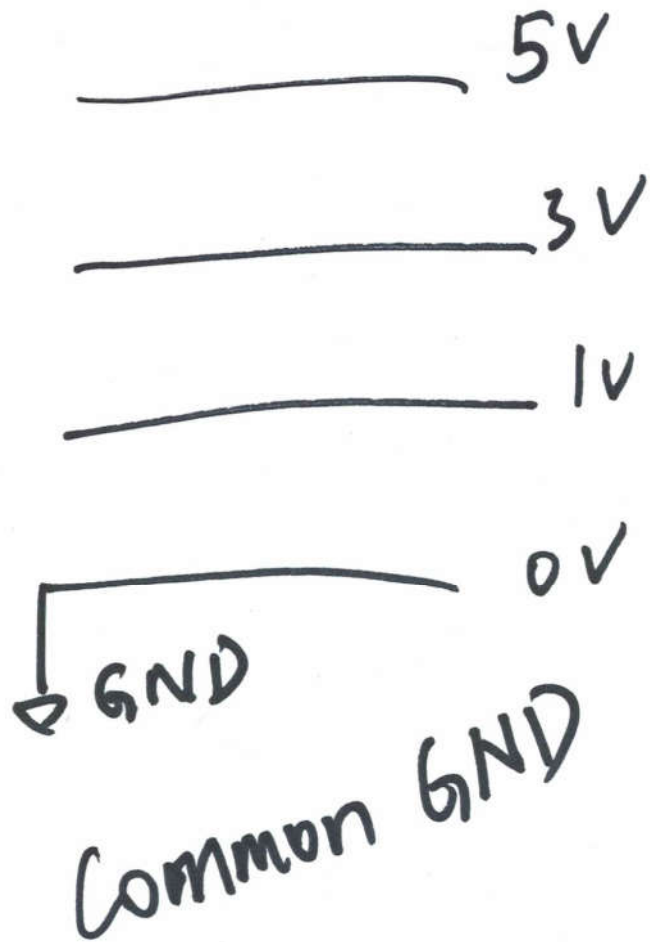

Voltage difference
potential drop

②

③ Ohm's Law

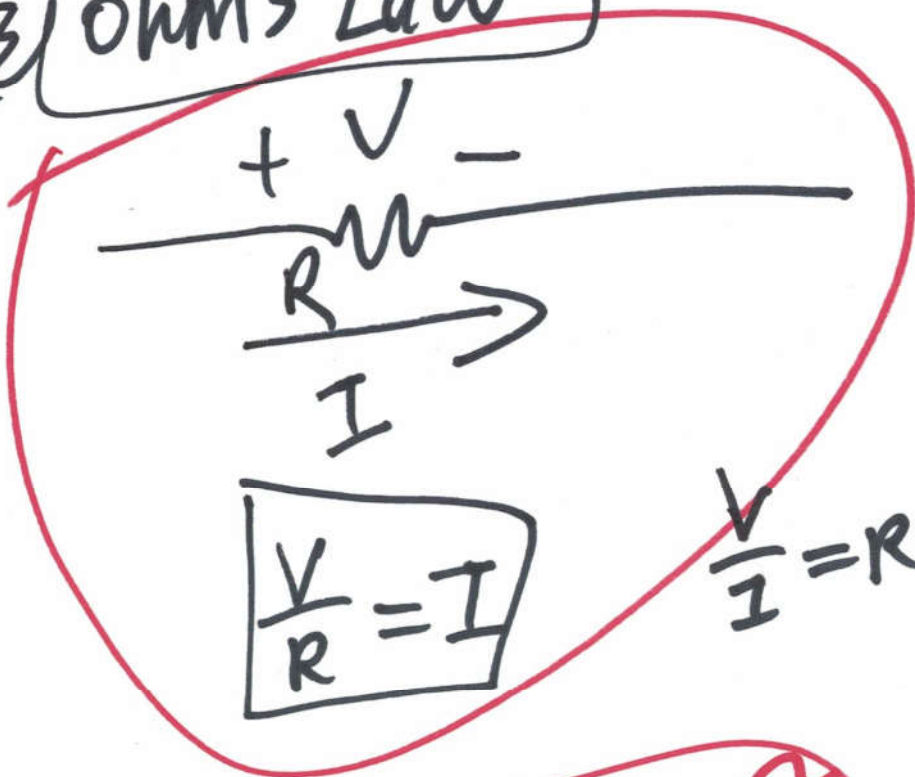


$$\frac{V}{R} = I$$

$$\frac{V}{I} = R$$

$$\frac{I \cdot R = V}{\downarrow}$$


$$I \cdot 0 = 0$$

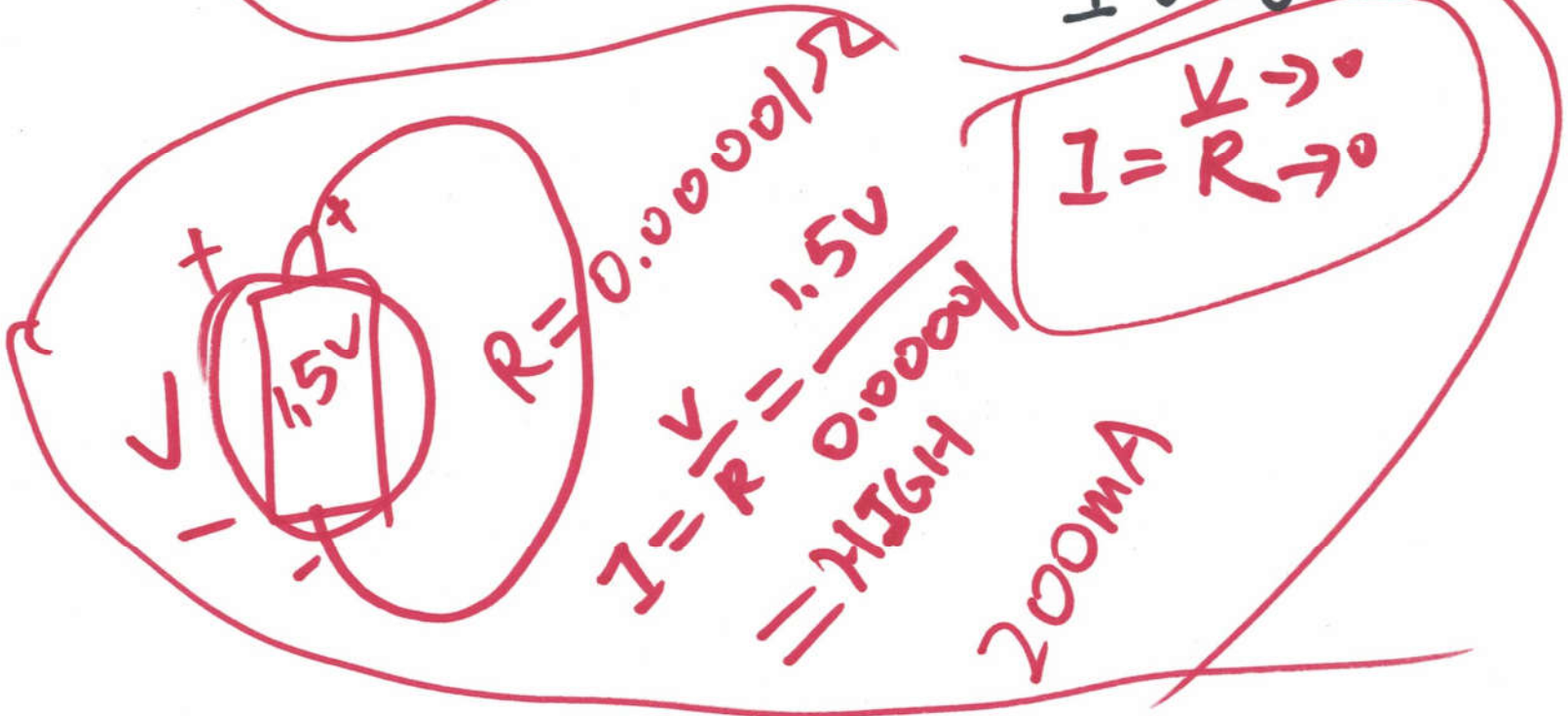


$$I = \frac{V}{R} \rightarrow 0$$

③


④ Polarities

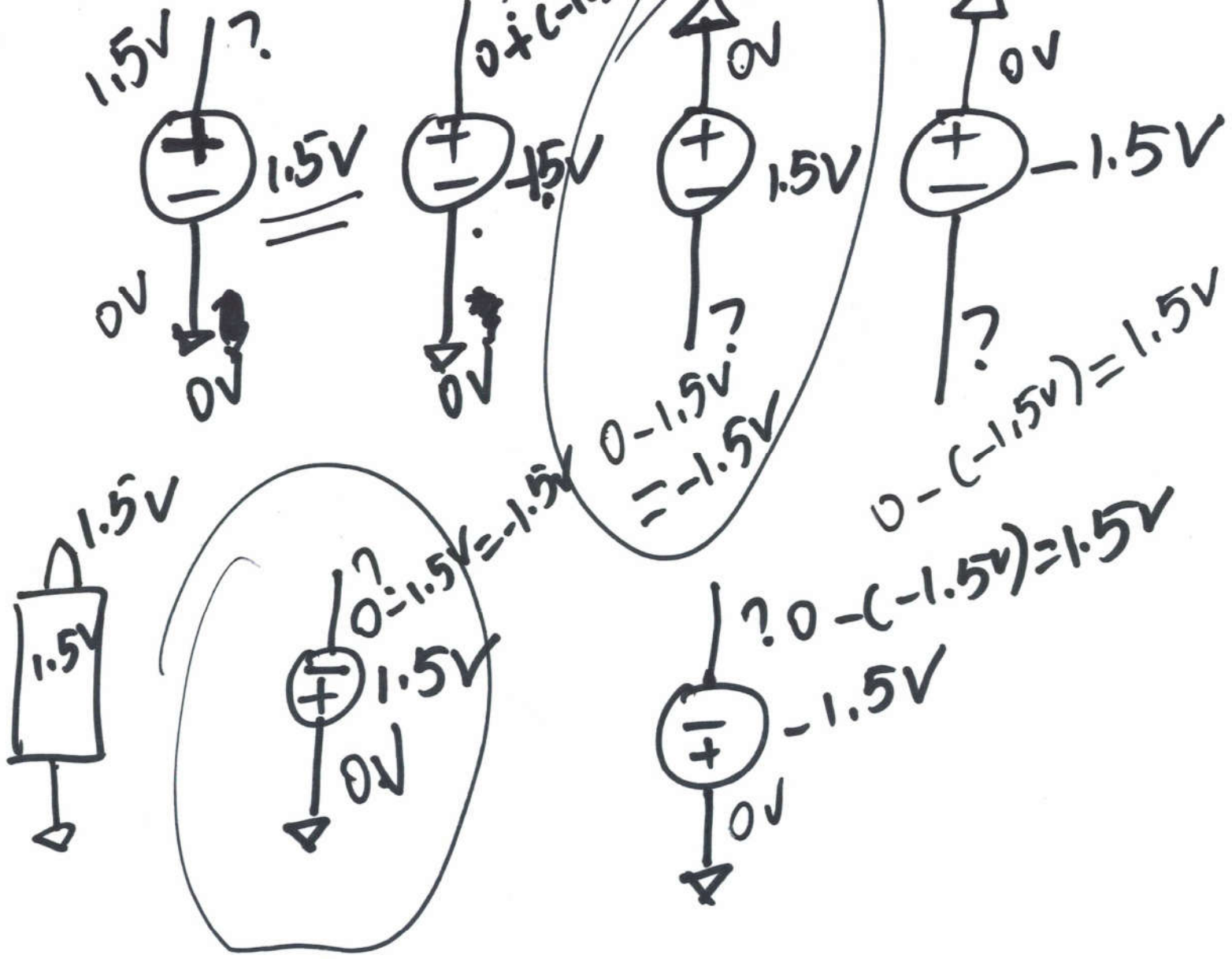

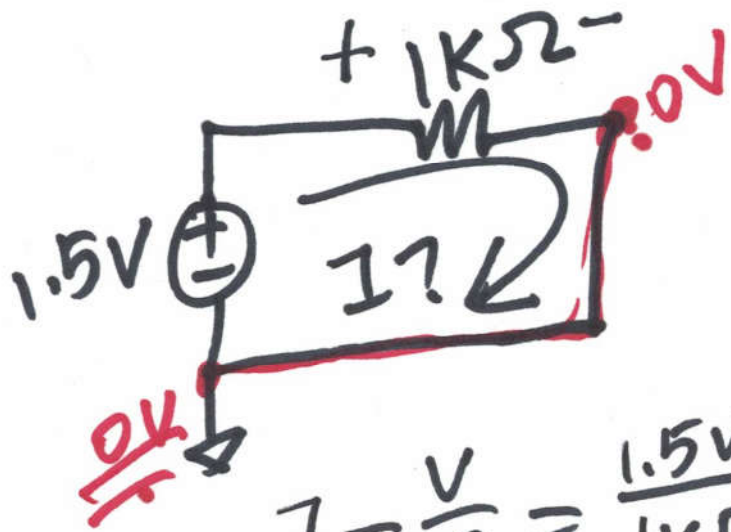


$$\begin{aligned} R \cdot I &= 0 \\ 0 \cdot I &= 0 \end{aligned}$$

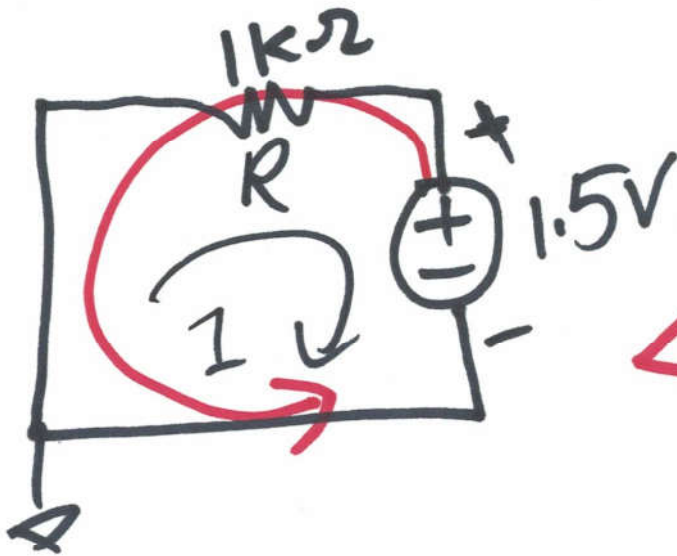
$$I = \frac{V}{R} = \frac{1.5V}{1k\Omega} = 1.5mA = 1.5 \times 10^{-3} A$$





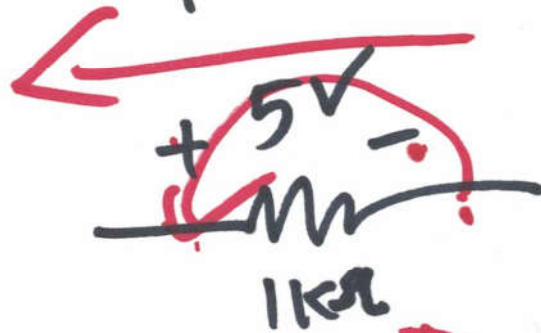
I can define the current flow in any direction


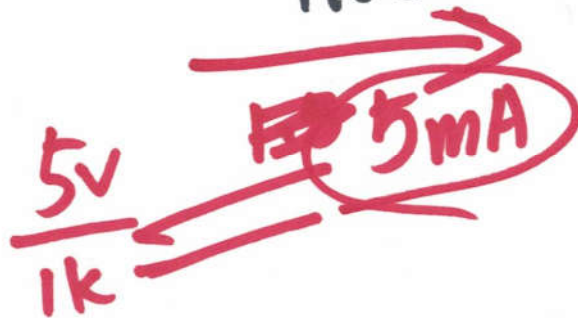
$$\begin{aligned} \frac{-5V}{R} &= \frac{-5V}{1k} \\ &= -5mA \end{aligned}$$



5

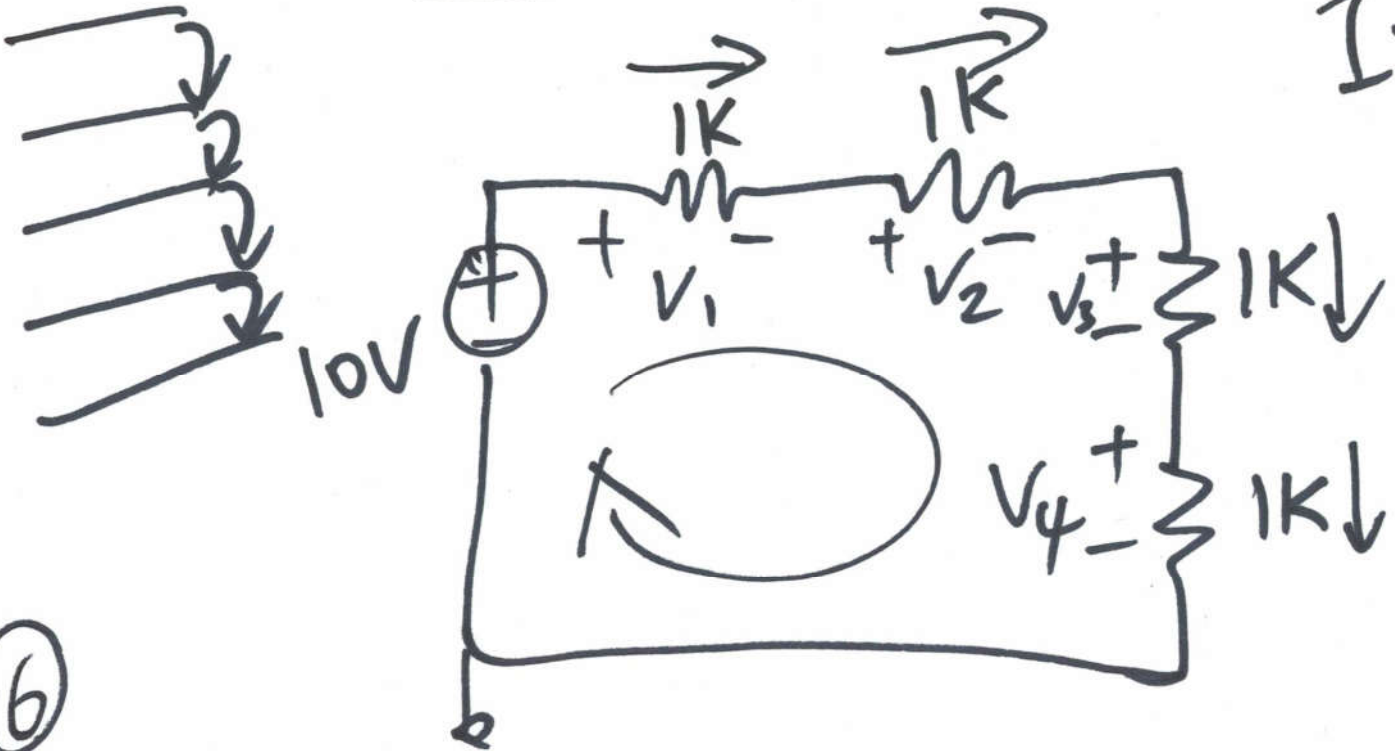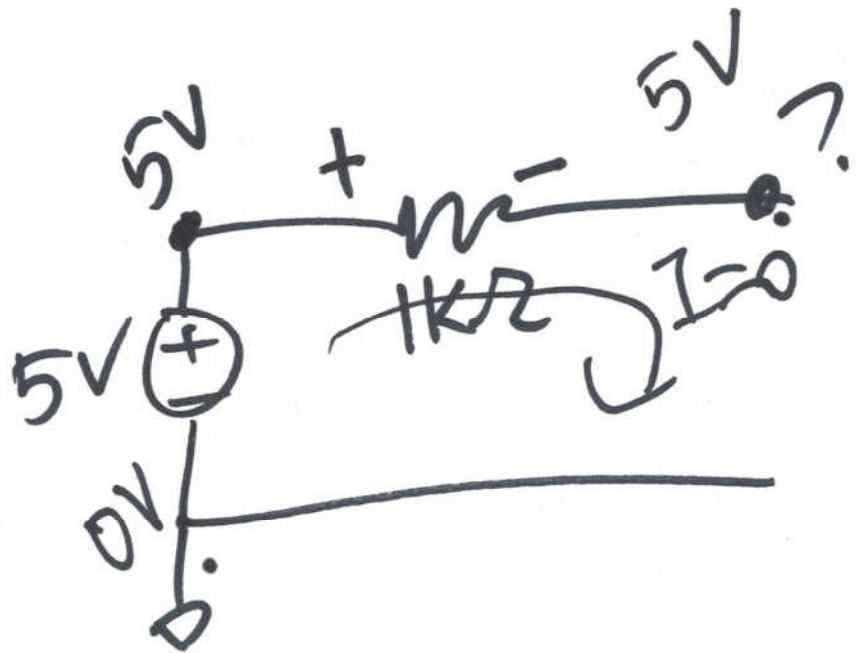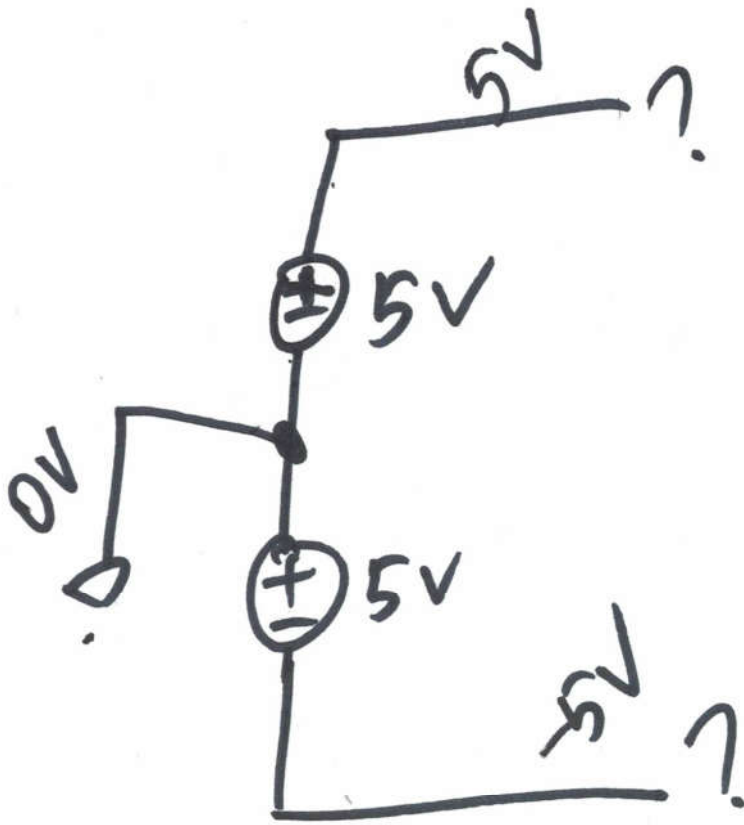


$$I = \frac{10V}{4K} = 2.5 \text{ mA}$$

$$V_1 = 2.5 \text{ mA} \cdot 1K = 2.5V$$

(6)

Voltage ~~Div~~ Dividers:

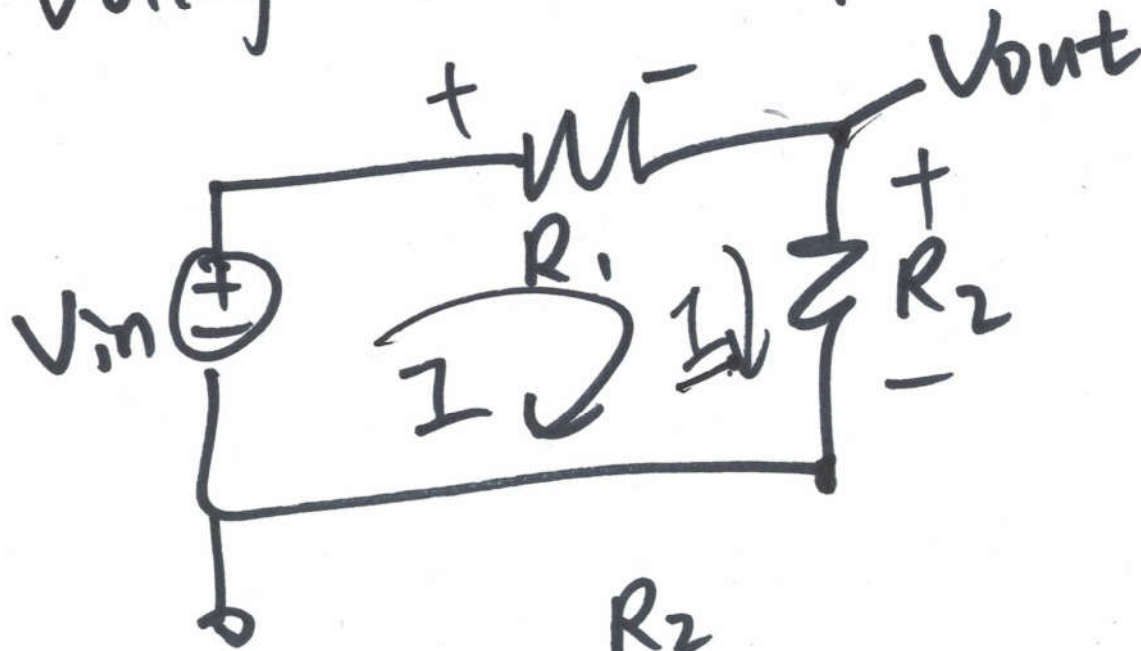

$$V_{out} = V_{in} \frac{R_2}{R_1 + R_2}$$

$$\begin{cases} V_{in} = I \cdot (R_1 + R_2) \\ V_{out} = I \cdot R_2 \end{cases}$$

$$\begin{aligned} \frac{V_{out}}{V_{in}} &= \frac{I \cdot R_2}{I \cdot (R_1 + R_2)} \\ &= \frac{R_2}{R_1 + R_2} \end{aligned}$$

$$\Rightarrow V_{out} = V_{in} \cdot \frac{R_2}{R_1 + R_2}$$

①