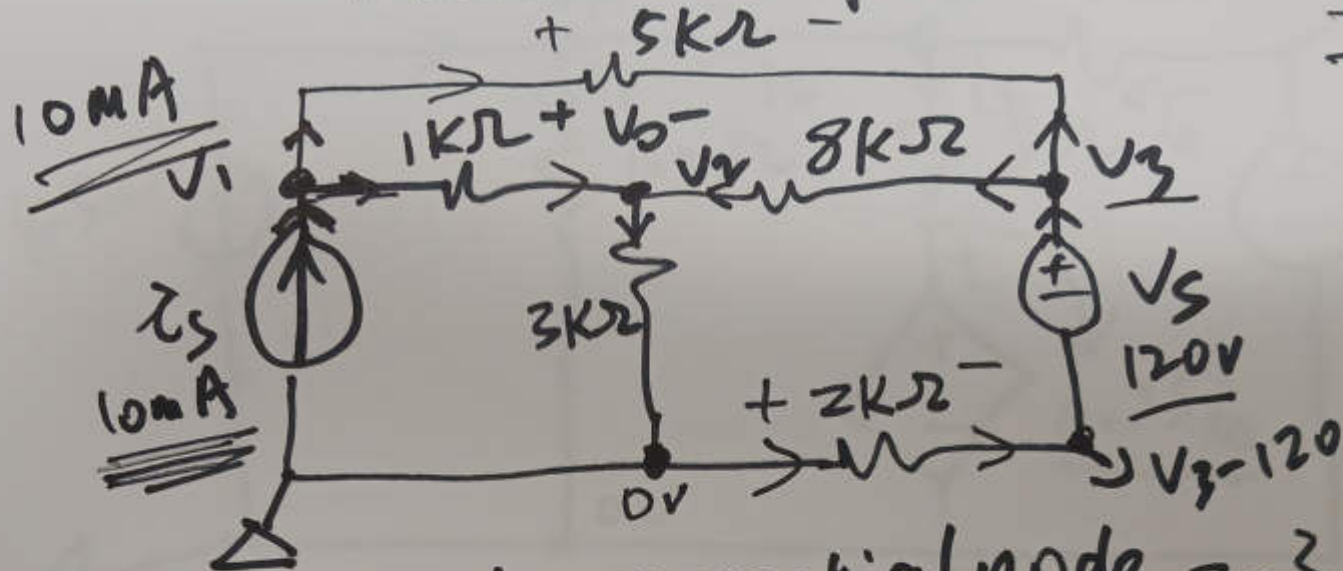


# Node Voltage Method (KCL)



node essential node  $\Rightarrow$  3 branches


$\hookrightarrow$  2 branches

$$i_s = 10\text{mA} = \frac{V_1 - V_3}{5\text{K}} + \frac{V_1 - V_2}{1\text{K}}$$

$$\frac{V_1 - V_2}{1\text{K}} + \frac{V_3 - V_2}{8\text{K}} = \frac{V_2}{3\text{K}}$$

$$0 - (V_3 - 120) = \frac{V_3 - V_2}{8\text{K}} + \frac{V_3 - V_1}{5\text{K}}$$

(1)

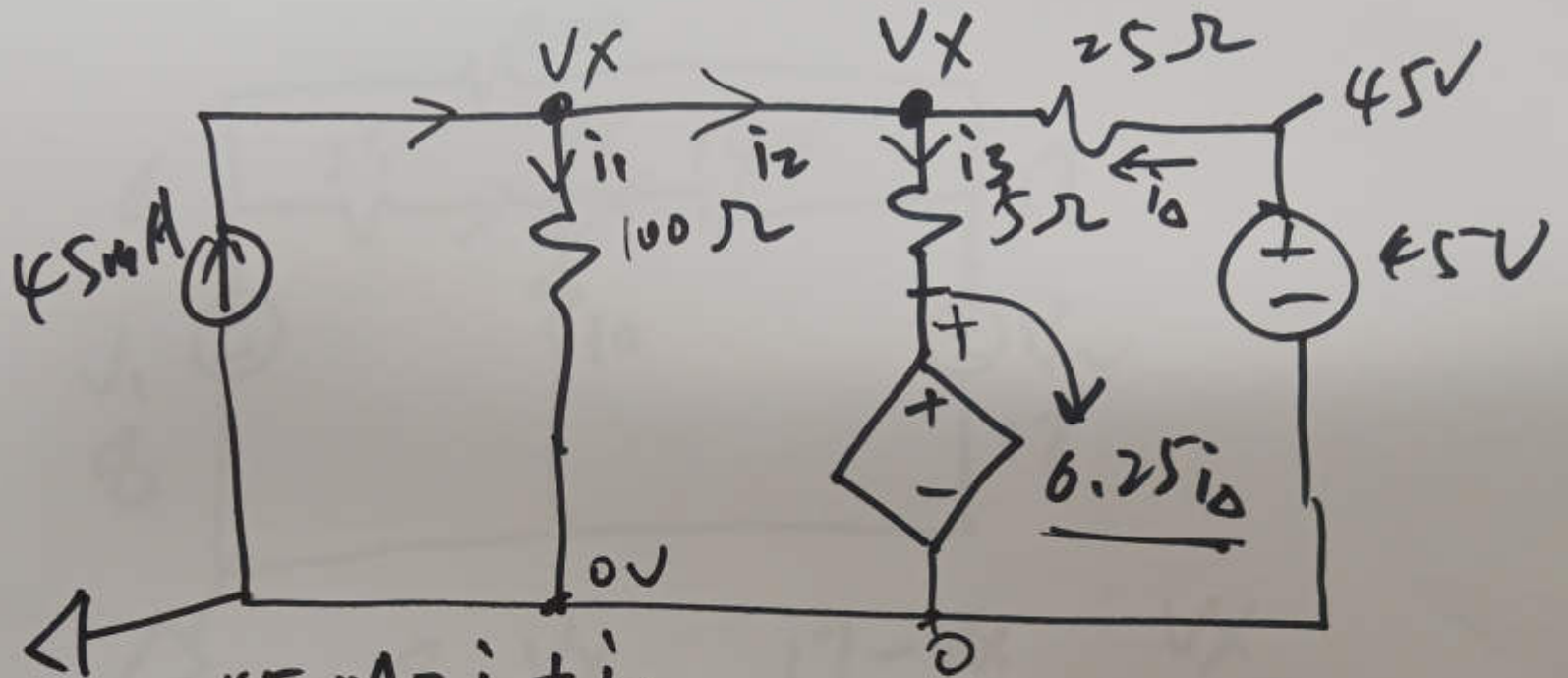

$$45\text{mA} = i_1 + i_2$$


$$i_2 + i_0 = i_3$$

$$i_0 = \frac{45 - V_x}{25}$$

$$i_3 = \frac{V_x - 6.25i_0}{5}$$

$$i_1 = \frac{V_x - 0}{100}$$


②

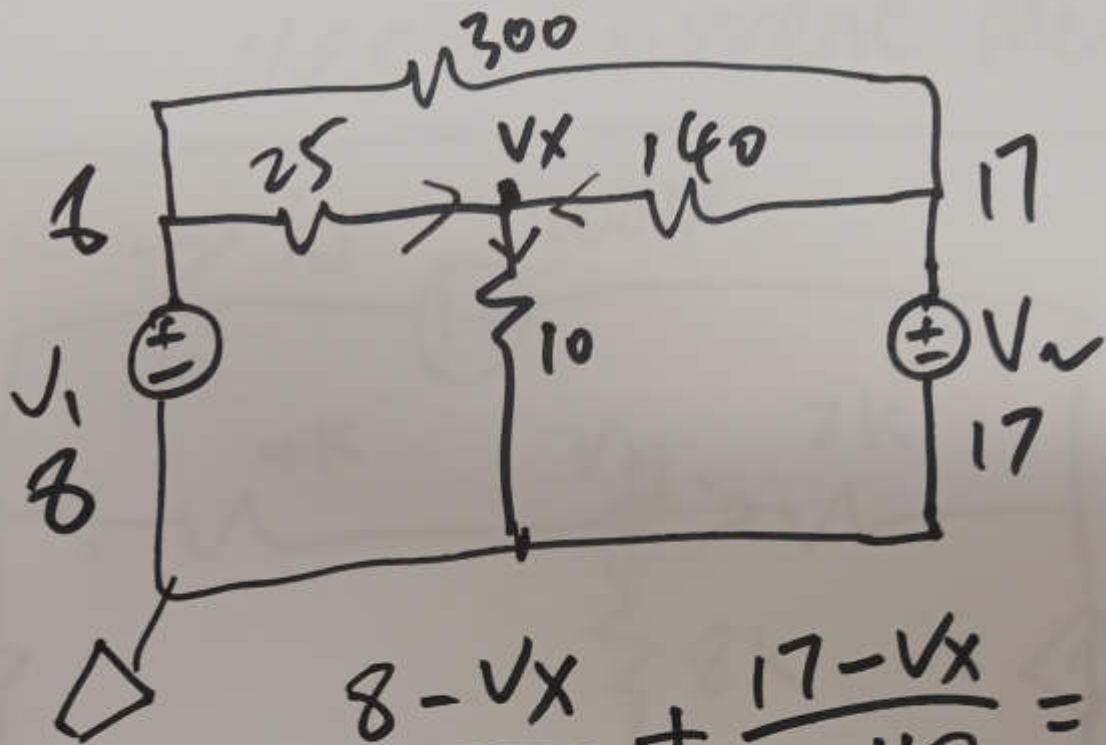


$$\frac{8 - V_x}{25} + \frac{17 - V_x}{140} = \frac{V_x}{10}$$

3

# MESH Current Method (KVL)

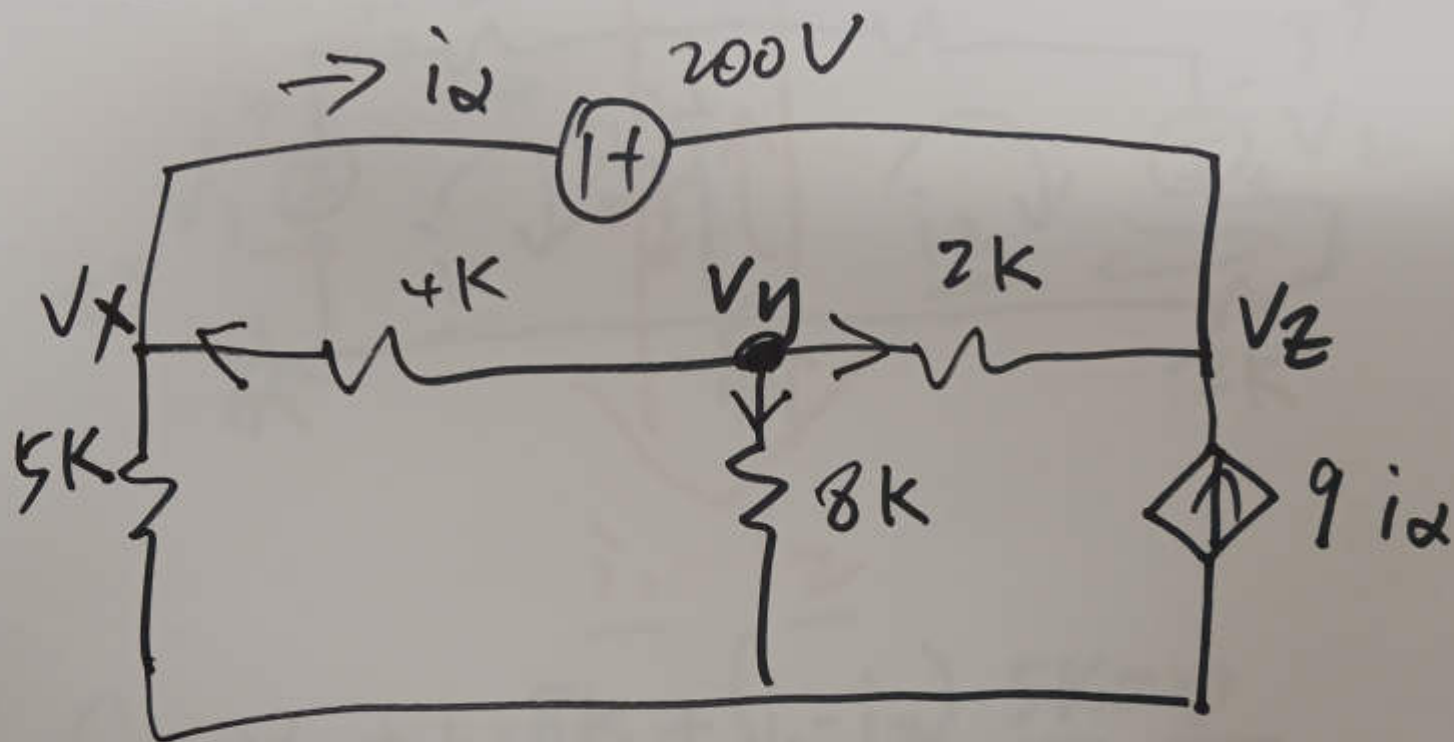
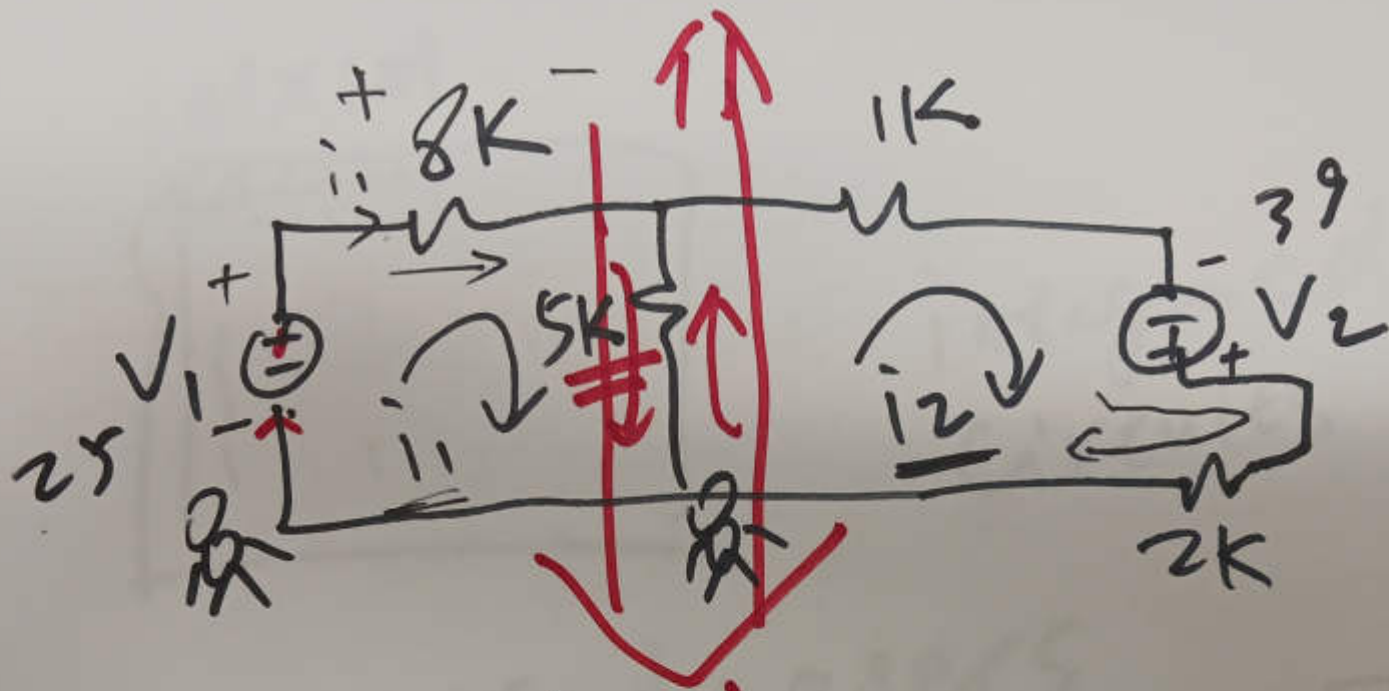
$$\frac{V_y - V_x}{4K} + \frac{V_y - V_z}{2K} + \frac{V_y - 0}{8K} = 0$$




$$\underline{i_1 - i_2}$$

$$\begin{cases} -V_1 + i_1 \cdot 8K + (i_1 - i_2) \cdot 5K = 0 \\ (i_2 - i_1) \cdot 5K + i_2 \cdot 1K - V_2 + i_2 \cdot 2K = 0 \end{cases}$$

$$\begin{cases} i_1 \cdot 13K - i_2 \cdot 5K = 25 \quad A \\ -i_1 \cdot 5K + i_2 \cdot 8K = 39 \quad B \end{cases}$$


$$\begin{bmatrix} 13K & -5K \\ -5K & 8K \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 25 \\ 39 \end{bmatrix}$$

1.5

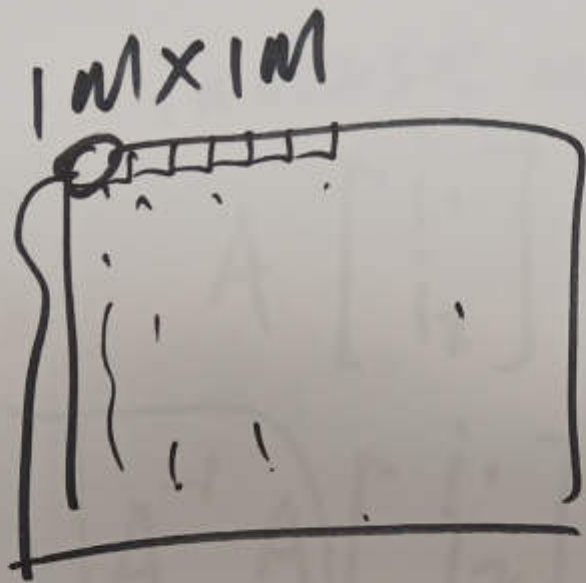

integrated  
circuits

CMOS imagers

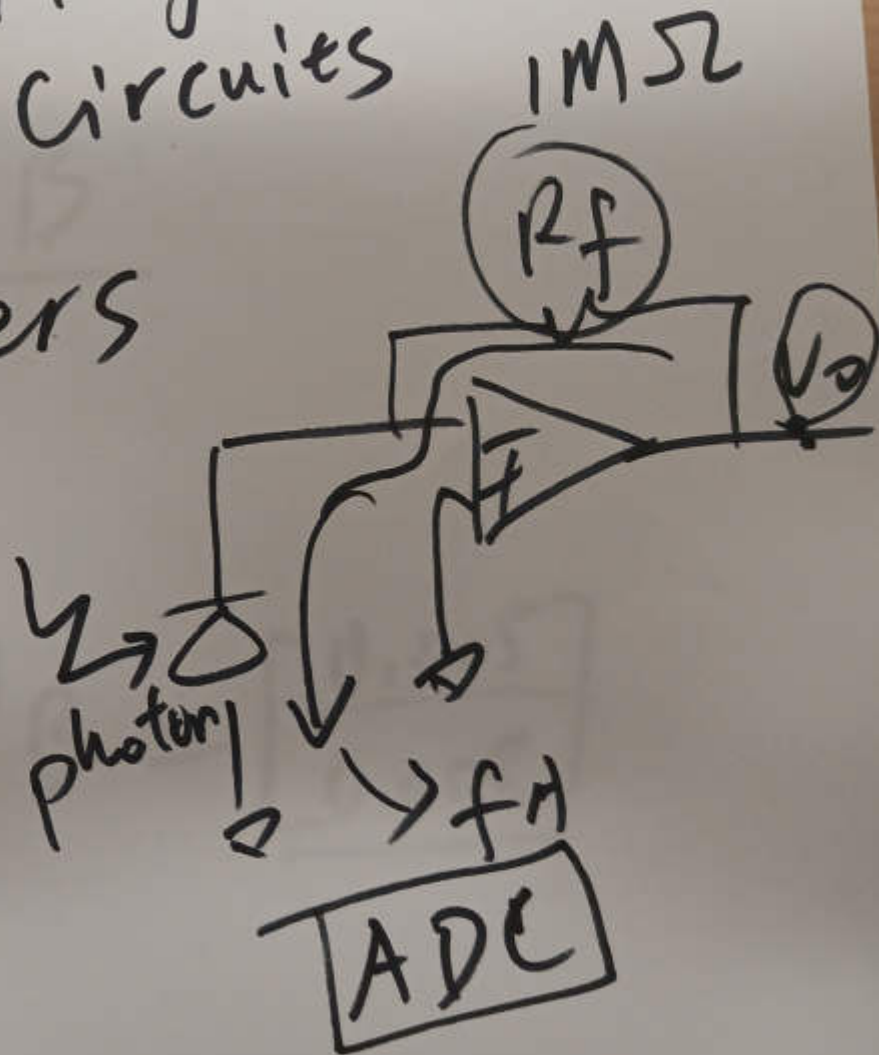

6

inverse matrix


$$A \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \cancel{A} B$$

$$\boxed{A^{-1} A} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \underline{A^{-1} B}$$

$$\begin{bmatrix} 1 \\ 1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = A^{-1} B = \begin{bmatrix} 0.005 \\ 0.008 \end{bmatrix}$$

①

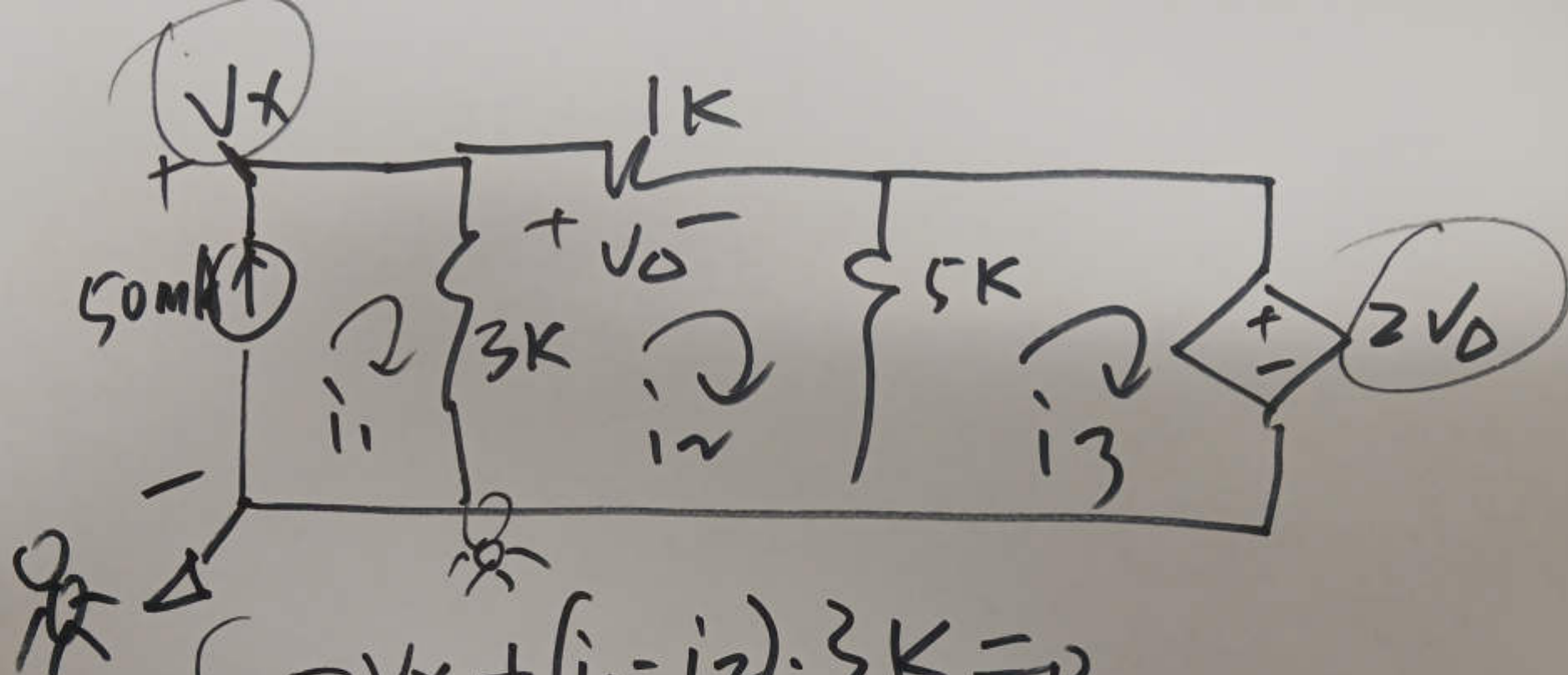

$$\begin{aligned}
 -V_x + (i_1 - i_2) \cdot 3K &= 0 \\
 (i_2 - i_1) \cdot 3K + i_2 \cdot 1K + (i_2 - i_3) \cdot 5K &= 0 \\
 (i_3 - i_2) \cdot 5K + 2V_o &= 0 \\
 V_o &= i_2 \cdot 1K \\
 i_1 &= 50mA
 \end{aligned}$$

(6)