


$$\left\{ \begin{array}{l} \frac{v_x}{2} = \underline{i_y} + \frac{v_1}{25} \\ v_1 - v_2 = 10 \\ v_2 = v_x \\ i_y = \frac{v_2}{5} + 27 \end{array} \right.$$

Source Transformation

Equivalent
Circuit
Problems




Thevenin's
equivalent

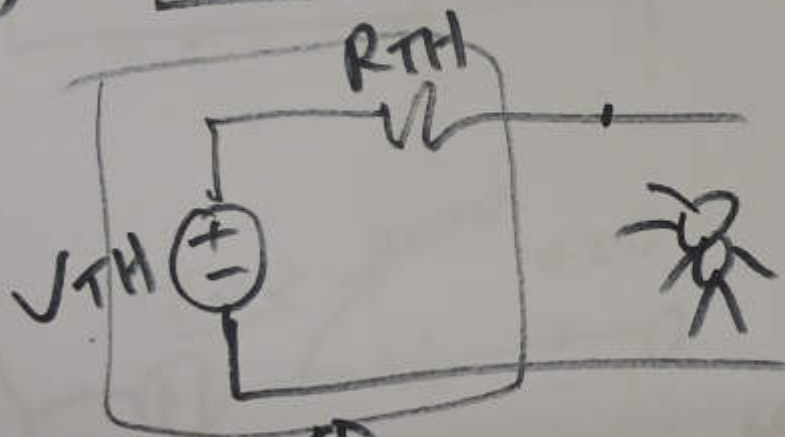




$$\underline{R_{TH} = R_N}$$

$$\frac{V_{TH}}{R_{TH}} = \underline{I_N}$$




Norton's
equivalent



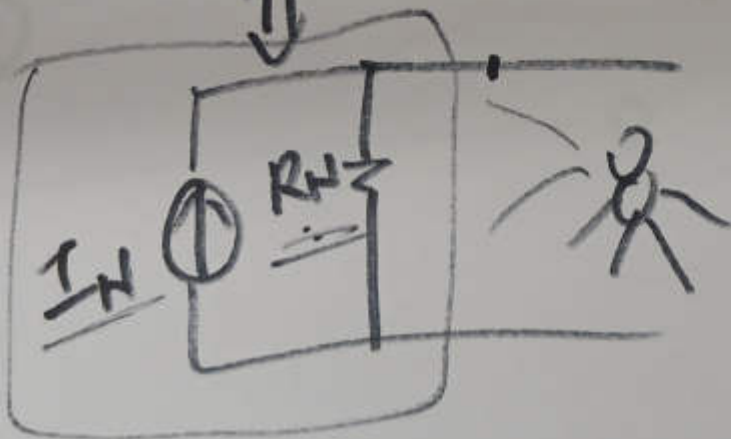


(2)

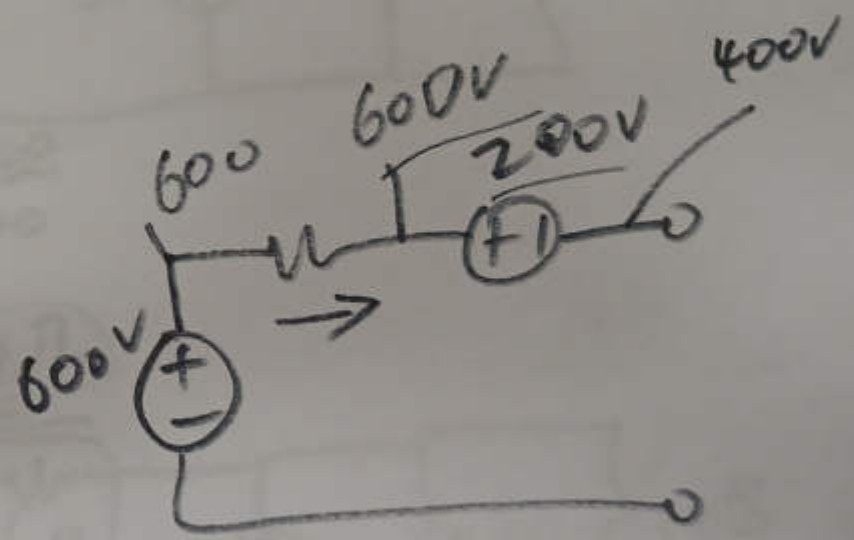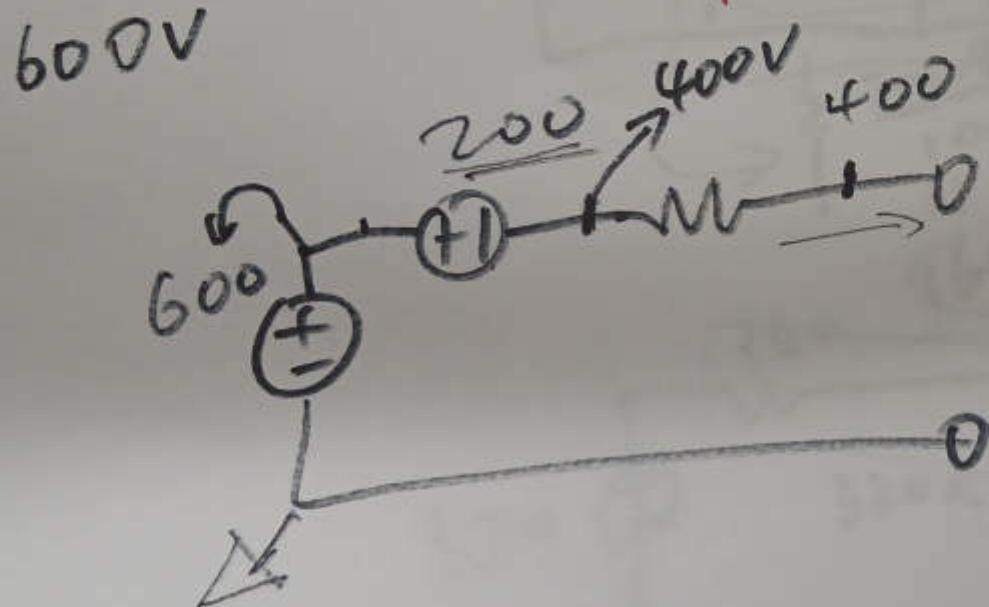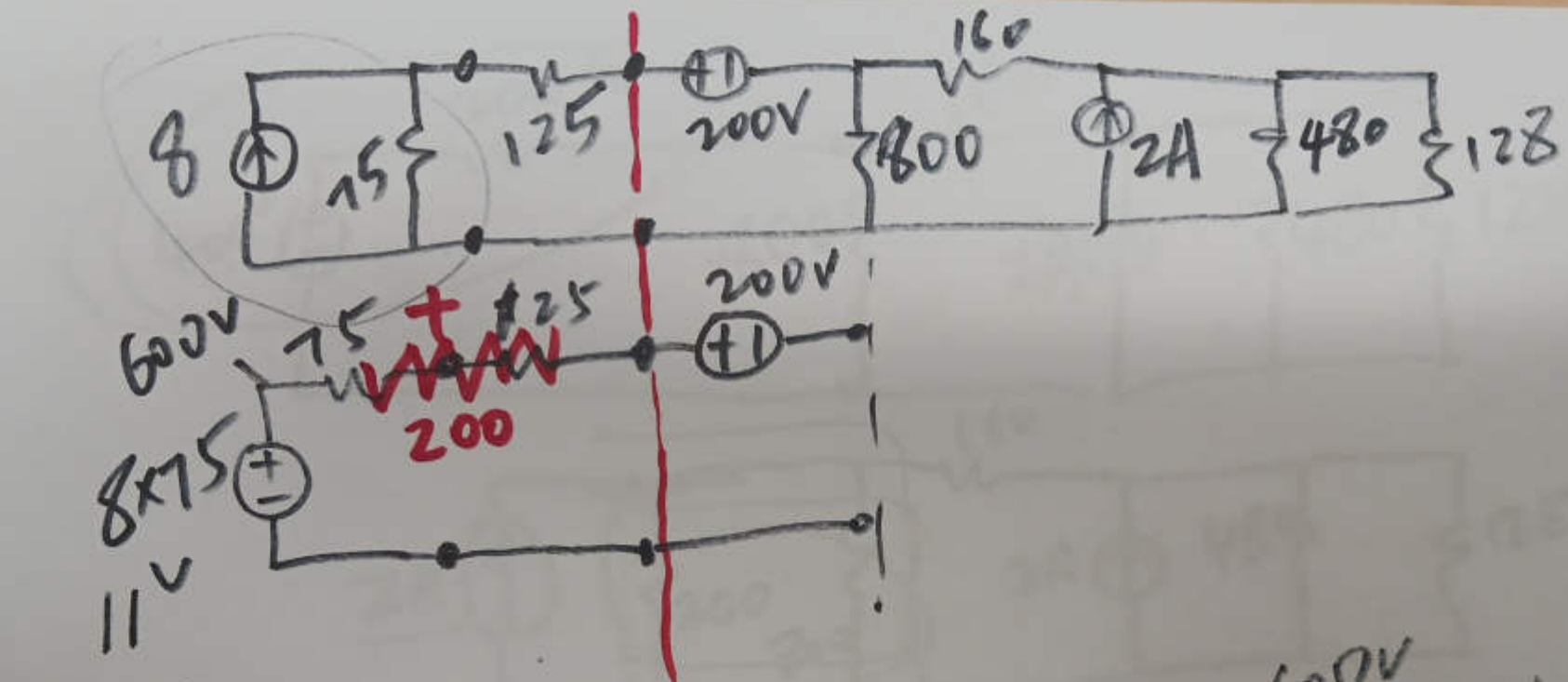


(3)

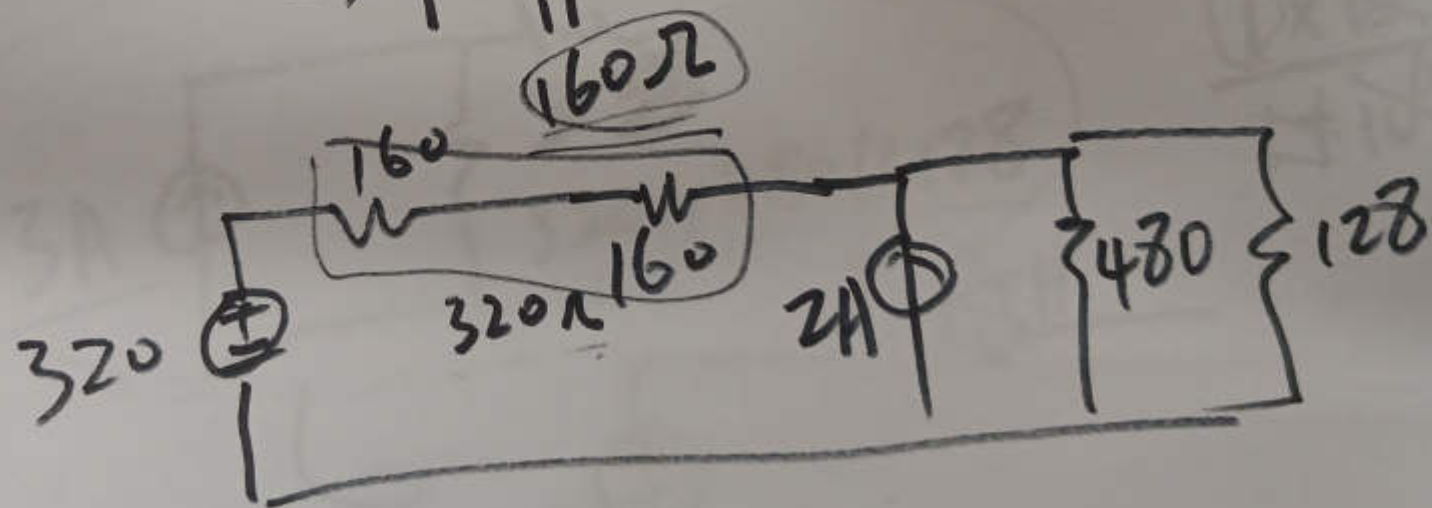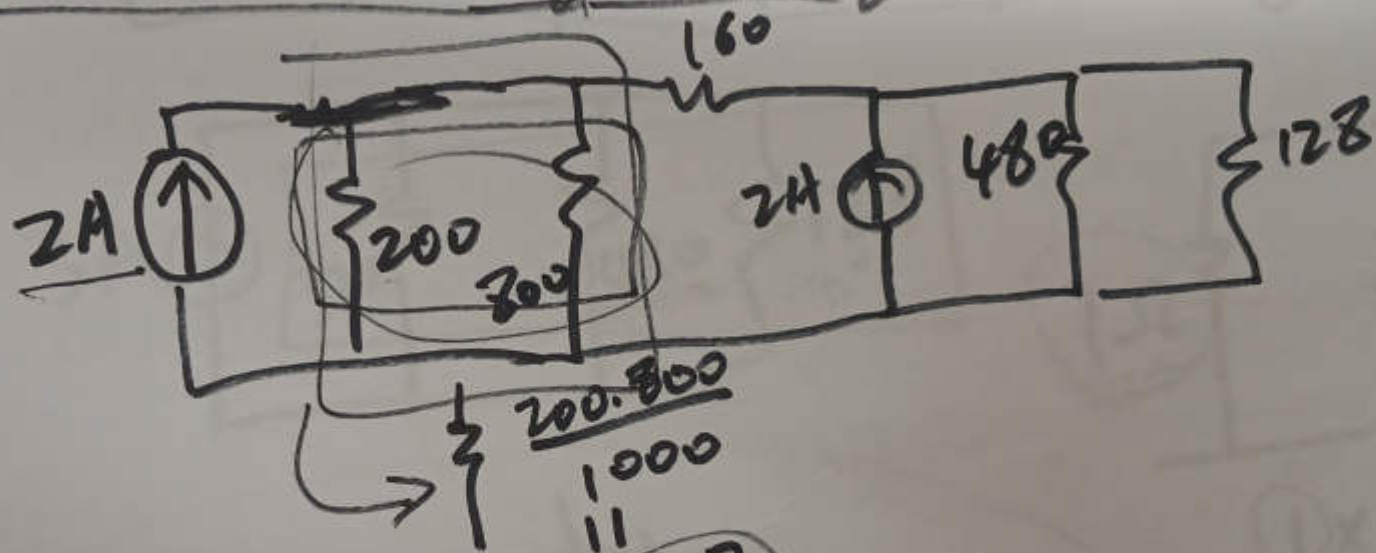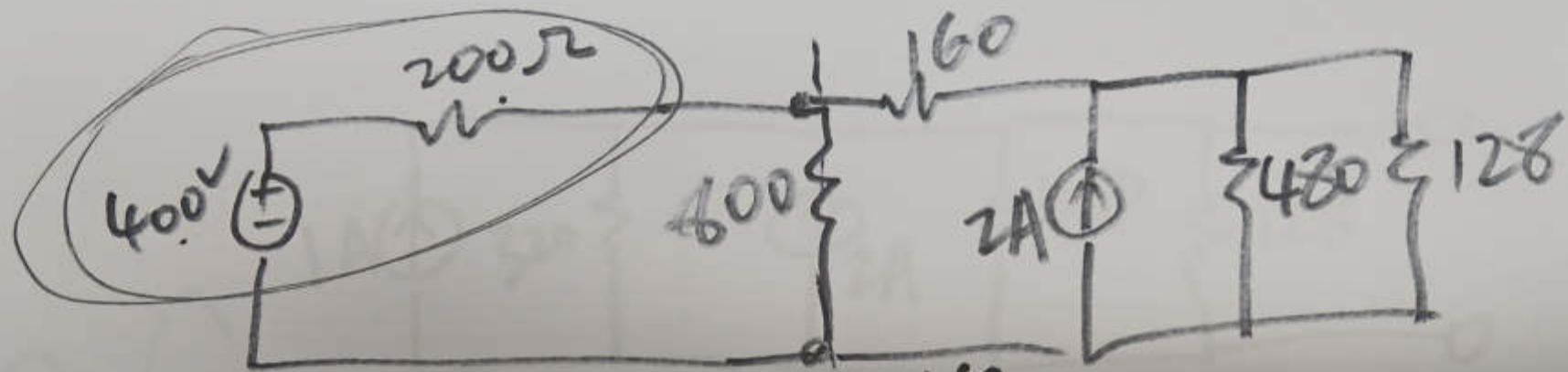

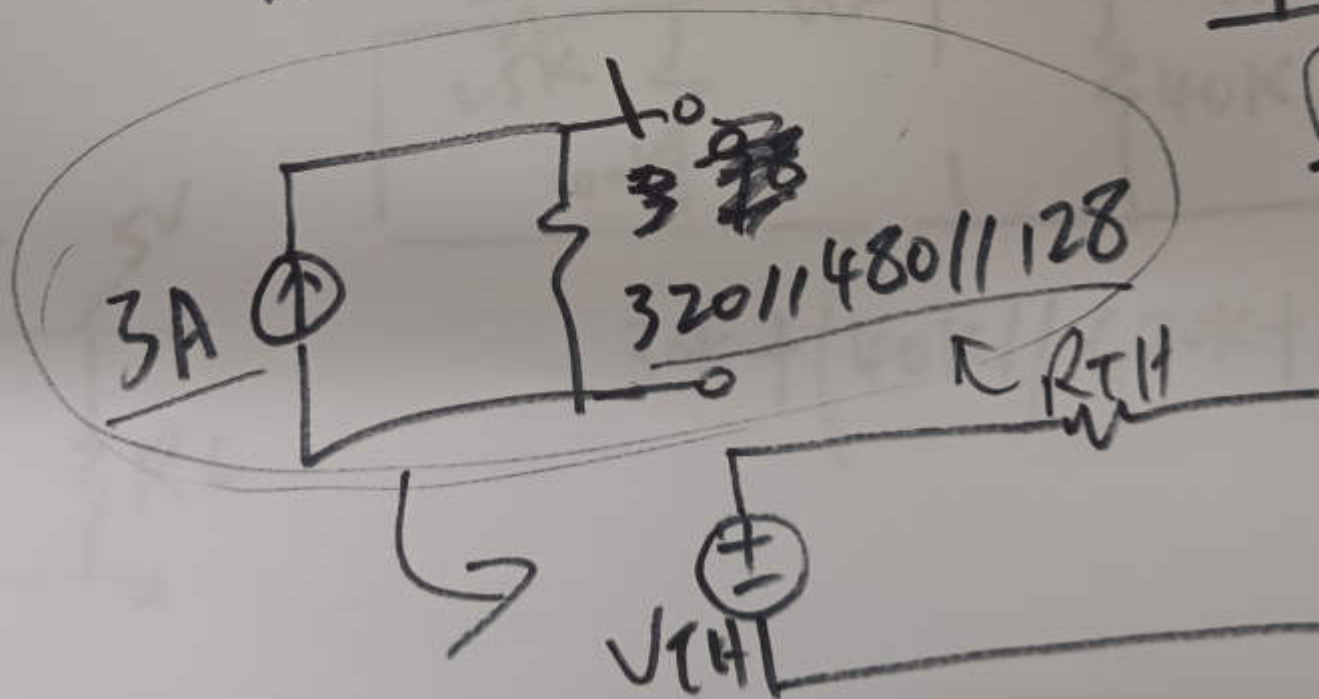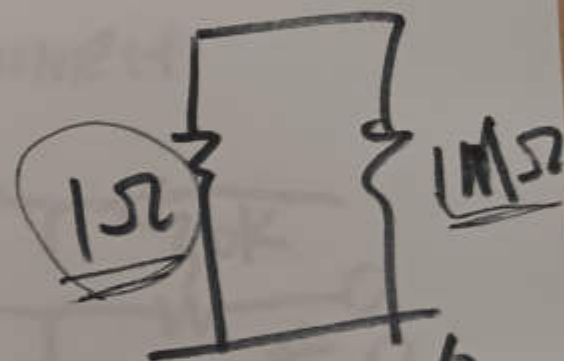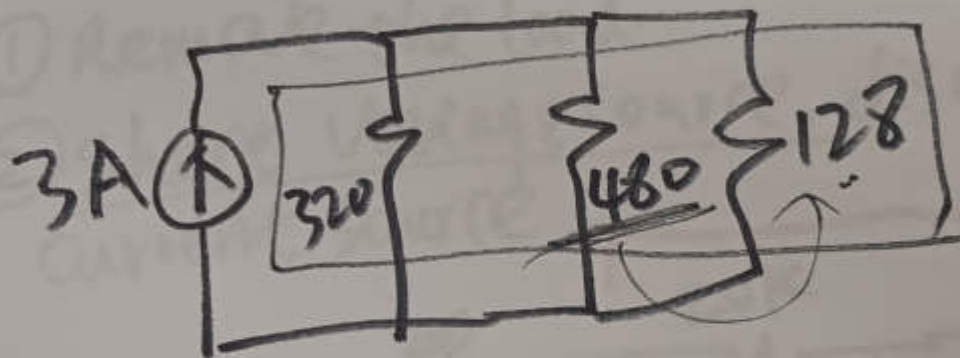


$$\frac{1 \times 10^6}{1 + 146}$$


KS

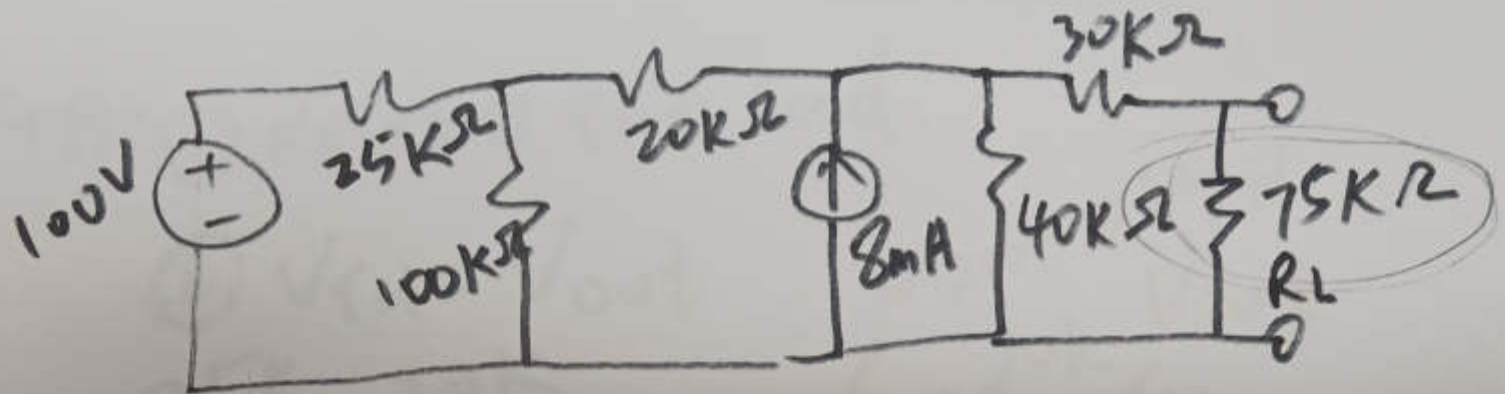

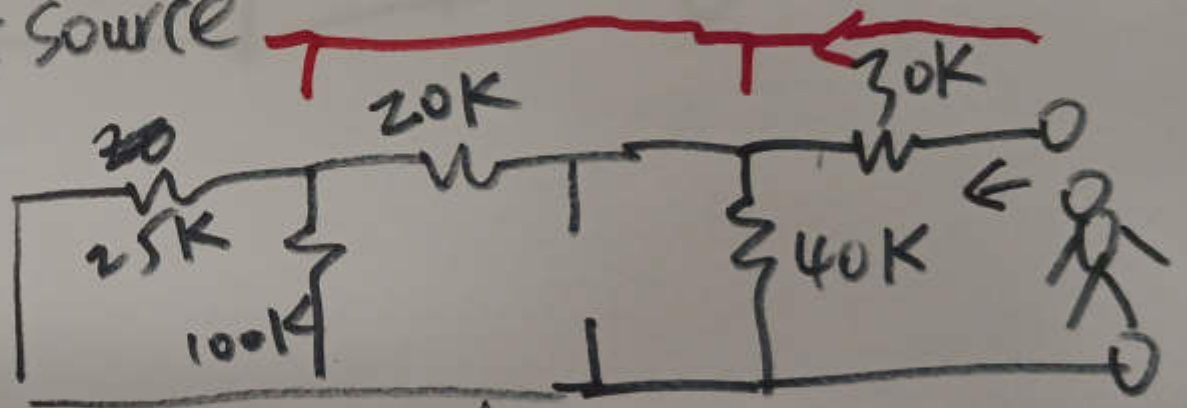- R_{TH}:**
- ① Remove the load.
 - ② Short voltage source, disconnect current source



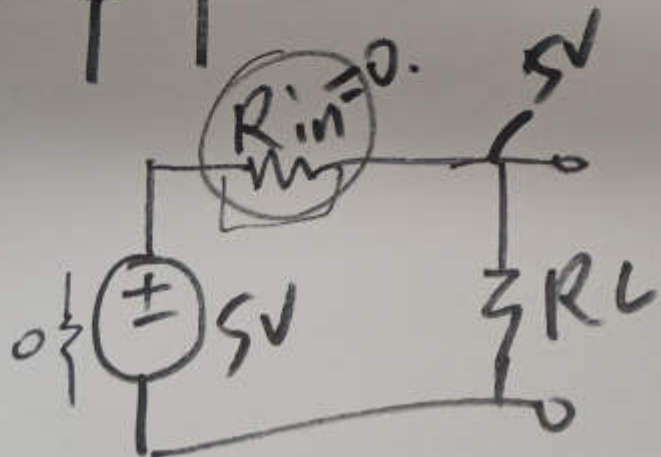
$$30k + \left(40k \parallel \left(20k + \left(25k \parallel 100k \right) \right) \right)$$



(b)

V_{TH} : ① Remove the load.

② $V_{TH} = V_{out}$

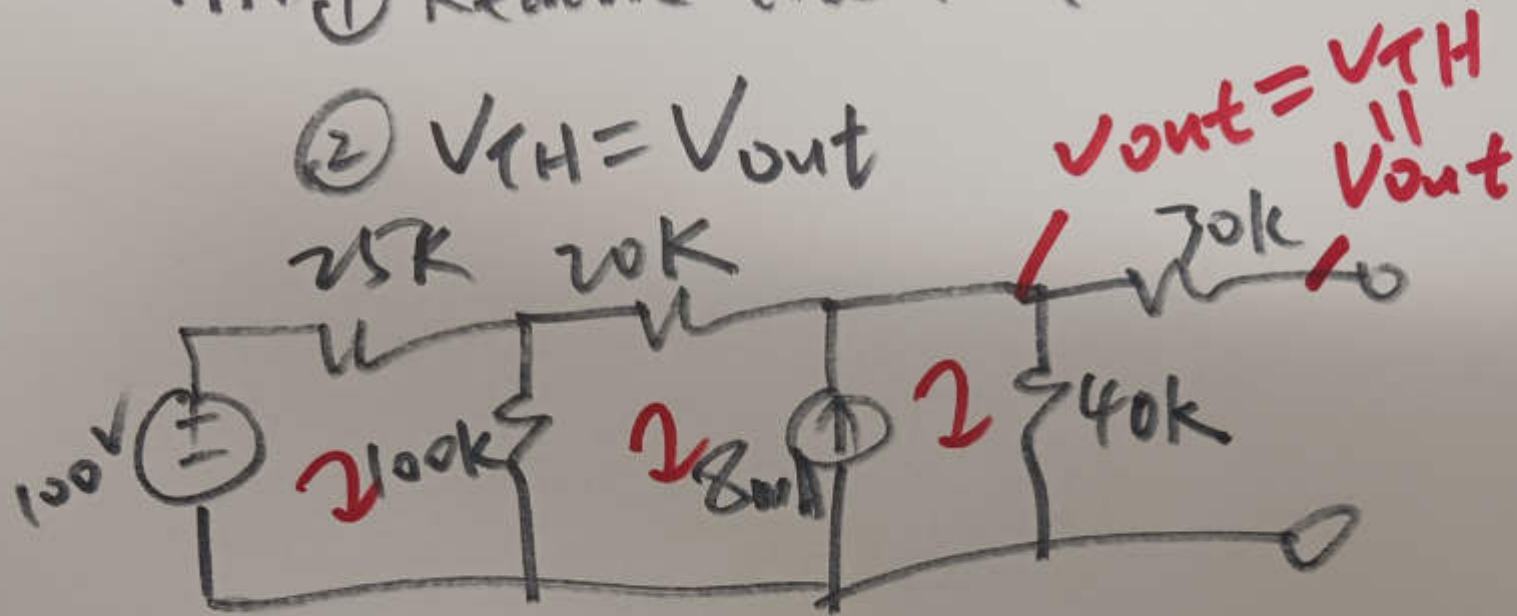

⑦