
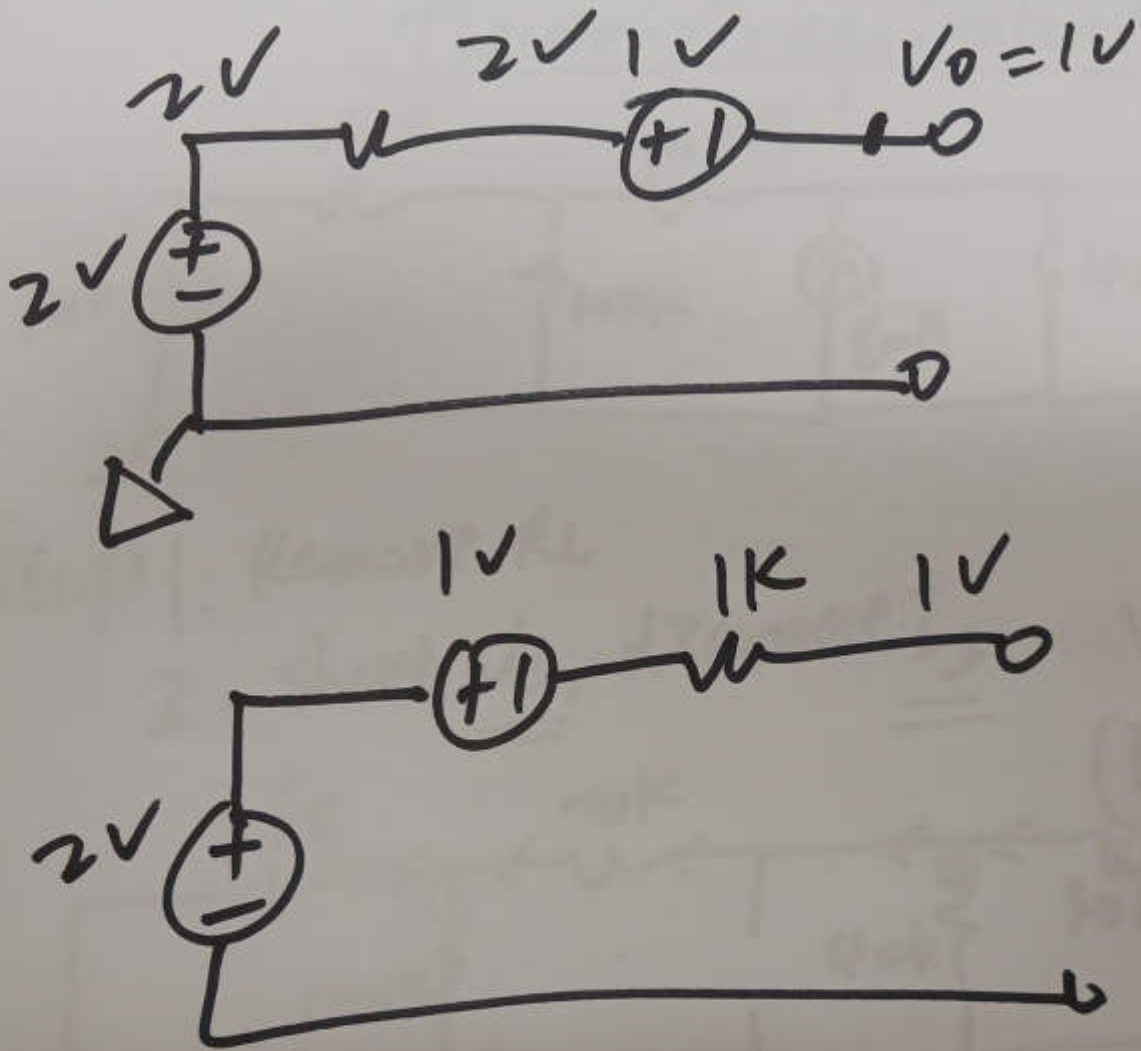


①

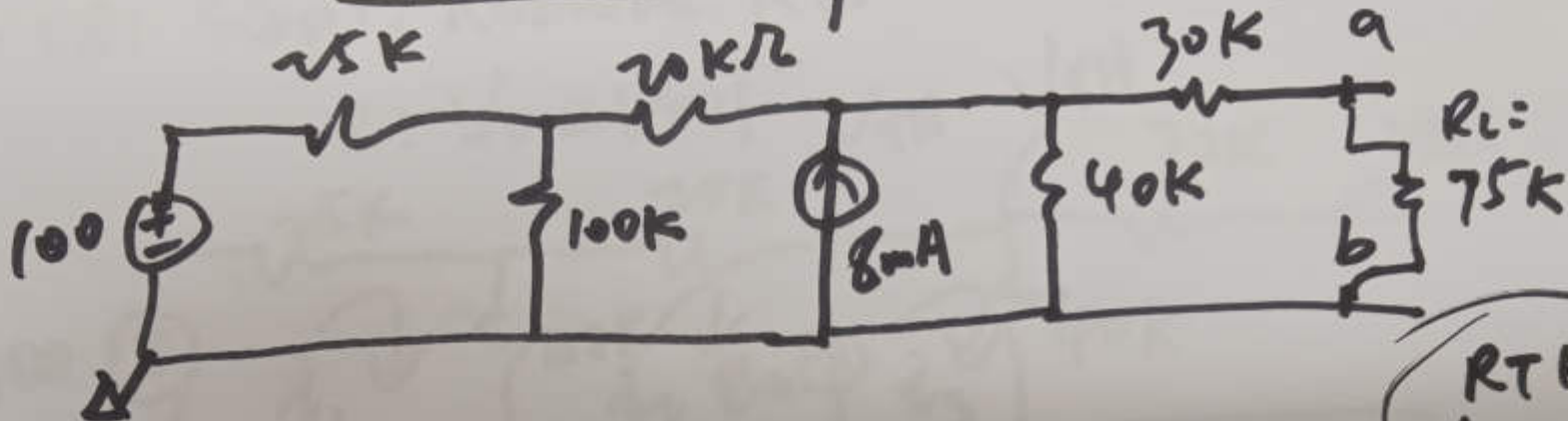

②



Thevenin's equivalent.



R_{TH}:

Step 1: Remove R_L


2: short V_s , disconnect I_s

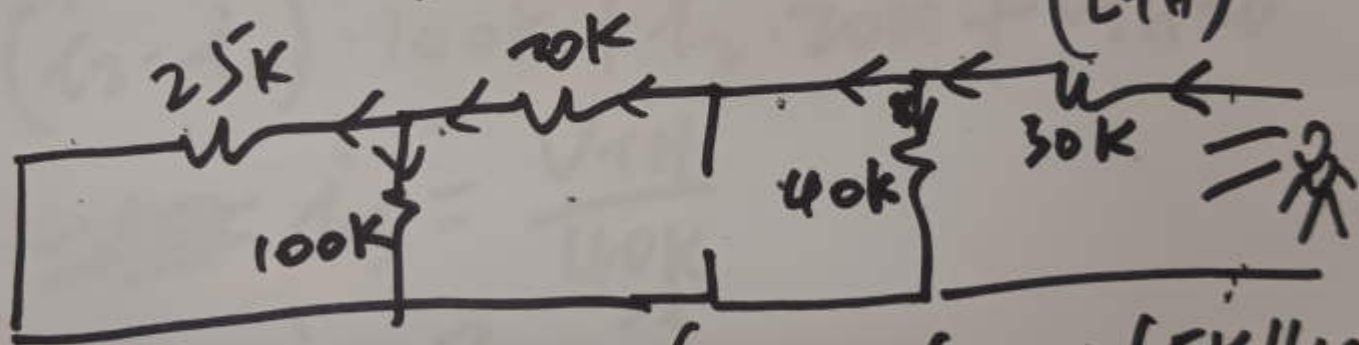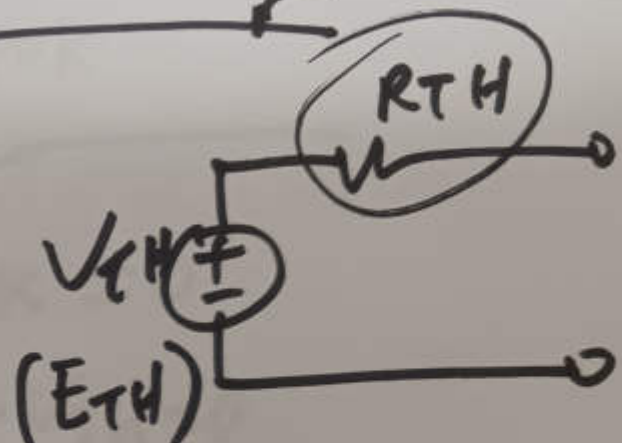

$$R_{TH} = 30k + \left(40k \parallel \left(20k + (25k \parallel 100k) \right) \right)$$

V_{TH} : Step 1: Remove R_L

2: $V_0 = V_{TH}$

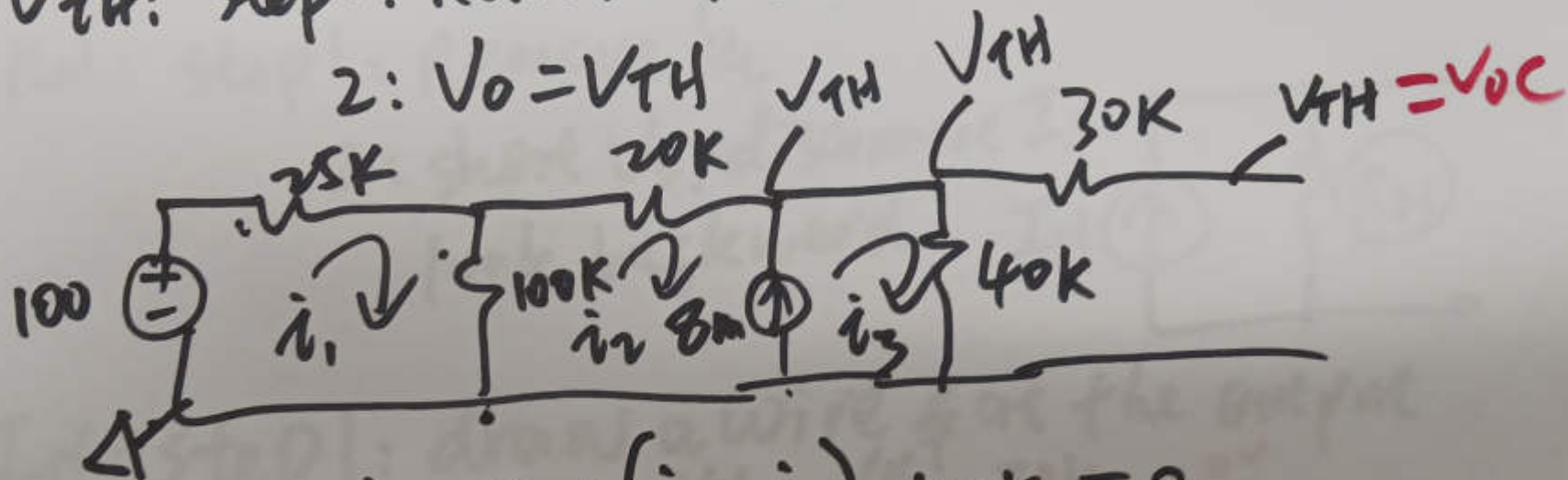

$$-100 + i_1 \cdot 25k + (i_1 - i_2) \cdot 100k = 0$$

$$(i_2 - i_1) \cdot 100k + i_2 \cdot 20k + V_{TH} = 0$$

$$\cancel{i_3} = \frac{V_{TH}}{40k}$$

$$i_3 - i_2 = 8 \times 10^{-3}$$

Norton's equivalent


RN: step 1: Remove R_L

2: short V_S , disconnect I_S

look backward



I_N : step 1: draw a wire at the output

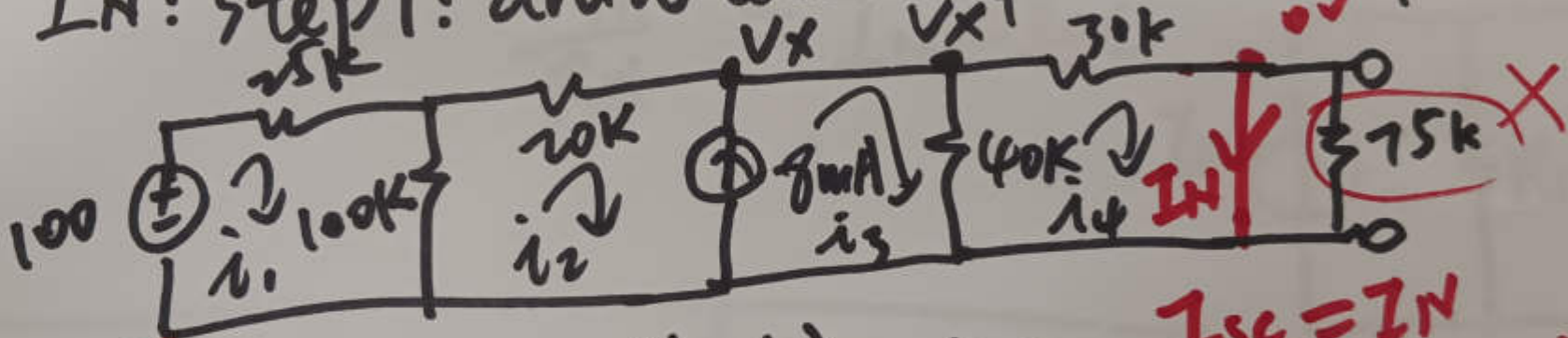

$I_{sc} = I_N$
short circuit

$$i_4 = I_N$$

$$\left\{ \begin{aligned} -100 + i_1 \cdot 25k + (i_1 - i_2) \cdot 100k &= 0 \\ (i_2 - i_1) \cdot 100k + i_2 \cdot 20k + V_X &= 0 \\ -V_X + (i_3 - i_4) \cdot 40k &= 0 \\ (i_4 - i_3) \cdot 40k + i_4 \cdot 30k &= 0 \\ (i_3 - i_4) \cdot 40k &= V_X \end{aligned} \right.$$


④

$$R_N \approx R_{TH}$$

$$V_{TH} = V_{OC}$$

$$\frac{V_{TH}}{R_{TH}} = I_N = I_{SC}$$

$$\frac{V_{TH}}{R_N} = I_N = I_{SC}$$

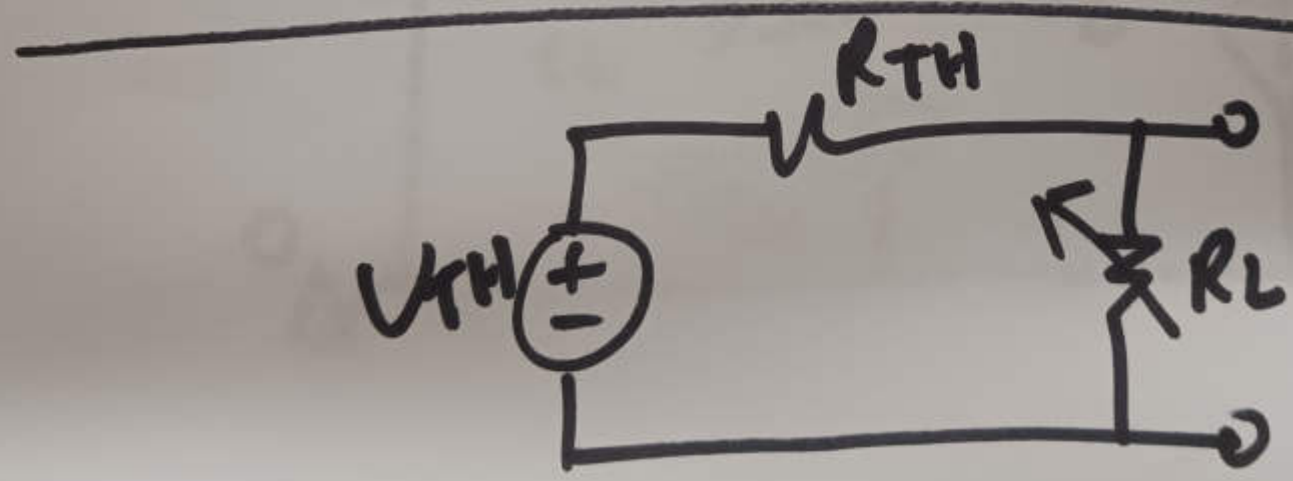


Maximum P_{RL}


$R_L?$

$$R_L = R_{TH}$$

⑤

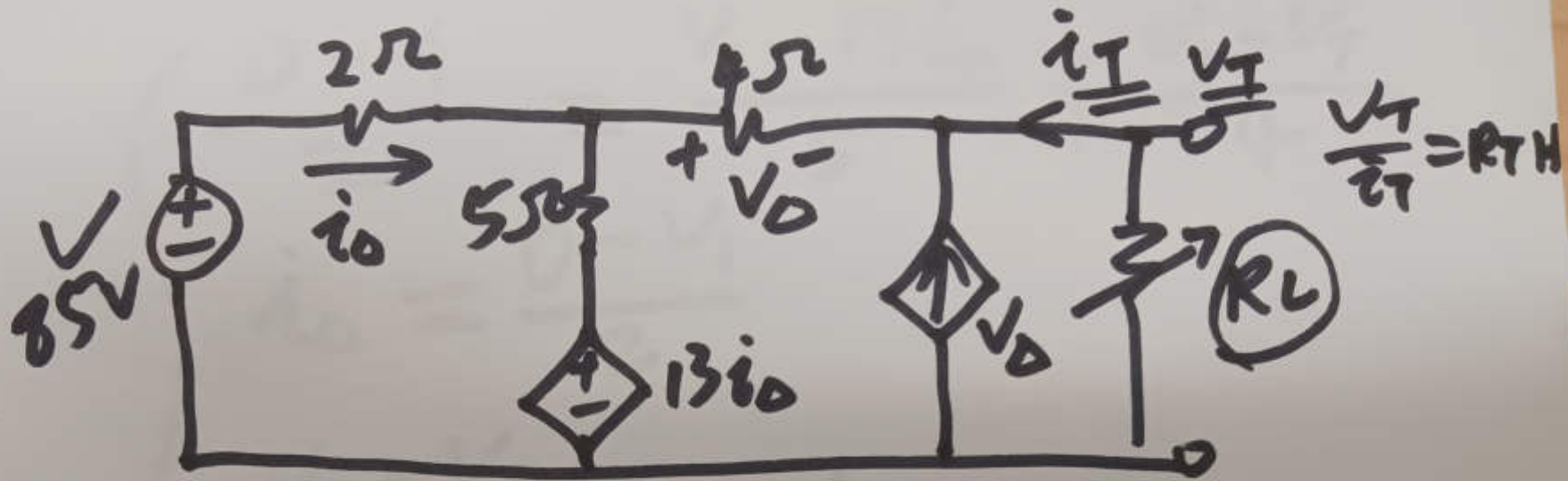

R_{TH}: step 1: Remove R_L

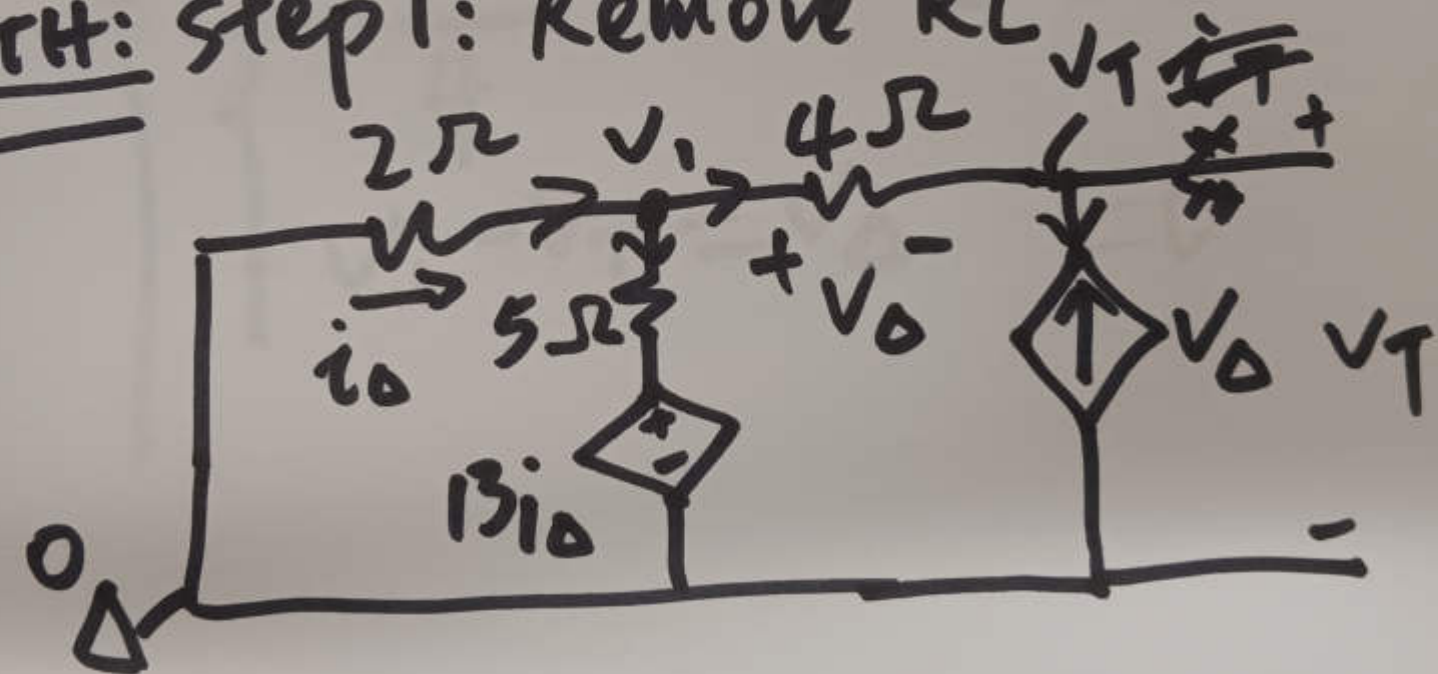

$$\left\{ \begin{array}{l} \frac{0 - v_1}{2} = \frac{v_1 - 13i_0}{5} + \frac{v_1 - v_T}{4} \\ i_0 = \frac{0 - v_1}{2} \\ \frac{v_1 - v_T}{4} = -v_\Delta = 0 \\ v_1 - v_T = v_\Delta = 0 \end{array} \right.$$