

$$-13.4 + (i_1 - i_3) \cdot 40 + (i_1 - i_2) \cdot 15 = 0 \quad (1)$$

$$(i_2 - i_1) \cdot 15 + (v_1 - v_2) + i_2 \cdot 10 + i_2 \cdot 4 = 0 \quad (2)$$

$$i_3 \cdot 26 + (v_2 - v_1) + (i_3 - i_1) \cdot 40 = 0 \quad (3)$$

$$i_2 - i_3 = 110 \cdot 10^{-3}$$

$$\frac{v_1}{15} = i_1 - i_2$$

$$v_1 = 15(i_1 - i_2)$$

$$\frac{v_2}{14} = i_2$$

$$v_2 = 14 \cdot i_2$$

(1)

$$\text{from } \textcircled{1} \quad i_1 \cdot 55 - i_2 \cdot 15 - i_3 \cdot 40 = 13.4$$

$$\textcircled{2} + \textcircled{3} \quad (i_2 - i_1) \cdot 15 + i_2 \cdot 10 + i_2 \cdot 4 + i_3 \cdot 26 + (i_3 - i_1) \cdot 40 = 0$$

$$\checkmark -i_1 \cdot 55 + i_2 \cdot 29 + i_3 \cdot 66 = 0$$

$$\checkmark i_1 \cdot 0 + i_2 \cdot 1 - i_3 \cdot 1 = 110 \times 10^{-3}$$

$$A = \begin{bmatrix} 55 & -15 & -40 \\ -55 & 29 & 66 \\ 0 & 1 & -1 \end{bmatrix}$$

$$b = \begin{bmatrix} 13.4 \\ 0 \\ 110 \times 10^{-3} \end{bmatrix}$$

$$X = \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 0.51 \\ 0.41 \\ 0.70 \end{bmatrix}$$

$$Ax = b$$

$$A^{-1} A x = A^{-1} b$$


$$x = A^{-1} b$$

②

$$V_2 = V_{TH} = i_2 \cdot 14 \Omega = 0.41 \cdot 14 \Omega$$


$$= 5.75 \text{ V}$$

R_{TH} :

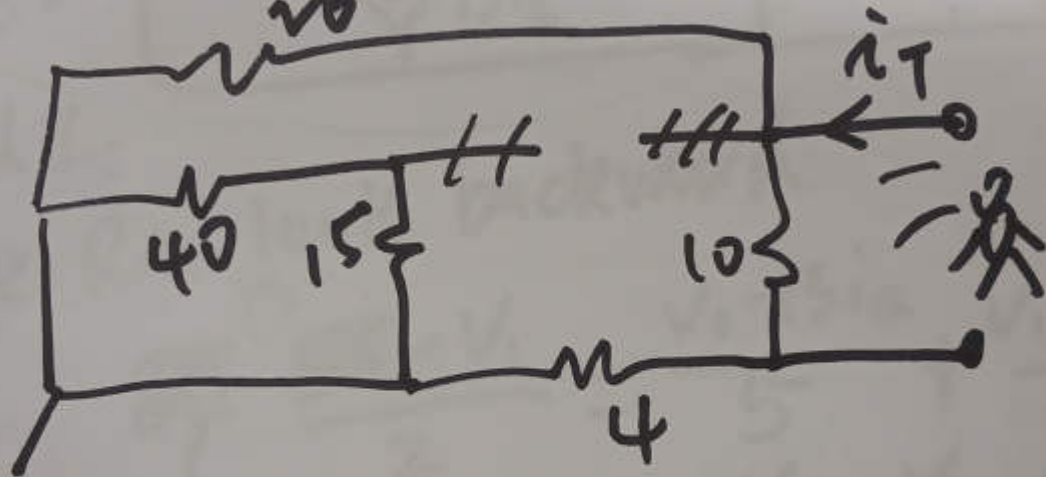


$$R_{TH} = 26 \parallel 14$$

$$I_N = \frac{V_{TH}}{R_{TH}}$$

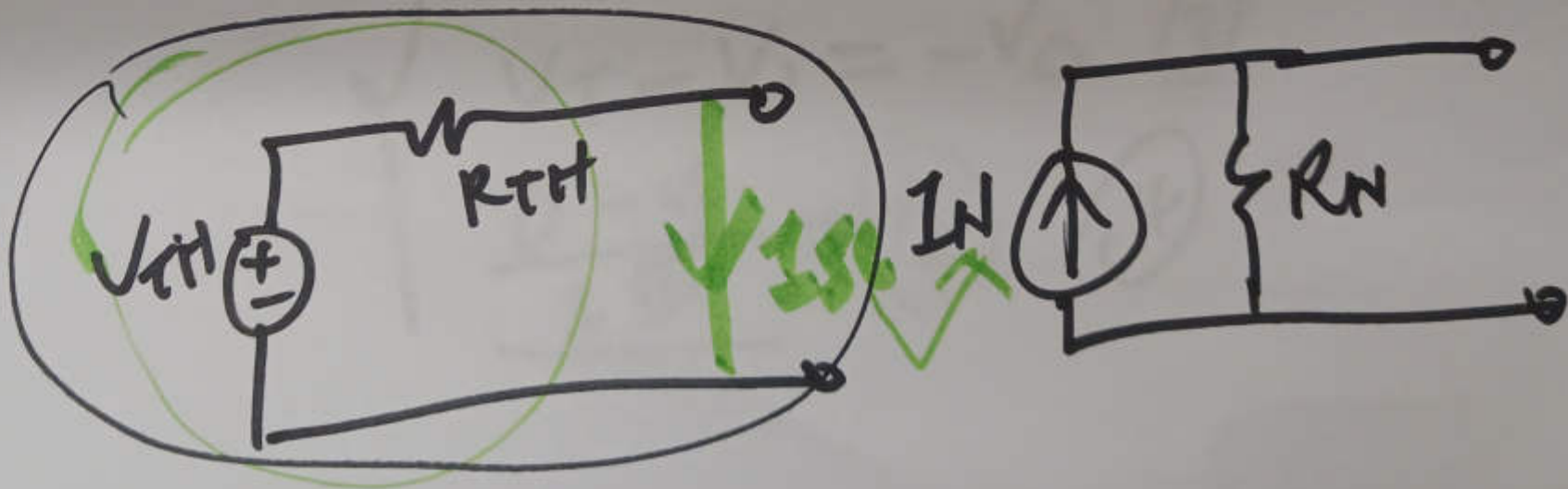

③

RTH

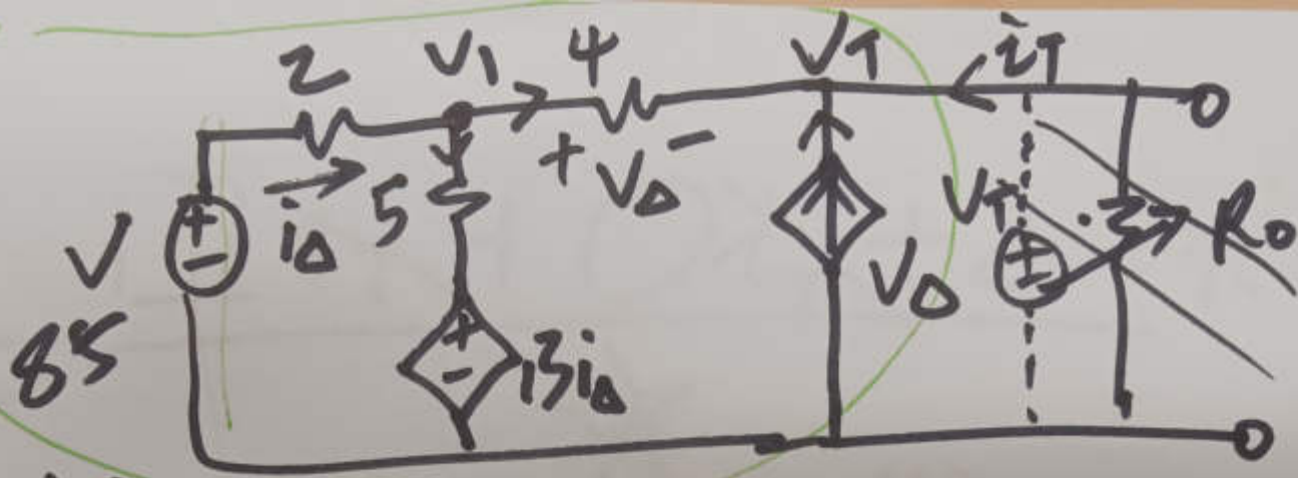

Method I:

Remove R_0 , look backward

$$\frac{V_T}{i_T} = \boxed{\text{RTH}}$$

$$85 - V_1 = \frac{V_1 - 13i_D}{5} + \frac{V_1 - V_T}{4} \quad (1)$$

$$V_D + i_T = \frac{V_T - V_1}{4} \quad (2)$$

$$V_T - V_1 = -V_D \quad (3)$$

$$\frac{0 - V_1}{2} = i_D \quad (4)$$

(4)

$$\text{RTH} \leftarrow \frac{\square i_T + \cancel{0 i_T} + \Delta i_T = \cancel{*} \frac{V_T}{2}}{\star}$$

$$\textcircled{4} \rightarrow \textcircled{1} \quad \frac{-V_1}{2} = \frac{V_1 - 13 \cdot \left(\frac{-V_1}{2}\right)}{5} + \frac{V_1 - V_T}{4}$$

$$-10V_1 = 4V_1 + 26V_1 + 5V_1 - 5V_T$$

$$-45V_1 = -5V_T$$

$$9V_1 = V_T \quad \textcircled{5} \Rightarrow V_1 = \frac{V_T}{9}$$

$$\textcircled{2} \text{ and } \textcircled{3} \Rightarrow V_1 - V_T + i_T = \frac{V_T - V_1}{4}$$

$$4V_1 - 4V_T + 4i_T = V_T - V_1$$

$$5V_1 = 5V_T - 4i_T \quad \textcircled{6}$$


$\textcircled{5}$

$$\textcircled{5} \text{ and } \textcircled{6} \rightarrow \frac{5}{9} V_T = 5V_T - 4i_T$$

$$\cancel{5} V_T = 45V_T - 36i_T$$

$$40V_T = 36i_T$$

$$\frac{V_T}{i_T} =$$

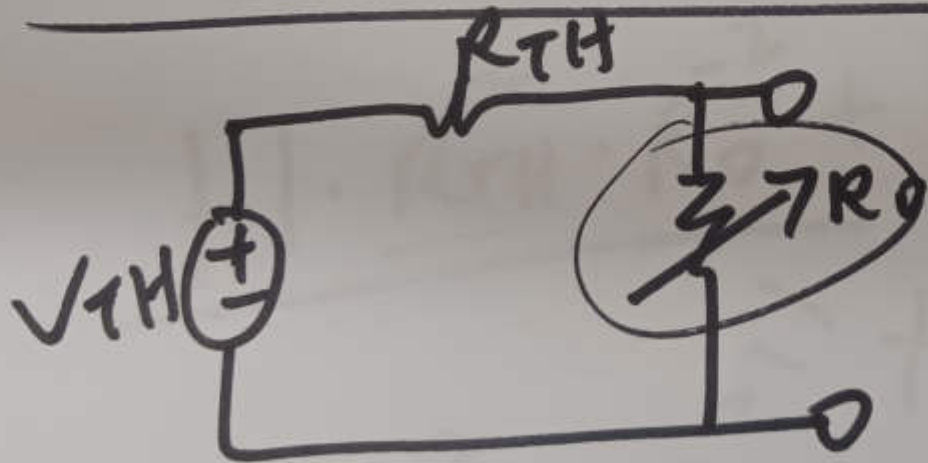

$$P_{\max R_O} = \left(\frac{V}{R_{TH} + R_O} \right)^2 \cdot R_O$$

when $R_O = R_{TH}$

$$= \frac{V^2 \cdot R_O}{R_{TH}^2 + R_O^2 + 2R_{TH} \cdot R_O}$$

⑤

$$= \frac{v^2}{\frac{R_{TH}^2}{R_0} + R_0 + 2R_{TH}}$$

$$\frac{d\left(\frac{R_{TH}^2}{R_0} + R_0\right)}{d R_0} = 0$$

$$+1 \cdot \frac{R_{TH}^2 \cdot R_0^{-2}}{R_0} + 1 = 0$$

$$R_{TH}^2 = R_0^2$$

$$R_{TH} = R_0$$

(b)