


$$-100V + (i_1 - i_2) \cdot 5 + (i_1 - i_3) \cdot 10 + i_1 \cdot 2 = 0$$

$$i_2 \cdot 2 + V_{CS} + (i_2 - i_1) \cdot 5 = 0$$

$$(i_3 - i_1) \cdot 10 - V_{CS} + i_3 \cdot 20 = 0$$



$$i_3 - i_2 = 1.2 i_b = 1.2 i_1$$

②

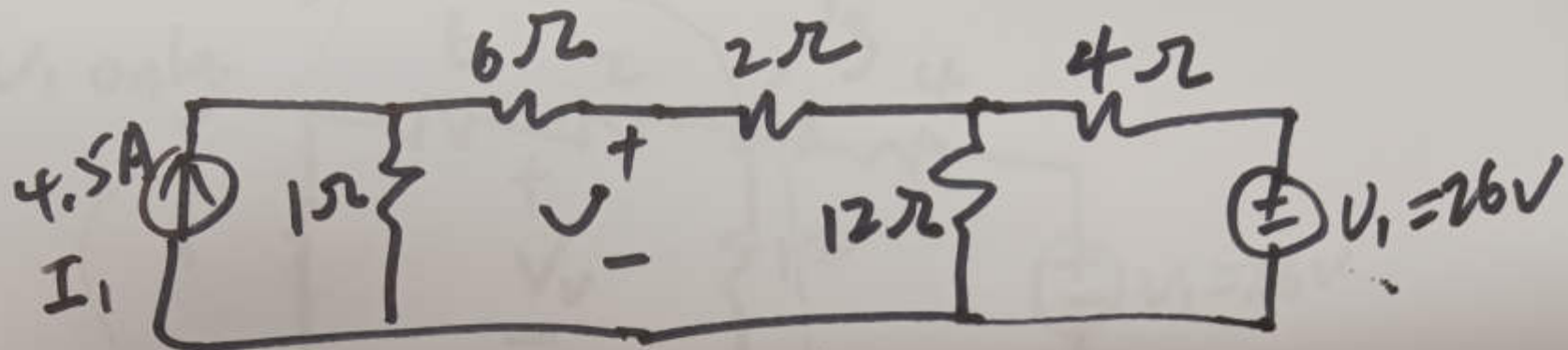

Apply one source at a time:

I₁ only:

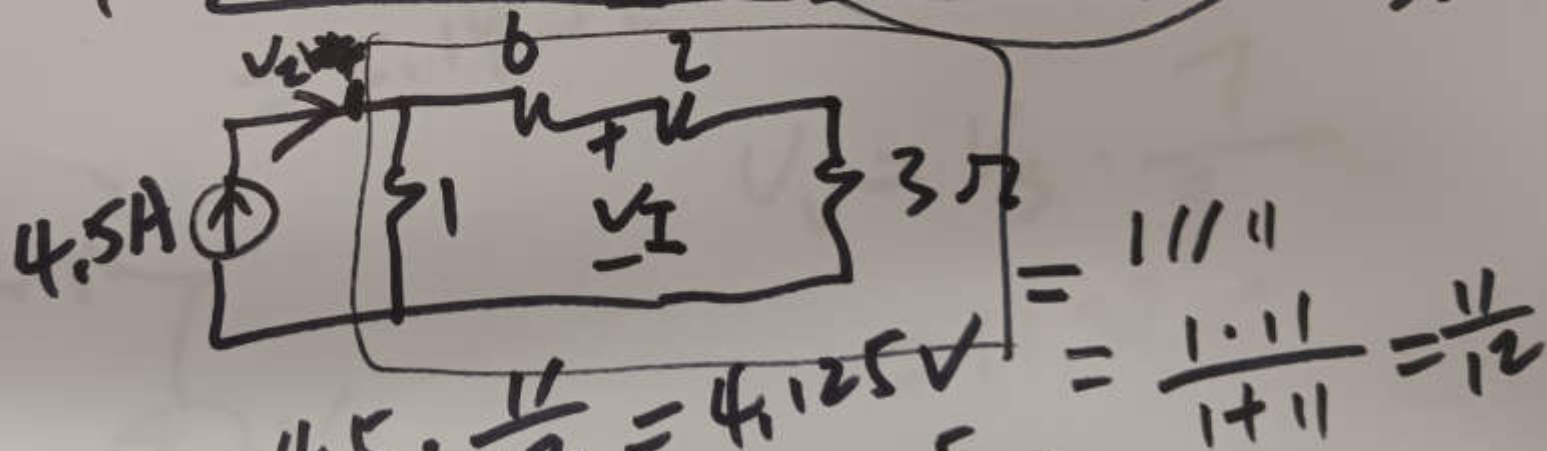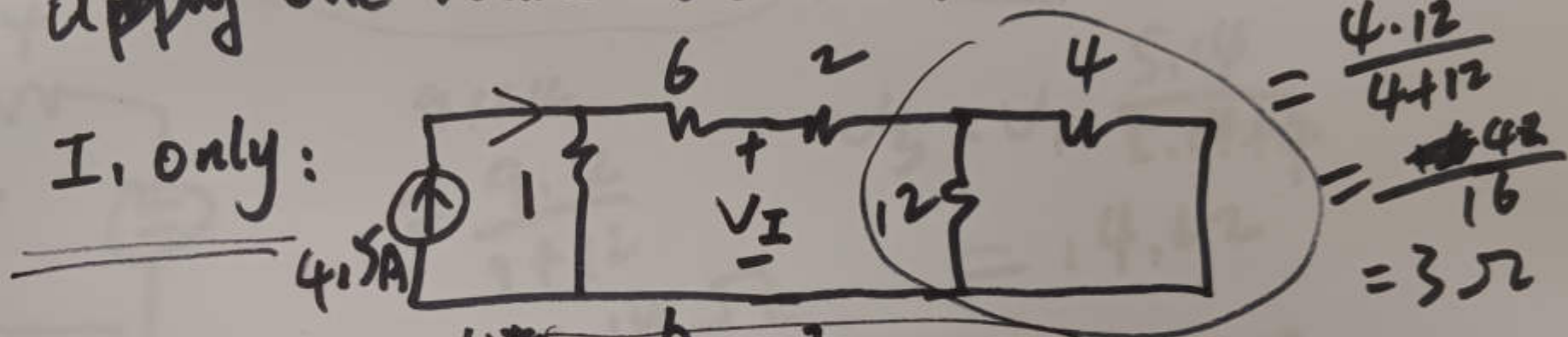


$$V_2 = 4.5 \cdot \frac{11}{12} = 4.125 \text{ V}$$

$$V_1 = 4.125 \cdot \frac{5}{6+5}$$


$$= 1.875 \text{ V}$$

V_1 only:

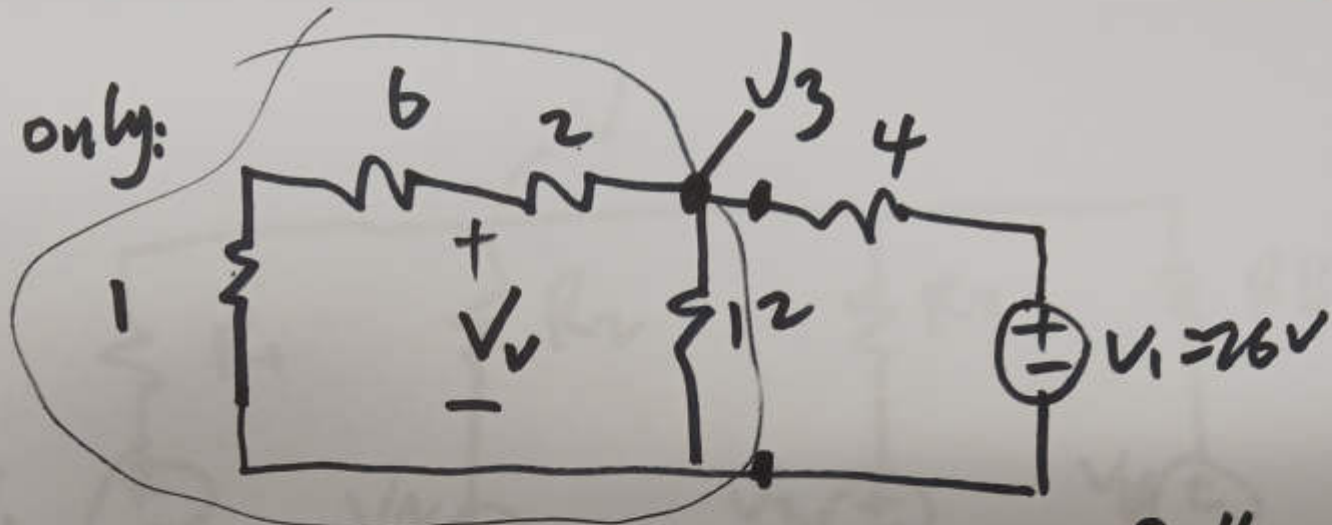

$$\begin{aligned} & 9 \parallel 12 \\ &= \frac{9 \cdot 12}{9 + 12} \\ &= 5.14 \Omega \end{aligned}$$
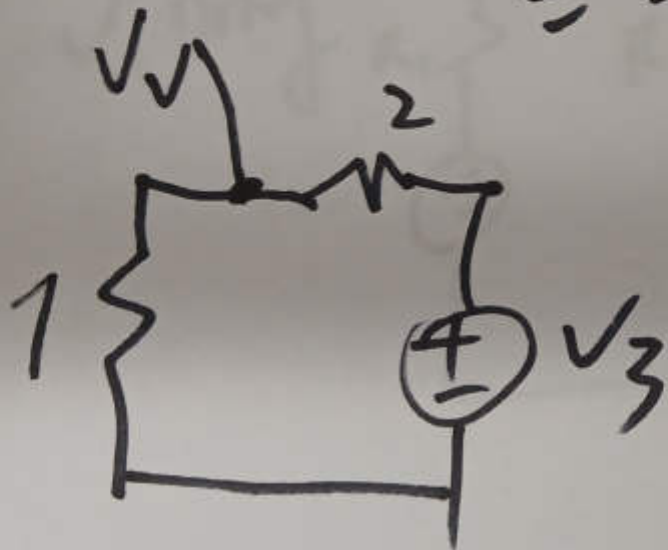
$$\begin{aligned} V_3 &= V_1 \cdot \frac{5.14}{5.14 + 4} \\ &= 14.62 \end{aligned}$$




$$\begin{aligned} V_v &= V_3 \cdot \frac{9}{9 + 12} \\ &= 11.37 \text{ V} \end{aligned}$$

So overall V is

$$V_I + V_v = 1.875 \text{ V} + 11.37 \text{ V}$$

(4)

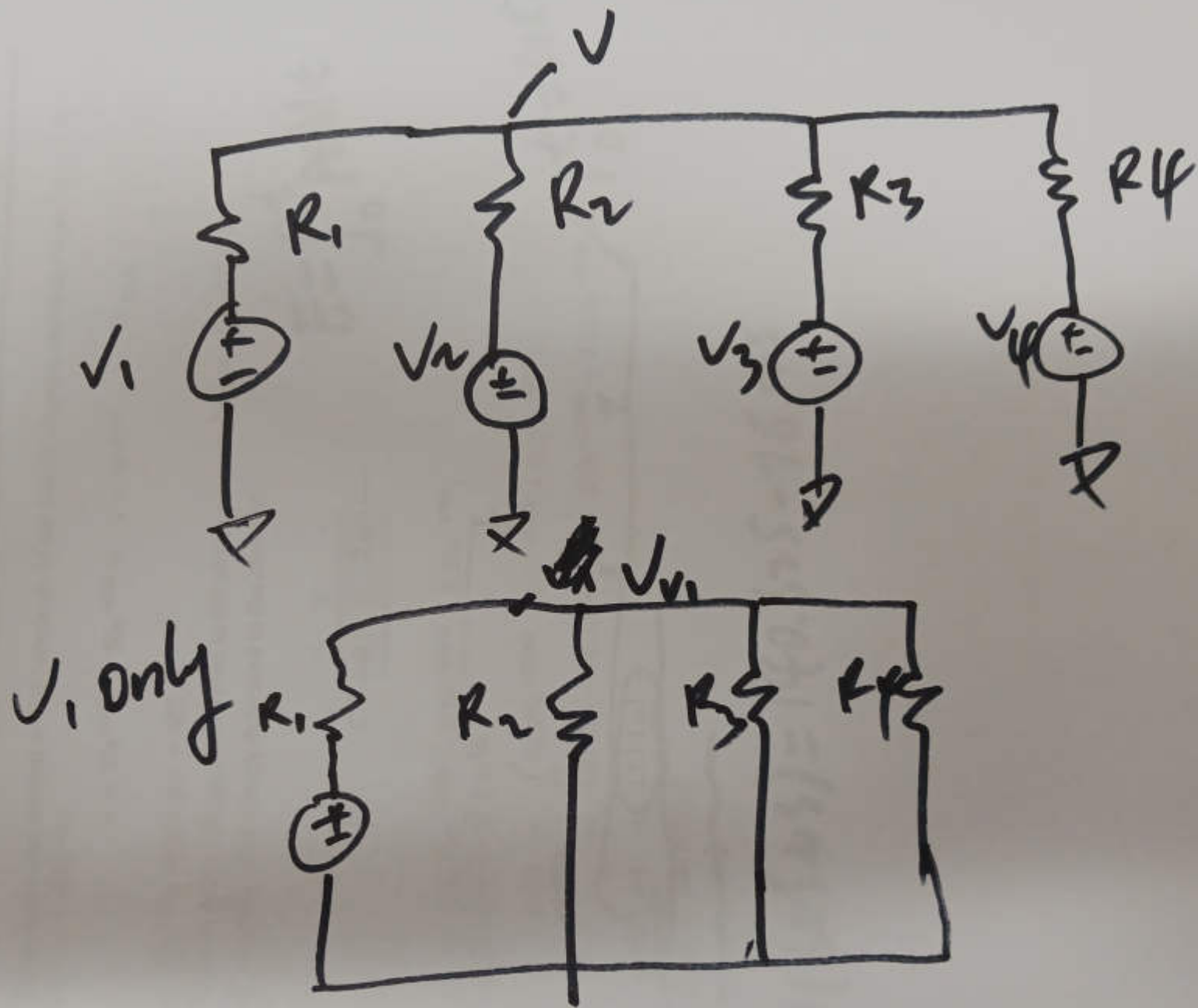

(5)

Colorado School of Mines
Midterm Exam I


Wednesday 10/02/2019 - 2:00 PM - 50 minutes - closed book, closed notes

Q1.

The voltage and current at the terminals of the circuit element shown are zero for $t < 0$. For $t \geq 0$ they are

$$v = 50e^{-1600t} - 50e^{-400t} \text{ V}, \quad i = 5e^{-1600t} - 5e^{-400t} \text{ mA.}$$

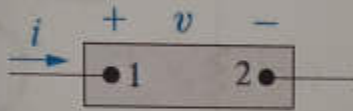- Find the power at $t = 625 \mu\text{s}$.
- How much energy is delivered to the circuit element between 0 and $625 \mu\text{s}$?
- Find the total energy delivered to the element.



$$E = \int_0^t P(t) dt$$

[a] $p = vi = 0.25e^{-3200t} - 0.5e^{-2000t} + 0.25e^{-800t}$;
 $p(625 \mu\text{s}) = 42.2 \text{ mW}$.

[b] $w(t) = \int_0^t (0.25e^{-3200t} - 0.5e^{-2000t} + 0.25e^{-800t})$
 $= 140.625 - 78.125e^{-3200t} + 250e^{-2000t} - 312.5e^{-800t} \mu\text{J}$;

$w(625 \mu\text{s}) = 12.14 \mu\text{J}$.

[c] $w_{\text{total}} = 140.625 \mu\text{J}$.


$$W(625 \mu\text{s}) = 140.625 - 78.125$$

$$\int_0^{t=625 \mu\text{s}}$$


Q2.

For the circuit shown below, find v_o and the total power absorbed in the circuit.

$$20 \cdot \frac{150}{450+150} = v_x$$

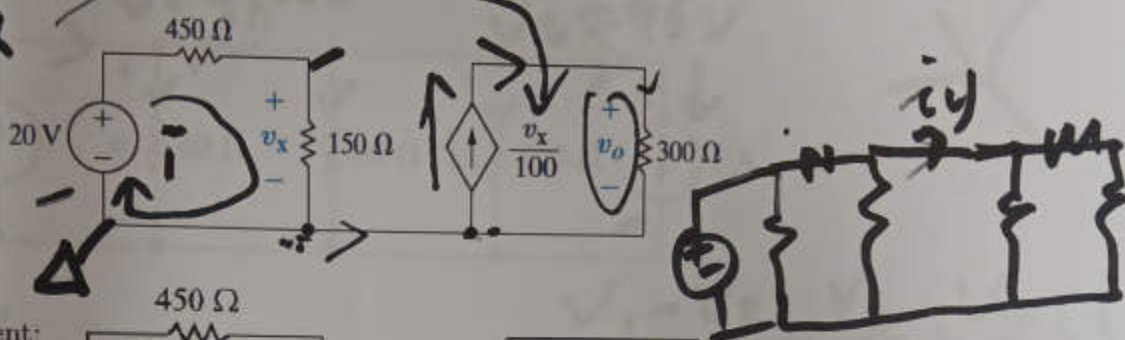

Label unknown current:

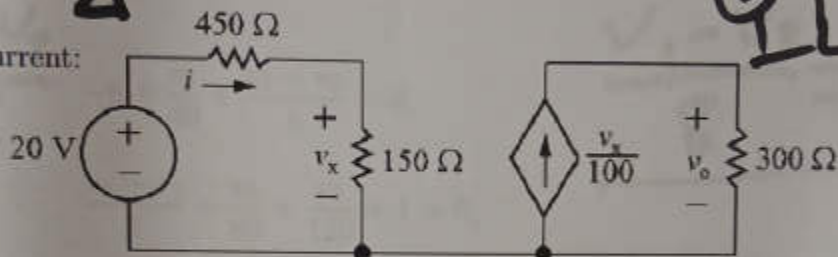

$$-20 + 450i + 150i = 0 \quad (\text{KVL and Ohm's law});$$

$$\text{so } 600i = 20 \rightarrow i = 33.33 \text{ mA.}$$

$$v_x = 150i = 150(0.0333) = 5 \text{ V} \quad (\text{Ohm's law});$$

$$v_o = 300 \left(\frac{v_x}{100} \right) = 300(5/100) = 15 \text{ V} \quad (\text{Ohm's law}).$$

Calculate the power for all components:

$$p_{20V} = -20i = -20(0.0333) = -0.667 \text{ W};$$

$$p_{d.s.} = -v_o \left(\frac{v_x}{100} \right) = -(15)(5/100) = -0.75 \text{ W};$$

$$p_{450} = 450i^2 = 450(0.033)^2 = 0.5 \text{ W};$$

$$p_{150} = 150i^2 = 150(0.033)^2 = 0.1667 \text{ W};$$


$$p_{300} = \frac{v_o^2}{300} = \frac{15^2}{300} = 0.75 \text{ W.}$$

Thus the total power absorbed is $p_{abs} = 0.5 + 0.1667 + 0.75 = 1.4167 \text{ W.}$

$$\begin{aligned} -20 + i \cdot 450 \\ + i \cdot 150 = 0 \end{aligned}$$

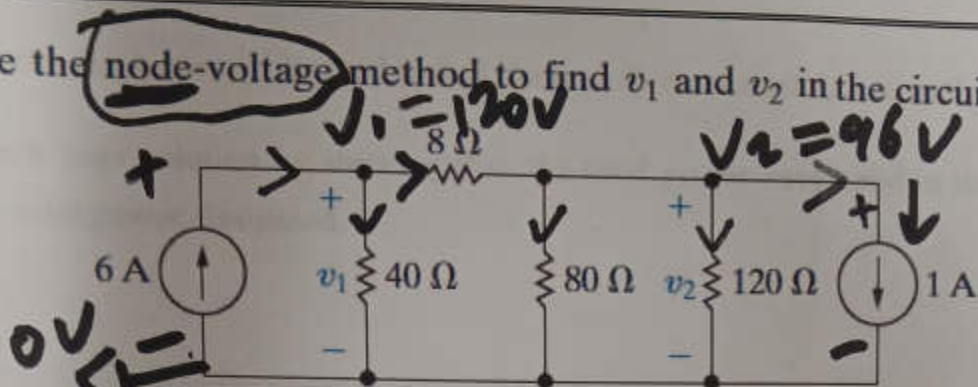Q3.

Use the node-voltage method to find v_1 and v_2 in the circuit below.



$$6 = \frac{v_1}{40} + \frac{v_1 - v_2}{8}$$

$$-6 + \frac{v_1}{40} + \frac{v_1 - v_2}{8} = 0;$$

$$\frac{v_1 - v_2}{8} = \frac{v_2}{80} + \frac{v_2}{120} + 1$$

$$\frac{v_2 - v_1}{8} + \frac{v_2}{80} + \frac{v_2}{120} + 1 = 0;$$

Solving, $v_1 = 120$ V; $v_2 = 96$ V.

CHECK:

$$p_{40\Omega} = \frac{(120)^2}{40} = 360 \text{ W};$$

$$p_{8\Omega} = \frac{(120 - 96)^2}{8} = 72 \text{ W};$$

$$p_{80\Omega} = \frac{(96)^2}{80} = 115.2 \text{ W};$$


$$p_{120\Omega} = \frac{(96)^2}{120} = 76.8 \text{ W};$$

$$p_{6A} = -(6)(120) = -720 \text{ W};$$

$$p_{1A} = (1)(96) = 96 \text{ W};$$

$$\sum p_{abs} = 360 + 72 + 115.2 + 76.8 + 96 = 720 \text{ W};$$

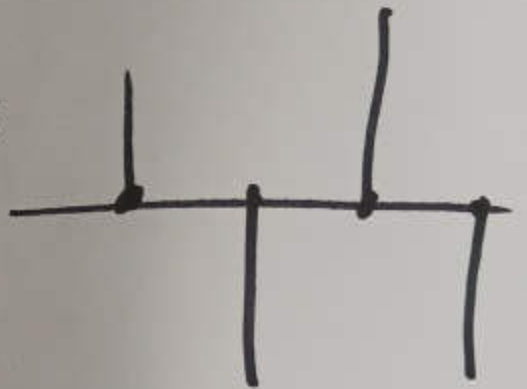
$$\sum p_{dev} = 720 \text{ W (CHECKS)}.$$



Q4.

- a) Use the mesh-current method to find the branch currents in $i_a - i_e$ in the circuit below.
- b) Check your solution by showing that the total power developed in the circuit equals the total power dissipated.

[a]

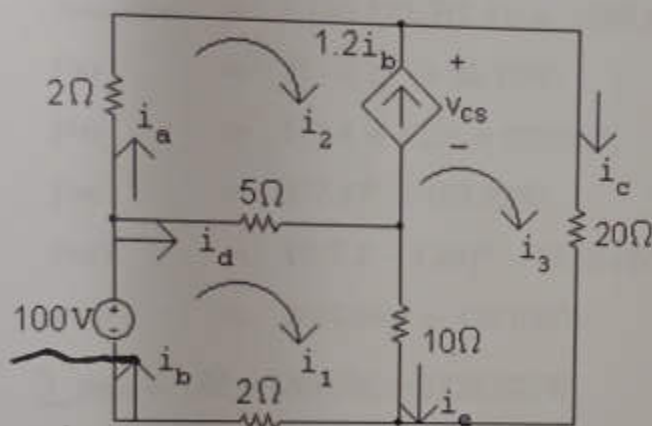

The i_1 mesh current equation:

$$-100 + 5(i_1 - i_2) + 10(i_1 - i_3) + 2i_1 = 0.$$

The $i_2 - i_3$ supermesh equations:

$$2i_2 + 20i_3 + 10(i_3 - i_1) + 5(i_2 - i_1) = 0.$$

The supermesh constraint:

$$i_3 - i_2 = 1.2i_b = 1.2i_1.$$

Place these equations in standard form:

$$i_1(5 + 10 + 2) + i_2(-5) + i_3(-10) = 100;$$

$$i_1(-10 - 5) + i_2(2 + 5) + i_3(20 + 10) = 0;$$

$$i_1(1.2) + i_2(1) + i_3(-1) = 0.$$

Solving, $i_1 = 7.4\text{A}; \quad i_2 = -4.2\text{A}; \quad i_3 = 4.68\text{A}.$

Solve for the requested currents:

$$i_a = i_2 = -4.2\text{A};$$

$$i_b = i_1 = 7.4\text{A};$$

$$i_c = i_3 = 4.68\text{A};$$

$$i_d = i_1 - i_2 = 11.6\text{A};$$

$$i_e = i_1 - i_3 = 2.72\text{A}.$$

[b] Find v_{cs} :

$$2i_2 + v_{cs} + 5(i_2 - i_1) = 0$$

$$\therefore v_{cs} = -2(-4.2) - 5(-4.2 - 7.4) = 66.4V.$$

Calculate the power:

$$P_{100V} = -(100)(7.4) = -740W;$$

$$P_{dep\ source} = -(66.4)[1.2(7.4)] = -589.632W;$$

$$P_{2\Omega} = 2(-4.2)^2 = 35.28W;$$

$$P_{5\Omega} = 5(7.4 + 4.2)^2 = 672.8W;$$

$$P_{2\Omega} = 2(7.4)^2 = 109.52W;$$

$$P_{10\Omega} = 10(7.4 - 4.68)^2 = 73.984W;$$

$$P_{20\Omega} = 20(4.68)^2 = 438.048W.$$

$$\sum P_{dev} = 740 + 589.632 = 1329.632W;$$

$$\sum P_{dis} = 35.28 + 672.8 + 109.52 + 73.984 + 438.048 = 1329.632W.$$
