

Inverting configuration

negative feedback
 Infinite open loop gain ∞

$$\frac{V_{in} - 0}{R_1} = \frac{0 - V_o}{R_f}$$


$$V_{in} R_f = -R_1 V_o$$

$$\frac{V_o}{V_{in}} = -\frac{R_f}{R_1}$$

TIA \rightarrow Transimpedance Amplifier
 Current \rightarrow Voltage


1Mx1M
 CMOS imager

Photodiode

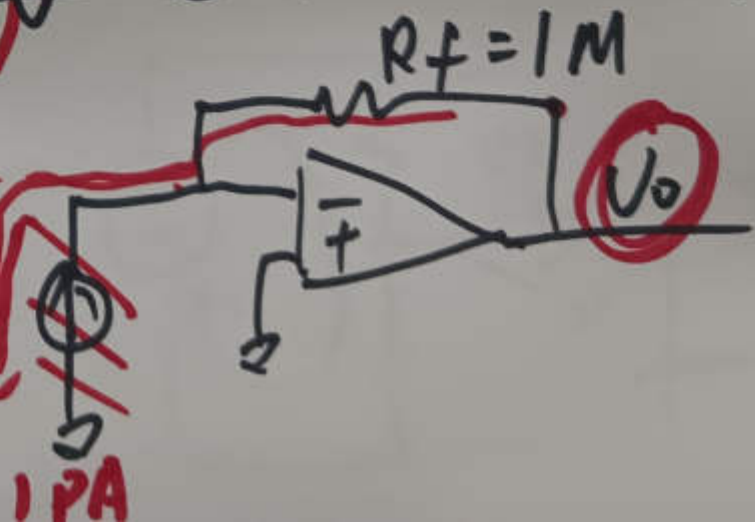

①

1 pA

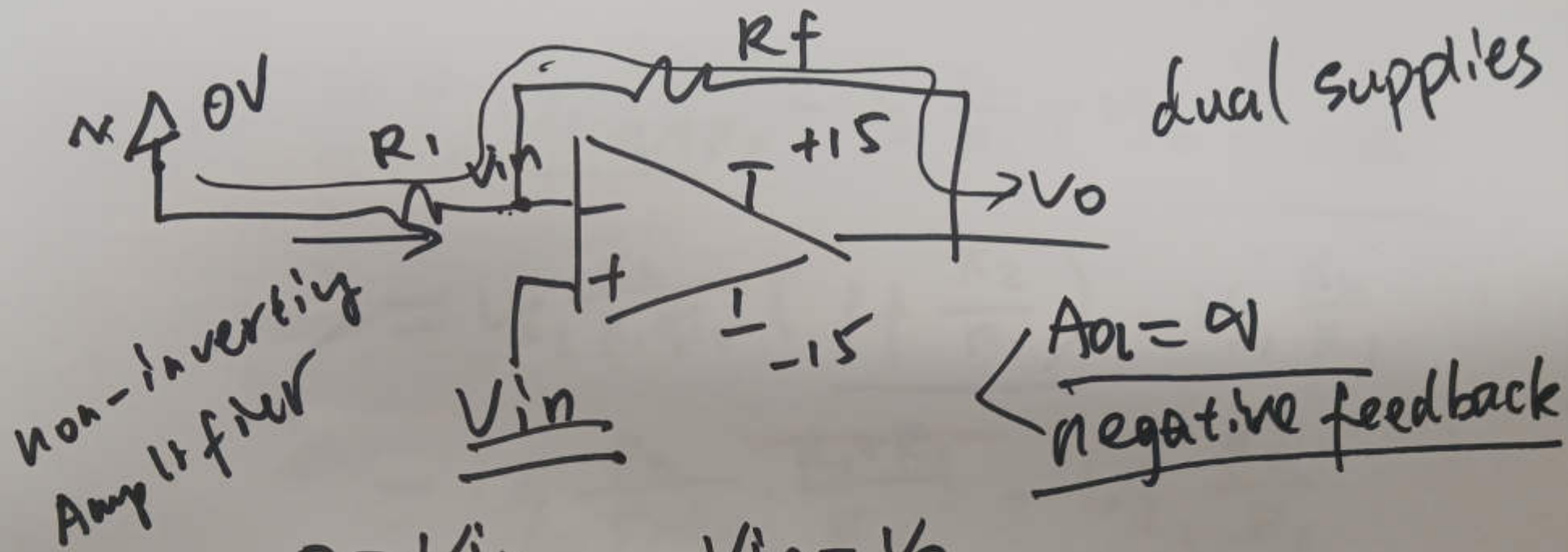




$$\frac{0 - V_{in}}{R_i} = \frac{V_{in} - V_o}{R_f}$$

$$-V_{in} R_f = V_{in} R_i - V_o R_i$$

$$V_o R_i = V_{in} (R_f + R_i)$$


$$\boxed{\frac{V_o}{V_{in}} = \frac{R_f + R_i}{R_i} = 1 + \frac{R_f}{R_i}}$$

(2)

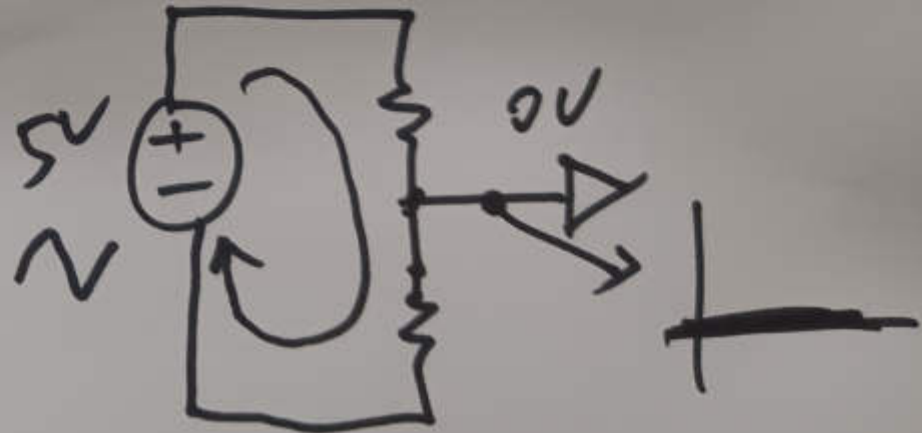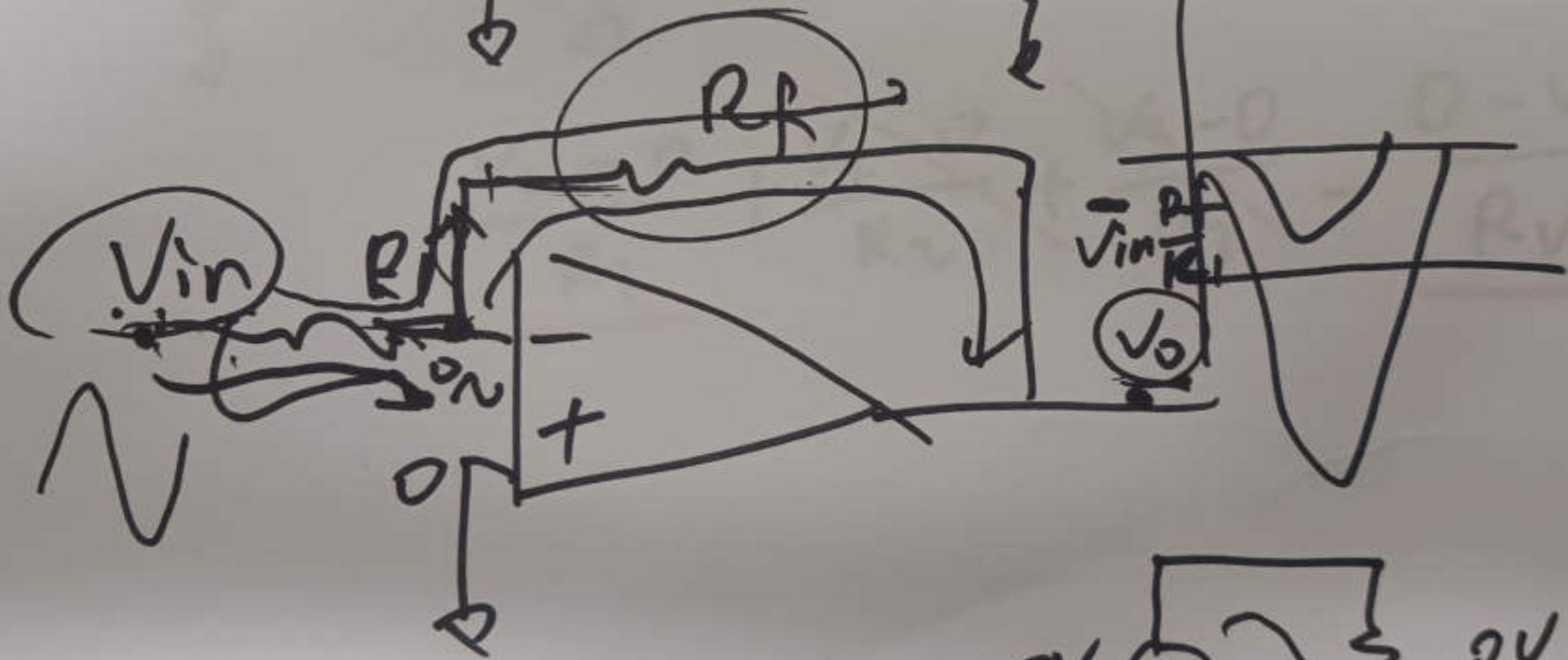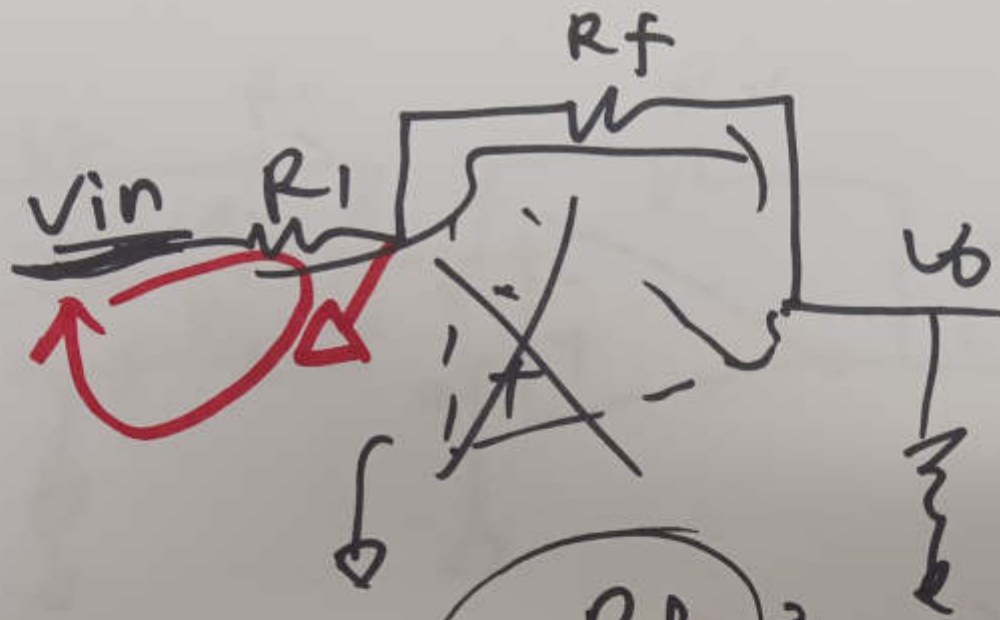

(3)


Load 500Ω

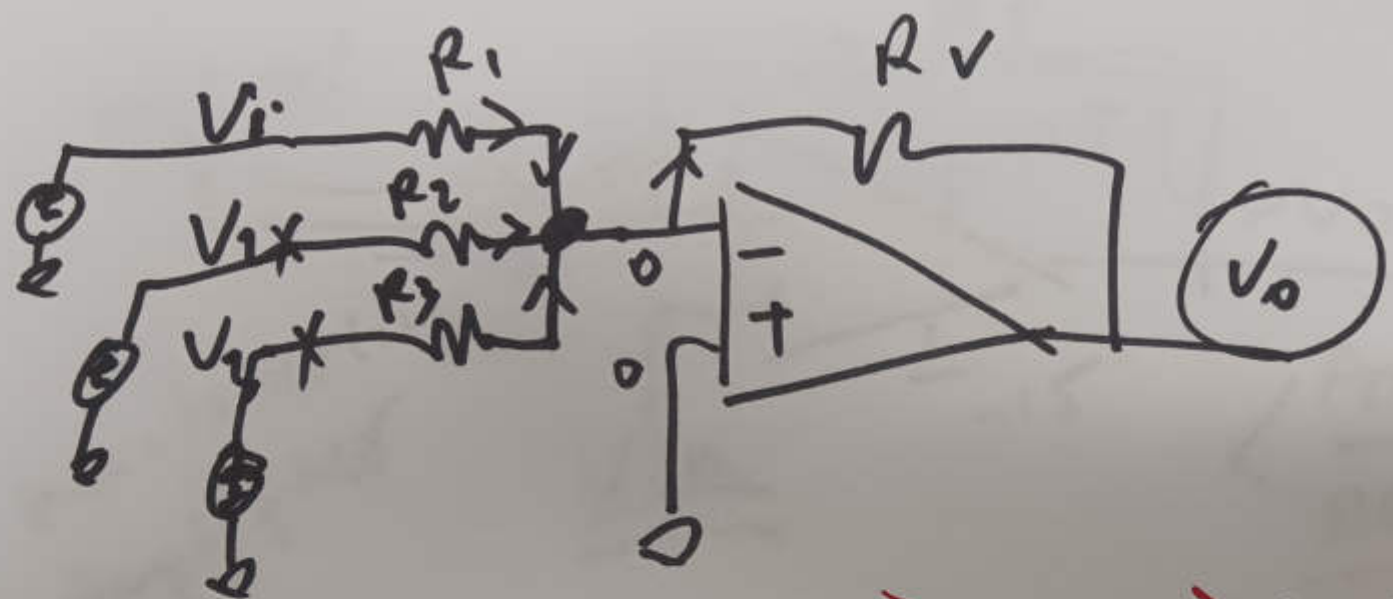


$$\frac{V_1 - 0}{R_1} + \frac{V_2 - 0}{R_2} + \frac{V_3 - 0}{R_3} = \frac{0 - V_0}{R_V}$$

$$\frac{V_0}{V_{in}} = \frac{R_F + R_1}{R_1} = 1 + \frac{R_F}{R_1} \quad \text{or } A_v$$

(4)

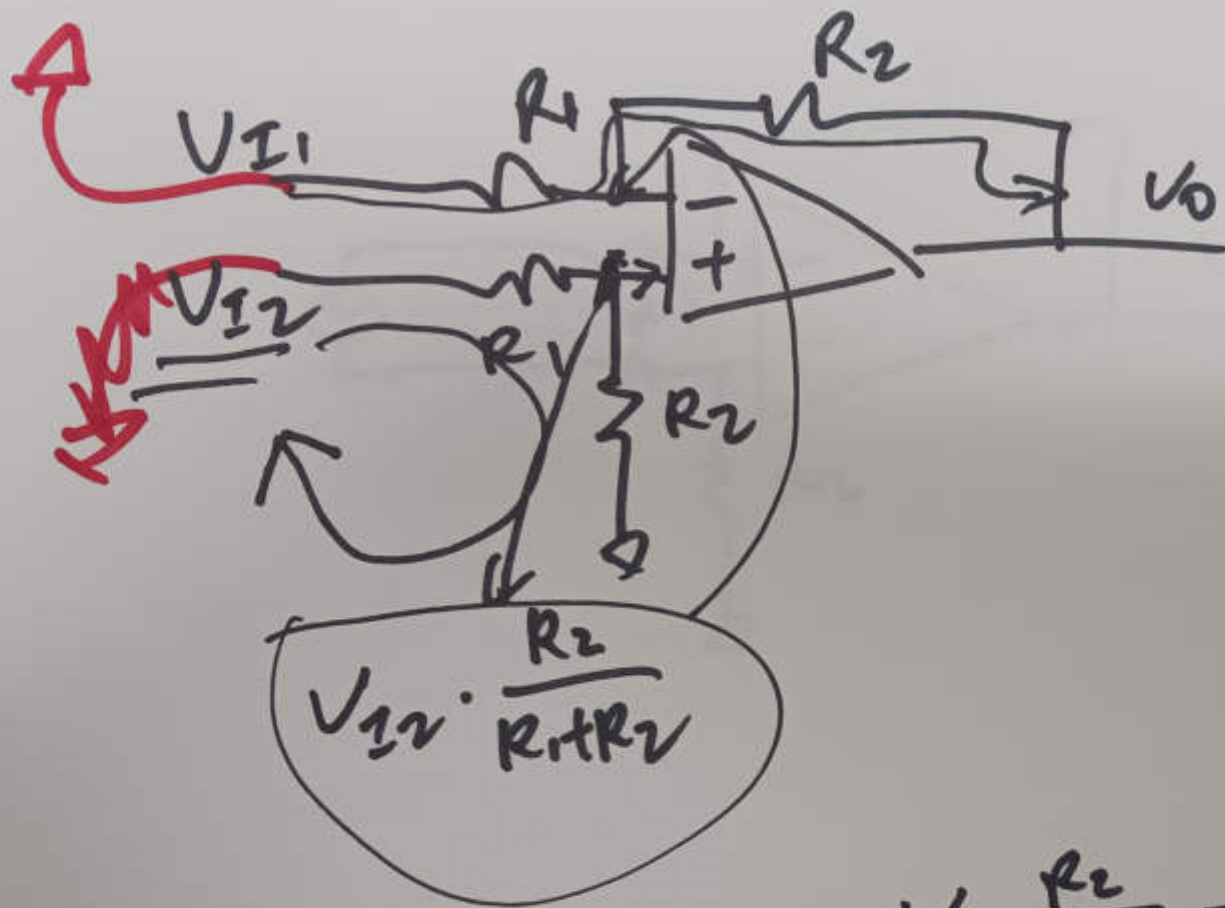

Difference/Differential Amplifier

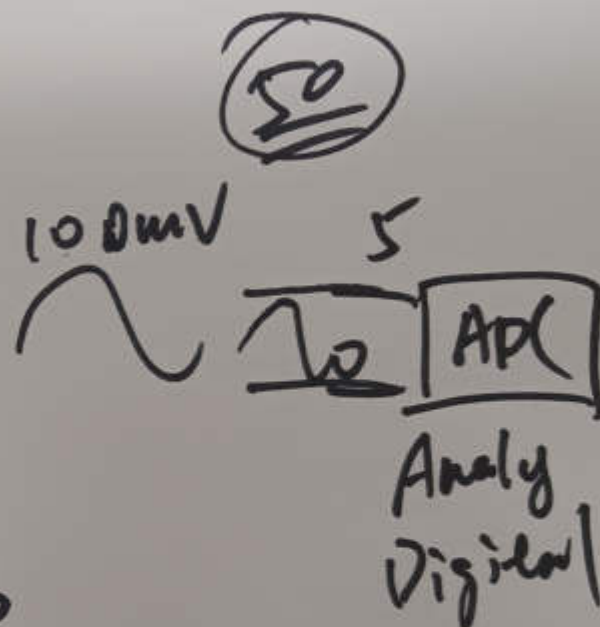

$$\frac{V_{I1} - V_{I2} \cdot \frac{R_2}{R_1 + R_2}}{R_1} = \frac{V_{I2} \cdot \frac{R_2}{R_1 + R_2} - V_O}{R_2}$$

$$V_{I1} \cdot R_2 - V_{I2} \frac{R_2^2}{R_1 + R_2} = V_{I2} \frac{R_1 R_2}{R_1 + R_2} - V_O R_1$$

$$V_O R_1 = V_{I2} \frac{R_1 R_2}{R_1 + R_2} - V_{I1} R_2 + V_{I2} \frac{R_2^2}{R_1 + R_2}$$

(5)

$$V_0 = \underline{V_{I_2} \frac{R_2}{R_1 + R_2}} - V_{I_1} \frac{R_2}{R_1} + \underline{V_{I_2} \frac{R_2}{R_1 (R_1 + R_2)}}$$


$$= V_{I_2} \frac{R_2}{R_1 + R_2} \left(\underline{1 + \frac{R_2}{R_1}} \right) - V_{I_1} \frac{R_2}{R_1}$$

$$= V_{I_2} \frac{R_2}{\cancel{R_1 + R_2}} \cdot \frac{\cancel{R_1 + R_2}}{R_1} - V_{I_1} \frac{R_2}{R_1}$$

$$= V_{I_2} \cdot \frac{R_2}{R_1} - V_{I_1} \frac{R_2}{R_1}$$

$$= \left(\cancel{V_{I_2}} - \cancel{V_{I_1}} \right) \left(\frac{R_2}{R_1} \right)$$

(6)

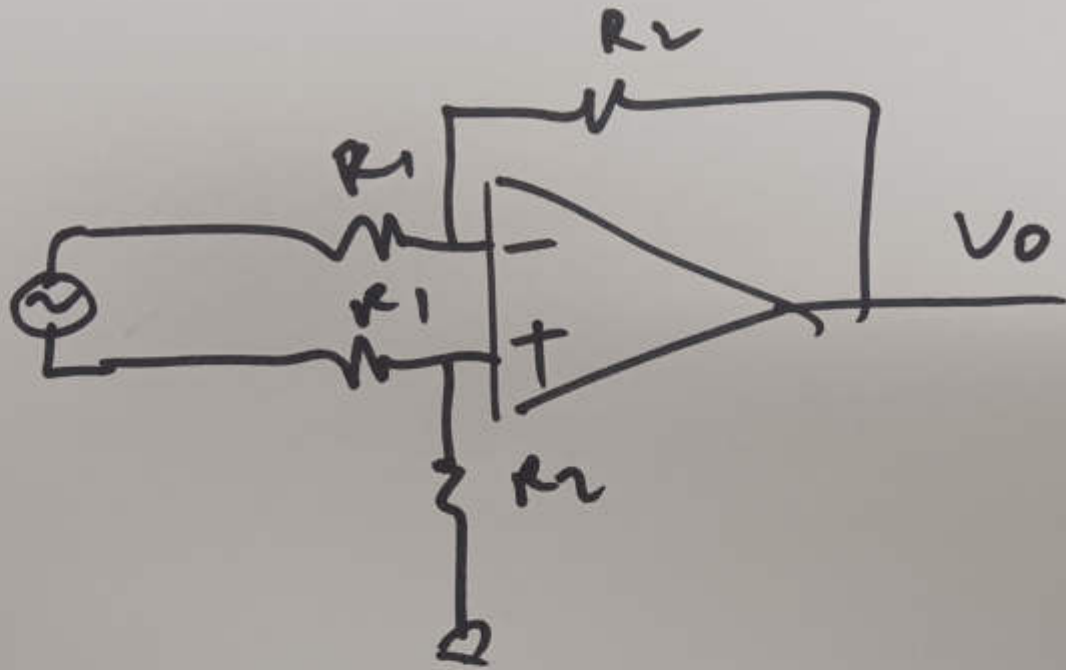

⑦