
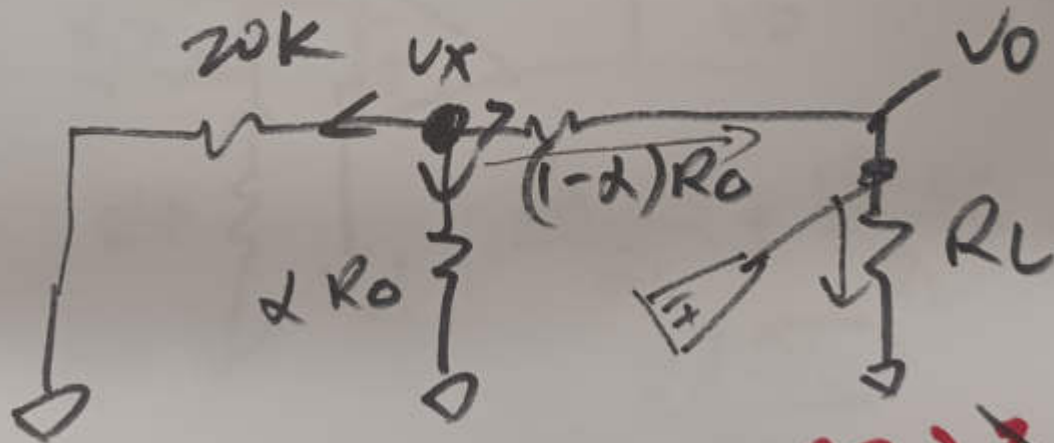


$$V_x = 0.6 \cdot \frac{20k}{4k} = -0.3V$$
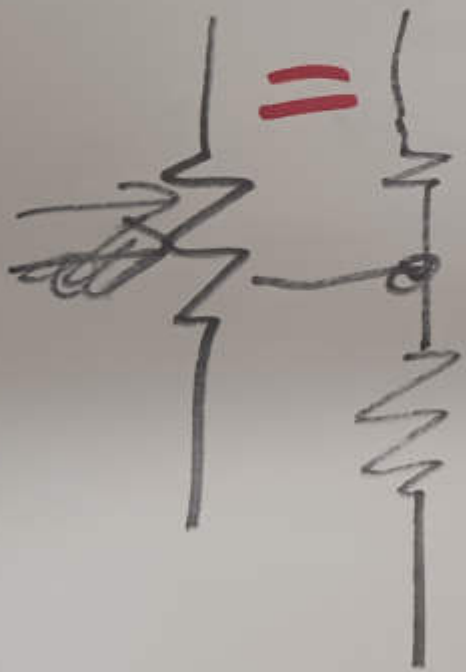
$$V_o = V_x \cdot \frac{R_L}{R_L + (1-\alpha)R_o}$$



$$\frac{V_o}{V_{in}} = \frac{(R_2) \cdot I}{(R_1 + R_2) \cdot I}$$


$V_o = R_2 \cdot I$

①

$$\frac{V_x - 0}{20K} + \frac{V_x}{\alpha R_0} + \frac{V_x - V_0}{(1-\alpha)R_0} = 0$$

\leftarrow $\begin{matrix} +12 \\ -12 \end{matrix}$

$$0.25 < \alpha < 0.8$$


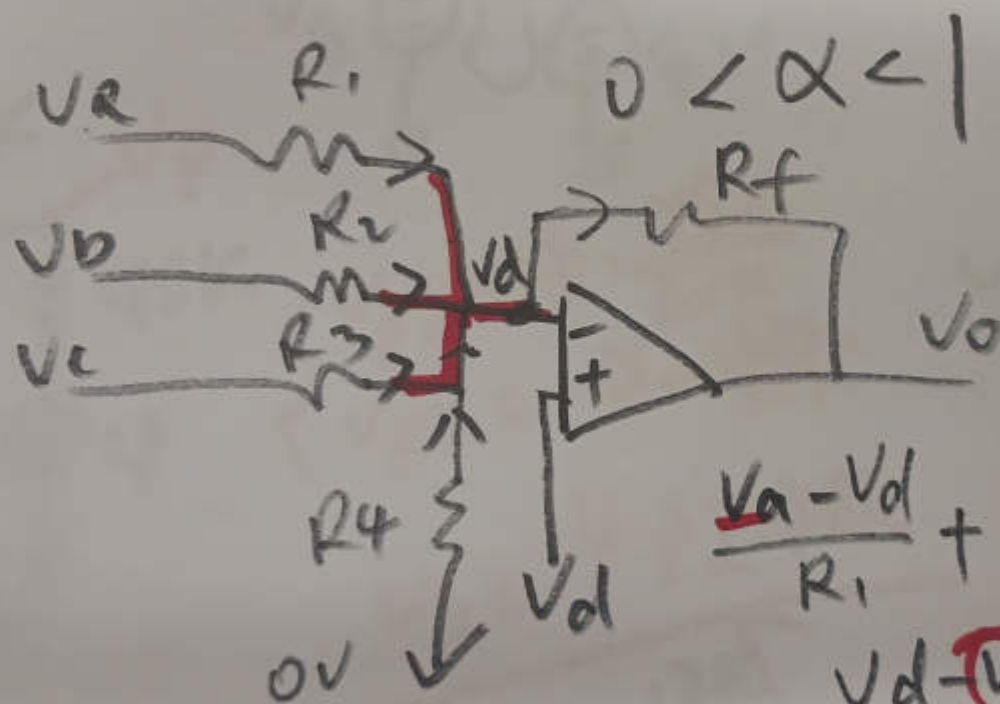


negative feedback
infinite
AOL

$$\frac{V_a - V_d}{R_1} + \frac{V_b - V_d}{R_2} + \frac{V_c - V_d}{R_3} + \frac{0 - V_d}{R_4}$$

$$= \frac{V_d - V_0}{R_f}$$

(1)

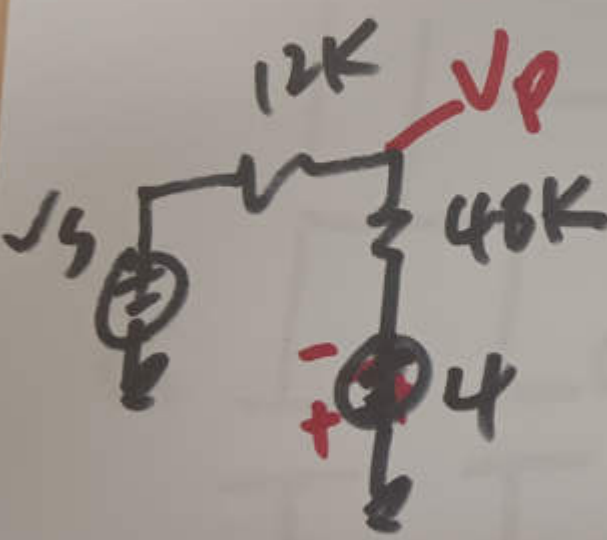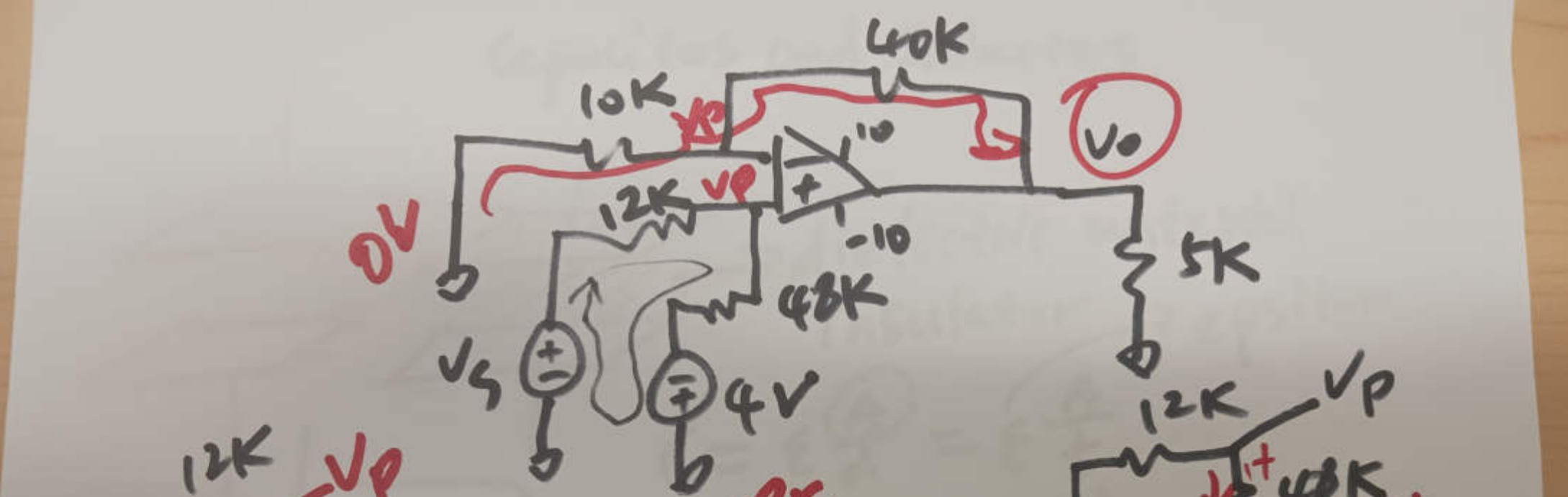


$$V_{p1} = V_s \cdot \frac{48K}{60K}$$

$$V_{p2} = -4 \cdot \frac{12K}{60K}$$

$$V_p = -4 + I \cdot 48K$$
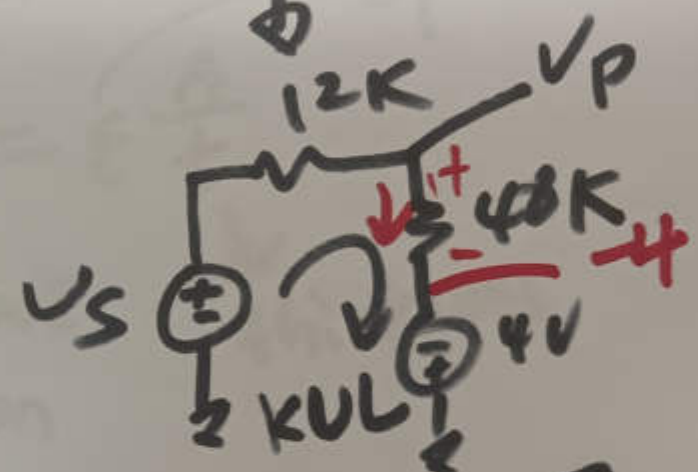
$$V_p = V_s \cdot \frac{48K}{60K} + (4) \cdot \frac{12K}{60K}$$




$$-V_s + I \cdot 12K + I \cdot 48K - 4V = 0$$

$$I = \frac{V_s + 4}{60K}$$

3

Capacitors and Inductors

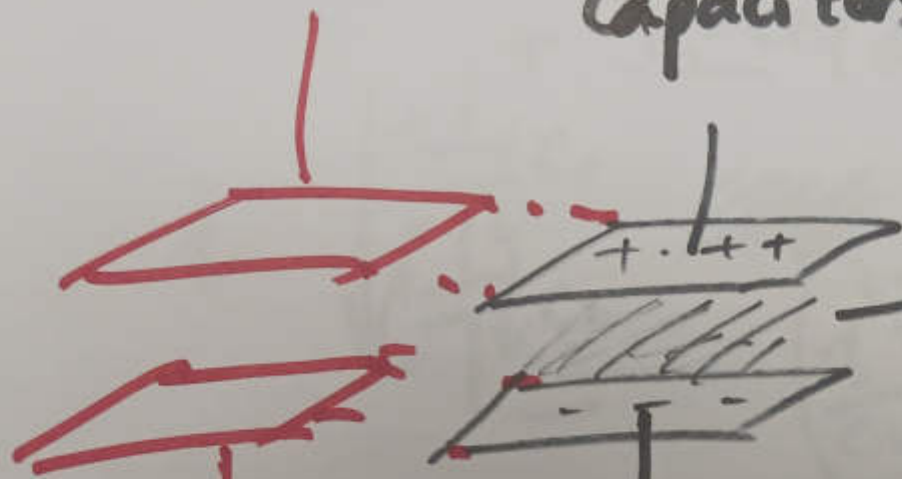

dielectric material
insulator → epsilon


$$C = \epsilon \frac{A}{d} = \epsilon \frac{A}{t}$$

distance

between

the two plates

↓
thickness




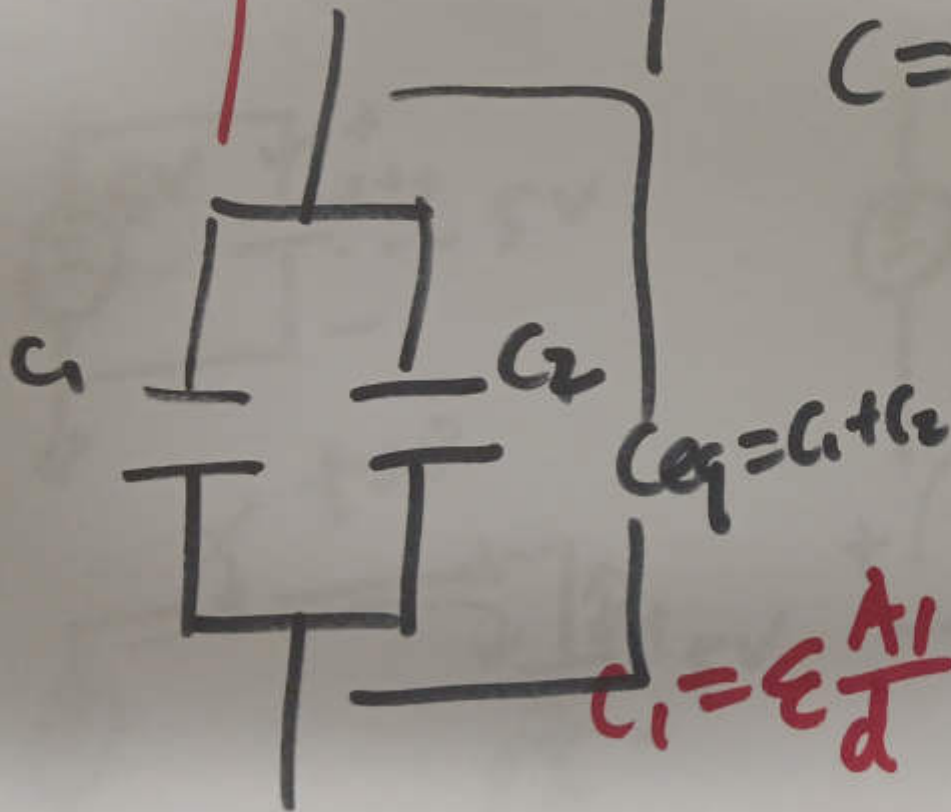


$$C_1 = \epsilon \frac{A_1}{d}$$

$$C_2 = \epsilon \frac{A_2}{d}$$

$$C_1 + C_2 = \frac{\epsilon}{d} (A_1 + A_2)$$

(A)

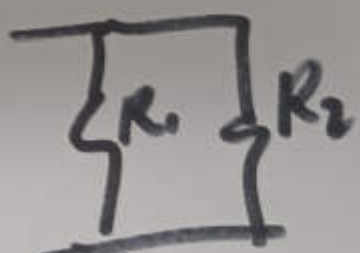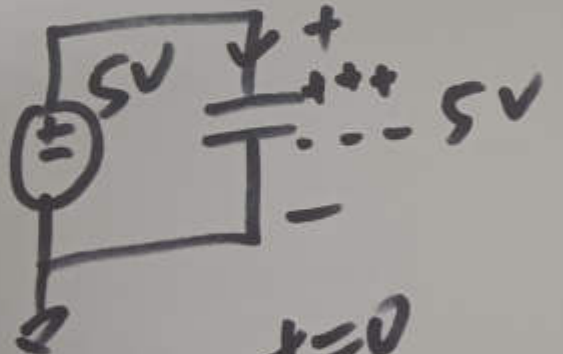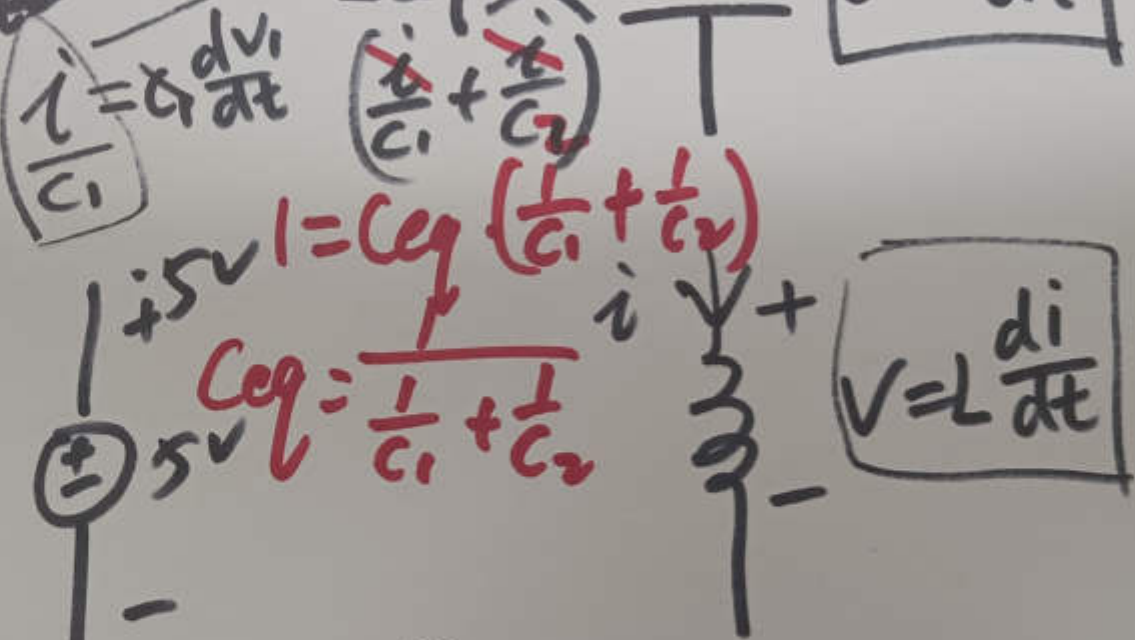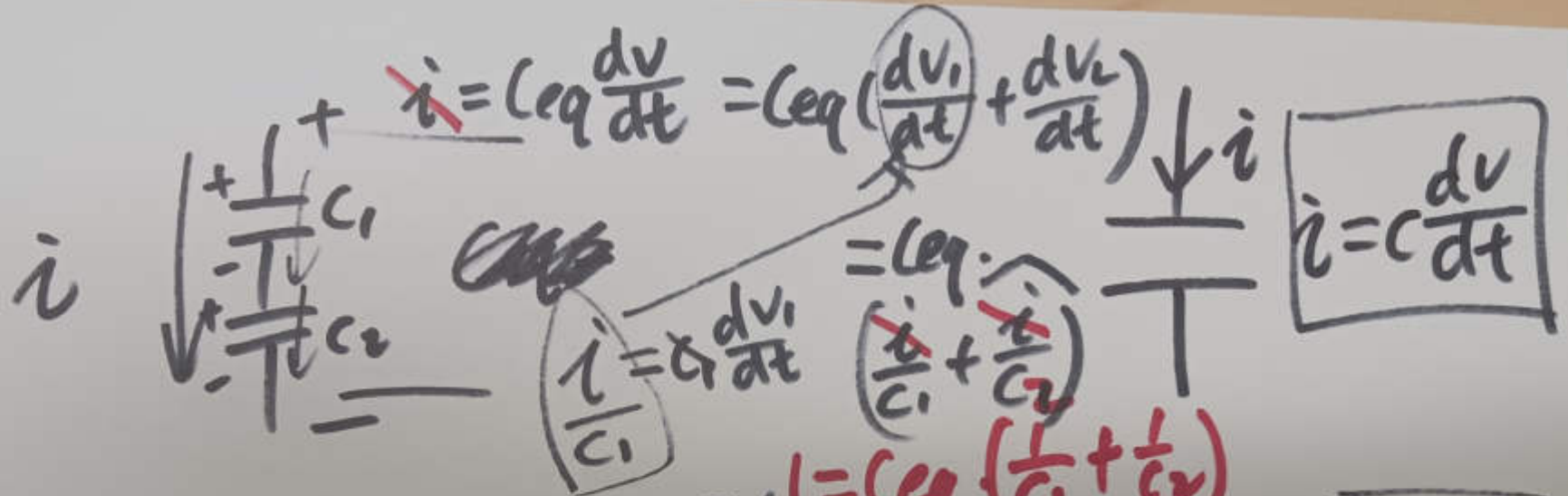

$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$

