
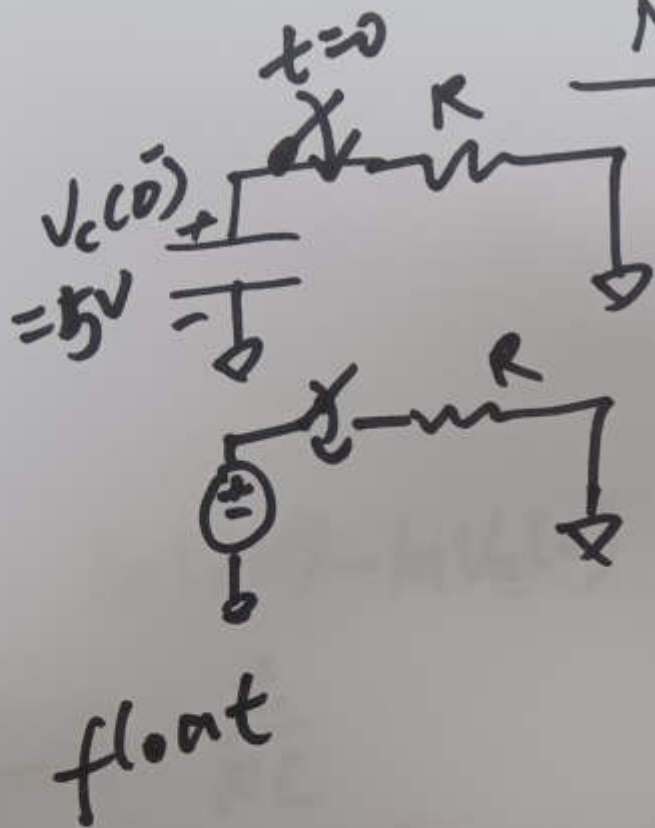


Natural Response

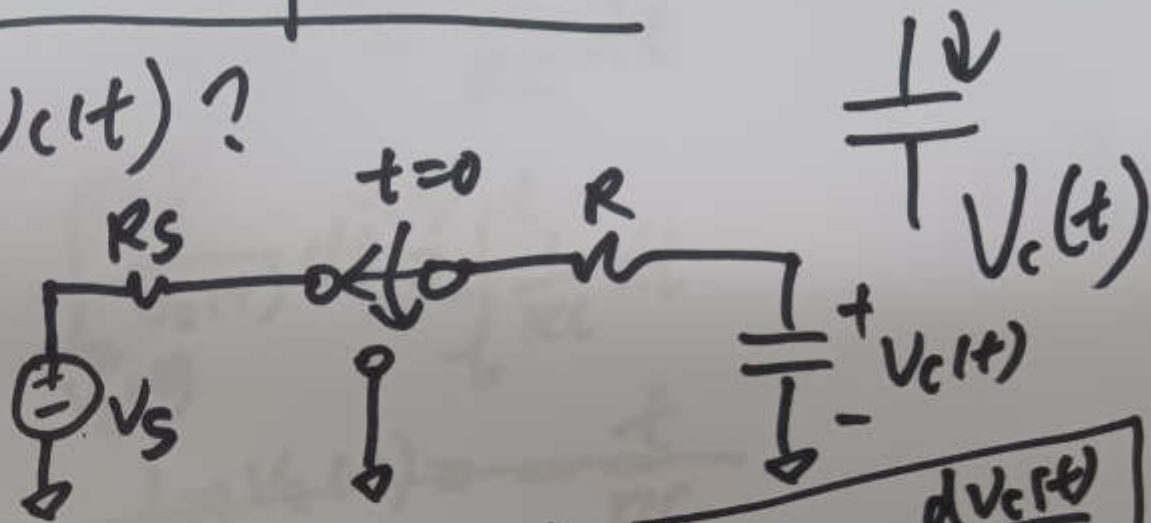


$V_C(t) ?$



$i_C(t)$

$$i_C(t) = C \frac{dV_C(t)}{dt}$$

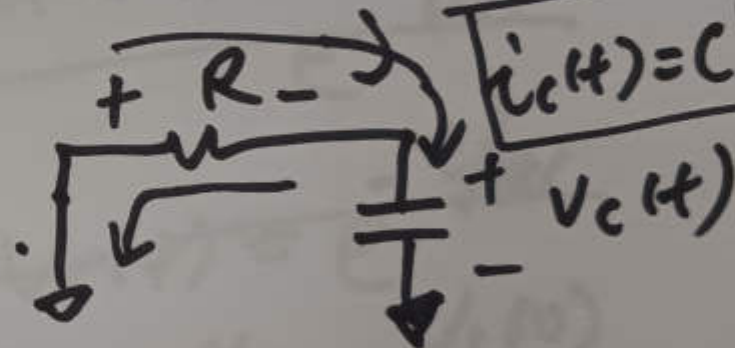

KVL:

$$R \cdot i_C(t) + V_C(t) = 0$$

$$R \cdot C \frac{dV_C(t)}{dt} + V_C(t) = 0$$

$$RC \frac{dV_C(t)}{dt} = -V_C(t)$$

$$\frac{1}{V_c(t)} dV_c(t) = -\frac{1}{RC} dt$$

$$\int_{V_c(0)}^{V_c(t)} \frac{1}{V_c(t)} dV_c(t) = -\int_0^t \frac{1}{RC} dt$$

$$\ln V_c(t) - \ln V_c(0) = -\frac{t}{RC}$$

$$\ln V_c(t) - \ln V_c(0)$$

$$= -\frac{t}{RC}$$

$$\Rightarrow \ln \frac{V_c(t)}{V_c(0)} = -\frac{t}{RC}$$

$$\Rightarrow \frac{V_c(t)}{V_c(0)} = e^{-t/RC}$$

$$V_c(t) = V_c(0) \cdot e^{-t/RC}$$

$$V_c(t) = e^{-t/RC} V_c(0)$$




$$e = 2.7 \quad \begin{matrix} \uparrow \\ -t/RC \\ \downarrow \end{matrix}$$

$2.7^{-1} = 0.36$



(2)

step response (Forced Response)

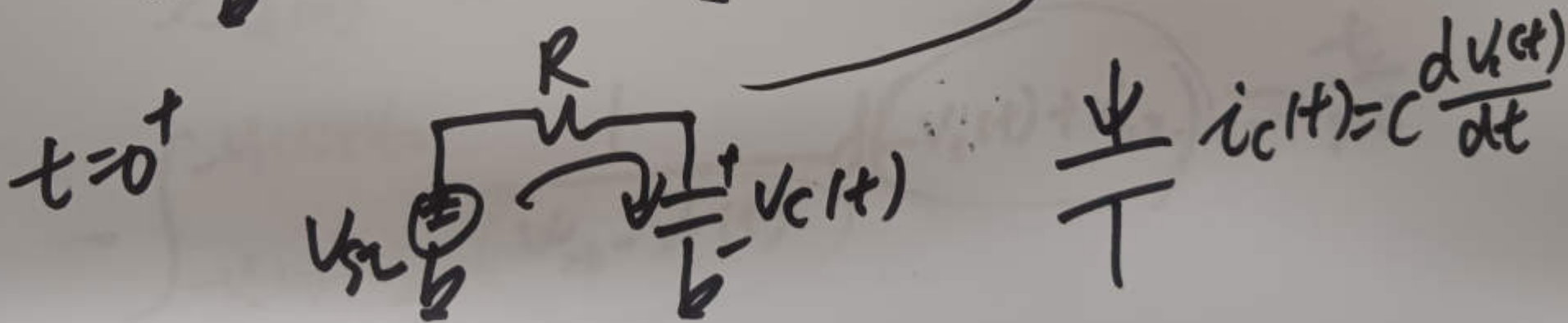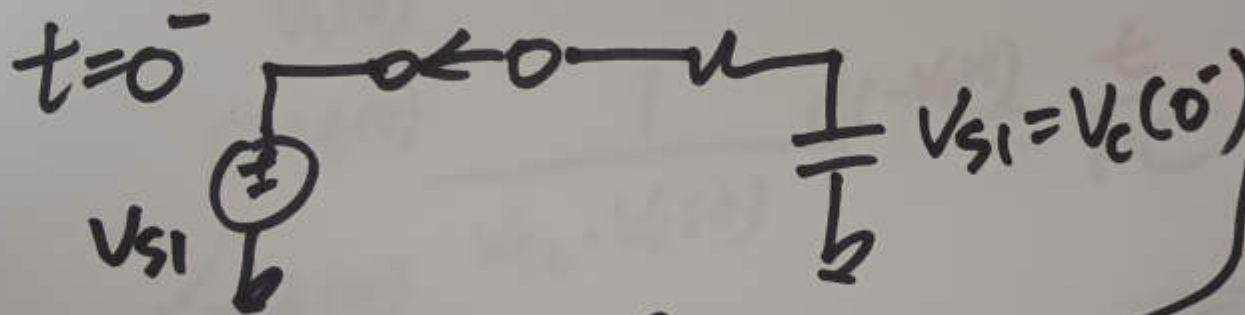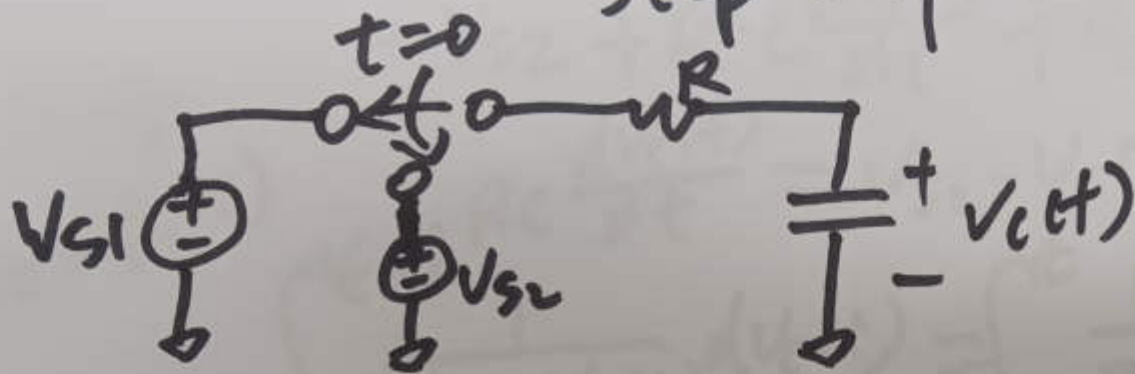

$$v_C(t) = \frac{1}{C} \int i_C(t) dt$$

(3)

$$V_c(0) = V_{s1}$$

$$V_{s2} = V_c(\infty)$$

$$-V_{s2} + R \cdot C \frac{dV_c(t)}{dt} + V_c(t) = 0$$

~~a + bj + y = 0~~

$$RC \frac{dV_c(t)}{dt} = V_{s2} - V_c(t)$$

$$\int_{V_c(0)}^{V_c(t)} \frac{1}{V_{s2} - V_c(t)} dV_c(t) = \int_0^t \frac{1}{RC} dt$$

$$-\int_{-V_c(0)}^{-V_c(t)} \frac{1}{V_{s2} - V_c(t)} d(-V_c(t)) = \frac{t}{RC}$$

$$-\int_{-V_c(0) + V_{s2}}^{-V_c(t) + V_{s2}} \frac{1}{V_{s2} - V_c(t)} d(-V_c(t) + V_{s2}) = \frac{t}{RC}$$

(4)

$$\frac{-V_C(t) + V_{S2}}{-V_C(0) + V_{S2}} = e^{-\frac{t}{RC}}$$

$$\frac{-V_C(t) + V_{S2}}{-V_C(0) + V_{S2}} = e^{-t/RC}$$

$$-V_C(t) + V_{S2} = (-V_C(0) + V_{S2}) e^{-t/RC}$$

$$V_C(t) = V_{S2} - (-V_C(0) + V_{S2}) e^{-t/RC}$$

$$= V_{S2} + (V_C(0) - V_{S2}) e^{-t/RC}$$


$$V_C(t) = V_C(\infty) + (V_C(0) - V_C(\infty)) e^{-t/RC}$$

5


$V_c(0) = 0$
 Special case for step response

$$\begin{aligned}
 V_c(t) &= V_c(\infty) + (0 - V_c(\infty))e^{-t/RC} \\
 &= V_c(\infty) - V_c(\infty)e^{-t/RC} \\
 &= V_c(\infty)(1 - e^{-t/RC})
 \end{aligned}$$

RC unit is time
 ↳ time constant

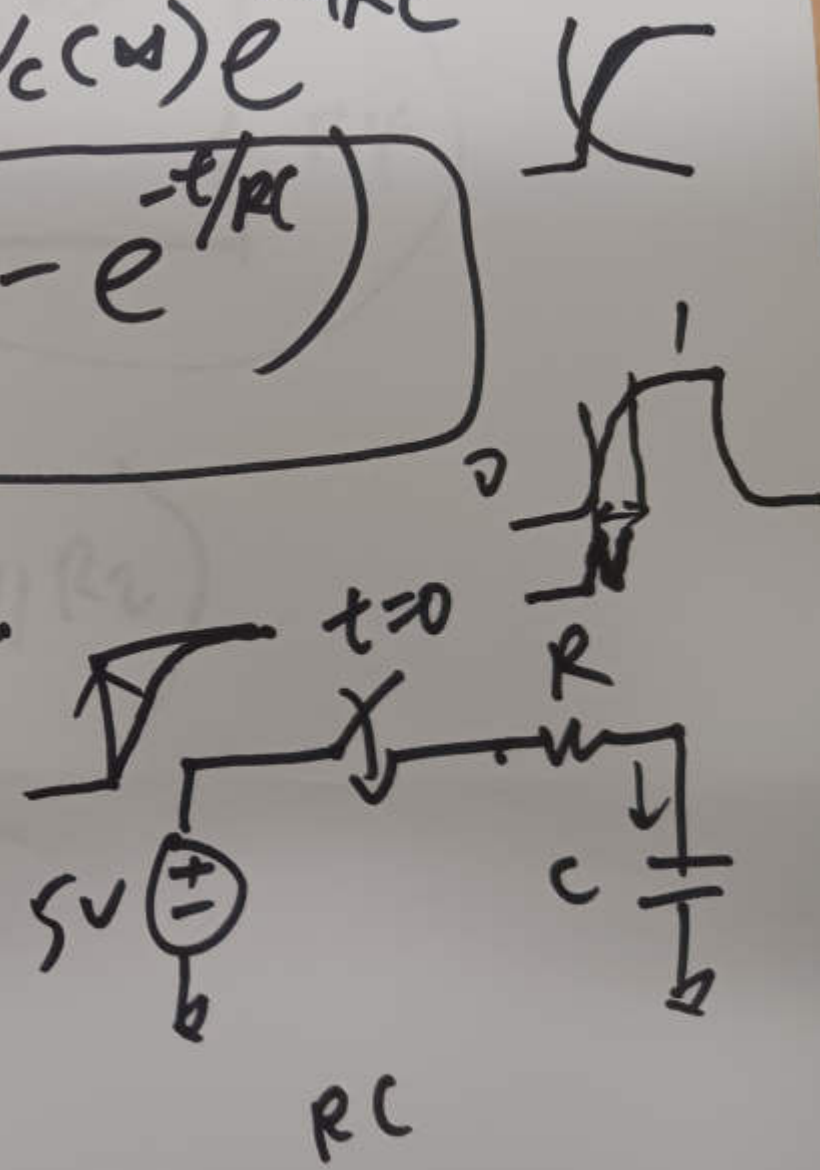

Q6

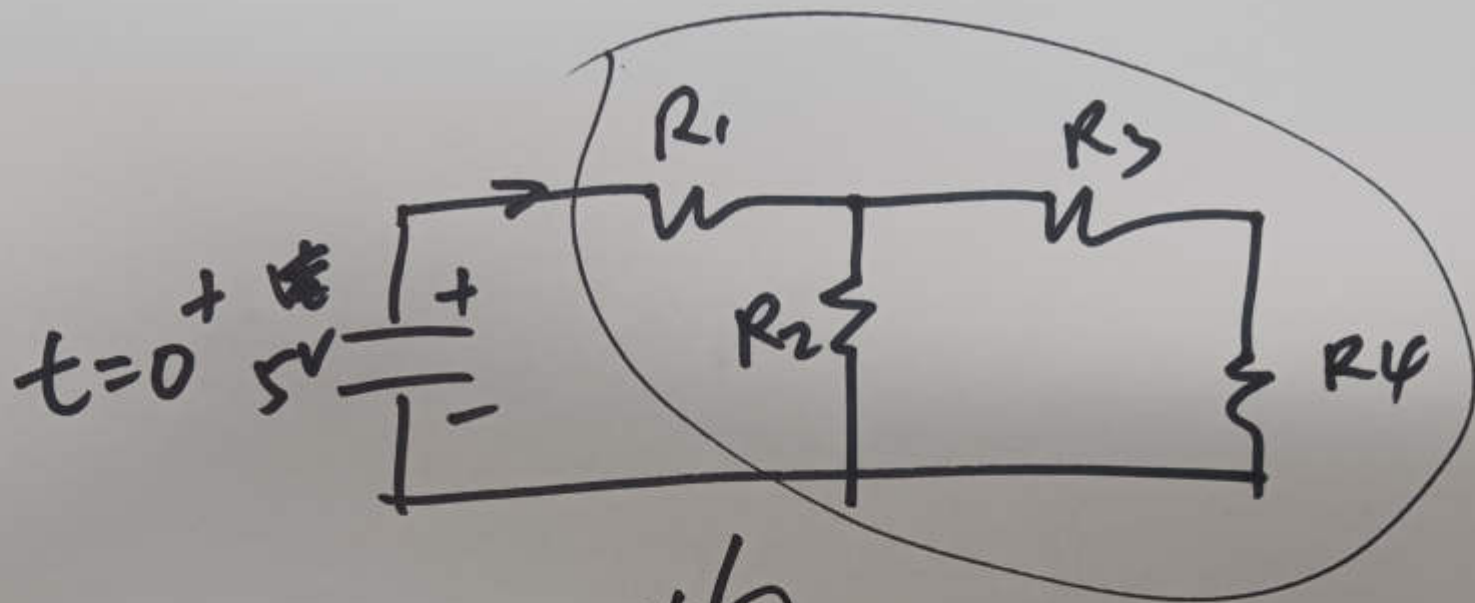

$$v_C(t) = V_C(0) e^{-t/\tau}$$

$$\tau = R_{TH} = R_1 + (R_3 + R_4) \parallel R_2$$