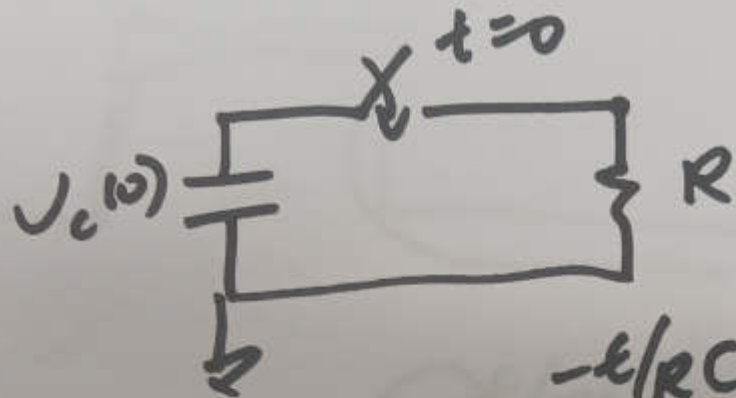



$$I_c(t) = C \frac{dV_c(t)}{dt} \quad \textcircled{1}$$



Natural Response

$$V_c(t) = V_c(0) e^{-t/RC} \rightarrow \text{time constant}$$

②

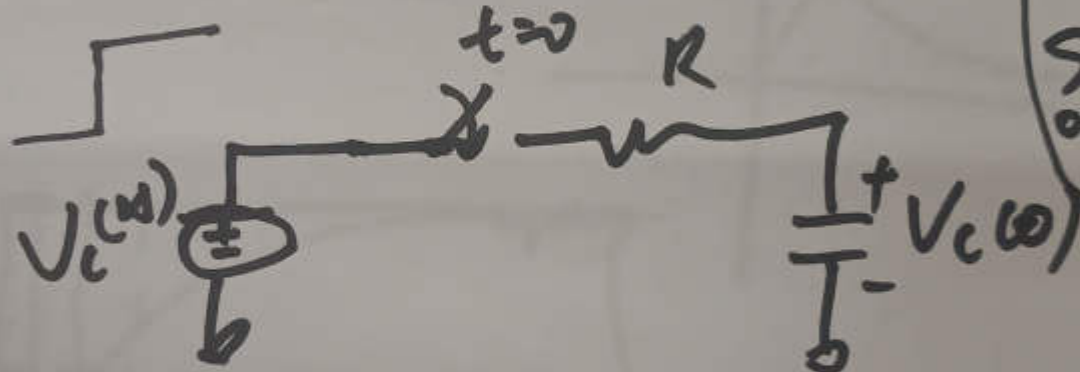


Step Response or Forced Response

$$V_c(t) = V_c(\infty) + (V_c(0) - V_c(\infty)) e^{-t/RC}$$



$$\textcircled{3} \quad V_c(0) = 0, \quad V_c(t) = V_c(\infty) \left(1 - e^{-t/RC} \right)$$

①

Steady State Response

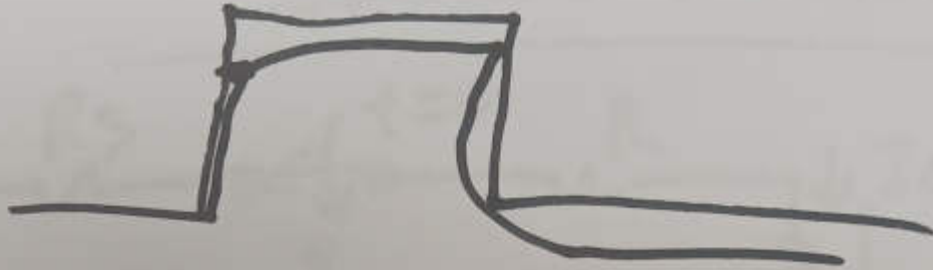


$\frac{1}{RC}$
 e

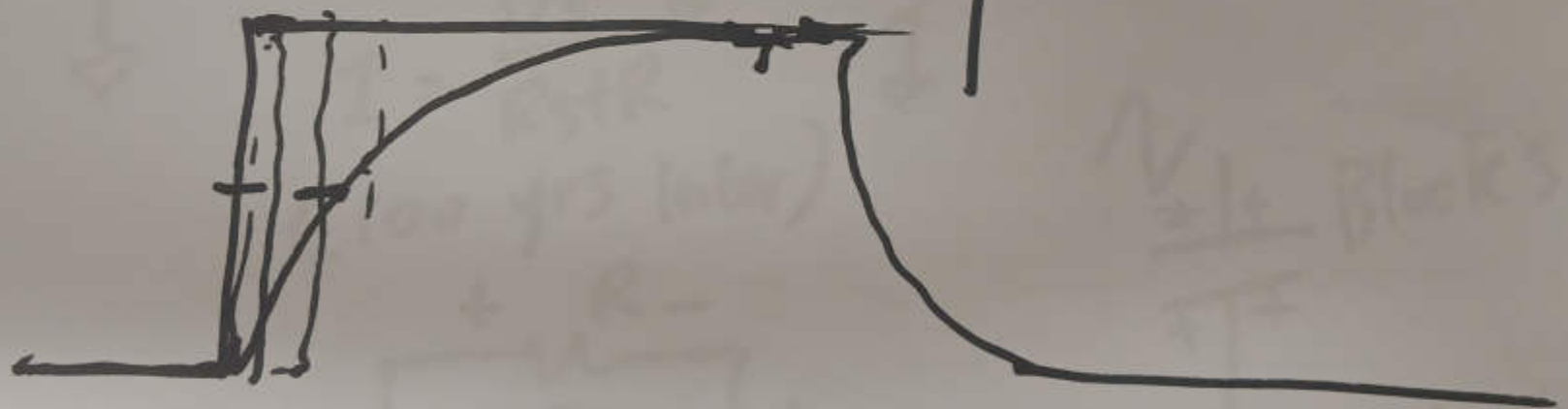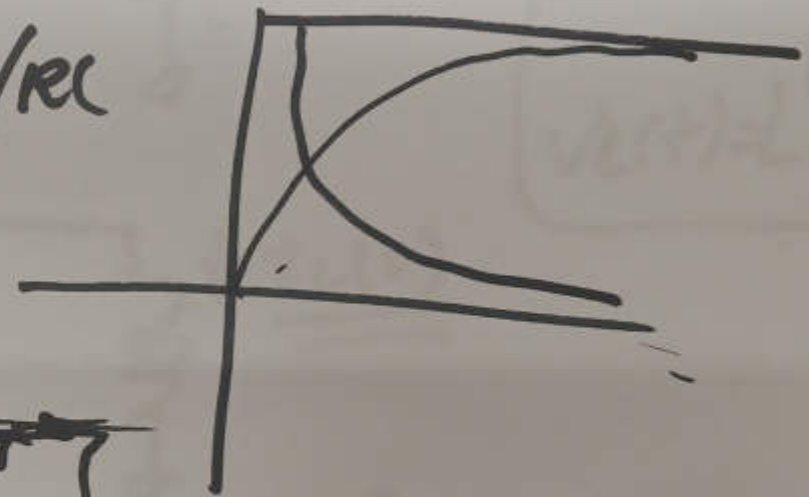


②

Inductor's Natural Response


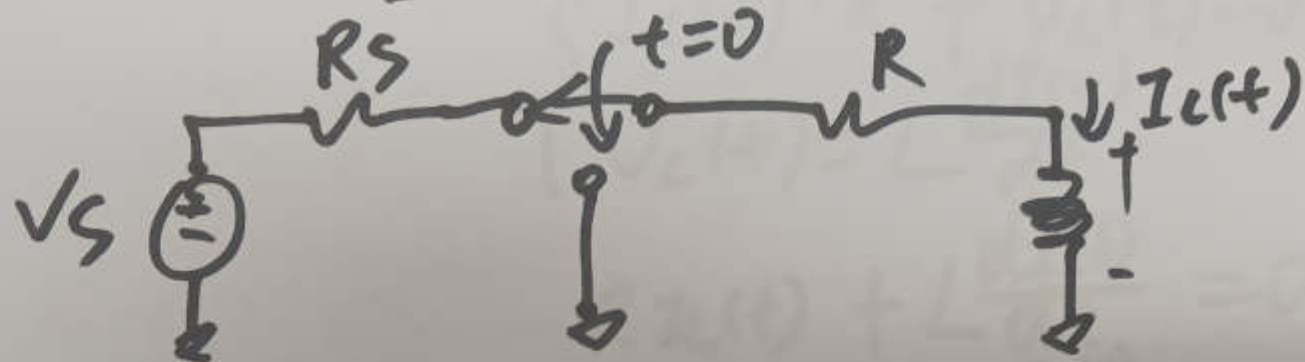


$$V_L(t) = L \frac{di(t)}{dt}$$

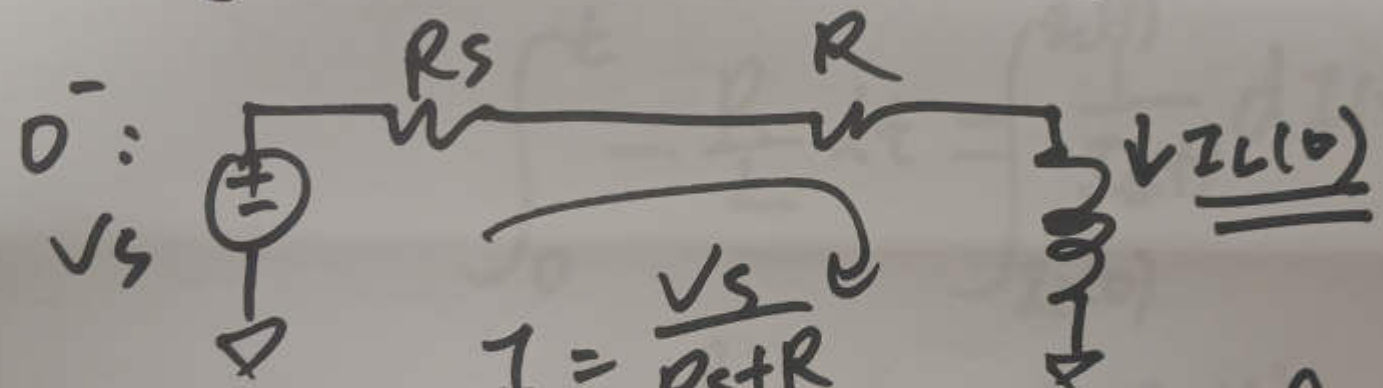

$$I = \frac{V_s}{R_s + R}$$

(100 yrs later)

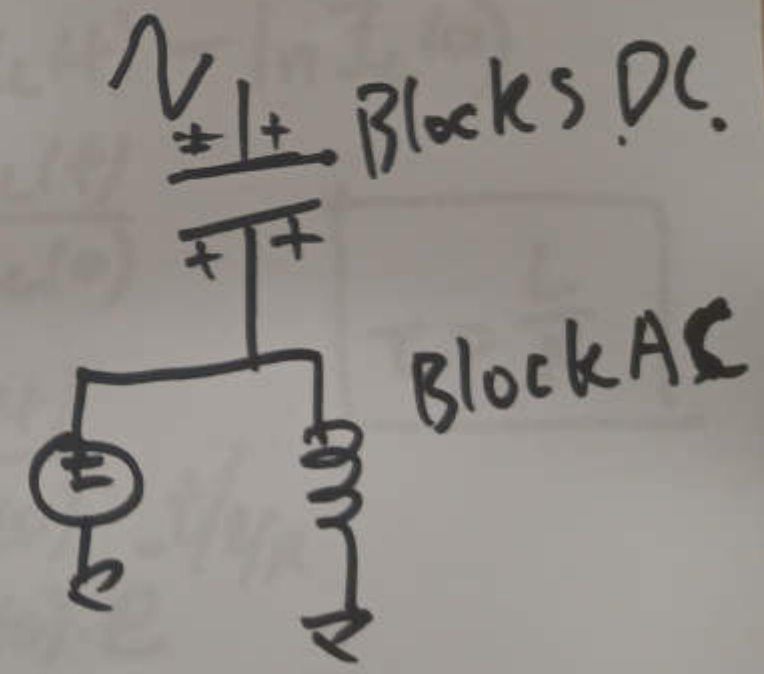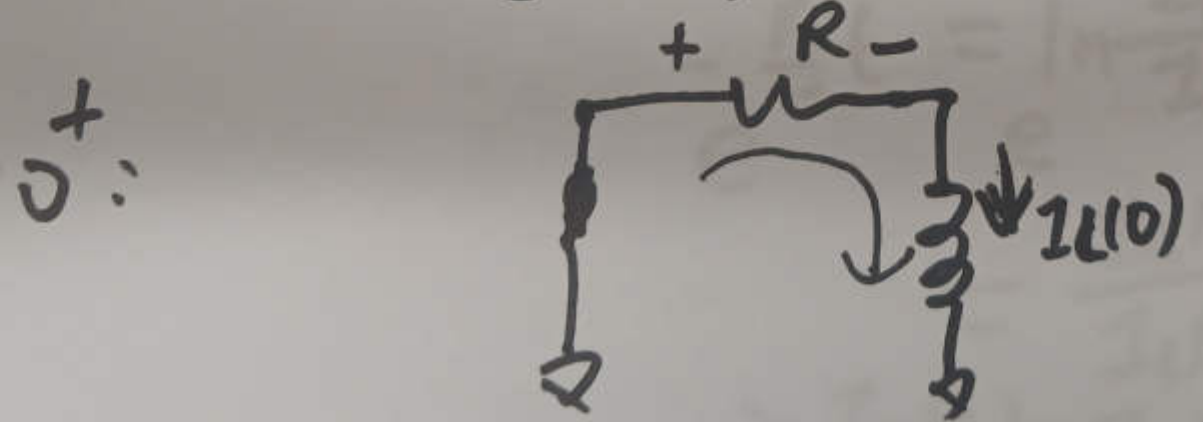

Blocks DC

Block AC

KVL:
$$\begin{cases} I_L(t) \cdot R + V_L(t) = 0 \\ V_L(t) = L \frac{dI(t)}{dt} \end{cases}$$

$$R I_L(t) + L \frac{dI(t)}{dt} = 0$$
$$\int_0^t -\frac{R}{L} dt = \int_{I_L(0)}^{I_L(t)} \frac{1}{I_L(t)} dI(t)$$

$$-\frac{R}{L} t = \ln I_L(t) - \ln I_L(0)$$



$$e^{-\frac{R}{L} t} = \ln \frac{I_L(t)}{I_L(0)}$$

$$\tau = \frac{L}{R}$$

$$= \frac{I_L(t)}{I_L(0)} \cdot t / \tau$$

$$\Rightarrow I_L(t) = I_L(0) \cdot e^{-t/\tau}$$

(4)

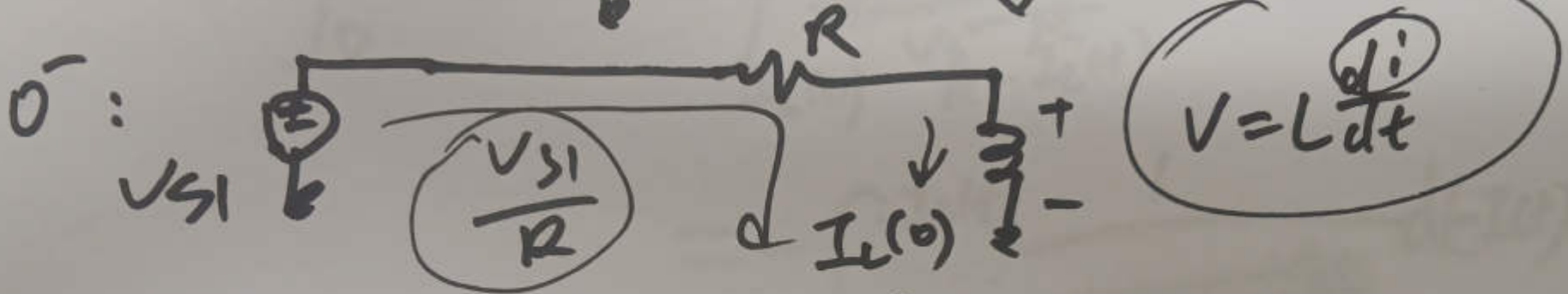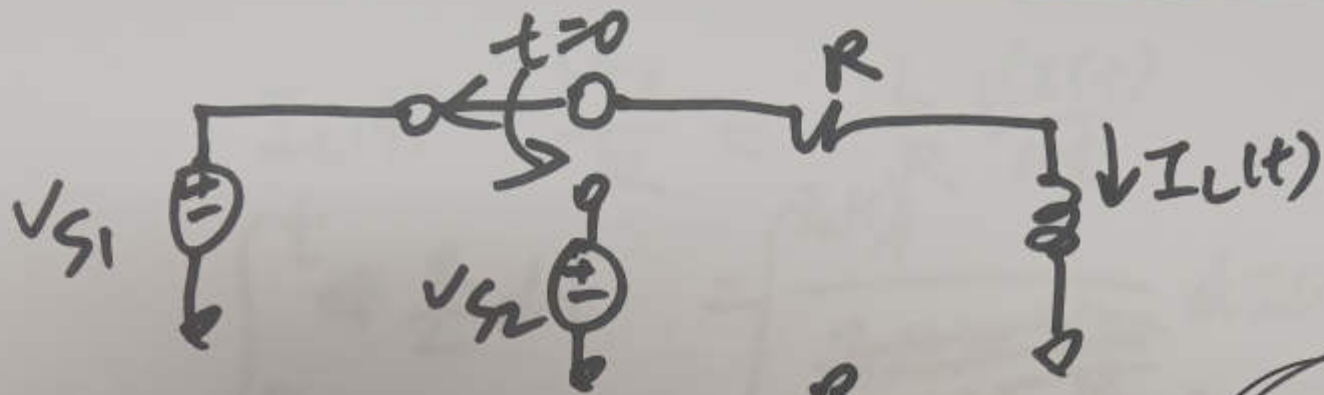

$$-V_{S2} + I_L(t) \cdot R + L \frac{dI_L(t)}{dt} = 0$$

$$-\frac{V_{S2}}{R} + I_L(t) + \frac{L}{R} \frac{dI_L(t)}{dt} = 0$$

(5)

$$I_L(t) - \frac{V_{S2}}{R} = -\frac{L}{R} \frac{dI_L(t)}{dt}$$

$$\int_0^t \frac{R}{L} dt = \int_{I_L(0)}^{I_L(t)} \frac{1}{\frac{V_{S2}}{R} - I_L(t)} dI_L(t)$$

$$= - \int_{-I_L(0)}^{-I_L(t)} \frac{1}{\frac{V_{S2}}{R} - I_L(t)} d(-I_L(t))$$

$$= - \int_{-I_L(0) + \frac{V_{S2}}{R}}^{-I_L(t) + \frac{V_{S2}}{R}} \frac{1}{\frac{V_{S2}}{R} - I_L(t)} d(-I_L(t) + \frac{V_{S2}}{R})$$

$$= - \left(\ln \left(\frac{V_{S2}}{R} - I_L(t) \right) - \ln \left(\frac{V_{S2}}{R} - I_L(0) \right) \right)$$

(b)

$$e^{-\frac{R}{L}t} = \left(\frac{\frac{V_{S2}}{R} - I_L(t)}{\frac{V_{S2}}{R} - I_L(0)} \right)$$

$$e^{-\frac{R}{L}t} = \frac{\frac{V_{S2}}{R} - I_L(t)}{\frac{V_{S2}}{R} - I_L(0)}$$

$$\left(\frac{V_{S2}}{R} - I_L(0) \right) e^{-\frac{R}{L}t} = \frac{V_{S2}}{R} - I_L(t)$$

$$I_L(t) = \frac{V_{S2}}{R} - \left(\frac{V_{S2}}{R} - I_L(0) \right) e^{-\frac{t}{\tau}}$$

$$= I_L(\infty) + (I_L(0) - I_L(\infty)) e^{-\frac{t}{\tau}}$$

$$\frac{V_{S2}}{R} = I_L(\infty)$$

(7)