
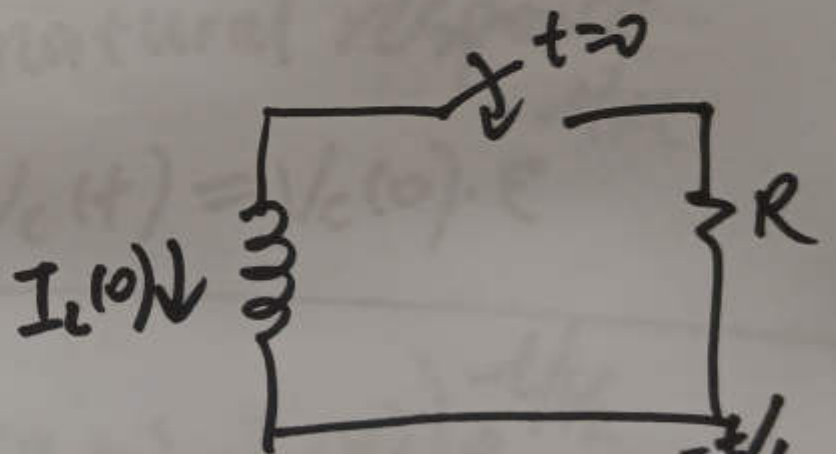
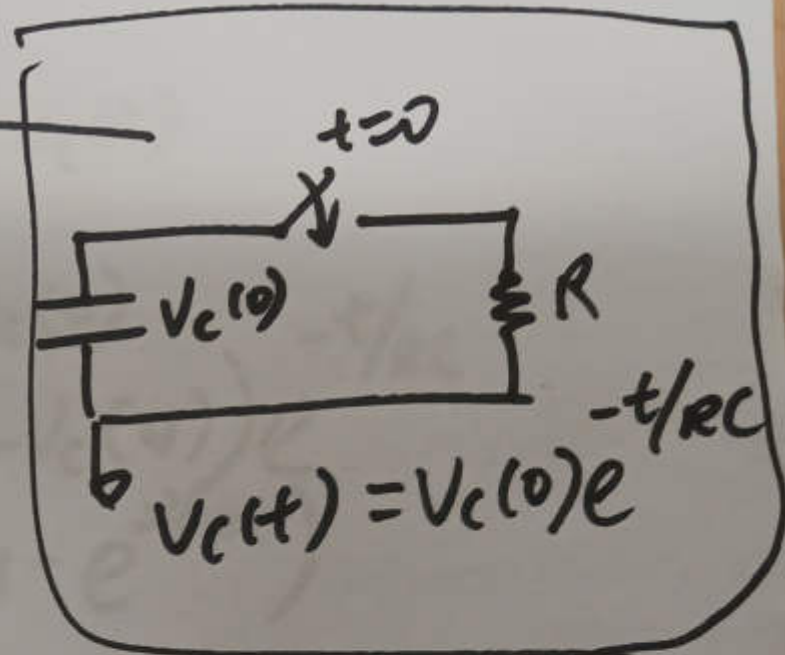
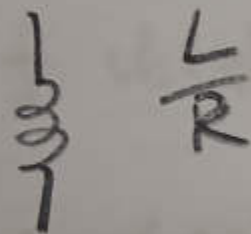



# Time constant

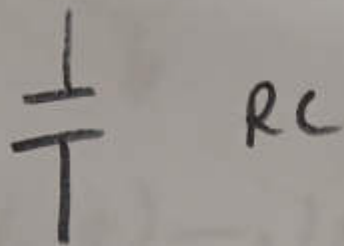

$$I_L(t) = I_L(0) \cdot e^{-\frac{t}{L/R}}$$
$$= I_L(0) \cdot e^{-\frac{R}{L}t}$$

①

# Step response

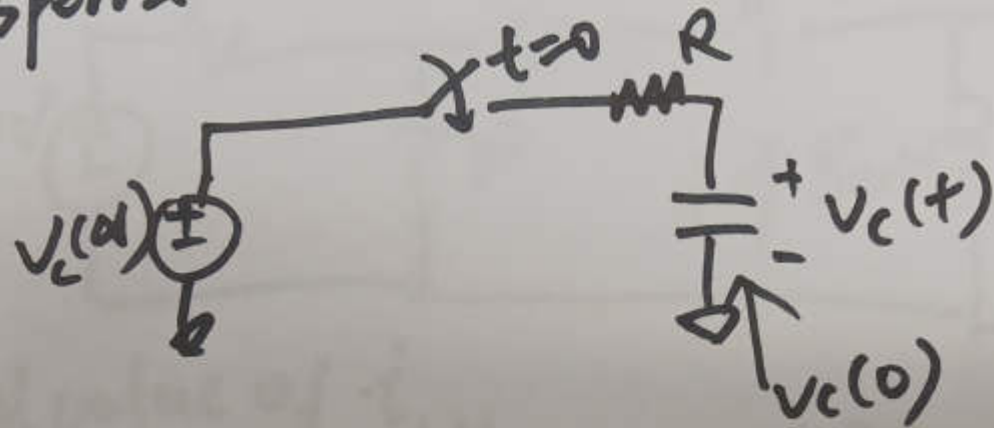

$$v_c(t) = v_c(u) + (v_c(0) - v_c(u)) e^{-t/RC}$$

if  $v_c(0) = 0 \rightarrow v_c(t) (1 - e^{-t/RC})$

if  $v_c(u) = 0 \rightarrow$  natural response  


$$v_c(t) = v_c(0) \cdot e^{-t/RC}$$

Two special cases


---
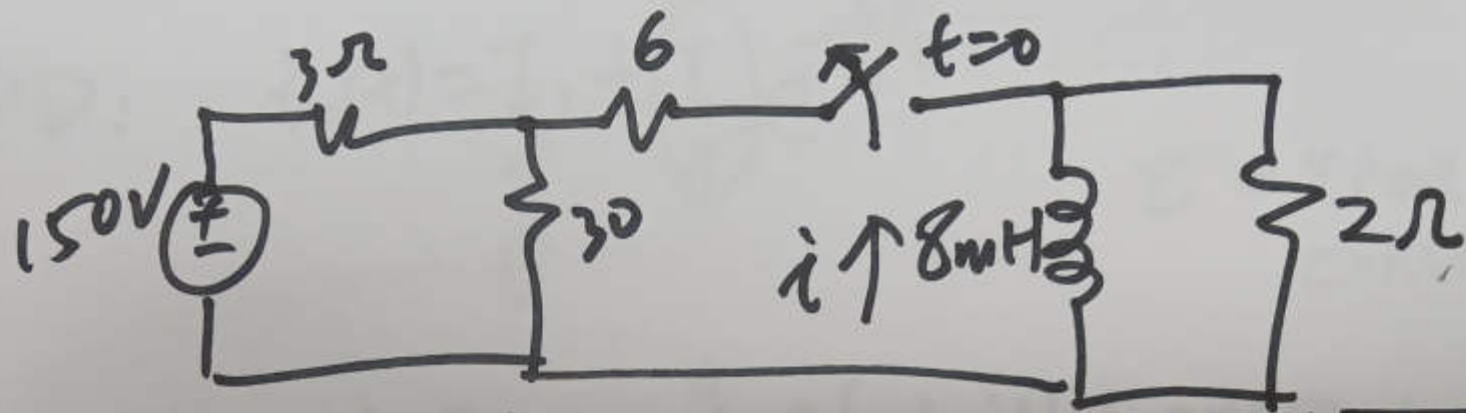
## step response for inductors:

$$I_L(t) = I_L(u) + (I_L(0) - I_L(u)) e^{-t/LR}$$



PA: initial value of  $i$

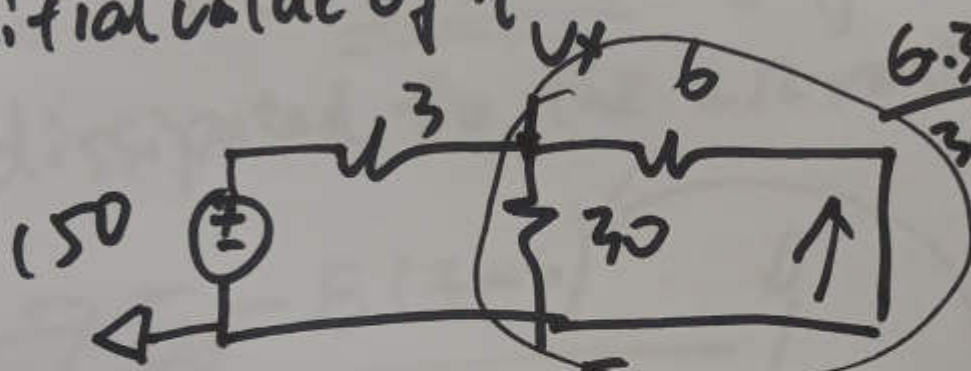

$$\frac{6 \cdot 30}{36} = 5\Omega$$

$$V_x = L \frac{di}{dt}$$

$$V_x = 150 \cdot \frac{5}{3+5} =$$

PB: initial energy in inductor

$$w_0 = E = \frac{1}{2} L \cdot I^2$$

L can't change current instantaneously

PC: time constant for  $t > 0$ .

$$\frac{L}{R} = \frac{8mH}{2} = 4ms$$

$$I_L(0^-) = I_L(0^+)$$

(3)

PD:  $i_0(t) = \underset{\substack{\uparrow \\ 0}}{I_1} + \underset{\substack{\uparrow \\ 0}}{I_2} e^{-t/\tau}$

$\tau =$  Time constant

PE: at  $t = 3\text{ms}$ , 10% of initial energy dissipated to the  $2\Omega$  resistor.


$$\frac{E_0 - E(3\text{ms})}{E_0} = \frac{0}{10}$$

$$E_0 = \frac{1}{2} \cdot L \cdot I_L(0)^2$$

$$E(3\text{ms}) = \frac{1}{2} L \cdot I_L(3\text{ms})^2 = \frac{1}{2} L \left( I_L(0) \cdot e^{-\frac{3\text{ms}}{4R}} \right)^2$$

$$3\text{ms} = 0.003$$

(4)

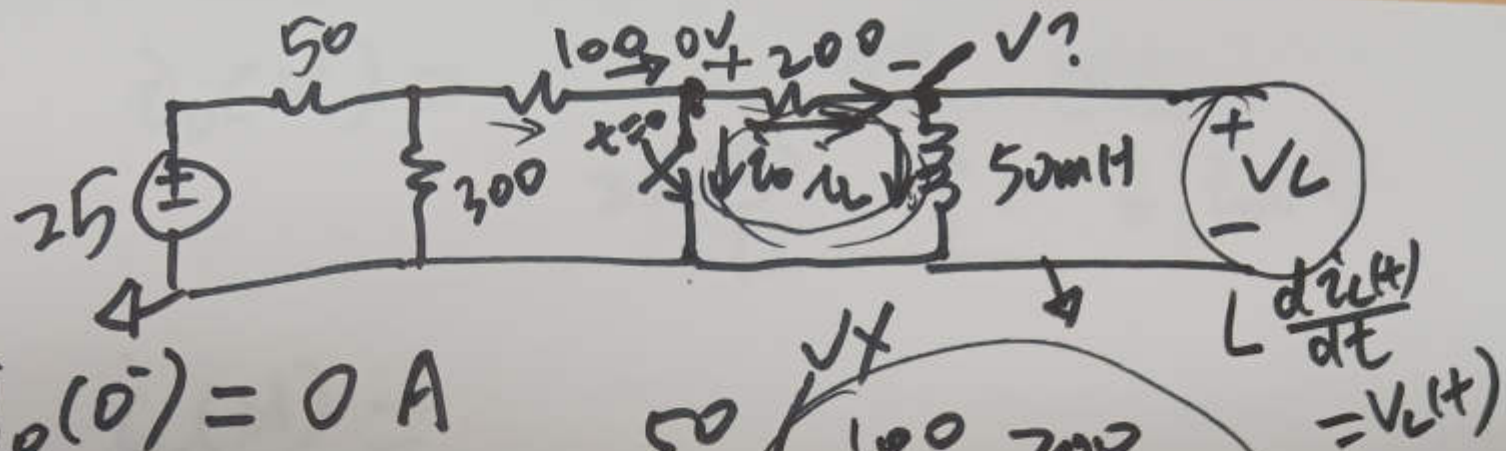

$$i_0(0^-) = 0 \text{ A}$$



$$i_L(0^-) =$$

$$i_0(0^+) = i_1 - i_L(0^+)$$

$$i_L(0^+) = i_L(0^-)$$

$$v_L(t) = L \frac{di(t)}{dt}$$

$$i(t) = \frac{1}{L} \int v_L(t) dt$$

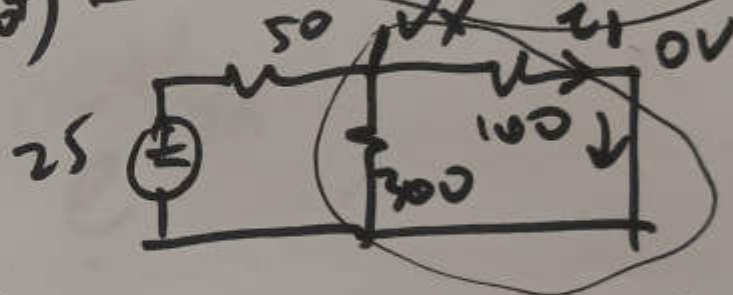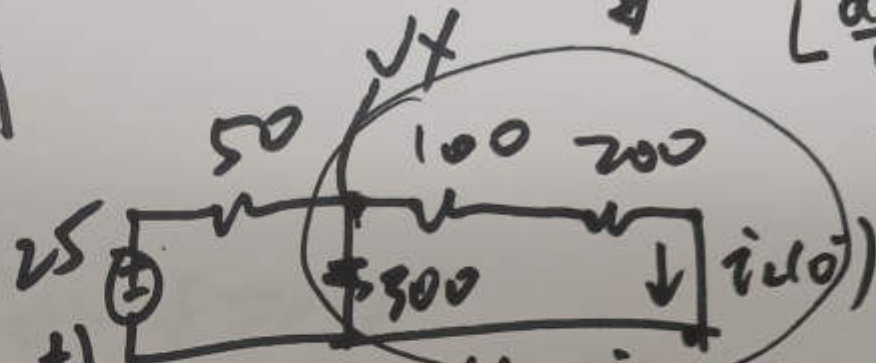


$$\frac{100 \cdot 300}{400} = \frac{30000}{400} = 75 \Omega$$

$$V_X = 25 \cdot \frac{75}{75+50}$$

$$i_1 = \frac{V_X}{100}$$

5

$$i_o(\alpha) =$$

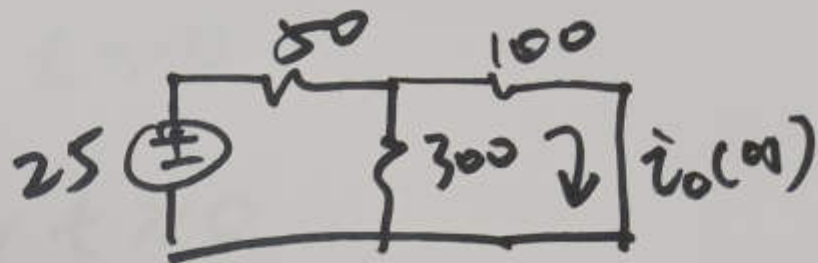

$$i_L(\alpha) =$$

$$i_L(t) \text{ for } t \geq 0$$

$$\parallel i_L(0) \cdot e^{-t/4R}$$

$$V_L(0^-) = 0 \text{ V.}$$

$$V_L(0^+) =$$

$$V_L(\alpha) =$$

(b)

$v_L(t)$  for  $t \geq 0$

$i_0(t)$  for  $t \geq 0$

• •  
•

②