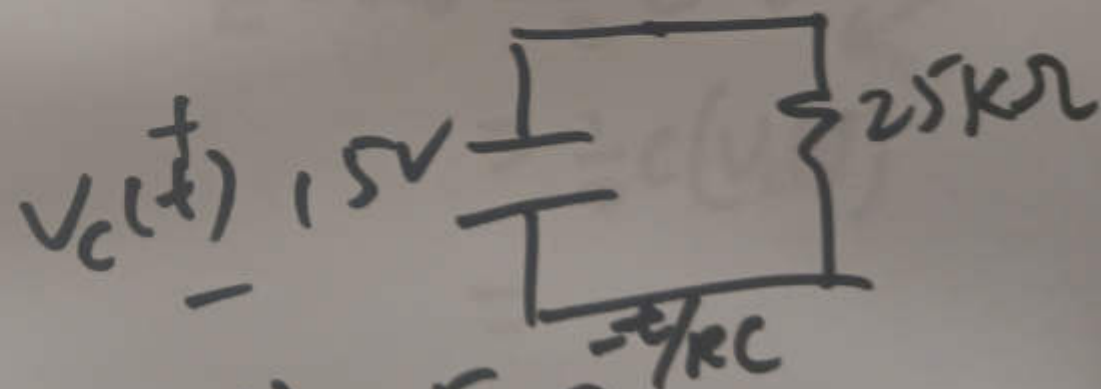


$$V_c(0^-) = 60 \cdot \frac{25K}{75K + 25K}$$

$$= 15V$$



$$V_c(t) = V_c(0^-) (1 - e^{-t/RC})$$




$$V_c(t) = 15 \cdot e^{-t/RC}$$

$C = 5nF, R = 25K\Omega$

①
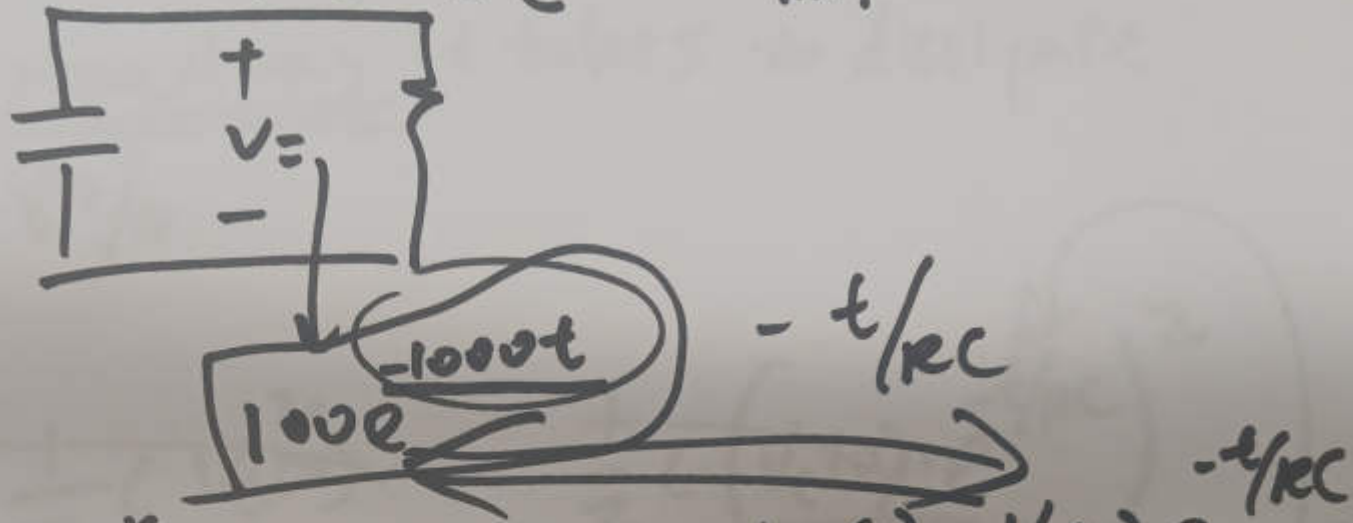
$$\rightarrow i = 5 \cdot e^{-1000t} \text{ mA}$$



$$R = \frac{V}{i} = 20 \text{ k}\Omega$$

$$V_c(t) = V_c(0) \cdot e^{-t/RC}$$

$$C = ? \quad \begin{cases} \int \frac{1}{RC} = 1000 \\ R = 20 \text{ k} \end{cases}$$

$$V_c(0) = 100 \text{ V}$$

$$E = W_0 = \frac{1}{2} C \cdot V^2$$

$$C =$$

$$= \frac{1}{2} C (V_c(0))$$

$$=$$

$$\tau = RC$$

(2)


How long it takes to dissipate
8.0%

$$\frac{\frac{1}{2} C V_C(t)^2}{\frac{1}{2} C \left(V_C(t_0) \cdot e^{-\frac{t}{RC}} \right)^2} = 8.0\%$$

$$\frac{\frac{1}{2} C V_C(t)^2}{\frac{1}{2} C V_C(t_0)^2}$$


$$= 1 - e^{-2t/RC} = \frac{4}{5}$$

(3)

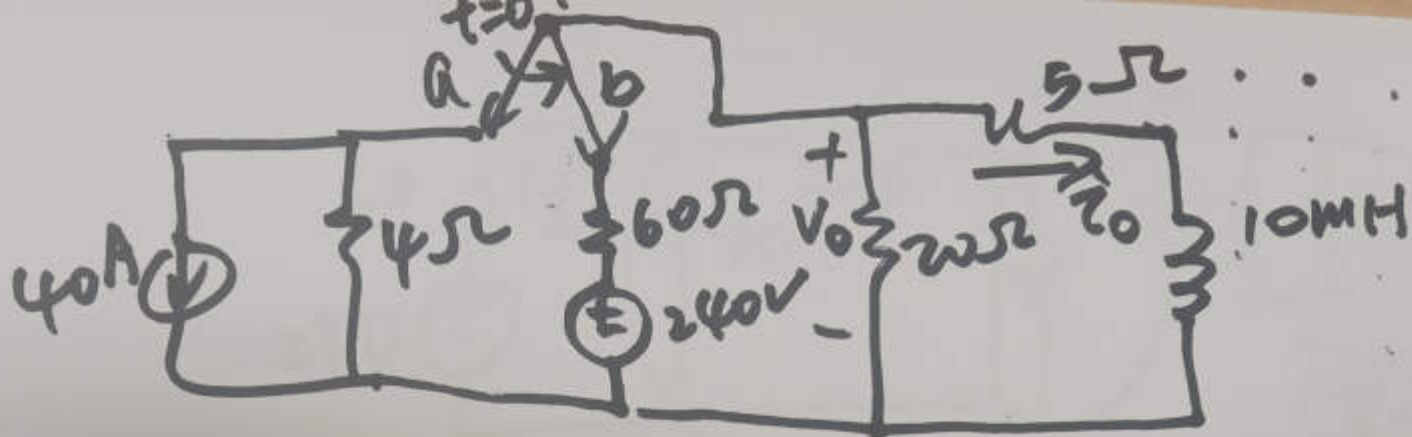

$i_o(t)$? when $t > 0$

$$i_o(0^-) \neq i_o(0^+)$$

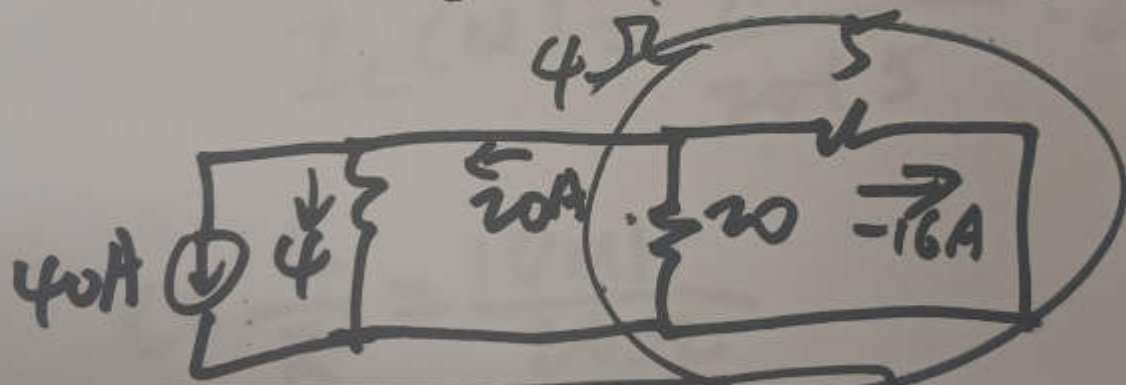

$$\frac{5 \cdot 20}{25} = 4$$


$$\frac{-20A}{25} \cdot 20 = \underline{\underline{-16A}}$$

$$i_L(t) = \underbrace{i_L(\infty)}_{(0A)} + (i_L(0^-) - i_L(\infty)) e^{-t/4R}$$

$$i_L(0) = -16A$$

$$i_L(\infty) =$$

(4)

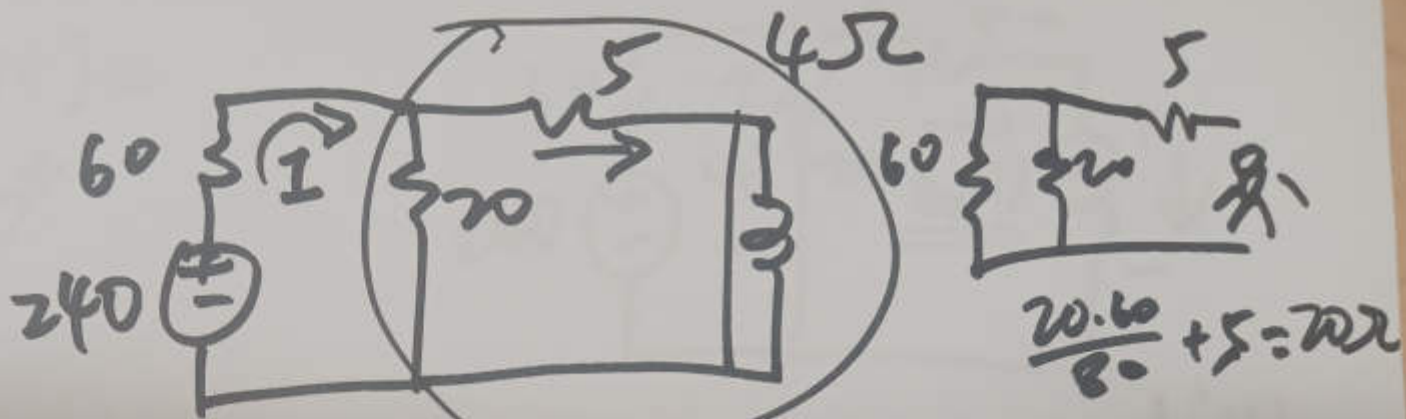


$$I \text{ (through } 4\Omega) = \frac{240V}{60 + 4} = 3.75A$$

$$I_L(\Omega) = \frac{3.75A}{20 + 5} \cdot 20 = 3A$$

$$\tau = \frac{L}{R} = \frac{10mH}{20\Omega}$$

(5)


$$V_o(t) = 2710^+$$

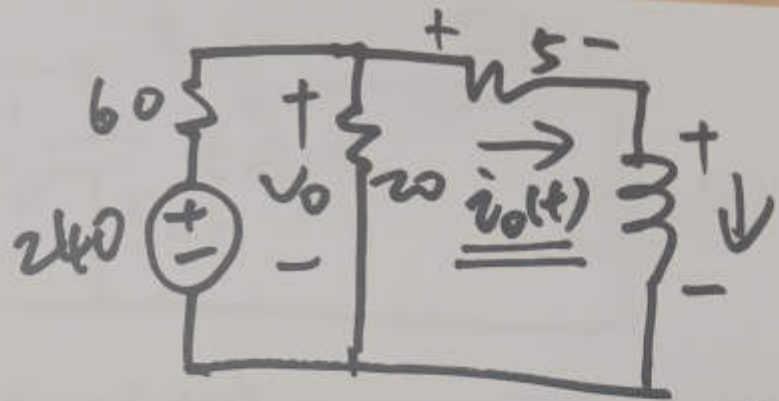

$$V_L(t) = L \frac{di(t)}{dt}$$

$$= 5 \cdot i_o(t) + V_L(t)$$

⑥

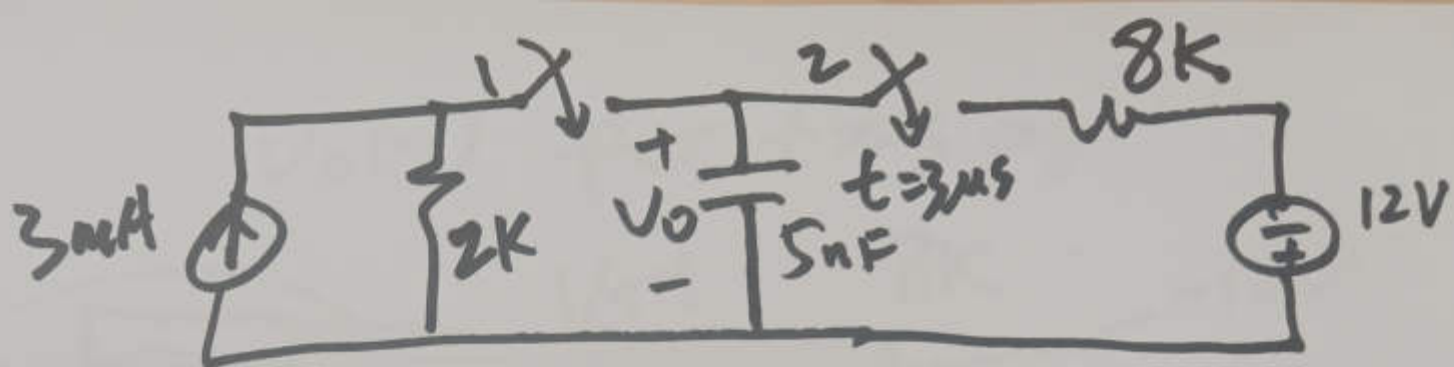

$t=0$, 1 closes. no $V_C(0)$


$0 < t < 3\mu s$

$$V_C(t) = V_C(\infty) (1 - e^{-t/\tau})$$

$$= 6V \cdot (1 - e^{-t/10\mu s})$$


$$RC = 2k \cdot 5nF = 10\mu s$$

$$\rightarrow = 6(1 - e^{-t/10\mu s})$$

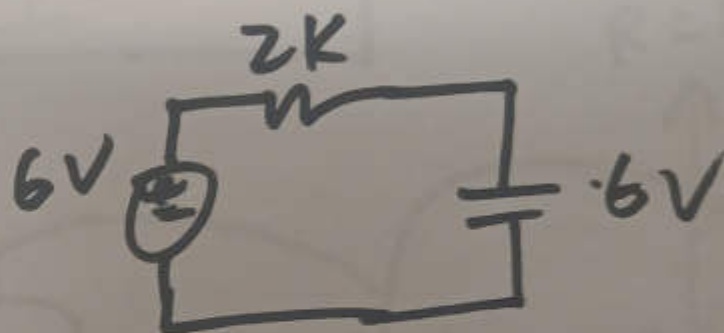

①

$V_o(t)$ for $t > 3 \mu s$

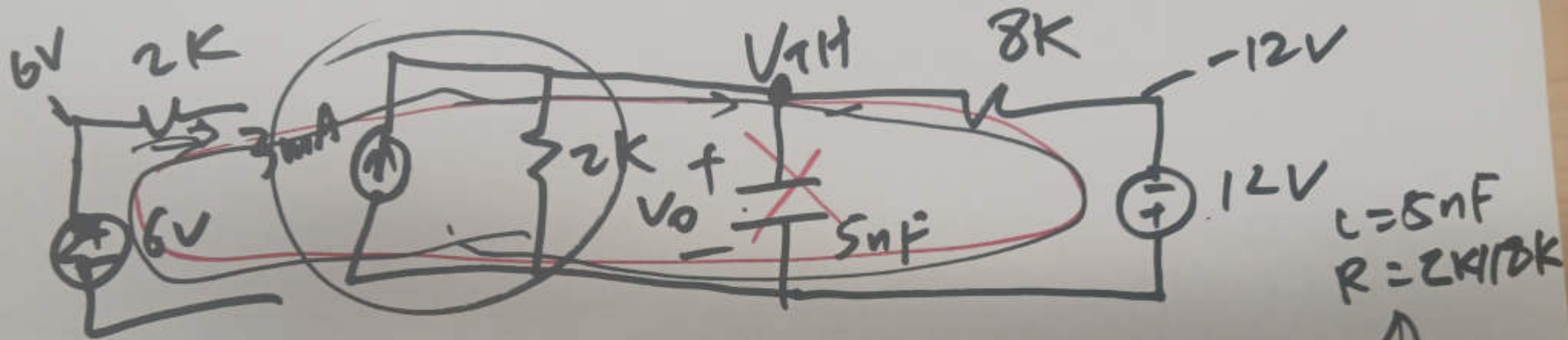

$V_c(3 \mu s)$

$$V_c(t) = \underbrace{V_c(\infty)}_{6V} + (V_c(0) - V_c(\infty)) e^{-t/\tau}$$

$t > 3 \mu s$

$$\cancel{6V} - \cancel{\frac{6V}{2K}} \left(\frac{6V - (-12V)}{2K + 8K} \cdot 2K \right) = V_{TH}$$

A