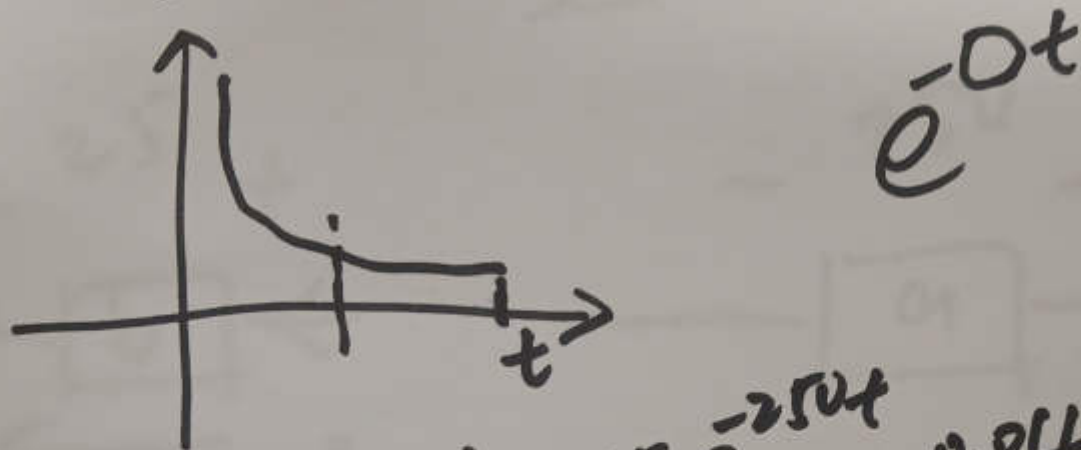


Tutorial 1. Problem 1





$$p(t) = U_i = 15 e^{-250t} \cdot 0.04 \cdot e^{-250t} = 0.6 e^{-500t}$$



$$\int_0^{\infty} p(t) dt = \int_0^{\infty} a b e^{-500t} dt$$

$$= \left. \frac{0.6}{-500} e^{-500t} \right|_0^{\infty} = 0 + \frac{0.6}{500} = 1.2 \text{ mJ}$$
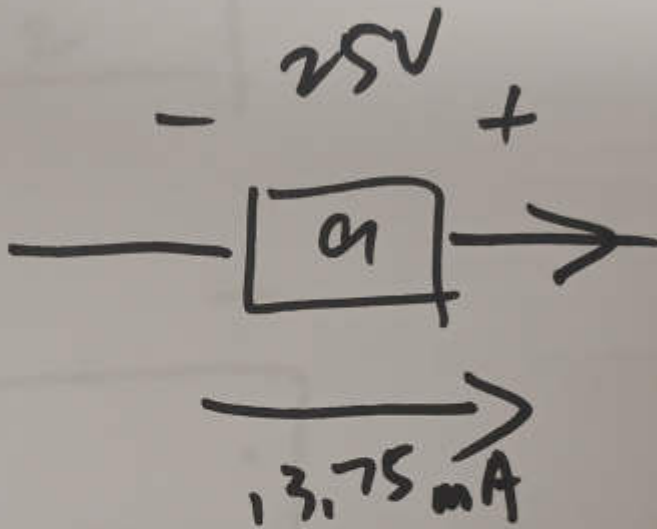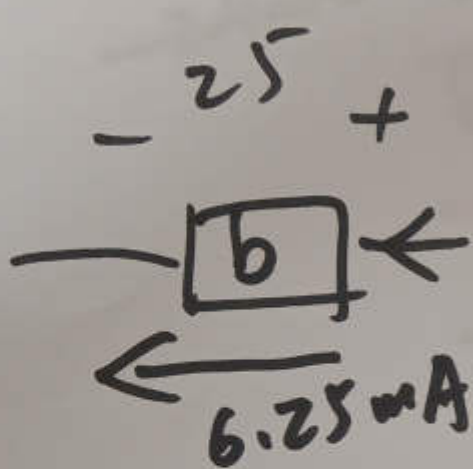
$$\frac{0.6 \text{ mJ}}{10} = \int_{-500}^{0} \frac{0.6}{-500} e^{-500t} dt$$



(2)

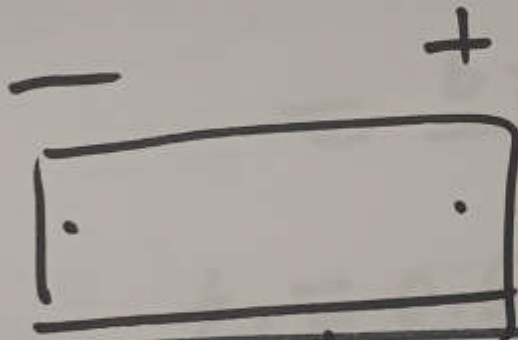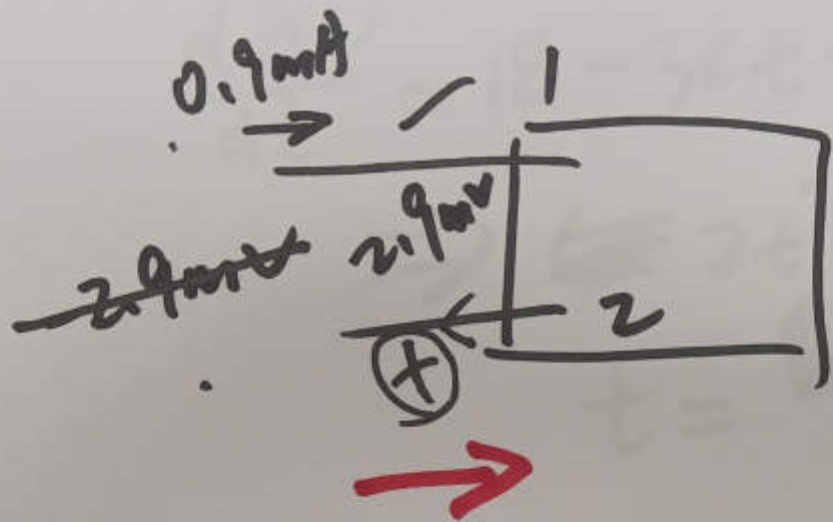

$$\begin{cases} v = t(3-t) \text{ V } 0 < t < 3 \text{ s} \\ i = (6-4t) \text{ mA } 0 < t < 3 \text{ s} \end{cases}$$

$$\begin{aligned} P = vi, \quad P(t) &= v(t) \cdot i(t) = (3t - t^2) \cdot (6 - 4t) \text{ mW} \\ &= 18t - 12t^2 - 6t^2 + 4t^3 \\ &= 18t - 18t^2 + 4t^3 \end{aligned}$$

(3)

$$\frac{dP(t)}{dt} = 18 - 36t + 12t^2 = 0$$

$$\Rightarrow \cancel{2}t^2 - 6t + 3 = 0$$

$$t = \frac{6 \pm \sqrt{36 - 4 \cdot 2 \cdot 3}}{4}$$

$$= \frac{6 \pm \sqrt{12}}{4} = \frac{3 \pm \sqrt{3}}{2}$$

$$t_1 = \underline{0.634 \text{ s}} \quad t_2 = \underline{2.366 \text{ s}}$$

$$P(t_1) = \underline{5.196 \text{ mW}}$$

$$P(t_2) = \underline{-5.196 \text{ mW}}$$

(*)


$$E(t) = \int_0^3 (18t - 18t^2 + 4t^3) dt$$

$E(0)$
 $E(1)$
 $E(2)$
 $E(3)$

$$\begin{cases} 0 < t < 15 \text{ ks} \\ 15 < t < 20 \text{ ks} \end{cases}$$

$$P_2 = -9.5 \text{ V} \cdot 2.5 \text{ A}$$

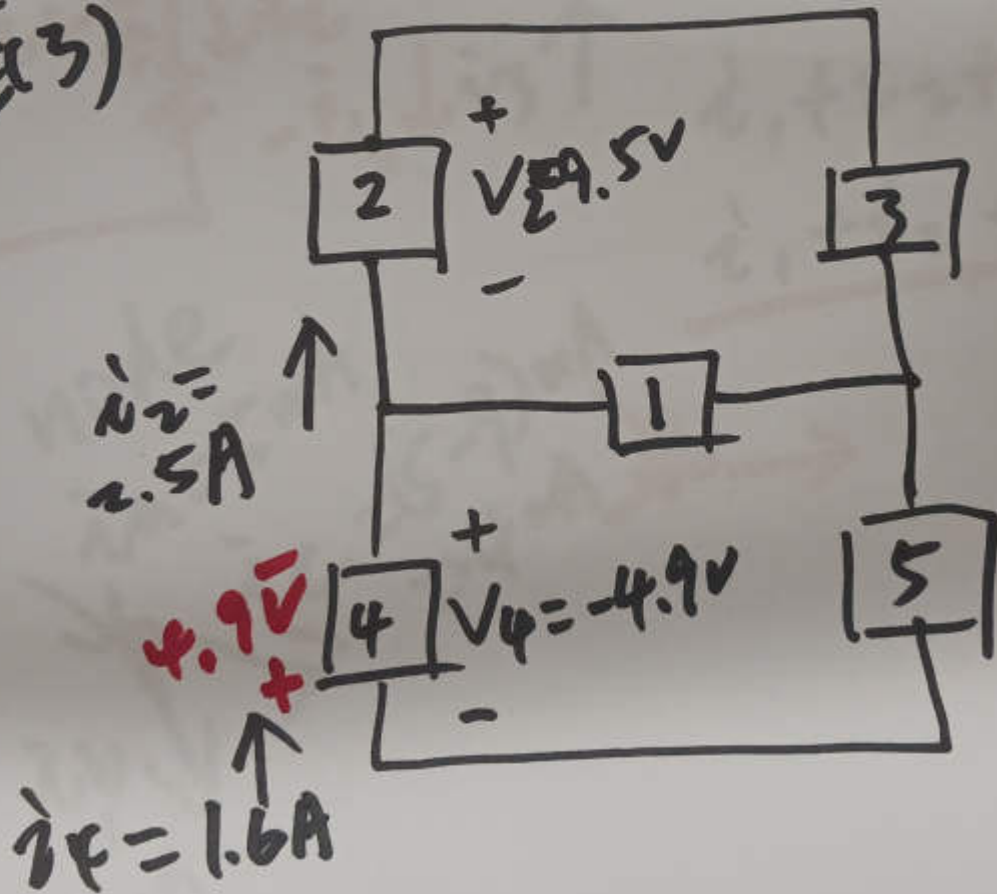
$$P_4 = 4.9 \text{ V} \cdot 1.6 \text{ A}$$



$$\sum P = 0$$

(5)


KCL: Kirchhoff's Current Law

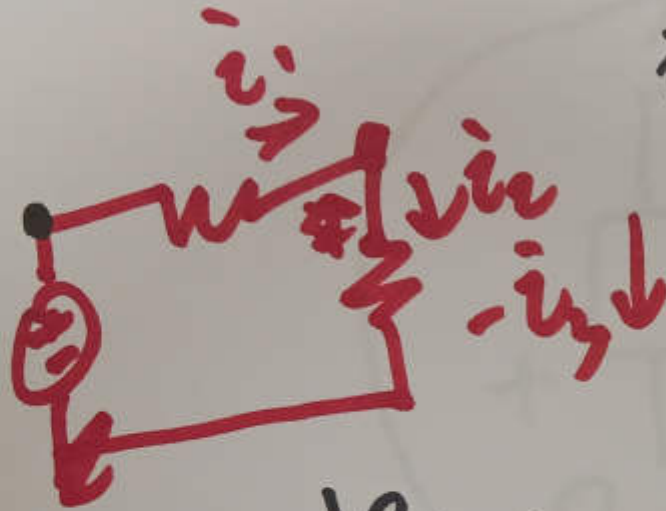

$$\sum i = 0$$


$$i_1 + i_2 + i_3 = 0$$

$$\underline{i_1 + i_2 = -i_3}$$

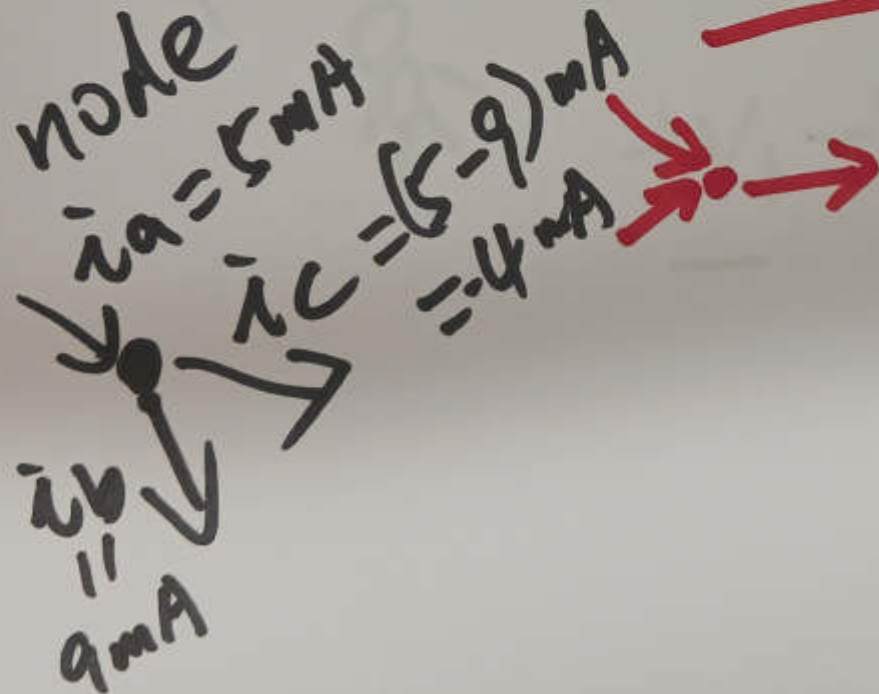

(6)

KVL: Kirchoff's Voltage Law

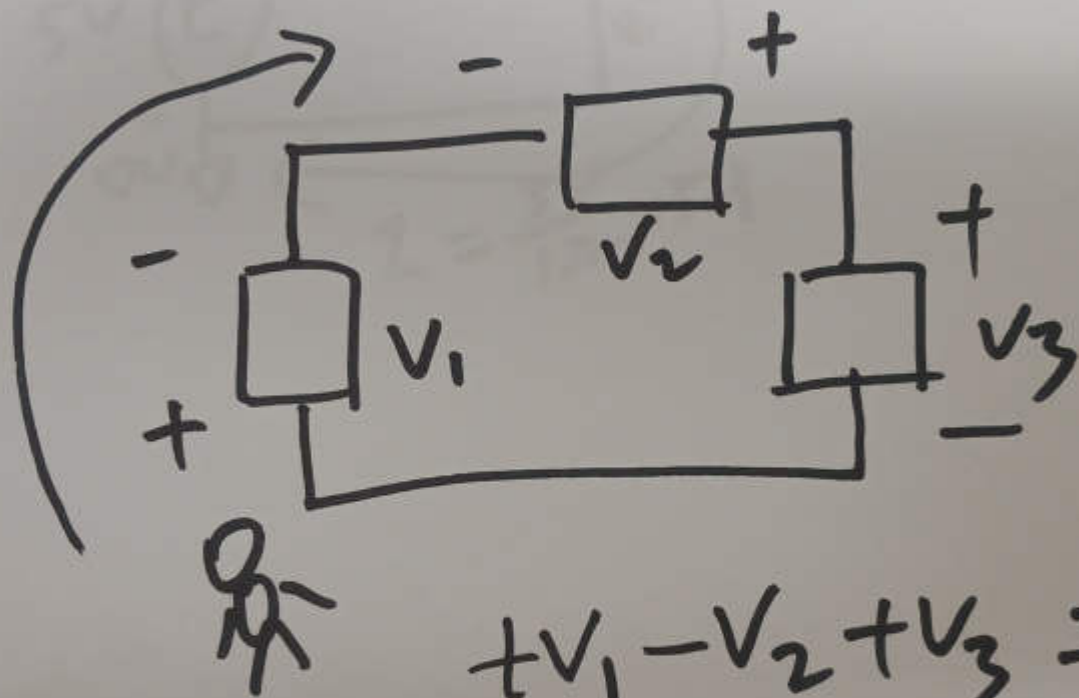

$$+V_1 - V_2 + V_3 = 0$$

①

