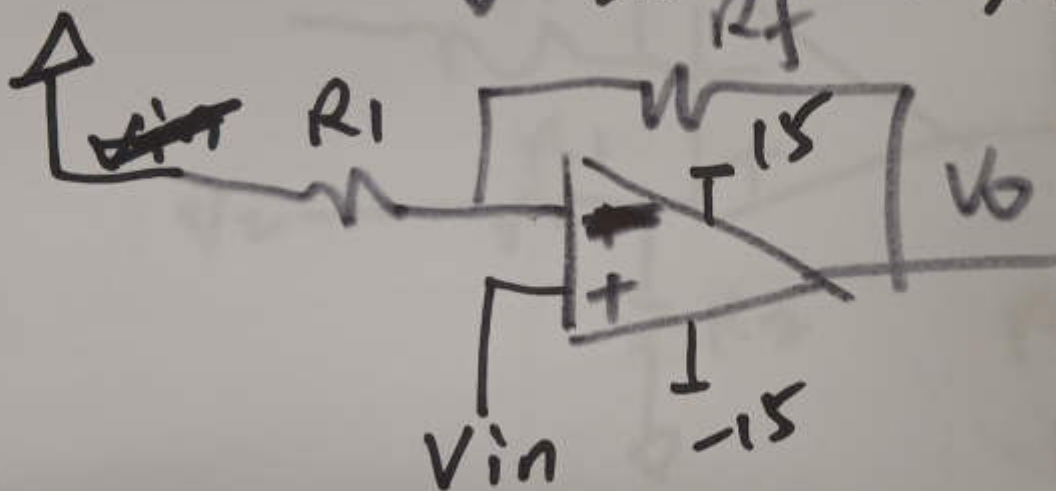


inverting


$$\frac{V_o}{V_i} = -\frac{R_f}{R_i}$$



non-inverting

$$\frac{V_o}{V_i} = 1 + \frac{R_f}{R_i}$$

Summing Amplifier

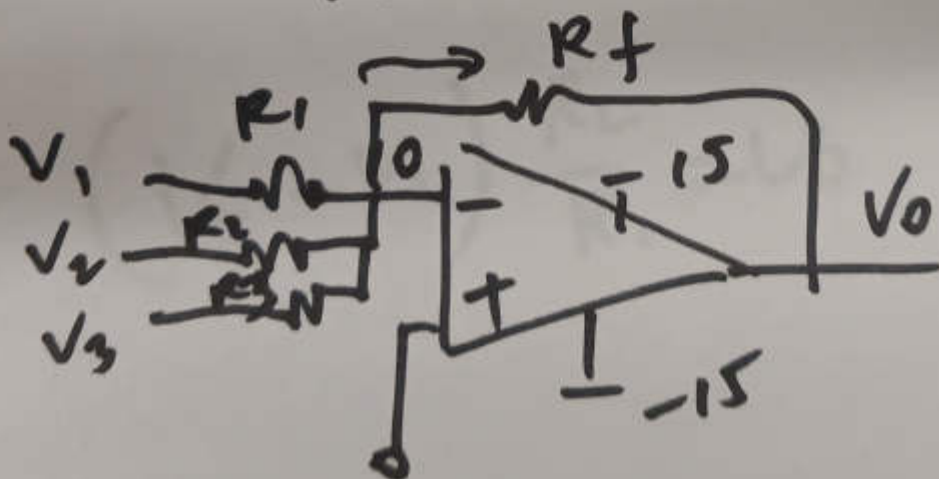


$$\frac{V_1 - 0}{R_i} + \frac{V_2 - 0}{R_i} + \frac{V_3 - 0}{R_i}$$

$$= \frac{0 - V_o}{R_f}$$


Difference Amplifier

~~Differential~~

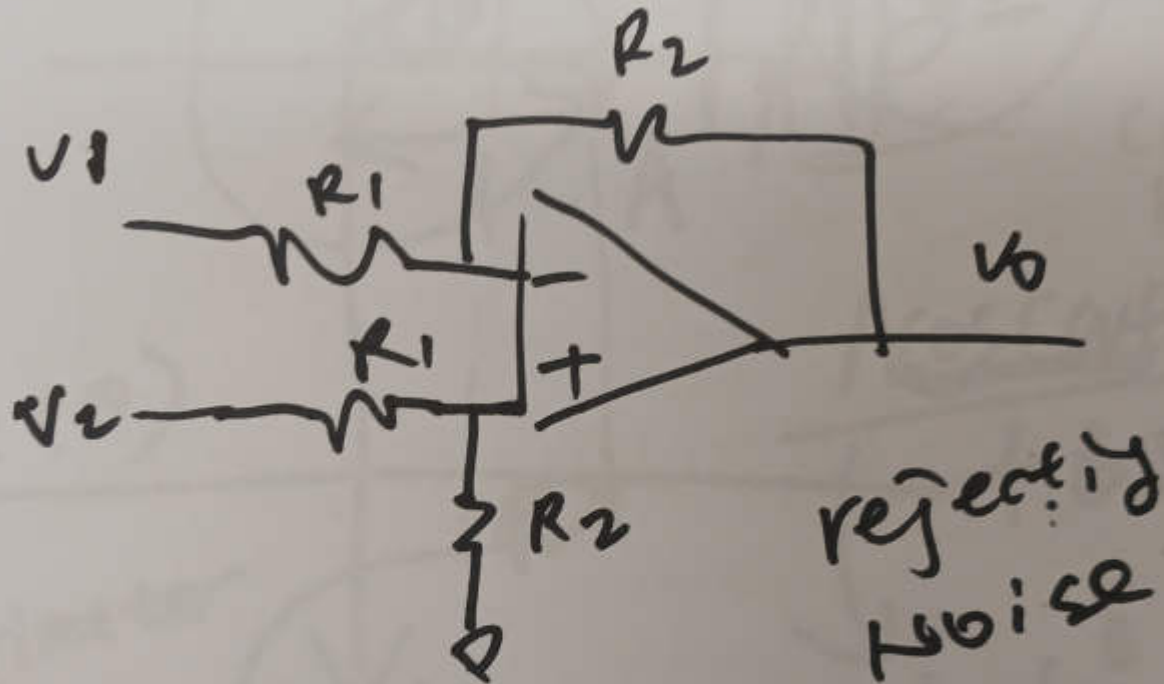


$$(V_2 - V_1) \frac{R_2}{R_1} = V_0$$

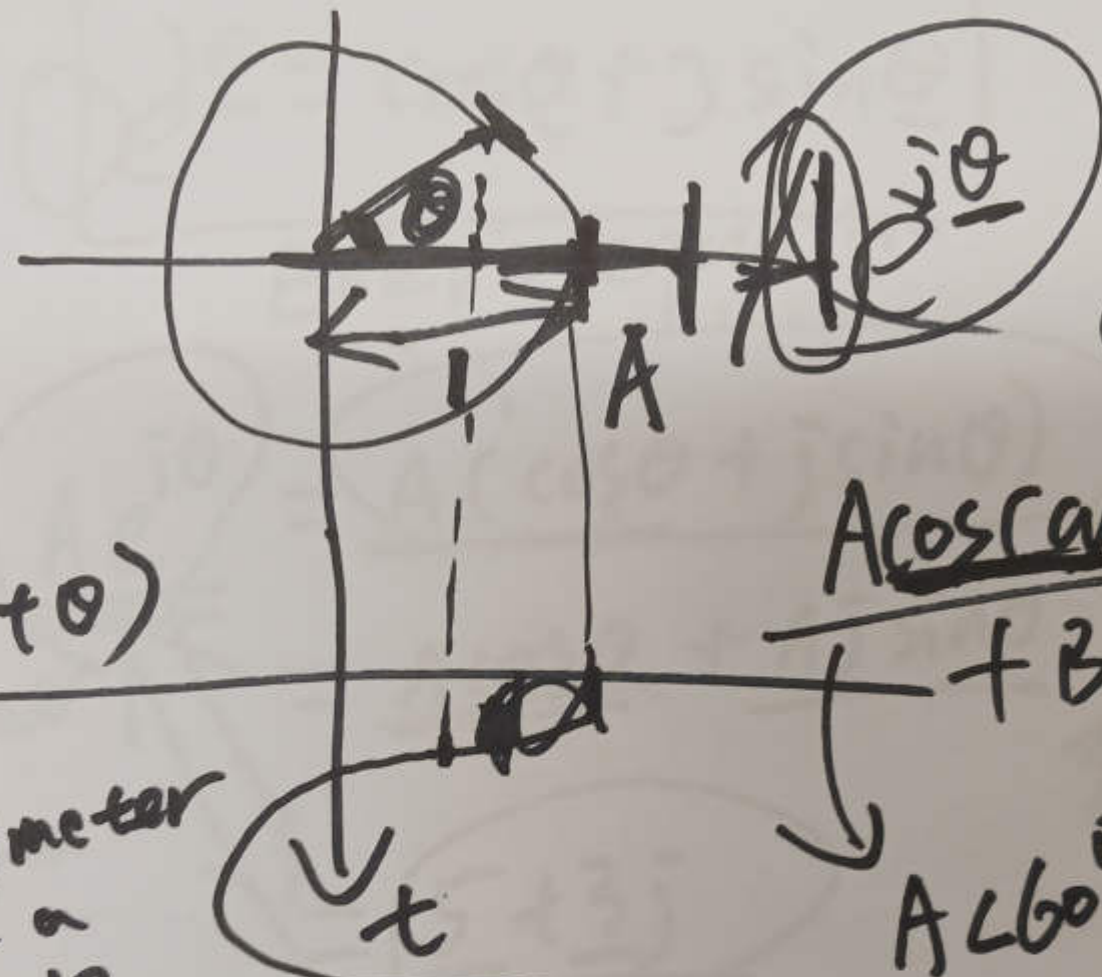$Ae^{j\theta}$
 $\Leftrightarrow A \angle \theta$
 (cos(wt) reference)



$Ae^{j\theta}$
 $= A \cos(\omega t + \theta)$

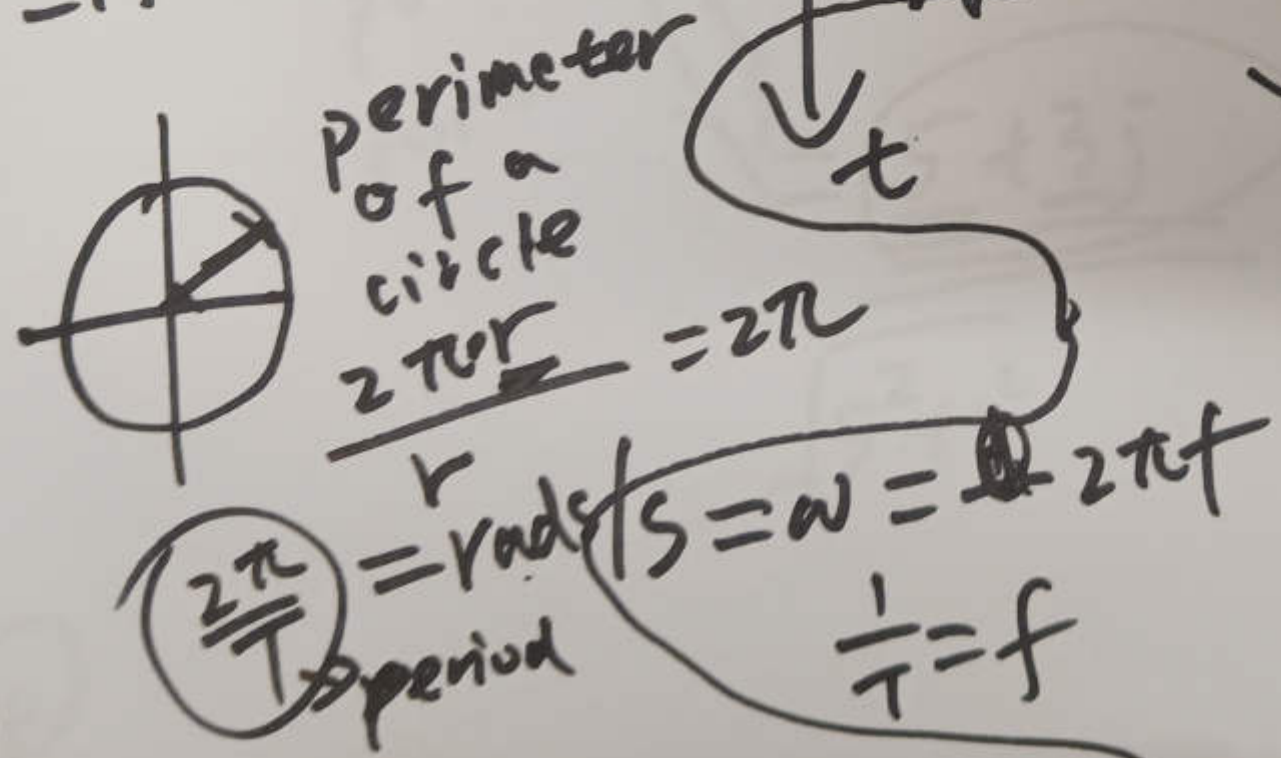$\frac{A \cos(\omega t + 60^\circ)}{+ B \sin(\omega t + 90^\circ)}$
 $A \angle 60^\circ$



$A \cos(\omega t + \theta)$
 $= A \cos(2\pi f t + \theta)$
 radians $\uparrow 60^\circ$

3

$$e^{j\theta} = \cos\theta + j\sin\theta$$

Euler's equation

Steady state

$$Ae^{j\theta} = A(\cos\theta + j\sin\theta)$$


polynomial form

$$= A\cos\theta + Aj\sin\theta$$

rectangular form

$$= 5 + 3j$$

$$\sqrt{5^2 + 3^2}$$

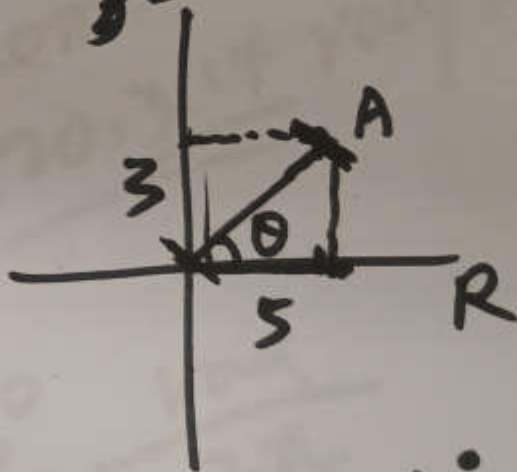


(4)

$$v(t) = 110 \cos\left(\underbrace{120\pi t}_{\omega t} - \underbrace{60^\circ}_{\downarrow}\right)$$

$$V_m = 110$$

↙
magnitude $f =$

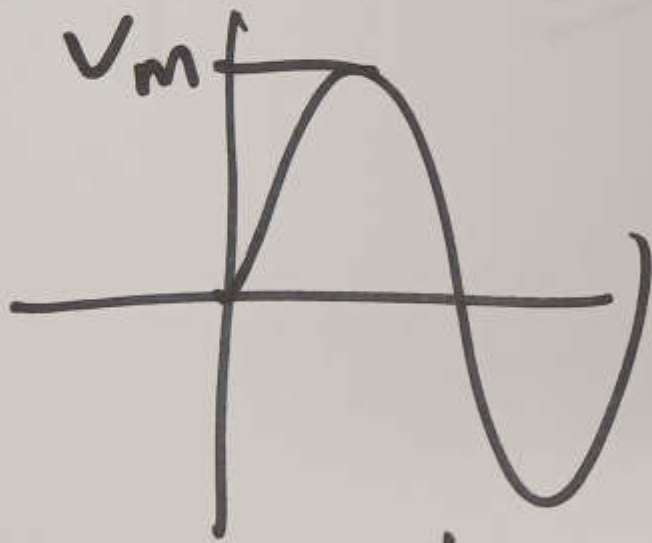

$$\omega = 2\pi f = 120\pi$$

$$f = ? \text{ } \underline{60 \text{ Hz}}$$

$$\omega = 2\pi f = 120\pi$$

$$= \underline{\underline{120 \cdot 3.14 \text{ rad/s}}}$$

$$\frac{60^\circ}{360^\circ} = \underline{\underline{\frac{\text{rad}}{2\pi}}}$$

$$\underline{\underline{\omega = \text{rad/s}}}$$

Angular velocity


$$\theta = \underline{\underline{-60^\circ}}$$

$$\frac{-60^\circ}{360^\circ} = \underline{\underline{\frac{\text{rad}}{2\pi}}}$$

$$T = \frac{1}{f}$$

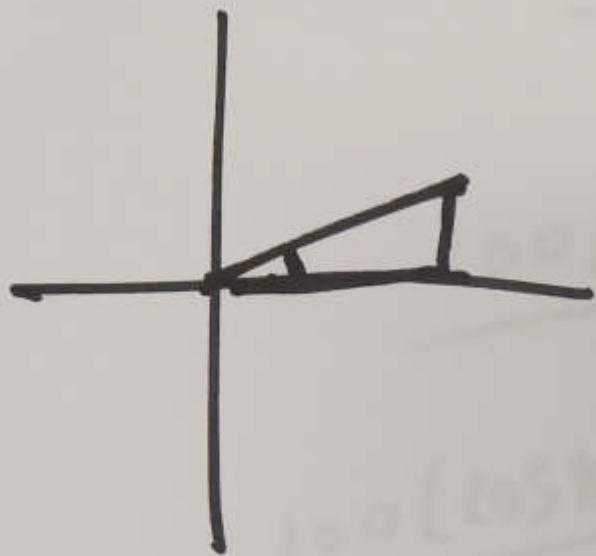(5)

What is the first time after $t=0$ that $v=110V$?



$$\cos(\quad) = 1$$

$$\underline{\underline{110}} \cos(\quad)$$

$$120\pi t - \frac{\pi}{3} = 0$$

$$\frac{60^\circ}{360^\circ} = \frac{\text{rad}}{2\pi}$$

$$v_{\text{rad}} = \frac{\pi}{3}$$

$$y = \underline{100 \cos(300t + 45^\circ)} + 500 \cos(300t + 60^\circ)$$

$$\underline{100 \angle 45^\circ} + 500 \angle -60^\circ$$

$$100(\underline{\cos 45^\circ + j \sin 45^\circ}) + 500(\cos 60^\circ + j \sin -60^\circ)$$

$$\underline{100 \cdot \cos 45^\circ} + \underline{j 100 \sin 45^\circ} + \underline{500 \cos 60^\circ} - \underline{500 j \sin 60^\circ}$$

$$\underline{a + j b} \Rightarrow \underbrace{A}_{\sqrt{a^2 + b^2}} \cos\left(\underbrace{}_{\arctan \frac{b}{a}}\right)$$

①



$$y = \cancel{100} \cos(100t + 60^\circ) - 120 \sin(100t - 125^\circ)$$

$$= 60 \angle 60^\circ - 120 \cos(100t - 125^\circ - 90^\circ)$$

$$\sin \theta = \cos(\theta - 90^\circ)$$


$$\cos \theta = -\cos(180^\circ - \theta)$$

$$= -\cos(\pi - \theta)$$

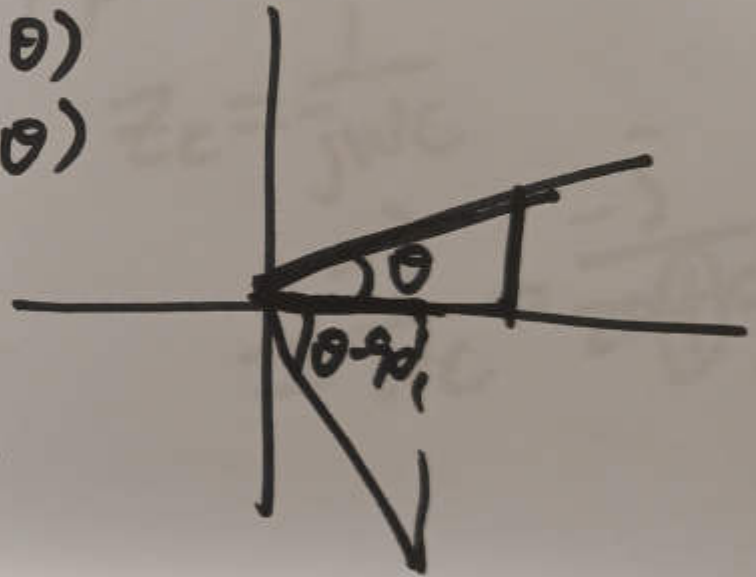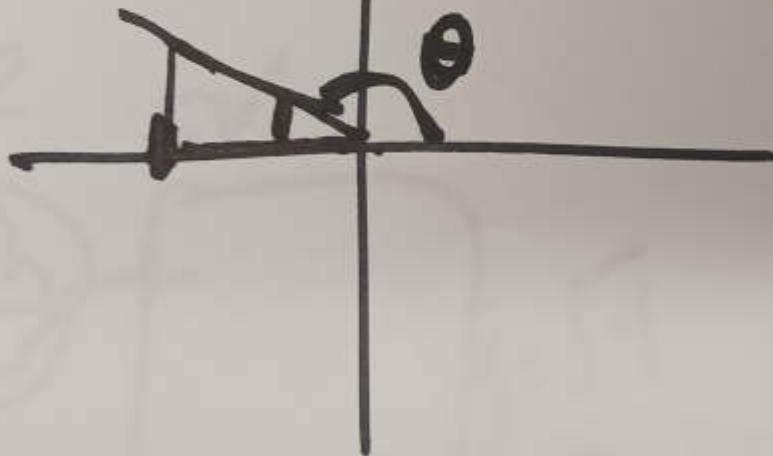

(A)


impedance

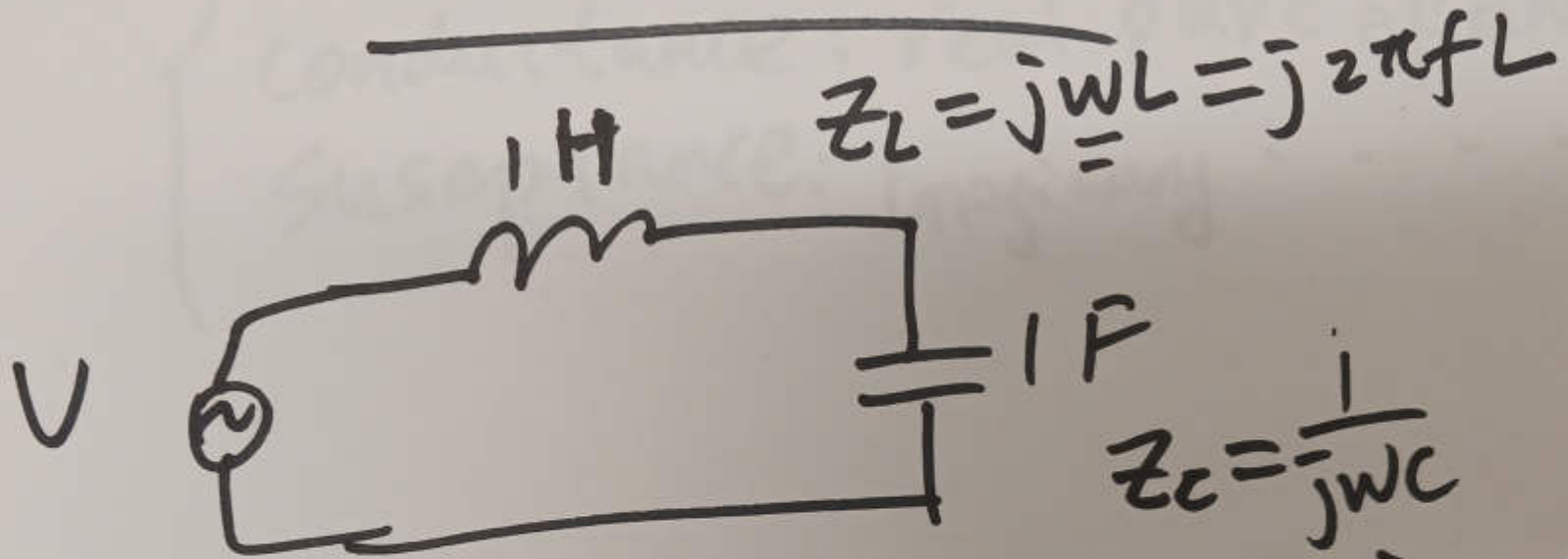

$$Z_L = j\omega L = j2\pi fL$$

$$Z_C = \frac{1}{j\omega C}$$
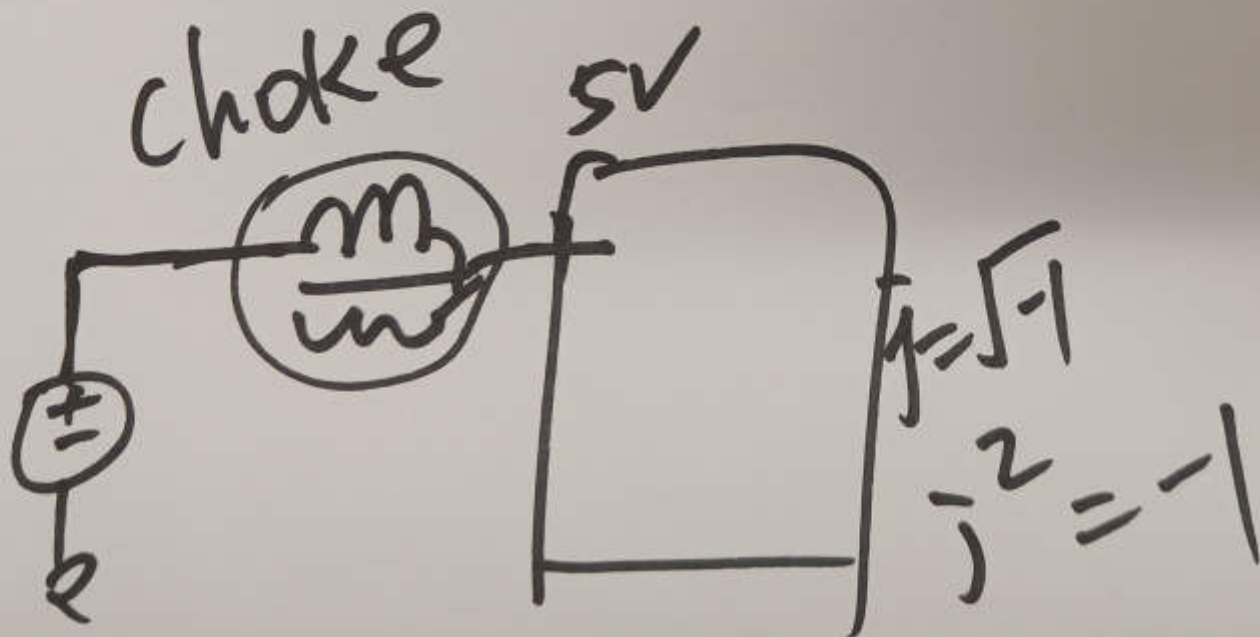
$$= \frac{-j}{\omega C} = \frac{-j}{2\pi f C}$$



$$j^2 = -1$$

{ Admittance : inverse of impedance
conductance : real part of admittance
susceptance : imaginary