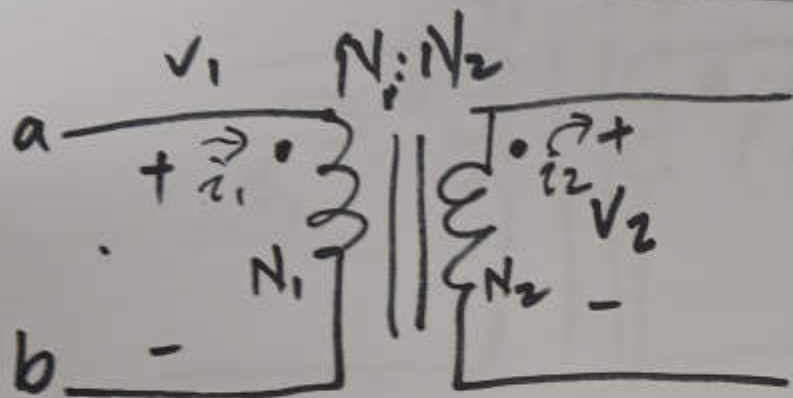


HW10


P9.80

If v_1 and v_2 are both positive or negative at the dotted terminal, then use a plus sign




$$\left| \frac{v_1}{N_1} \right| = \left| \frac{v_2}{N_2} \right|$$

$$\frac{v_1}{N_1} = \frac{v_2}{N_2}$$

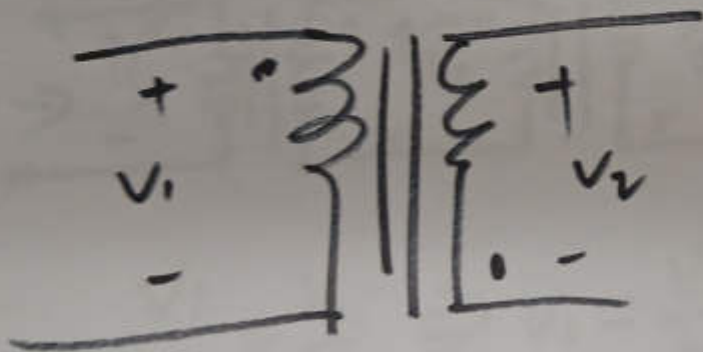


$$\frac{v_1}{N_1} = - \frac{v_2}{N_2}$$

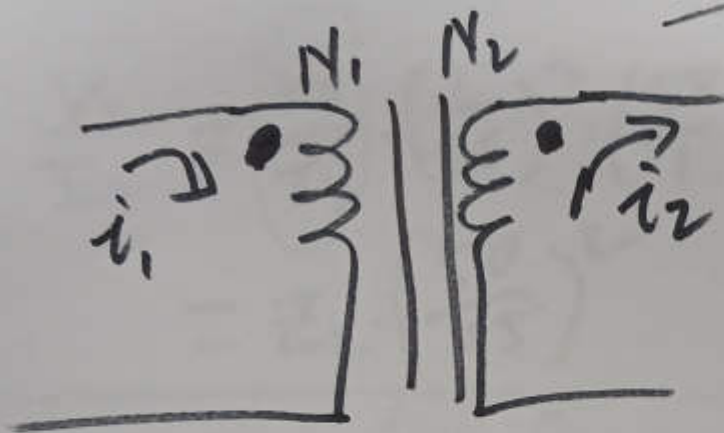If I_1 and I_2 are both directed into or out of the dotted terminal, use a minus sign.



$$|i_1 N_1| = |i_2 N_2|$$

$$i_1 N_1 = i_2 N_2$$

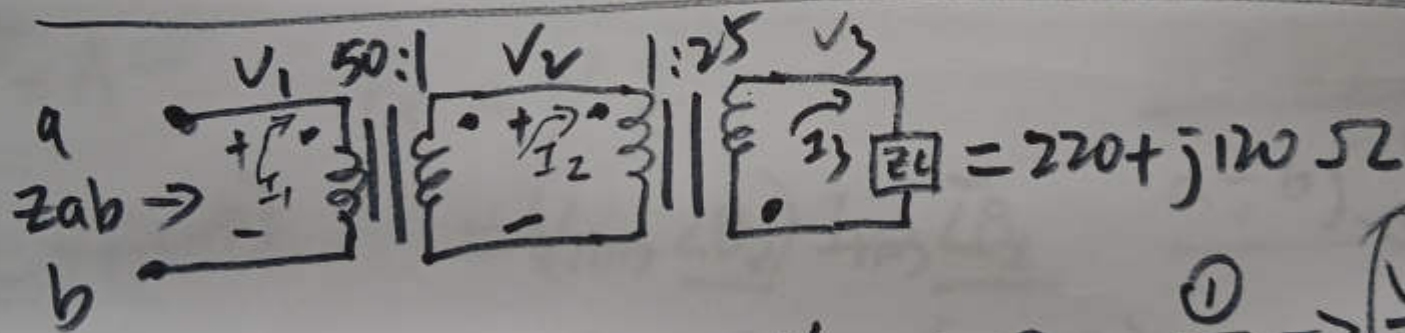

$$\frac{V_1}{N_1} = \frac{V_2}{N_2} \Rightarrow V_1 = \frac{V_2}{N_2} \cdot N_1 \quad (1)$$

$$I_1 N_1 = \pm I_2 N_2$$

$$\Rightarrow I_1 = \frac{I_2}{N_1} N_2 \quad (2)$$

$$\frac{(1)}{(2)} \Rightarrow \frac{V_1}{I_1} = \frac{V_2 N_1}{\frac{I_2}{N_1} N_2}$$


$$= \frac{V_2}{I_2} \left(\frac{N_1}{N_2} \right)^2$$

(2)

$$\frac{V_2}{I_2} = \frac{V_3}{I_3} \cdot \left(\frac{1}{25}\right)^2$$

$$\frac{V_1}{I_1} = \left(\frac{V_3}{I_3}\right) \cdot \left(\frac{1}{25}\right)^2 \cdot \left(\frac{50}{1}\right)^2$$
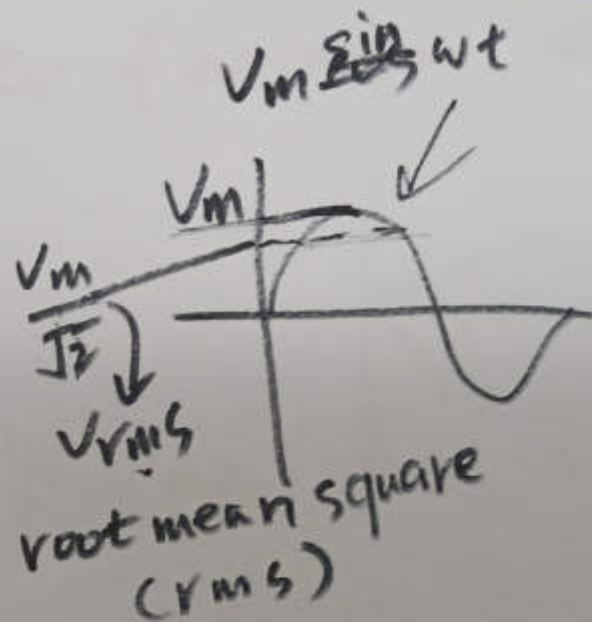
$$= Z_L \cdot \left(\frac{50}{25}\right)^2$$



Complex Power

$$P_x = \underline{V} \cdot \underline{I}^*$$

$$= (V_{rms} \angle \theta_v) I_{rms} \angle \theta_i$$

$$= V_{rms} \cdot I_{rms} \angle (\theta_v - \theta_i)$$

$$= V_{rms} \cdot I_{rms} (\cos(\theta_v - \theta_i) + j \sin(\theta_v - \theta_i))$$

$$= \underbrace{V_{rms} \cdot I_{rms} \cos(\theta_v - \theta_i)}_{\text{average power}} + j \underbrace{V_{rms} I_{rms} \sin(\theta_v - \theta_i)}_{\text{reactive power}}$$

average power
real power "P" watts
reactive power
"Q". VAR, volts amp reactive

$$Ae^{j\theta} = A \cos \theta$$

$$\Downarrow$$

$$A(\cos \theta + j \sin \theta)$$

$$\frac{a + bj}{a - bj} \rightarrow \frac{a + bj}{a + bj} \angle \frac{a + bj}{a - bj}$$


conjugate

$$\frac{a - bj}{a + bj} \rightarrow \sqrt{a^2 + b^2} \angle -\frac{a - bj}{a + bj}$$

(3)

$\cos(\theta_v - \theta_i)$ Power factor

Pf

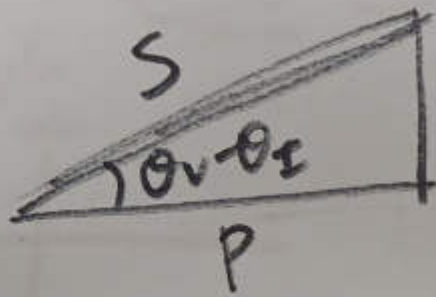

$$S = \sqrt{P^2 + Q^2}$$

→ Apparent Power




$$S \cdot \text{Pf} = P$$

$$S \cdot \sin(\theta_v - \theta_i) = Q$$

$\theta_v > \theta_i$, current lagging,
Pf lagging
 $Q > 0$, → inductive load





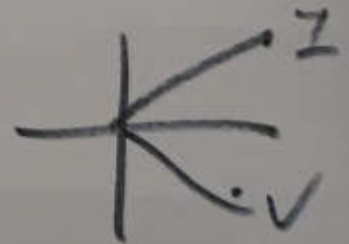$\theta_v < \theta_i$, current leading,
Pf leading, $Q < 0$, → capacitive load



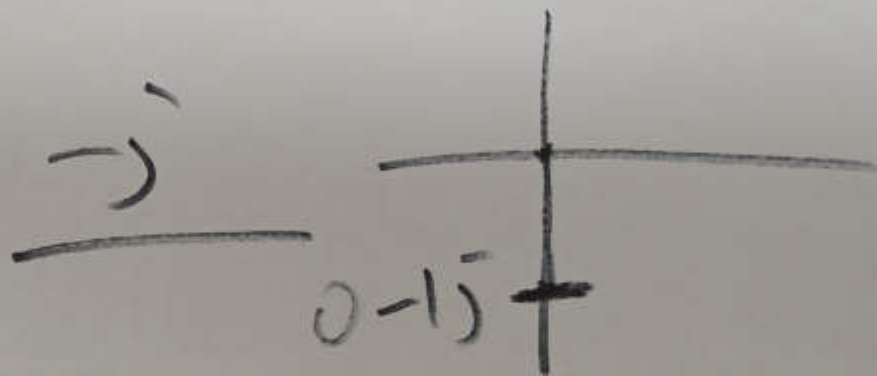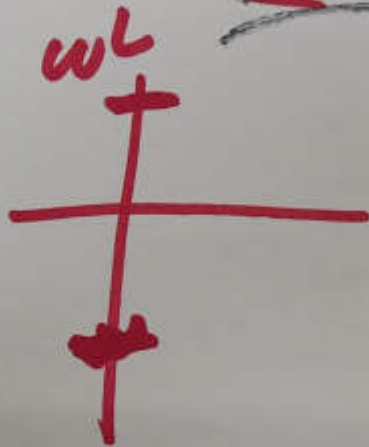(4)

$$I = \frac{V \angle 0^\circ}{j\omega L} = \frac{V}{\omega L} \angle -90^\circ$$



$$I = \frac{V \angle 0^\circ}{\frac{-j}{\omega C}} = \frac{V}{\omega C} \angle 90^\circ$$

(5)