

$$E = \frac{1}{2} C V^2$$


$$V(t) = \frac{-40 \text{ mA} (100 \mu\text{s} - 0) + 10 \text{ V}}{200 \cdot 10^{-9} \text{ F}}$$

↑


$0 < t < 100 \mu\text{s}$

$$V(t) = \frac{80 \text{ mA}}{200 \cdot 10^{-9} \text{ F}} (300 \mu\text{s} - 100 \mu\text{s}) + \underline{\underline{V(100 \mu\text{s})}}$$


$100 \mu\text{s} < t < 300 \mu\text{s}$

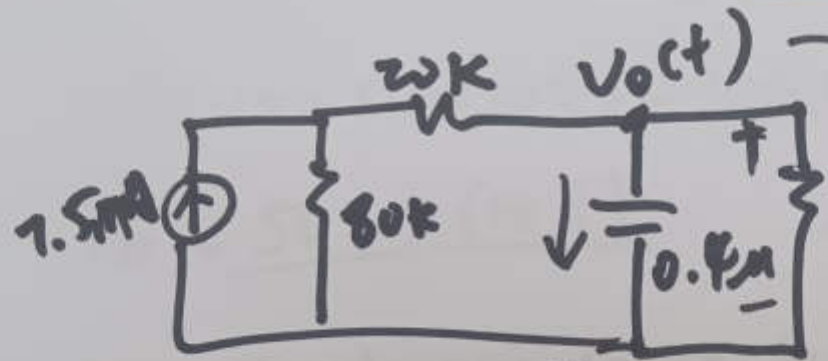

$$V(s) = V_o(s) \cdot e^{-s/\omega_c}$$

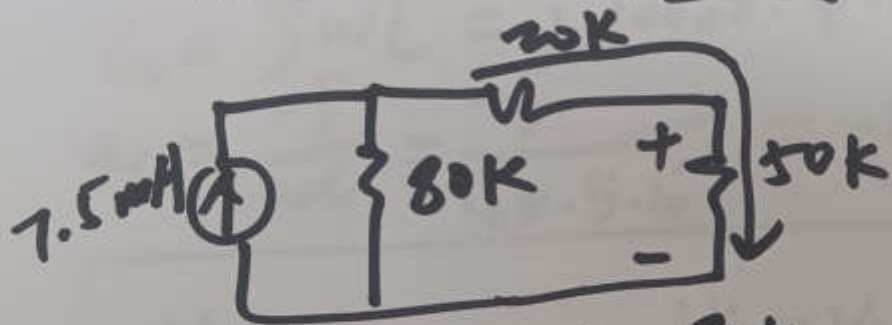
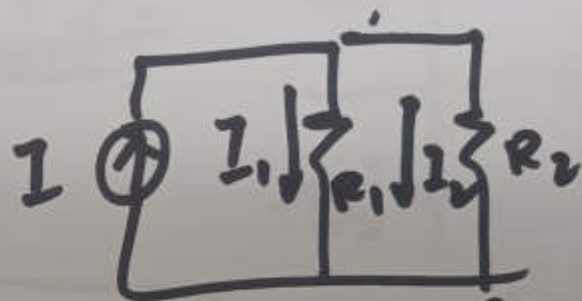
$$V_o(s) = \frac{7.5 \text{ mA} \cdot 80 \text{ K}}{150 \text{ K}} \cdot 50 \text{ K}$$



$$I_1 = \frac{I \cdot R_2}{R_1 + R_2}$$


$$I_2 = \frac{I \cdot R_1}{R_1 + R_2}$$

$$V_a = 100 \sin(\omega t) = \underline{100 \cos(\omega t - 90^\circ)}$$

$$V_b = \underline{50 \cos(\omega t)} \quad \underline{100 \angle -90}$$

$$Z_L = j\omega L = j \cdot 10000 \cdot 4 \cdot 10^{-3} = \underline{40j}$$
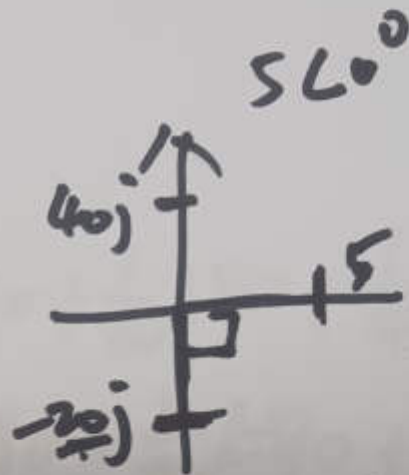
$$Z_C = \frac{-j}{\omega C} = \frac{-j}{10k \cdot 5 \cdot 10^{-6}} = \underline{-20j}$$



$20 \angle -90^\circ$

$$\boxed{\frac{V_a - V_1}{40j} + \frac{V_b - V_1}{-20j} = \frac{V_1}{40}}$$

$$\frac{100 \angle -90^\circ - V_1}{40 \angle 90^\circ} + \frac{50 \angle 0^\circ - V_1}{-20 \angle -90^\circ} = \frac{V_1}{40}$$

$$\frac{100 \angle -90}{40 \angle 90} - \frac{V_1 \angle 0}{40 \angle 90} + \frac{50 \angle 0}{20 \angle -90} - \frac{V_1 \angle 0}{20 \angle -90} = \frac{V_1}{40}$$

(3)

$$2.5 \angle -180^\circ - \frac{V_1}{40} \angle -90^\circ + 2.5 \angle 90^\circ$$

$$- \frac{V_1}{20} \angle 90^\circ = \frac{V_1}{40}$$

$$2.5 \angle -180^\circ + 2.5 \angle 90^\circ = V_1 \left(\frac{1}{40} \angle -90^\circ + \frac{1}{20} \angle 90^\circ + \frac{1}{40} \right)$$

$$= V_1 \left(\frac{1}{40} \angle -90^\circ - \frac{1}{20} \angle 90^\circ + \frac{1}{40} \right)$$

$$2.5 \angle -180 + 2.5 \angle 90$$

$$3.5 \angle 135$$

$$= V_1 \left(\frac{1}{40} \angle 90 + \frac{1}{40} \right) \frac{1}{40}$$

$$= \frac{V_1}{40} \cdot 1.41 \cdot \angle 45^\circ$$

$$V_1 = 3.5 \angle 135 \cdot \frac{1.41}{40} \angle 45^\circ$$

$$= 0.12 \cdot \angle 180$$

$$= 0.12 (\cos 180 + j \sin 180)$$

$$= 0.12 (-1 + j0) = -0.12$$



$$\frac{-100\bar{j} - V_1}{40j} + \frac{50 - V_1}{-20j} = \frac{V_1}{40}$$

$$\times 40j: \quad -100\bar{j} - V_1 - 2(50 - V_1) = V_1\bar{j}$$

$$-100\bar{j} - \underline{V_1} - 100 + \underline{2V_1} = V_1\bar{j}$$

$$-100\bar{j} - 100 \neq = -V_1 + V_1\bar{j}$$

$$-100\bar{j} - 100 = V_1(\bar{j} - 1)$$

$$V_1 = \frac{-100\bar{j} - 100}{\bar{j} - 1}$$

-1-1

~~$$= \frac{100}{-2}$$~~

$$\begin{aligned}
 V_1 &= 100 \frac{j+1}{1-j} \\
 &= 100 \frac{(j+1)(1+j)}{(j+1)(1-j)} \\
 &= 50 \cdot \left(\frac{2}{1+1+2j} \right) \\
 &= 100j
 \end{aligned}$$

$$\begin{aligned}
 v_b &= \frac{V_b - 100j}{-20j} = \frac{50 - 100j}{-20j} = \frac{50j + 100}{20} \\
 &= 5 + 2.5j \\
 &= \sqrt{5^2 + 2.5^2} \cdot \cos(\omega t + \arctan \frac{2.5}{5})
 \end{aligned}$$

(6)