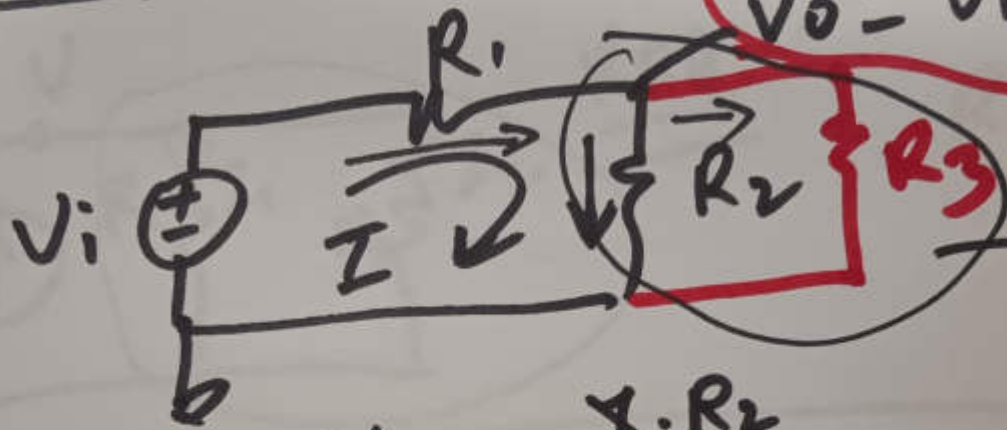


①

Voltage divider




$$V_o = V_i \frac{R_2}{R_1 + R_2}$$

$$\frac{V_o}{V_i} = \frac{I \cdot R_2}{I \cdot (R_1 + R_2)} = \frac{R_2}{R_1 + R_2}$$

$$V_o = V_i \cdot \frac{R_2 \parallel R_3}{R_1 + R_2 \parallel R_3}$$

② Current Divider

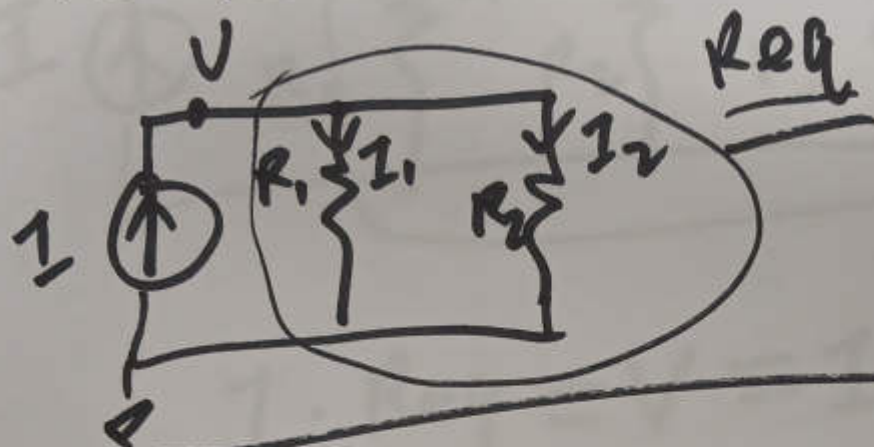


$$R_{eq} = R_1 \parallel R_2 \\ = \frac{R_1 \cdot R_2}{R_1 + R_2}$$

$$I \cdot R_{eq} = V = R_1 \cdot I_1 = R_2 \cdot I_2$$

$$I \cdot \frac{R_1 \cdot R_2}{R_1 + R_2} = R_1 \cdot I_1$$

$$I_1 = I \cdot \frac{R_2}{R_1 + R_2}$$

②

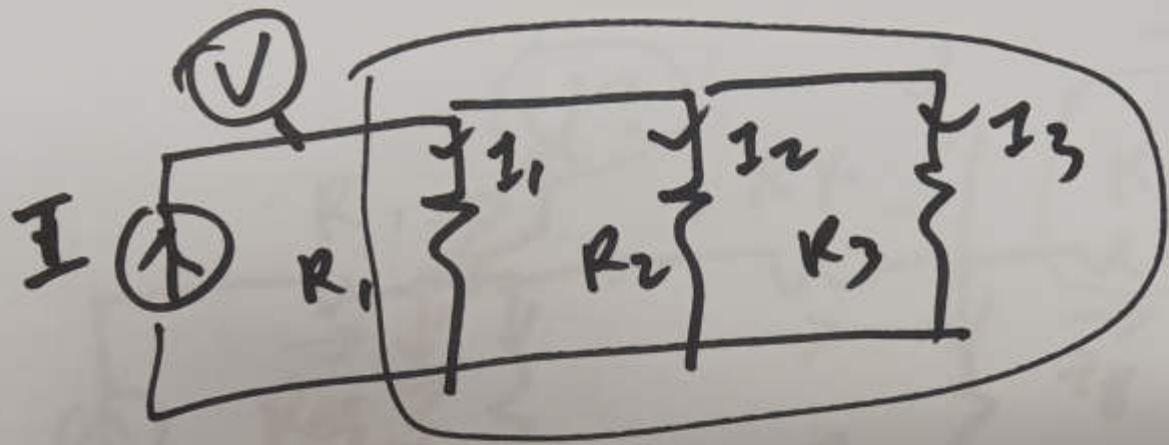


$$I \cdot R_{eq} = V = I_1 \cdot R_1 = I_2 \cdot R_2 = I_3 \cdot R_3$$

$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$



$$I \cdot \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} = I_1 \cdot R_1$$

$$I_1 = I \cdot \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) \cdot R_1$$



③

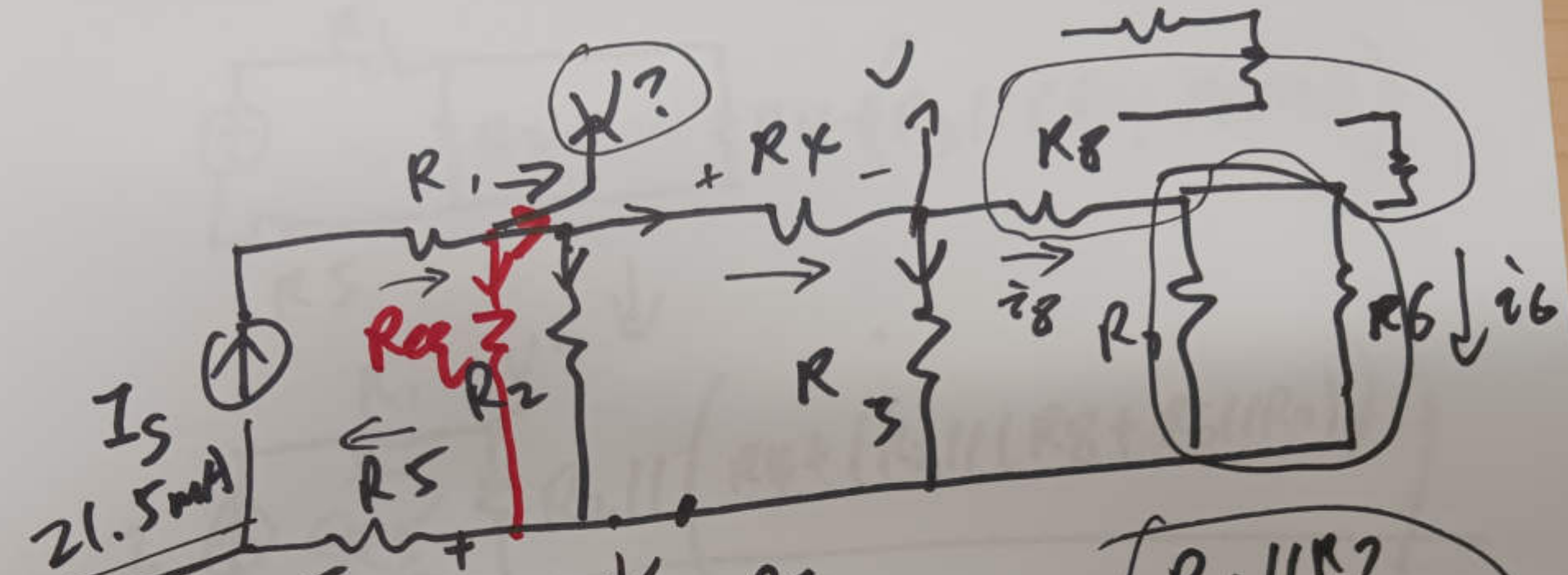

$$R_6 || R_7 = \frac{R_6 \cdot R_7}{R_6 + R_7}$$

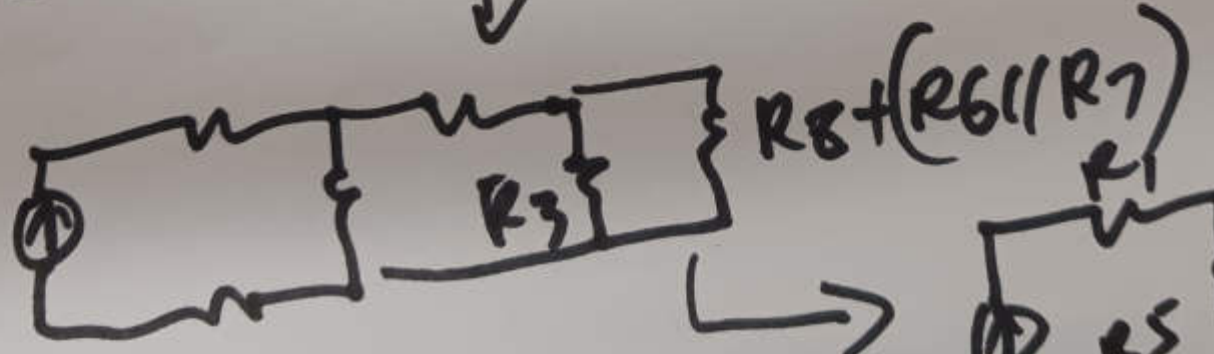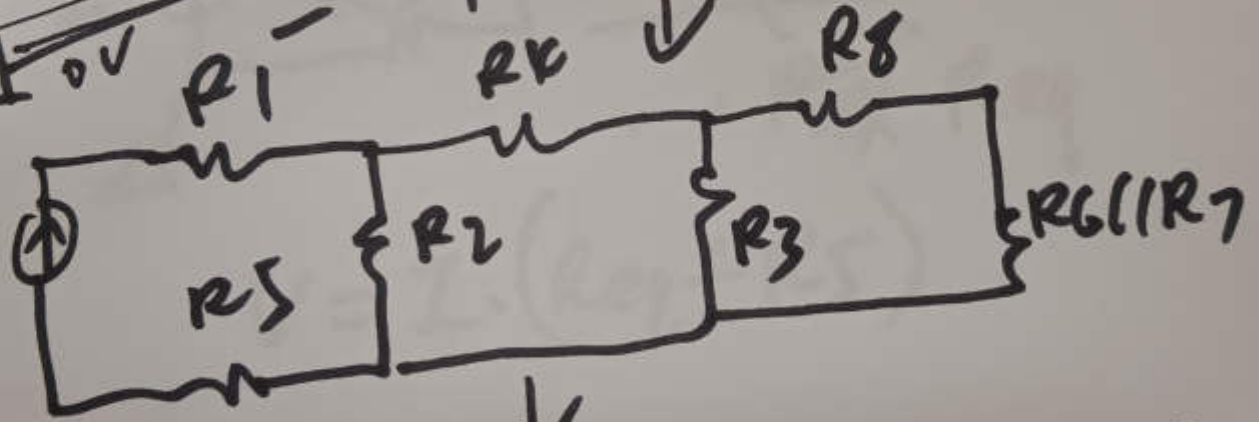


(4)

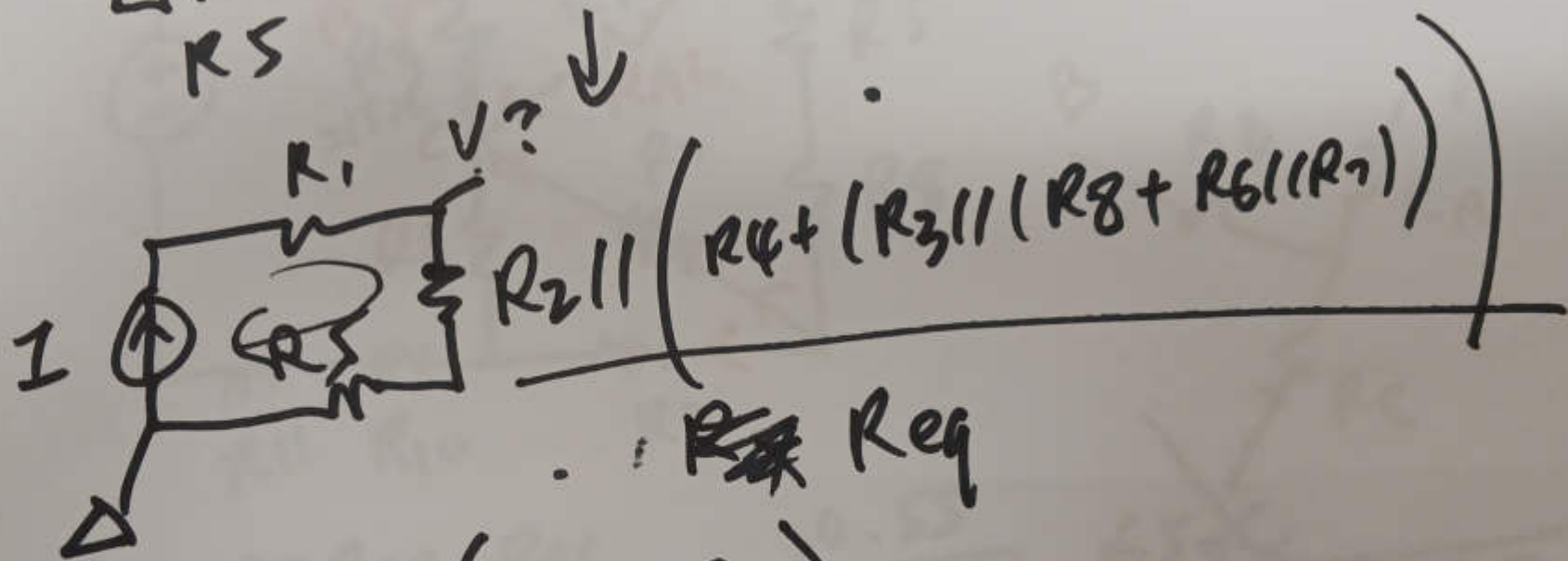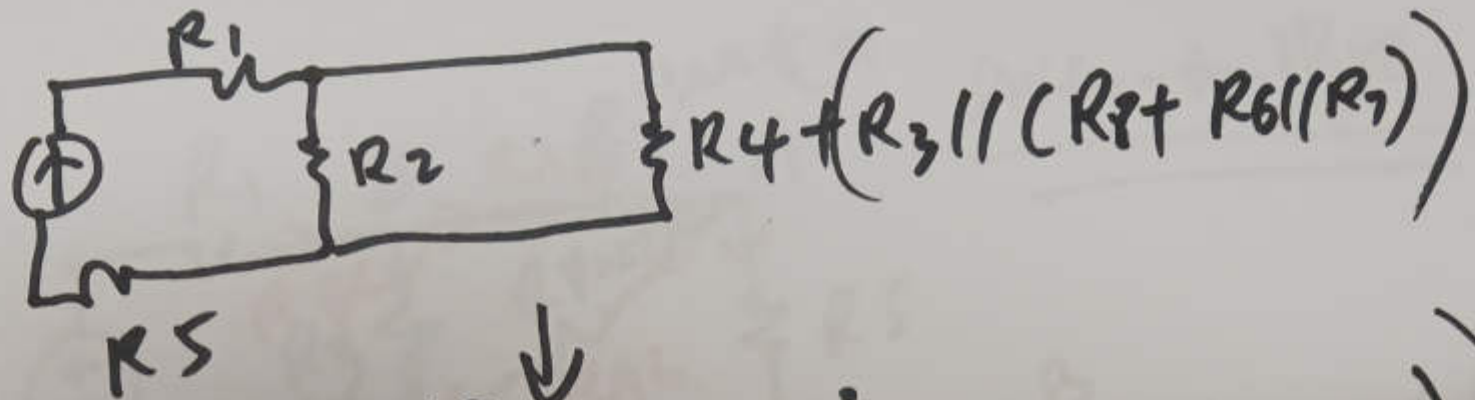


$$V = I \cdot (R_{eq} + R_5)$$

5

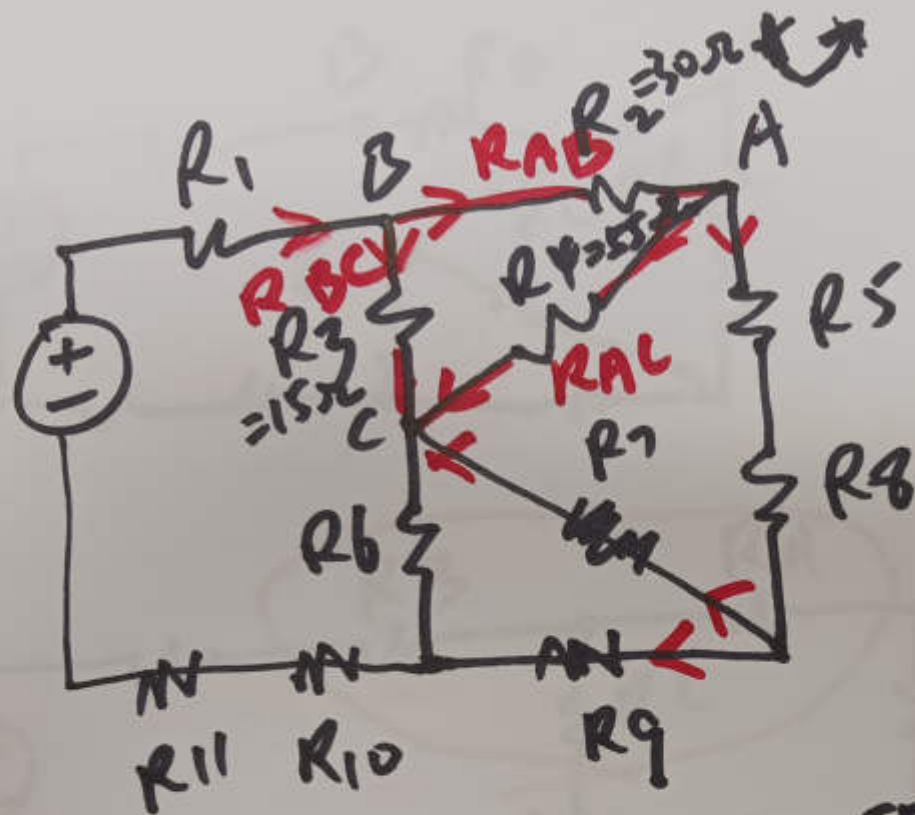

Delta-to-Wye



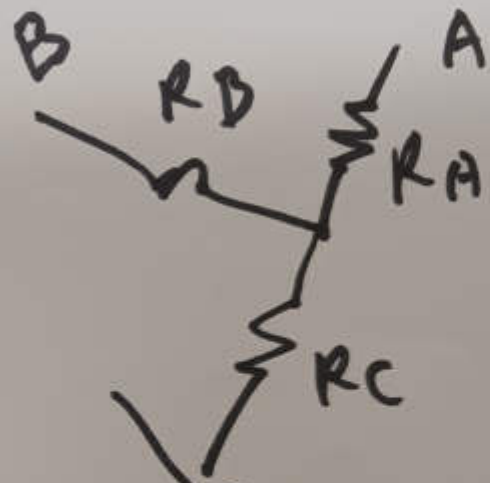


$$R_A = \frac{R_{AB} \cdot R_{AC}}{R_{AB} + R_{AC} + R_{BC}} = \frac{30 \cdot 55}{100} = \frac{1650}{100} = 16.5 \Omega$$



$$R_B = \frac{R_{AB} \cdot R_{BC}}{R_{AB} + R_{AC} + R_{BC}} = \frac{30 \cdot 15}{100} = \frac{450}{100} = 4.5 \Omega$$

$$R_C = \frac{R_{AC} \cdot R_{BC}}{R_{AB} + R_{AC} + R_{BC}} = \frac{55 \cdot 15}{100} = \frac{825}{100} = 8.25 \Omega$$

⑥

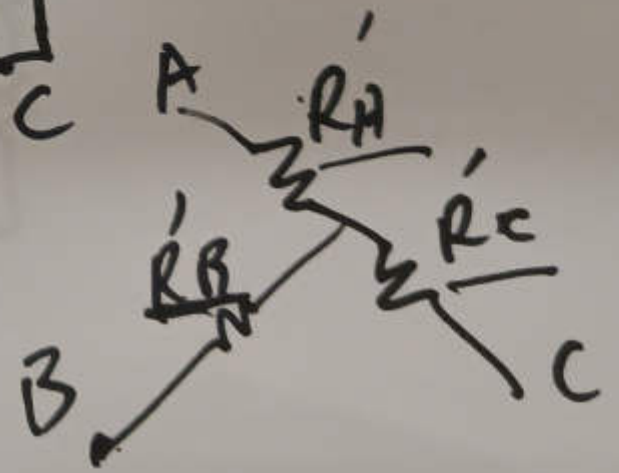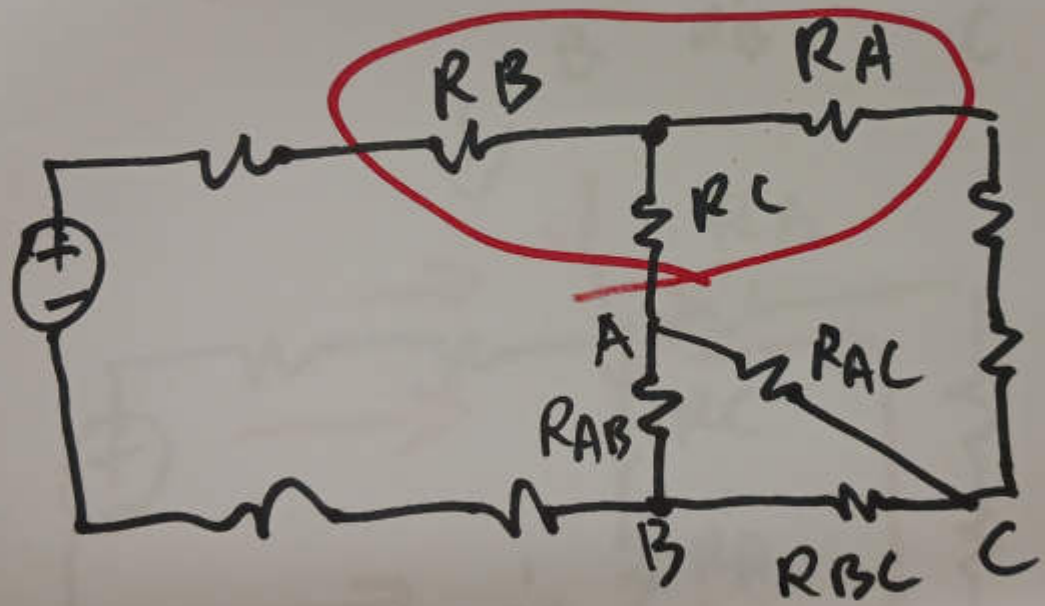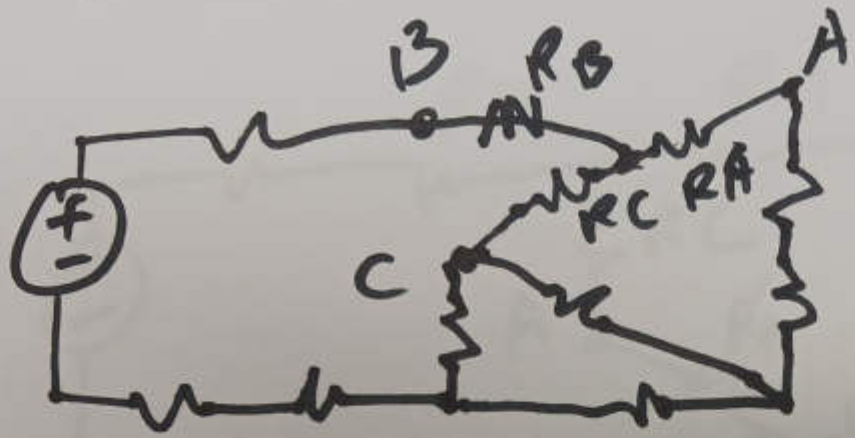

①

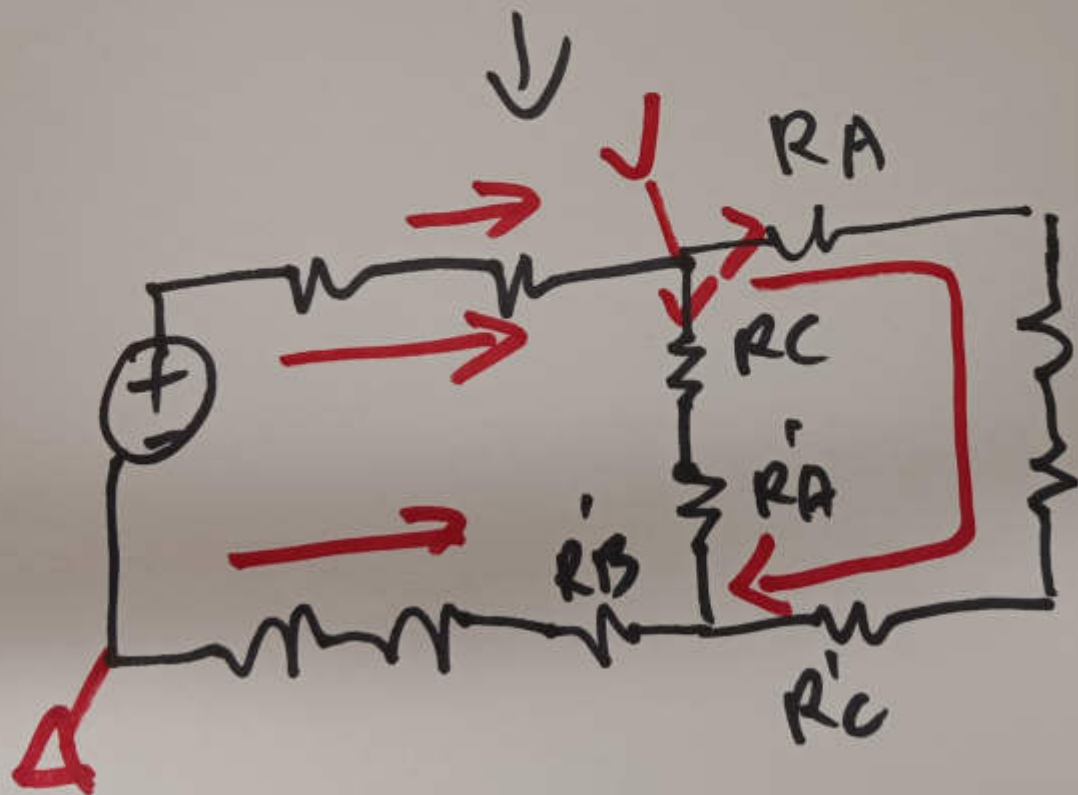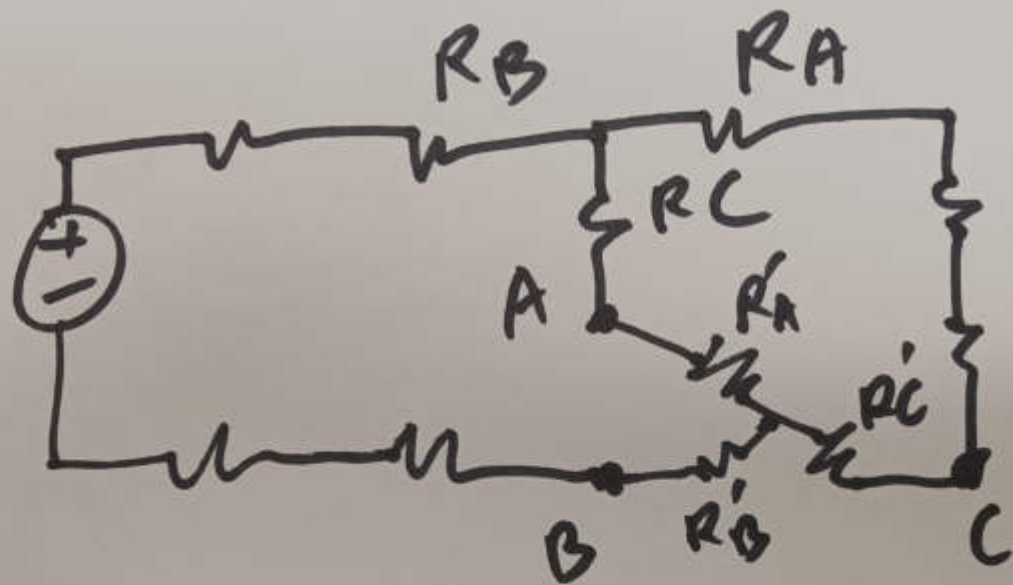

(8)