


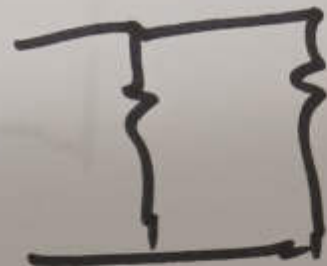
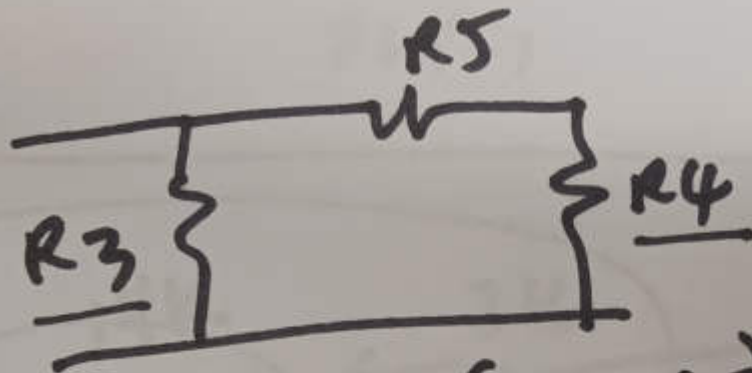
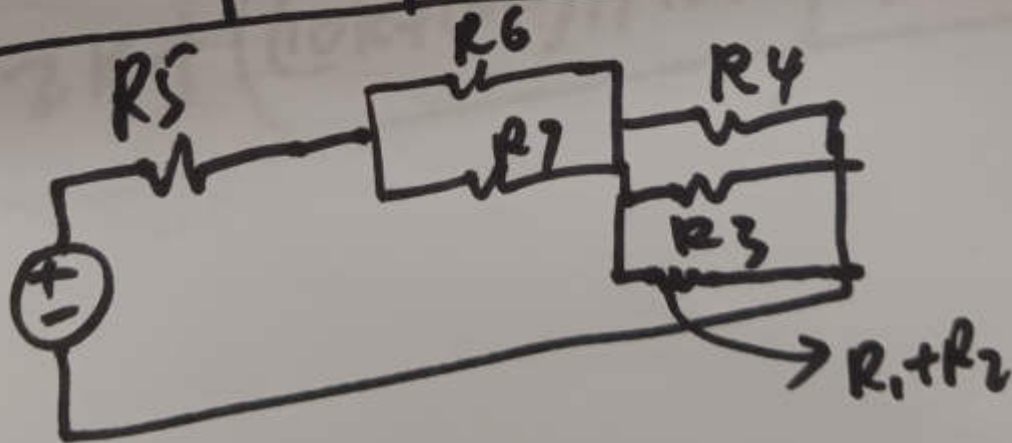


# HW 3

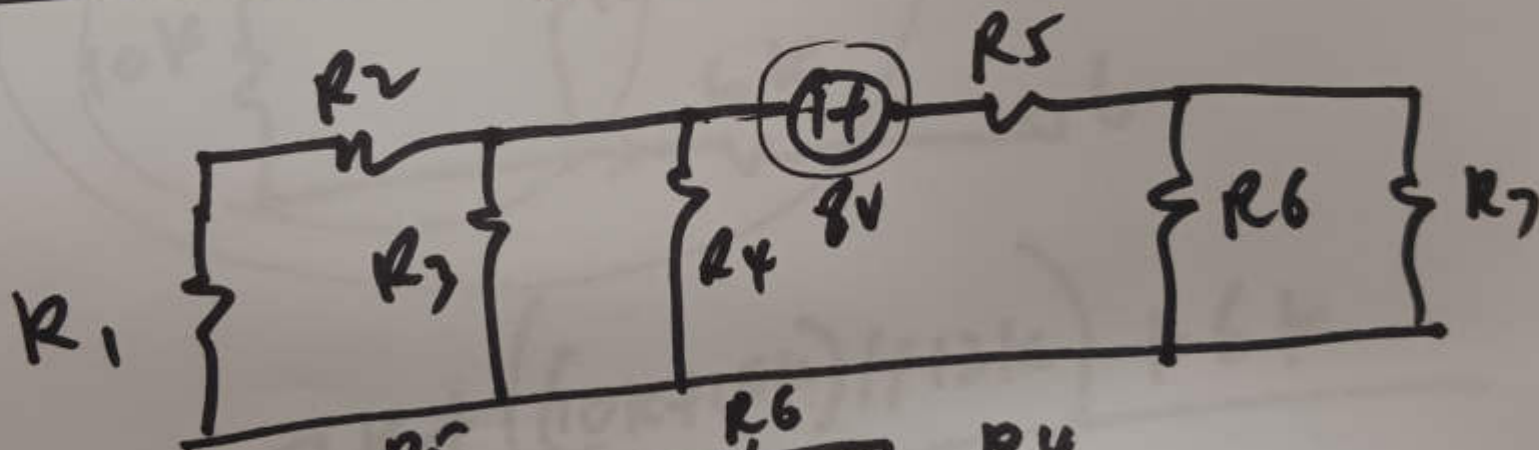



$$R_3 \parallel (R_4 + R_5)$$

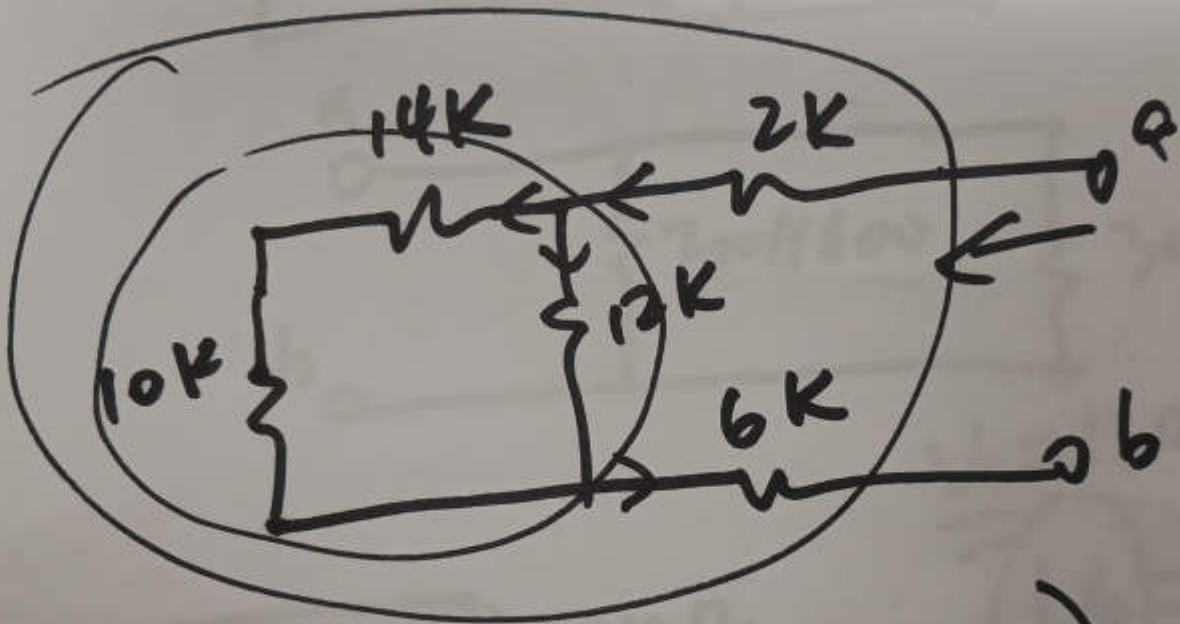

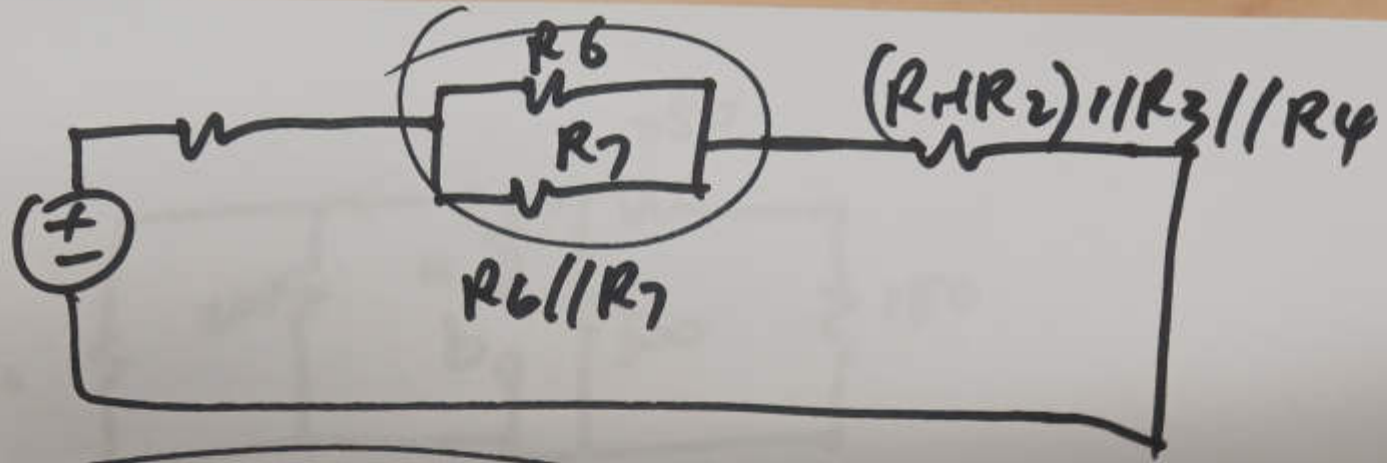


$$2k + \left( (10k + 14k) || 12k \right) + 6k$$

②

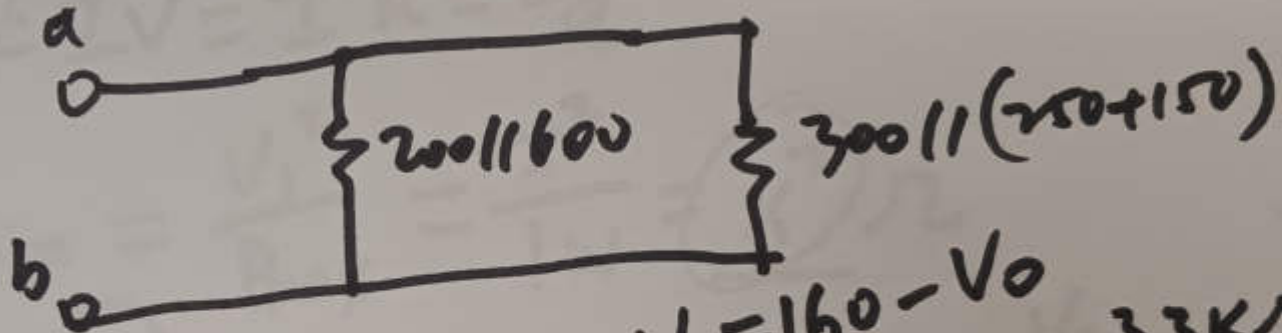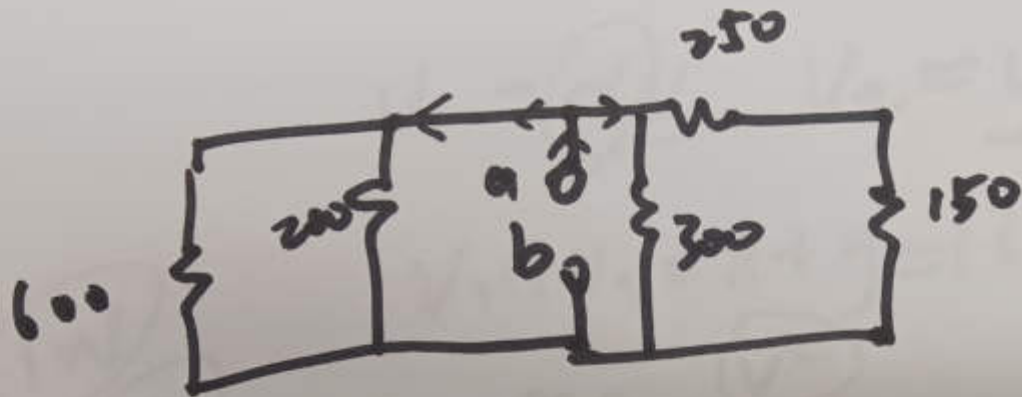

$$V_1 = 160 - V_0$$
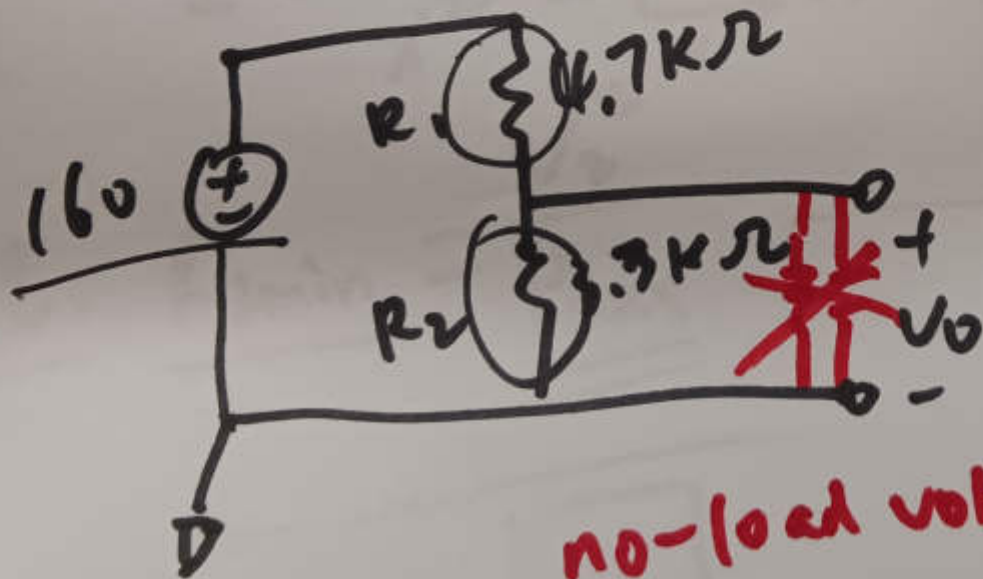
$$V_0 = 160 \cdot \frac{3.3K\Omega}{4.7K\Omega + 3.3K\Omega}$$



$R_{min}$  and  $R_{min}$   
if  $P_{max}$  1.0W

$$V_1 = xV \quad V_2 = yV.$$

$$V_1 + V_2 = x + y = 160V$$

$$P = IV = I^2 R = \frac{V^2}{R}$$


$$\text{Case 1: } R_{\min} = \frac{V_1^2}{P_{\max}} = \frac{x^2}{1W} = x^2 \Omega$$

$$I = \frac{V_1}{x^2} = \square A \Rightarrow R_2 = \frac{V_2}{I} = \square \Omega$$

$$\text{Case 2: } \underline{\underline{R_{\min}}} = \underline{\underline{\frac{V_2^2}{P_{\max}}}}$$



$$R_1 = \square$$

④

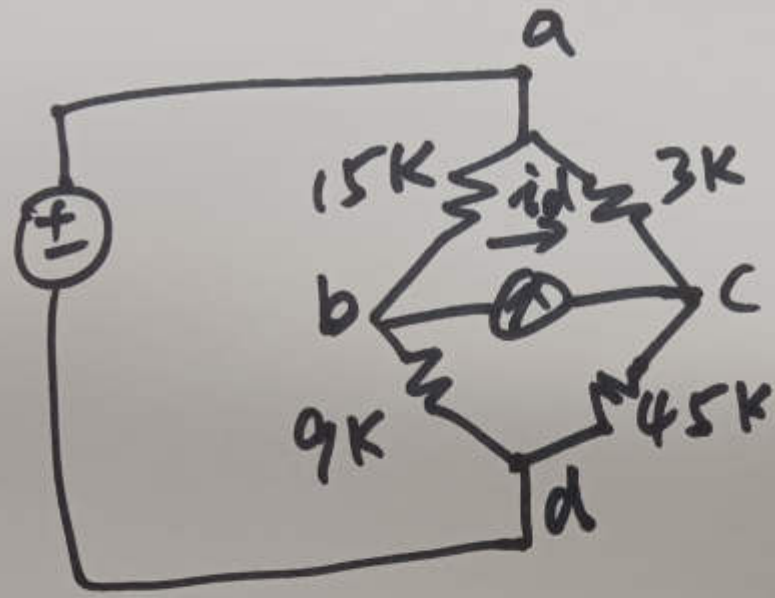

$V_{bc} \rightarrow 0$   
 $i_d?$

$V_{ad} = V_s$

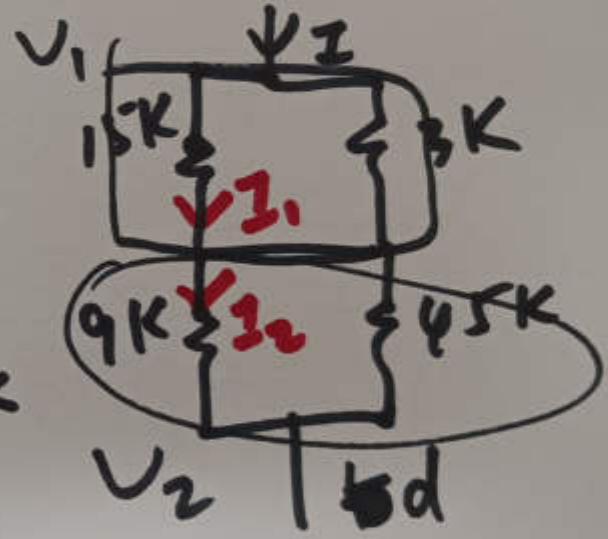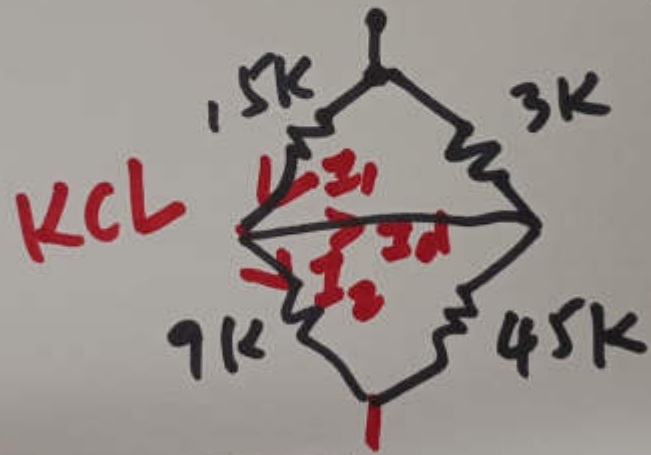

$$I = \frac{V_s}{\frac{15K \cdot 3K}{15K + 3K} + \frac{9K \cdot 45K}{9K + 45K}}$$

$$V_1 = I \cdot \frac{15K \cdot 3K}{15K + 3K}$$

$$V_2 = I \cdot \frac{9K \cdot 45K}{9K + 45K}$$

15