
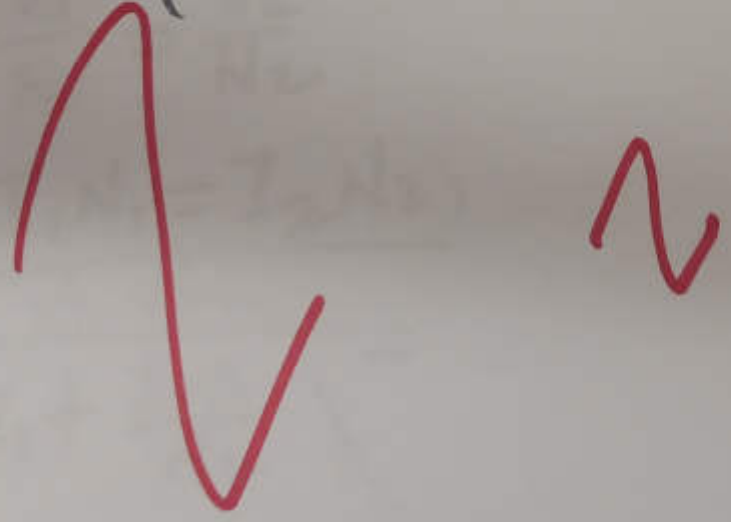


$$\left| \frac{V_1}{N_1} \right| = \left| \frac{V_2}{N_2} \right|$$

$$\left| \frac{V_1}{V_2} \right| = \left| \frac{N_1}{N_2} \right|$$

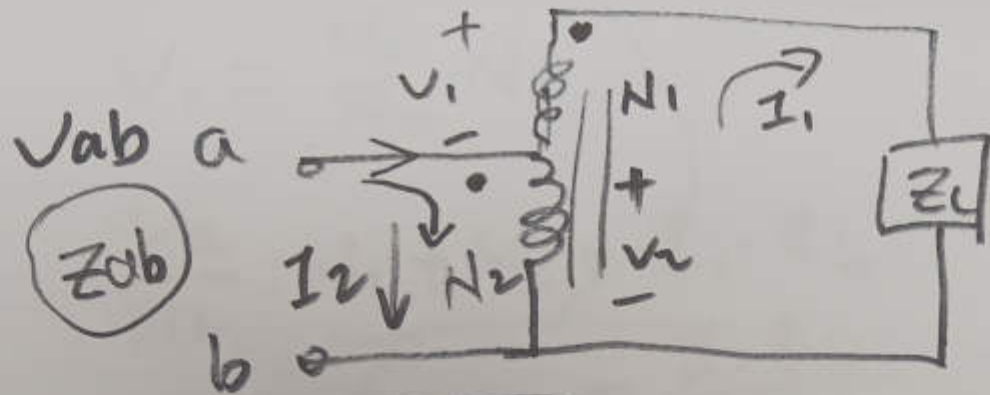

①



$$Z_{ab} = \frac{V_{ab}}{I_1 + I_2}$$

$$V_{ab} = V_2$$

$$V_1 + V_2 = I_1 \cdot Z_L$$

$$\frac{V_1}{N_1} = \frac{V_2}{N_2}$$

$$I_1 N_1 = I_2 N_2$$

$$Z_{ab} = \frac{V_2}{I_1 + \frac{I_1 N_1}{N_2}} =$$

$$\left| \frac{V_1}{N_1} \right| = \left| \frac{V_2}{N_2} \right| \quad |I_1 N_1| = |I_2 N_2|$$

$$\frac{V_1}{N_1} = \pm \frac{V_2}{N_2}, \quad I_1 N_1 = \pm I_2 N_2$$

Both + or -
at the dot

$$\frac{V_1}{N_1} = \frac{V_2}{N_2}$$

One current
goes into,
one goes
out of the
dot

$$I_1 N_1 = I_2 N_2$$

(2)

$$V_1 = \frac{V_2}{N_2} \cdot N_1$$


$$\frac{V_2}{N_2} \cdot N_1 + V_2 = I_1 \cdot Z_L$$

$$V_2 = \frac{I_1 \cdot Z_L}{1 + \left(\frac{N_1}{N_2}\right)}$$

Part B.

$$\frac{V_1}{N_1} = -\frac{V_2}{N_2}$$

$$I_1 \cdot N_1 = -I_2 \cdot N_2$$

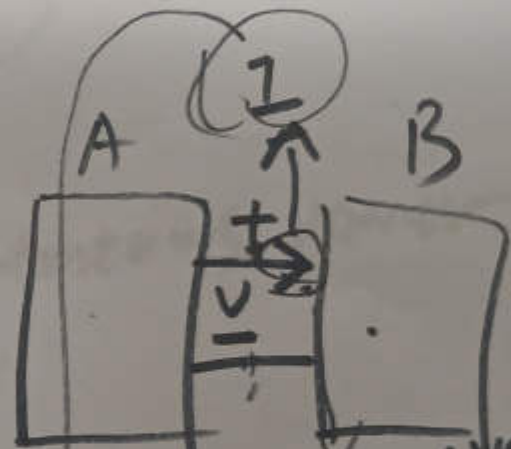

pos reactive power.
B is absorbing

P10.1

$$v = 120 \cos(\omega t - 45^\circ) \text{ V}$$


$$i = 25 \cos(\omega t + 15^\circ) \text{ A}$$

reactive power $\frac{v_m \cdot i_m}{2} \sin(-45 - 15)$

Average power: $\frac{v_m \cdot i_m}{2} \cos(-45 - 15)$

(3)

P10.7.

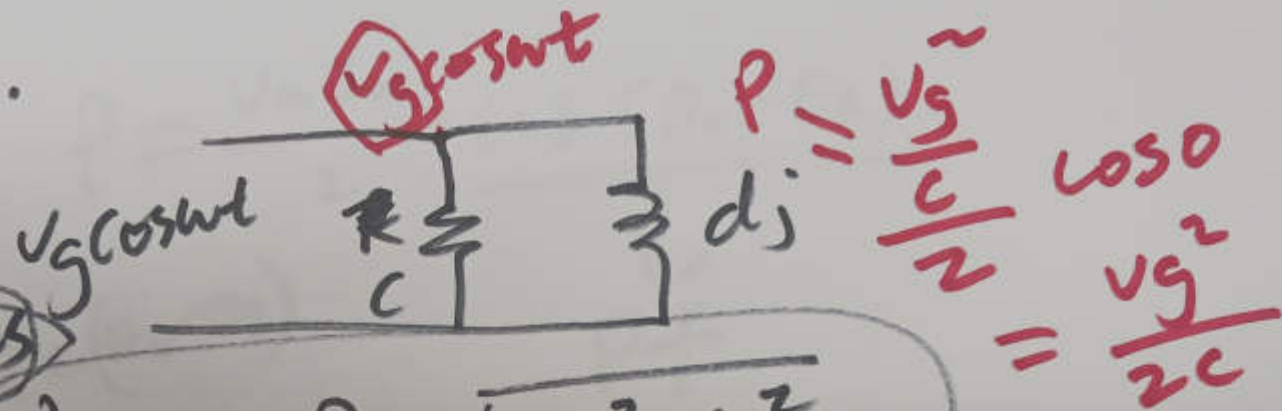

instantaneous power

$$P_{\max} = P + \sqrt{P^2 + Q^2}$$

$$P_{\min} = P - \sqrt{P^2 + Q^2}$$

Part A

Peak value of instantaneous power delivered by source.

Part B:

absorbed

$$P = \frac{V_m I_m}{2} \cos(\theta_1 - \theta_2)$$

$$\frac{V \cos \theta_1}{I \cos \theta_2} = Z \angle (\theta_1 - \theta_2)$$

↓
PF

OC PF < 1

↘ Higher efficiency

$$PF = \cos(\theta_1 - \theta_2) = \frac{P}{\sqrt{P^2 + Q^2}} = \frac{P}{S}$$

↓
impedance
angle

↓
apparent
power

(5)

$$S = \sqrt{P^2 + Q^2}$$

$$Pf = \frac{P}{\sqrt{P^2 + Q^2}} = \frac{P}{S} = \cos(\theta_v - \theta_i)$$

P10.41.

