
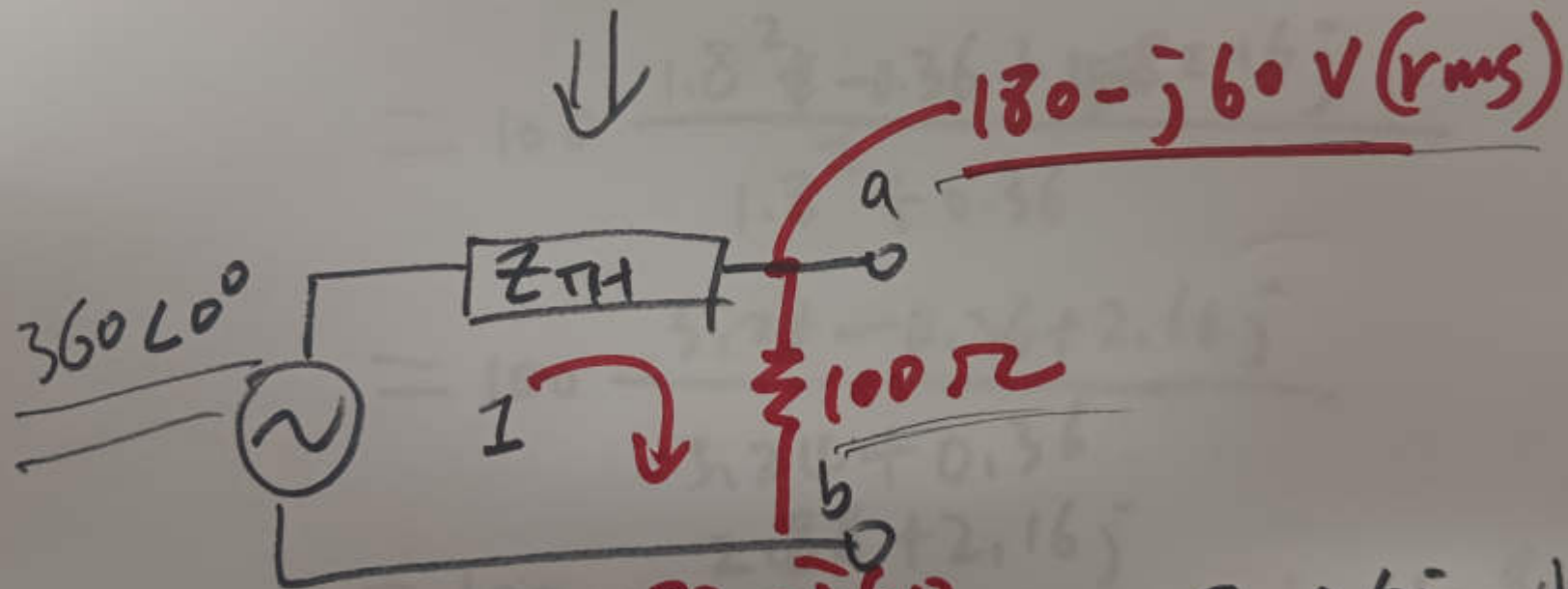


10.41.

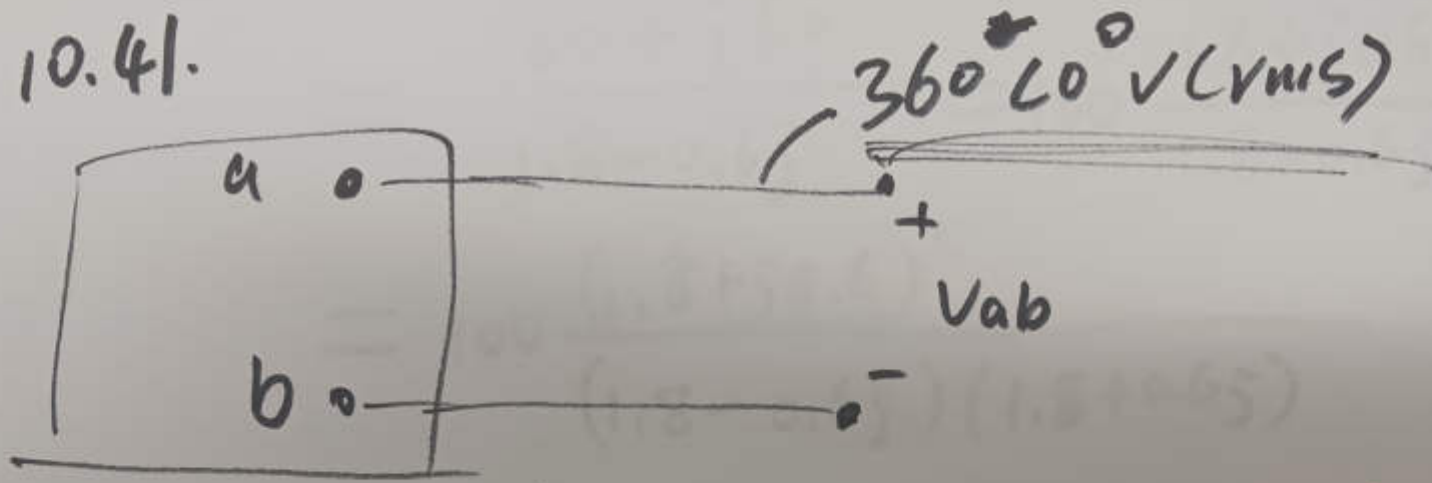


$$I = \frac{180 - j60}{100} = 1.8 - 0.6j \text{ A (rms)}$$

$$Z_{TH} = \frac{360 \angle 0^\circ - 180 + j60}{I} = \frac{360 - 180 + j60}{1.8 - 0.6j}$$

①

$$\begin{aligned}
&= \frac{180 + j60}{1.8 - 0.6j} = 100 \frac{1.8 + j0.6}{1.8 - 0.6j} \\
&= 100 \frac{(1.8 + j0.6)^2}{(1.8 - 0.6j)(1.8 + 0.6j)} \\
&= 100 \frac{1.8^2 - 0.36 + \cancel{108} 2.16j}{1.8^2 + 0.36} \\
&= 100 \frac{3.24 - 0.36 + 2.16j}{3.24 + 0.36} \\
&= 100 \cdot \frac{2.88 + 2.16j}{3.6} = 100(0.8 + 0.6j) \\
&= 80 + 60j
\end{aligned}$$

(2)

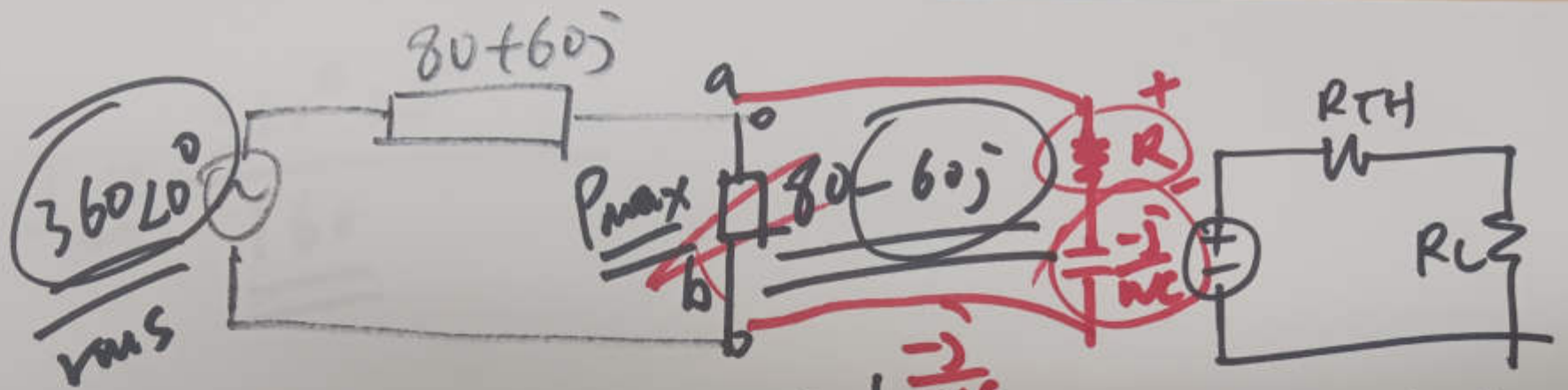

Corrected $\frac{-j}{\omega C}$

power correction

$$P = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$$

$$\frac{-j}{\omega C} = -j60 \Rightarrow \underline{\underline{C = 0}}$$



$$I = \frac{V \cos \theta_v}{R} = \frac{V}{R} \cos \theta_v$$

44 μF




220 μF

$$I_{\text{rms}} = \frac{360^\circ 40^\circ}{\underline{\underline{160}}}$$

$$P = I_{\text{rms}}^2 \cdot R$$

$$P = \frac{(I_{\text{rms}} \cdot R)^2}{R}$$

source, Line | Load

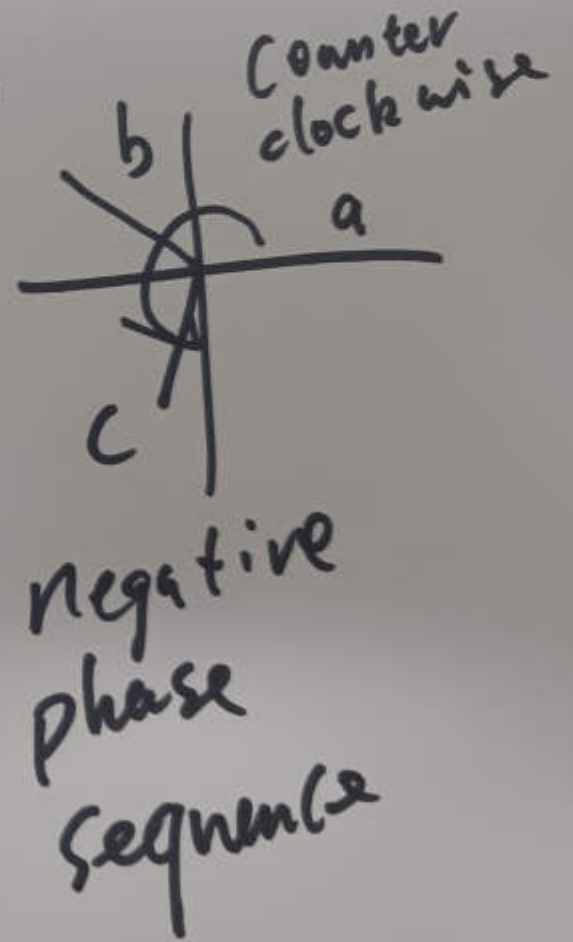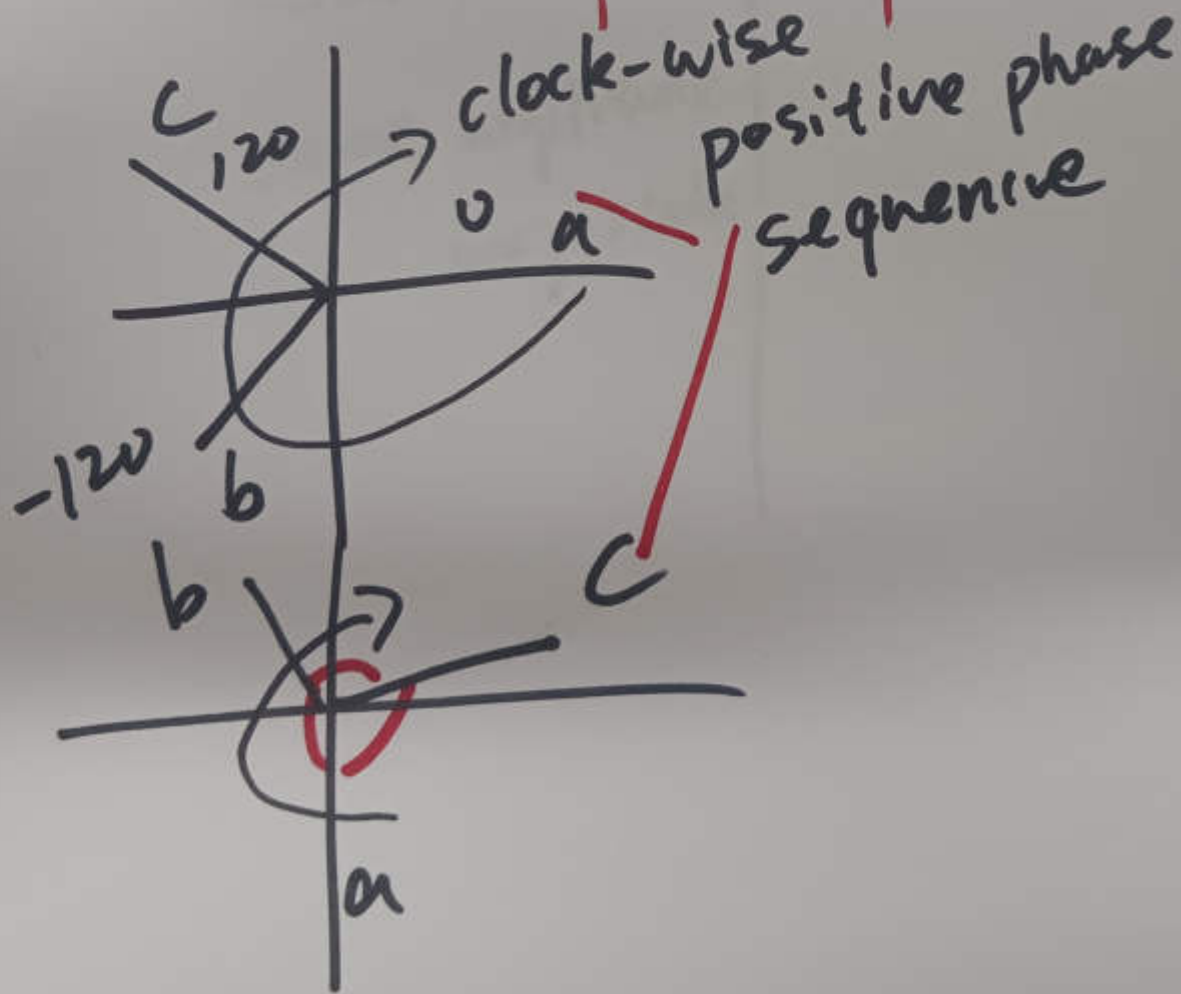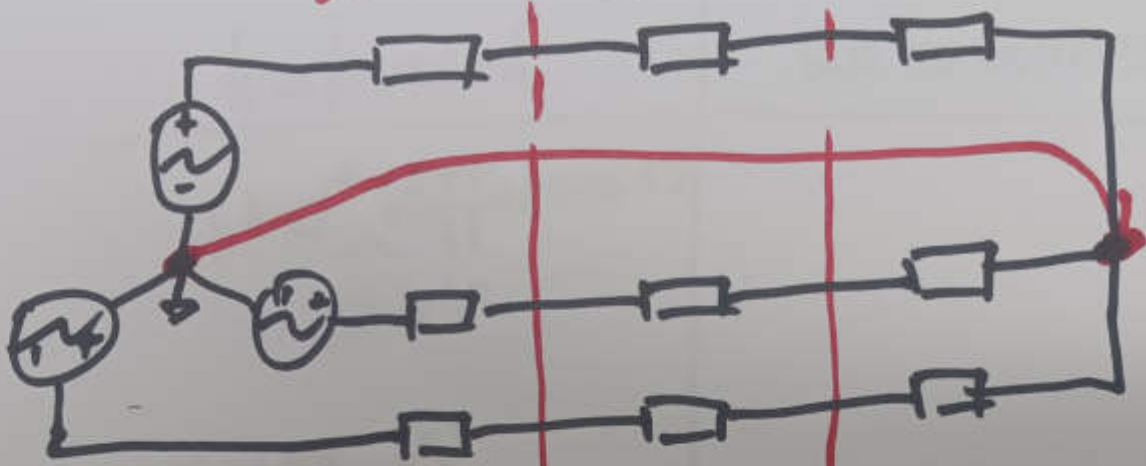

5

balanced	un balanced
120° differences phase	
same ω	
same amplitude magnitude	

6