

$$I_a = \frac{240 \angle 0^\circ}{80 + 60j} = \frac{240 \angle 0^\circ}{100 \angle 36.87^\circ} = 2.4 \angle -36.87^\circ$$

$$I_b = \frac{240 \angle -120^\circ}{80 + 60j} = \frac{240 \angle -120^\circ}{100 \angle 36.87^\circ} = 2.4 \angle -156.87^\circ$$

$$I_c = \frac{240 \angle 120^\circ}{80 + 60j} = \frac{240 \angle 120^\circ}{100 \angle 36.87^\circ} = 2.4 \angle 83.13^\circ$$

$$I_o = I_a + I_b + I_c = \cancel{2.4 \angle -96.87^\circ} + 0 \text{ A}$$

$$V_{AN} = I_a \cdot (19 + j55) = 2.4 \angle -36.87^\circ \times 96.26 \angle 34.85^\circ$$

$$= 231.024 \angle -2.02^\circ$$

$$\underline{V_{AB}} = \underline{V_{AN}} - \underline{V_{BN}} = V_A - V_N - (V_B - V_N)$$

$$= V_A - V_B = \underline{V_{AB}}$$

$$\underline{V_{BN}} = \underline{I_B} \times \underline{(19 + j52)}$$

Balanced three phase system:  
 Same magnitude, frequency,  $120^\circ$  apart

(2)

$$\frac{\sqrt{1.6^2 + 0.2^2}}{\sqrt{0.3^2 + 2.4^2}}$$

$$\begin{cases} V_a = 240 \angle 0^\circ - I_a \cdot (0.2 + j1.6) \\ V_b = 240 \angle 120^\circ - I_b (0.3 + j2.4) \end{cases}$$



②

P.11.9 Balanced, Three phase, Y-Y connected

- Line voltage at the source  $V_{ab} = 90\sqrt{3} \angle 0^\circ \text{ V}$
- phase sequence is positive


- Line impedance  $(2 + j3) \Omega/\phi$
- Load impedance  $(28 + j37) \Omega$

Part A  
 $V_{an} = V_a$

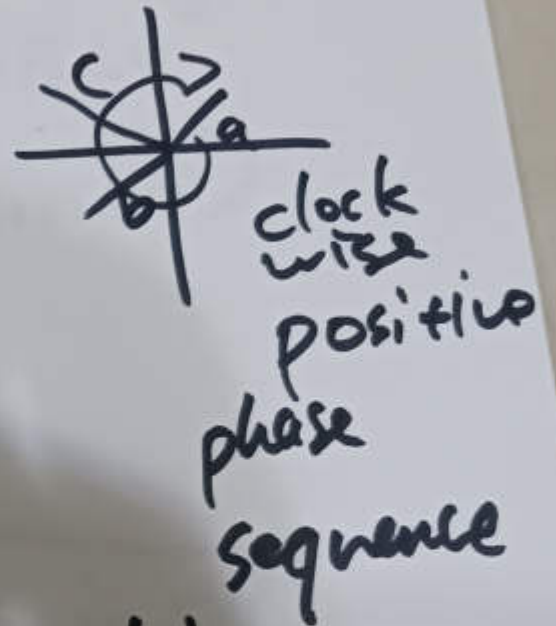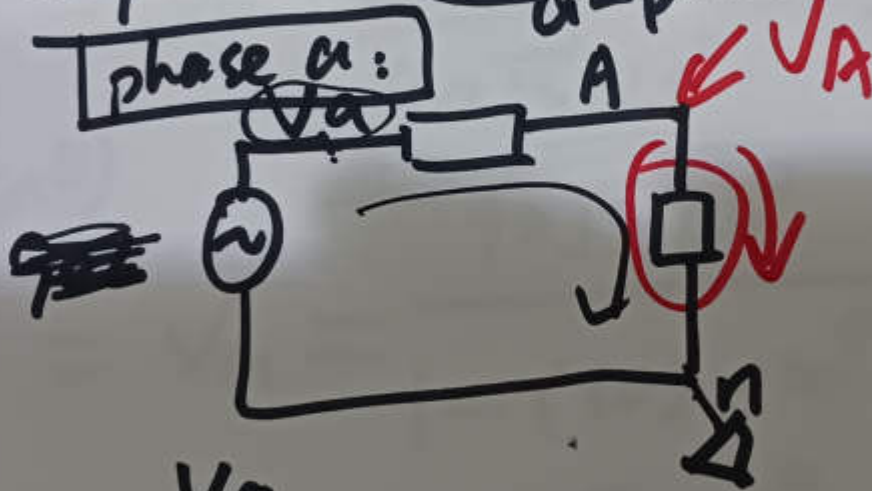

Part B  

$$I_a = \frac{V_a}{30 + j40}$$

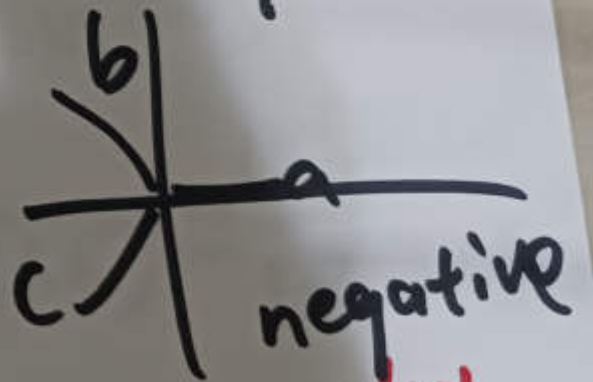

Part C: Line voltage at the load in the a-phase

$$V_{AB} = V_{AN} - V_{BN} = V_A - V_B$$

$$\begin{aligned}
 \underline{V_{ab}} &= V_a \angle 0^\circ - V_a \angle -120^\circ = 90\sqrt{3} \angle 0^\circ \\
 &= V_a (1 \angle 0^\circ - 1 \angle -120^\circ) = 90\sqrt{3} \angle 0^\circ \\
 &= V_a (1 - e^{-j120^\circ}) = 90\sqrt{3} \angle 0^\circ \\
 &= V_a (1 - (\cos -120^\circ - j \sin 120^\circ))
 \end{aligned}$$

$$= \underline{90\sqrt{3}} \angle 0^\circ$$

$$\frac{90\sqrt{3} \angle 0^\circ}{90\sqrt{3} \angle 0^\circ}$$

$$= V_a = \frac{90\sqrt{3} \angle 0^\circ}{1 - (\cos -120^\circ - j \sin 120^\circ)}$$

$$= \frac{155.88 \angle 0^\circ}{1 - (-0.5 - j0.866)} = \frac{155.88 \angle 0^\circ}{1.732 \angle 30^\circ}$$

$$= \underline{90} \angle -30^\circ$$

$$\begin{aligned}
 Ae^{j\theta} &= A \angle \theta \\
 &= A(\cos \theta + j \sin \theta)
 \end{aligned}$$

②

## 11.24. Complex power

$$= V \times I^*$$

$$= V_m \angle \theta_v \cdot I_m \angle \theta_i^*$$

$$= V_m \angle \theta_v \cdot I_m \angle -\theta_i$$

$$= \frac{V_m I_m \angle \theta_v - \theta_i}{?}$$

$$= \frac{V_m I_m \cos(\theta_v - \theta_i)}{?} + \frac{V_m I_m \sin(\theta_v - \theta_i)}{?}$$

$$\begin{aligned} a + bj & \quad a + kb \\ \rightarrow a - bj, & \quad -a - kb \end{aligned}$$